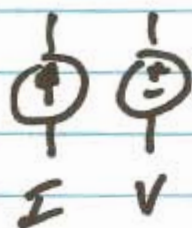


# Sources




INDEPENDENT  
Sources

Numeric value

$$V = 1.5V$$

$$I = 5A$$

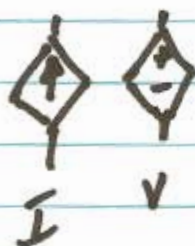

DEPENDENT  
Sources


functional relation

$$V_1 = 3I_1$$


$$I_2 = 4I_1$$

R

RESISTANCE  
 $R = \frac{V}{I}$

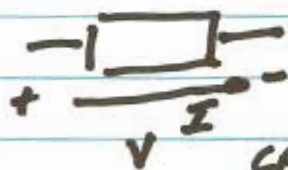

positive convention

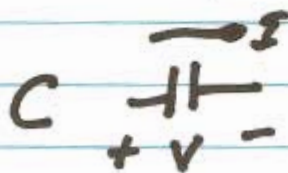


CAPACITANCE

$$i(t) = C \frac{dv}{dt}$$

$$I = j\omega C V$$

$$V = \frac{1}{j\omega C} I$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{sC} \Big|_{s=j\omega}$$

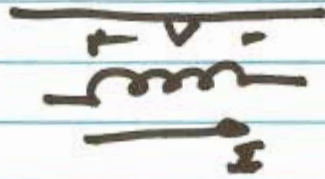
INDUCTANCE

$$V(t) = L \frac{di}{dt}$$

$$V = j\omega L I$$

$$Z_L = j\omega L = sL / s_0 \omega$$


## Current Source

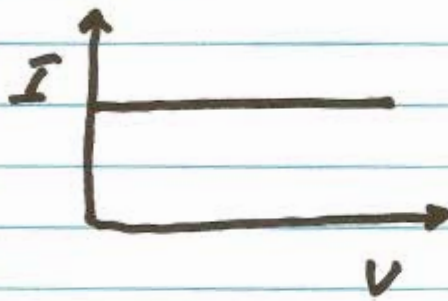

Constant  $I$   
Independent of  $V$   
 $\therefore$  infinite impedance

$$\begin{array}{c} \circ \\ | \\ \circ \end{array} I = 0$$


## Voltage Source

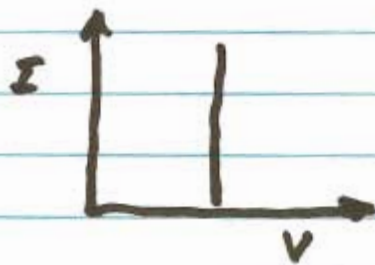


Constant voltage  
Independent of  $I$   
 $\therefore$  zero impedance

$$\begin{array}{c} \circ \\ | \\ \circ \end{array} V = 0$$


# Bipolar Transistor (BJT)

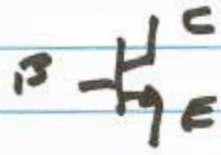

|||

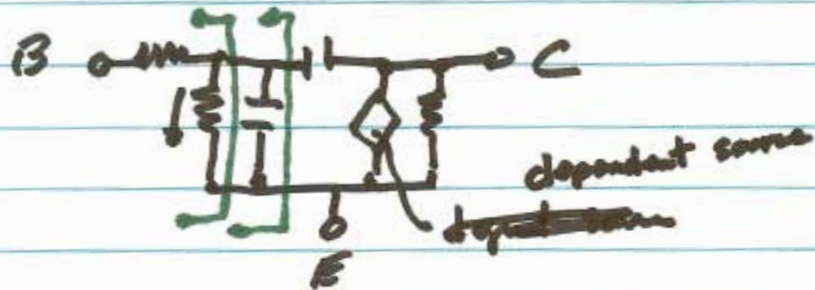

## THEVENIN/NORTON EQUIVALENT

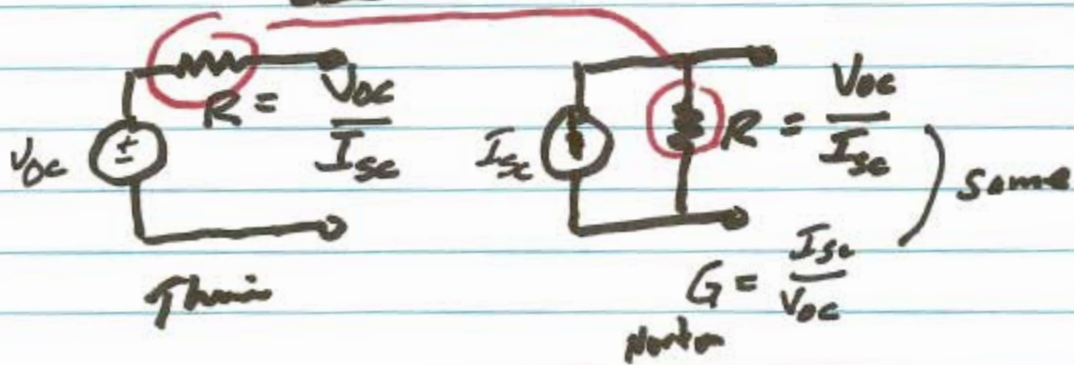

8/27/07

4/5


$$Z_C = \frac{1}{j\omega C} = X_C \quad \text{capacitive reactance}$$

$$Z_L = j\omega L = X_L \quad \text{inductive reactance}$$

$L$  &  $C$  = reactive elements  
store energy


$Z$ 's are functions of  $\omega$ .

Contrast:

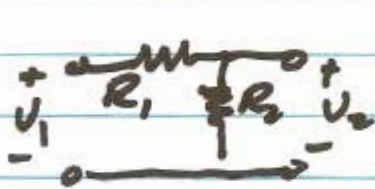

$$V_2 = \left( \frac{R_2}{R_1 + R_2} \right) V_1$$


no freq dependence

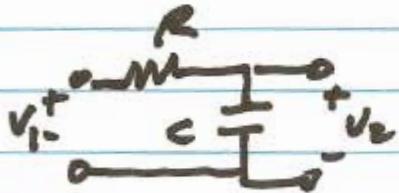

$$V_2 = \left( \frac{X_C}{R + X_C} \right) V_1$$

$X_C(\omega) \rightarrow$  freq dependent

frequency response


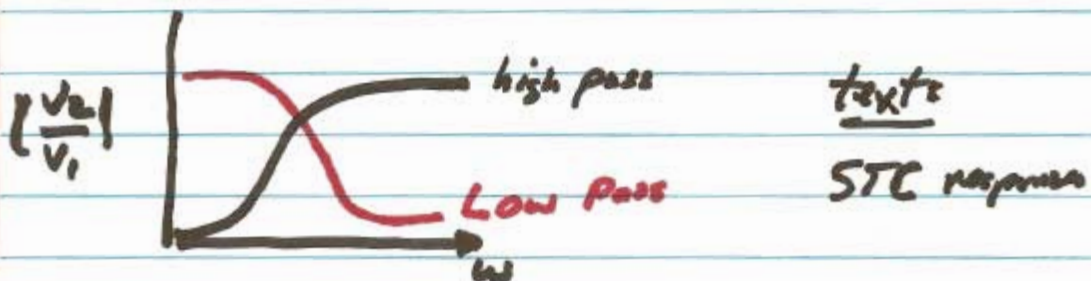


8/22/07 S/S

high Pass



Low Pass

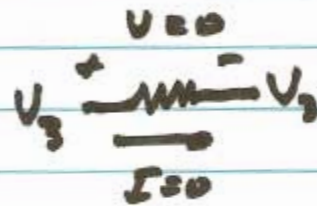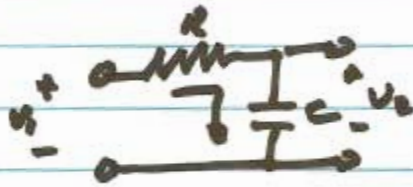

Appendix Test

STC Appendix D-1