

$$\omega_0 = \frac{2\pi}{T}$$

$$f(t) = v(t) = \sum_{n=1}^{\infty} (a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t))$$



Symmetric wave


$\rightarrow 10^{-3} \text{ s}$

$1 \text{ ms} \leftrightarrow 1 \text{ kHz} \quad (f = \frac{1}{T})$

$\omega_0 = 6.28 \times 10^3 \text{ rad/sec}$






Superposition of sinusoids

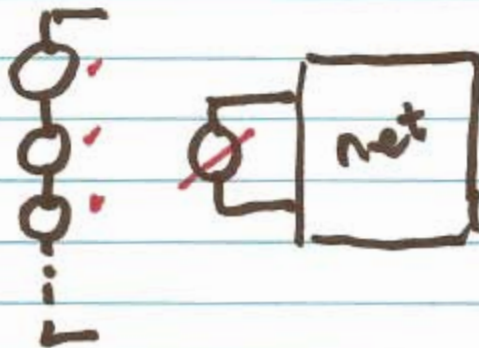


8/29/07 3/8

APERIODIC

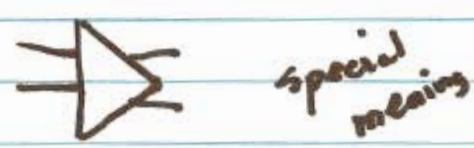
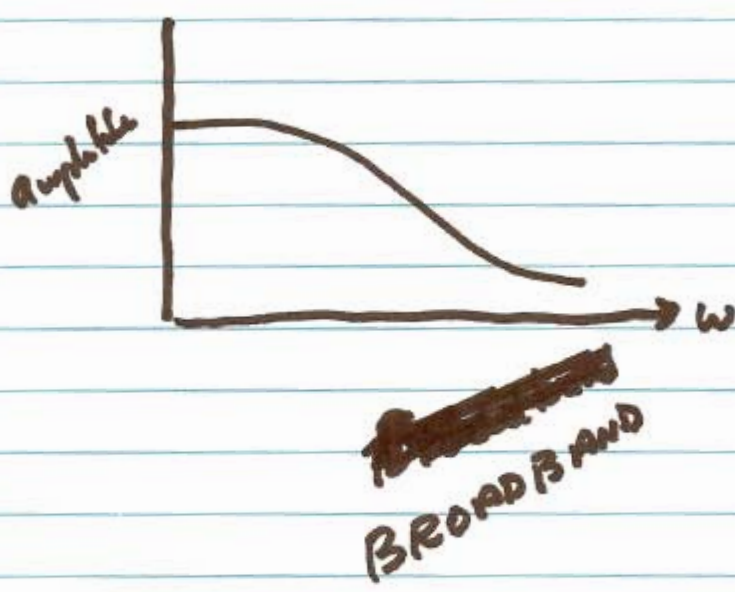
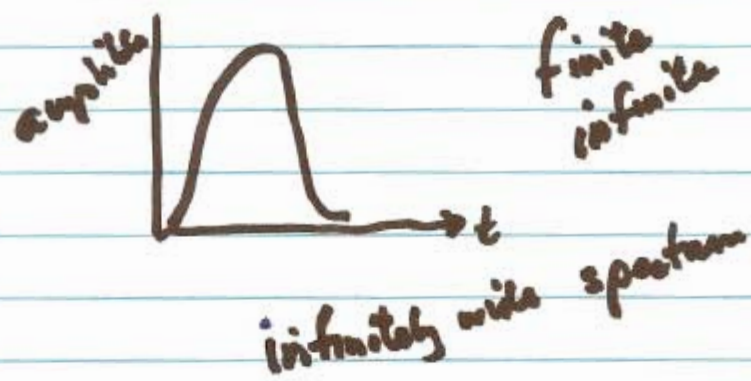


special meaning

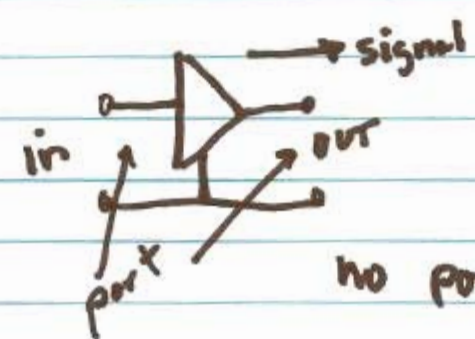

no power input

8/29/07 4/8

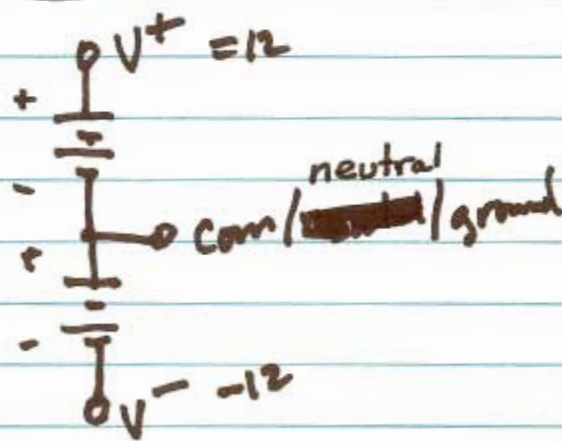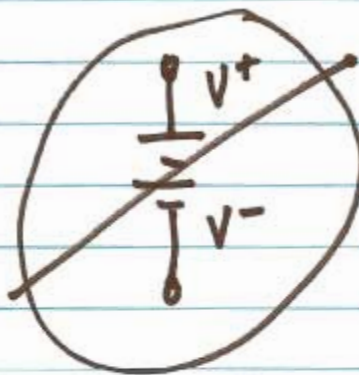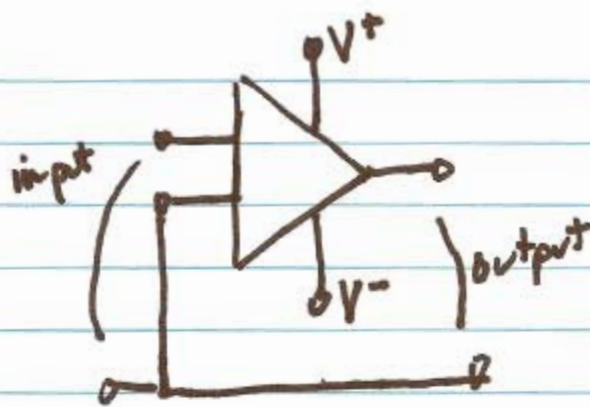


Complimentary Supply

8/29/07 5/8

$$\text{Gain} = M e^{j\phi} = M \angle \phi$$

$$20 \log_{10}(\text{Gain}) = \overset{20}{\log_{10} M} + j\phi \overset{20 \leftarrow \text{ignore}}{\log_{10} e} \leftarrow \text{omitted in lecture}$$

\Rightarrow log measure + phase angle

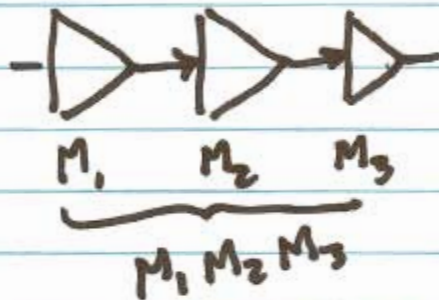

$$M_1(\text{dB}) + M_2(\text{dB}) + M_3(\text{dB})$$

Two Port



port \equiv terminal pair

linear network
reciprocal

$$\text{Gain} = \frac{\text{out}}{\text{in}}$$

$$\begin{array}{ll} V \rightarrow V & V \rightarrow I \\ I \rightarrow I & I \rightarrow V \end{array}$$

$$\begin{array}{l} \frac{I}{V} = Y \mid G \\ \frac{V}{I} = Z \mid R \end{array}$$


8/29/07 6/8

$$Z = R + jX$$

$$Y = G + jB$$

$$\frac{V}{I} = Z = R + jX$$

"trans"

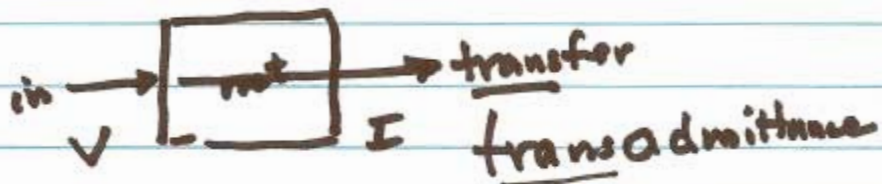


$$Z_T = \frac{V_{out}}{I_{in}} \Omega$$

$$Y_T = \frac{I_{out}}{V_{in}} \mathcal{V}$$




$$A_V = \frac{V_{out}}{V_{in}} -$$

$$A_I = \frac{I_{out}}{I_{in}} -$$

Pretend World Is Linear


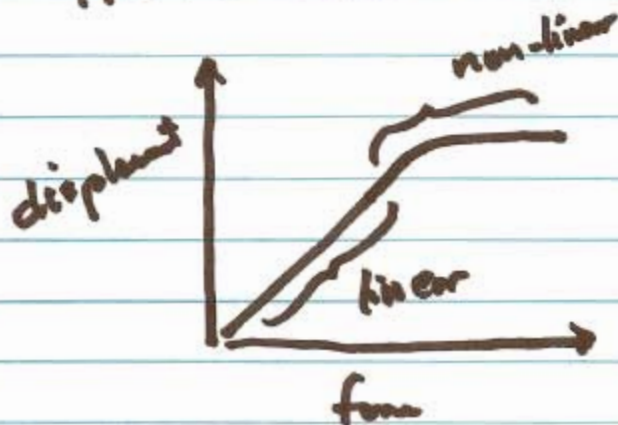


8/29/03 7/8

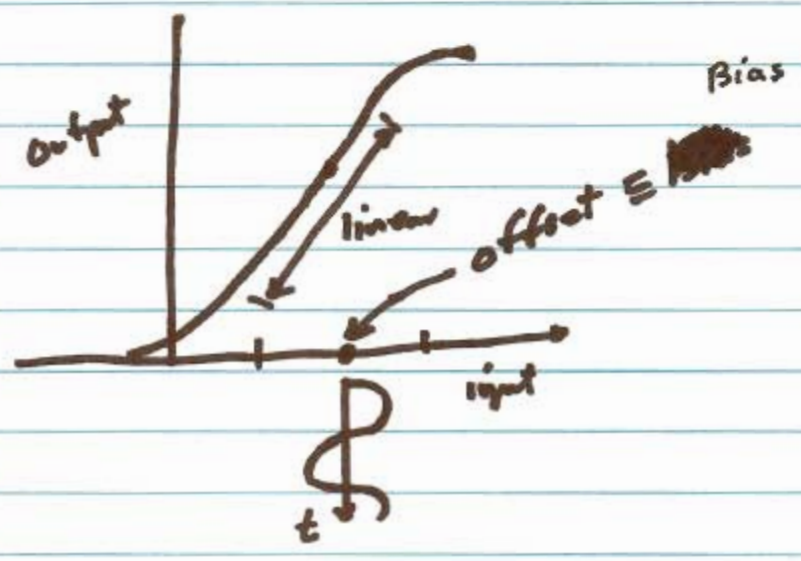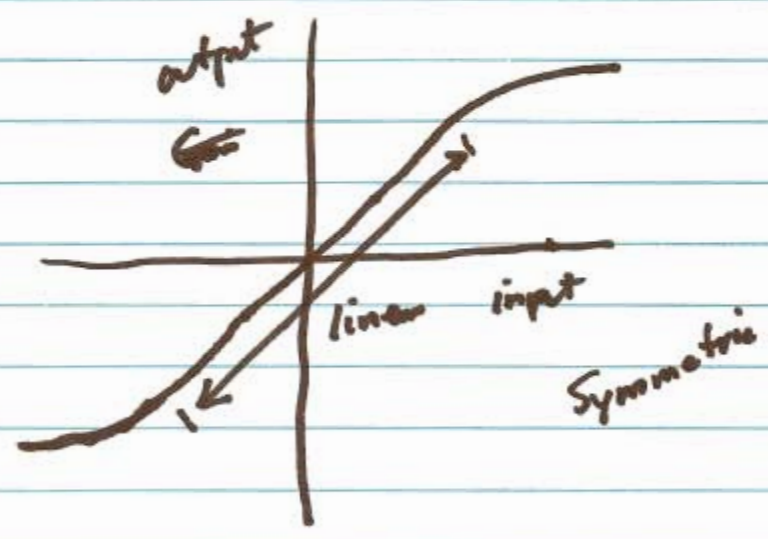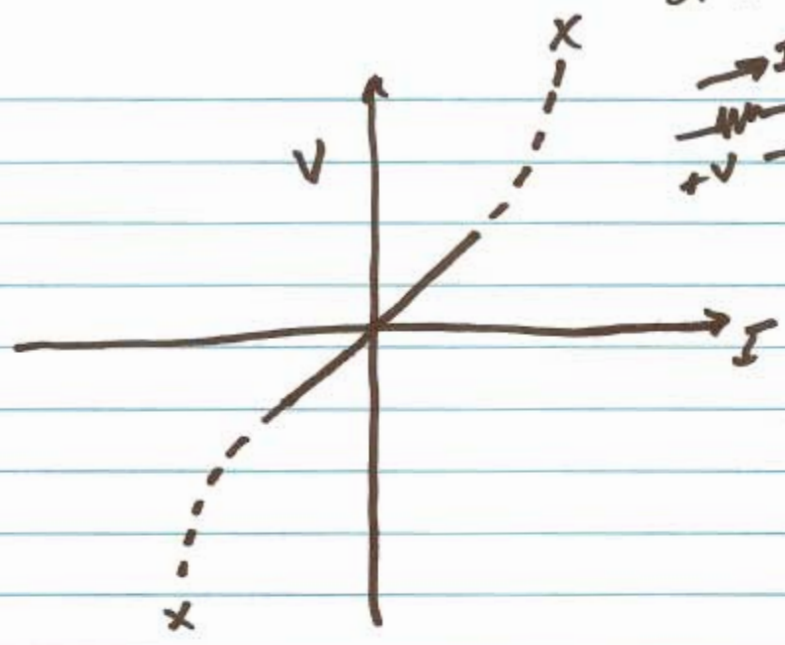

8/29/02 8/B

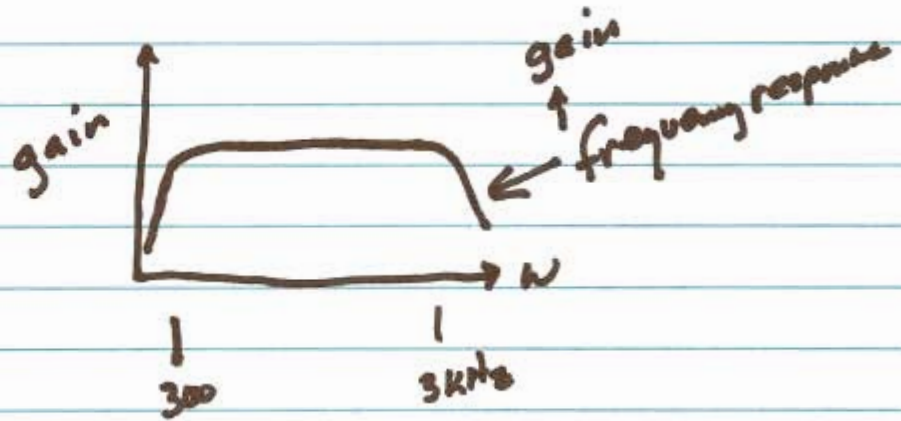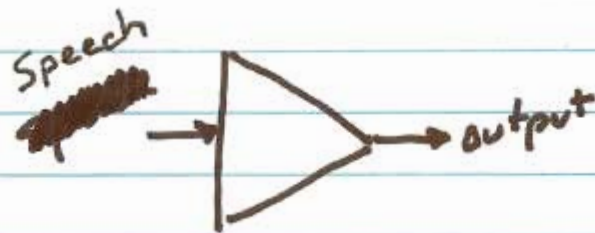Speech
~~Speech~~ : $300\text{Hz} - 3000\text{Hz}$ (A.T.T.)
3kHz BANDWIDTH



Bode Plot

