

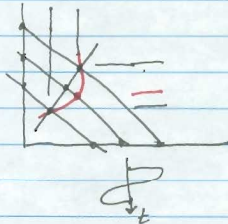
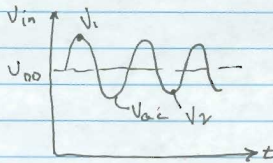





Add AC source

$$V_{in} = V_{DD} + V_{ac}$$


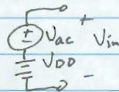


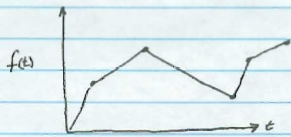



Example of piecewise linear

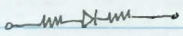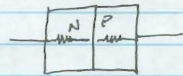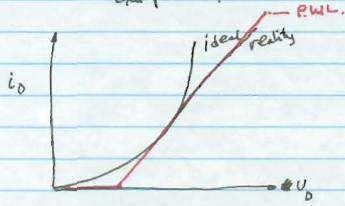



BULK RESISTANCE


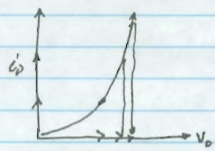
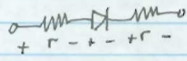


9/12/07 3/4

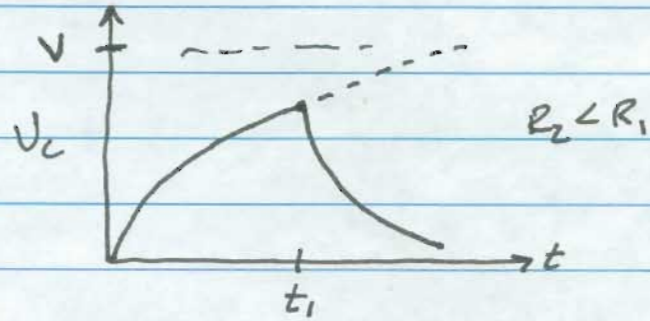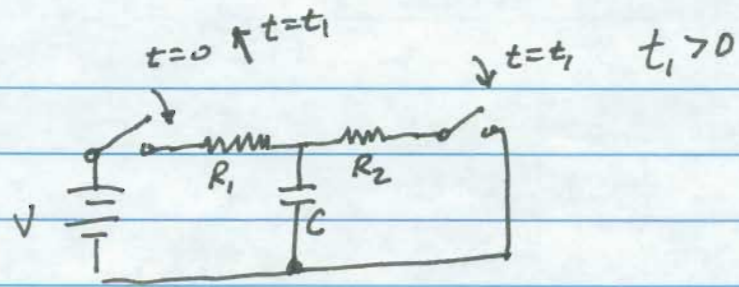

Reference Diode Model

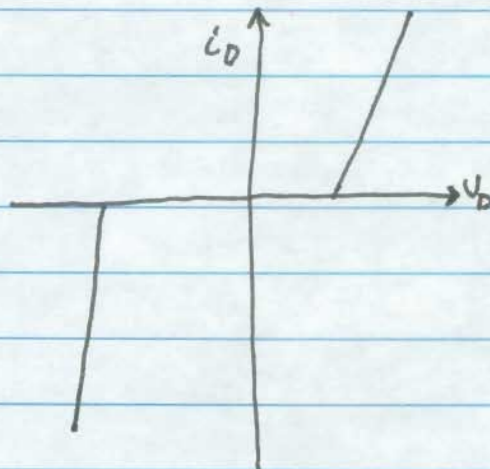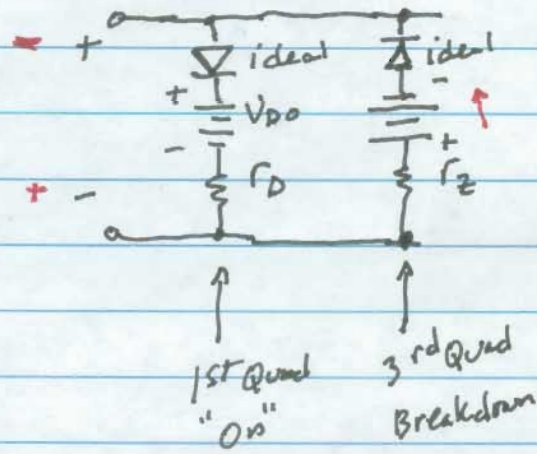

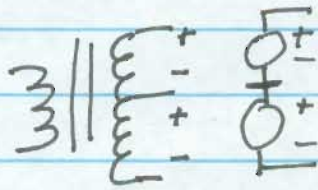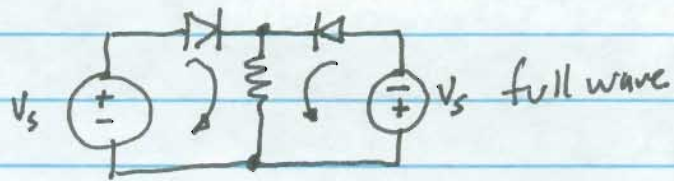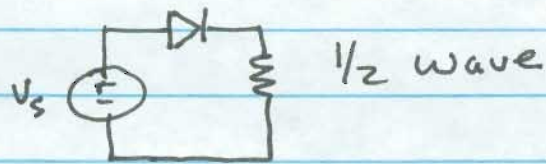

Full Wave Bridge
Next Time
