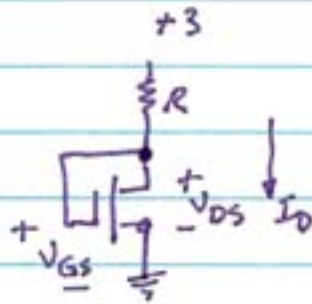


- 1)  $R_1 I_1 + R_2 I_2 = V_{DD}$       C       $I_1$
- 2)  $R_D I_D + R_S I_D + V_{DS} = V_{DD}$       C       $I_D$
- 3)  $-I_2 R_2 + V_{GS} + I_D R_S = 0$       C       $V_{DS}$
- 4)  $I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$       D       $V_{GS}$
- 5)  $I_1 = I_2$       C

C = circuit eqn  
 D = device eqn

Example 4.3



$$V_{GS} = V_{DS} <$$

$$I_G = 0$$



$$3 = R I_D + V_{DS} <$$

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 <$$

Example 4.4

as with Ex 4.3 but  $V_{GS} = 5$

Example 4.5

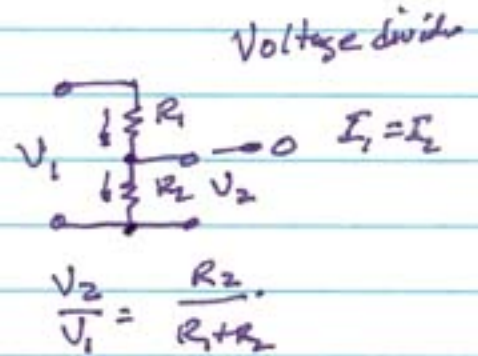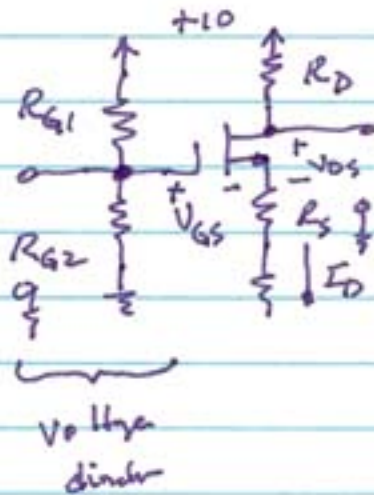


$$V_G = \left(\frac{R_{G1}}{R_{G1} + R_{G2}}\right) 10 = \text{known value}$$

$$V_G = V_{GS} + R_S I_D <$$

$$10 = R_D I_D + R_S I_D + V_{DS} <$$

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 <$$

## Example 4.6

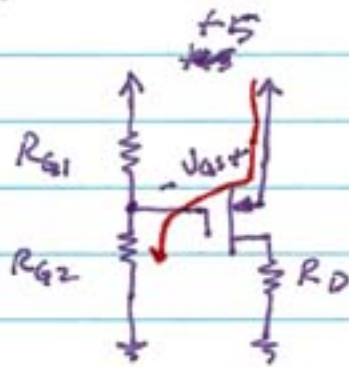

$$\left( \frac{R_{G2}}{R_{G1} + R_{G2}} \right) 5 = V_{GS}$$

$$I_D = 0.5 \text{ mA}$$

$$I_D = \frac{1}{2} K_P' \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$I_D \rightarrow V_{GS}$$

$$5 = V_{GS} + V_{R_{G2}} = V_{GS} + V_G$$

$$V_{GS} \rightarrow V_{R_{G2}}$$

$$5 = I_{R_{G1}} R_{G1} + I_{R_{G2}} R_{G2}$$

$$I_{R_{G1}} = I_{R_{G2}}$$

$$V_{R_{G1}} + V_{R_{G2}} = 10$$

$$I_{R_{G1}} = I_{R_{G2}} = I_{R_{G2}} = \frac{5}{R_{G1} + R_{G2}}$$


$$R_{G1} = \checkmark$$

$$R_{G2} = \checkmark$$

$$V_D = 3$$



$$R_D I_D = 3$$

$$R_D = \frac{3}{I_D} = \checkmark$$

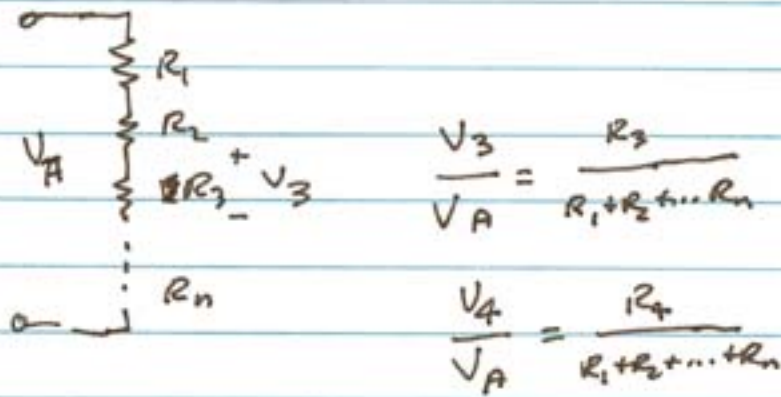

$$\frac{V_3 + V_4}{V_A} \neq \frac{R_3 + R_4}{R_1 + R_2 + \dots + R_n}$$
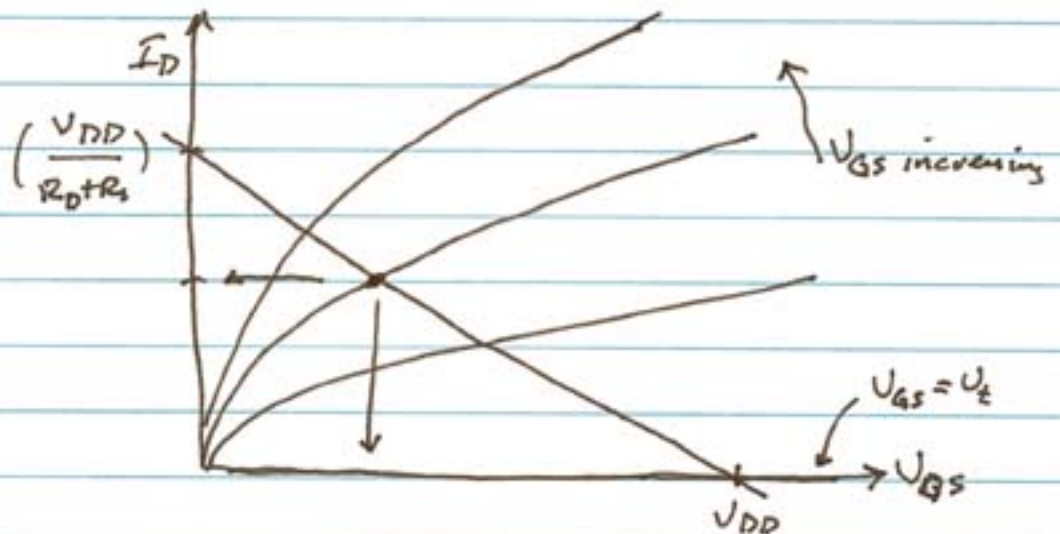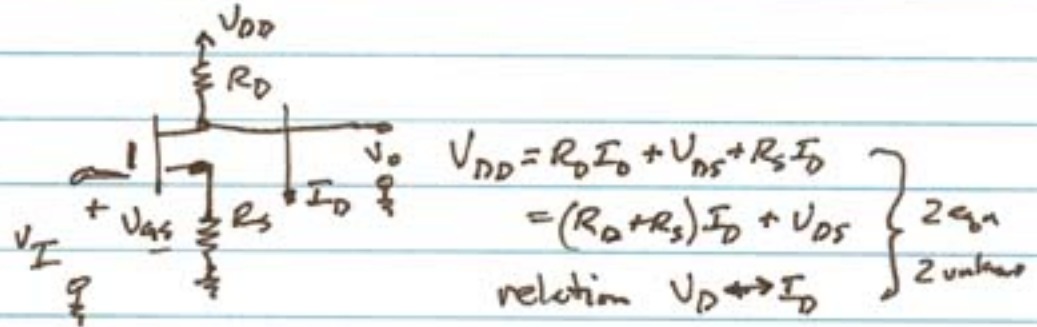
### Graphic Analysis of DC Voltages + Currents



Simultaneous solution: V-I characteristic


$$V_{DD} = (R_D + R_S) I_D + V_{DS} \text{ circuit}$$

need  $V_{GS}$  to determine operating point


$$V_{GS} = V_{GS} + I_D R_S$$

$$I_D = \frac{1}{2} K_n \left( \frac{W}{L} \right) (V_{GS} - V_{th})^2$$

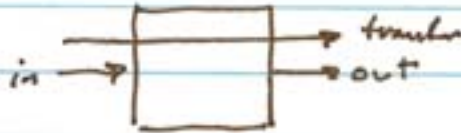Transfer characteristic  $\rightarrow$  Gain


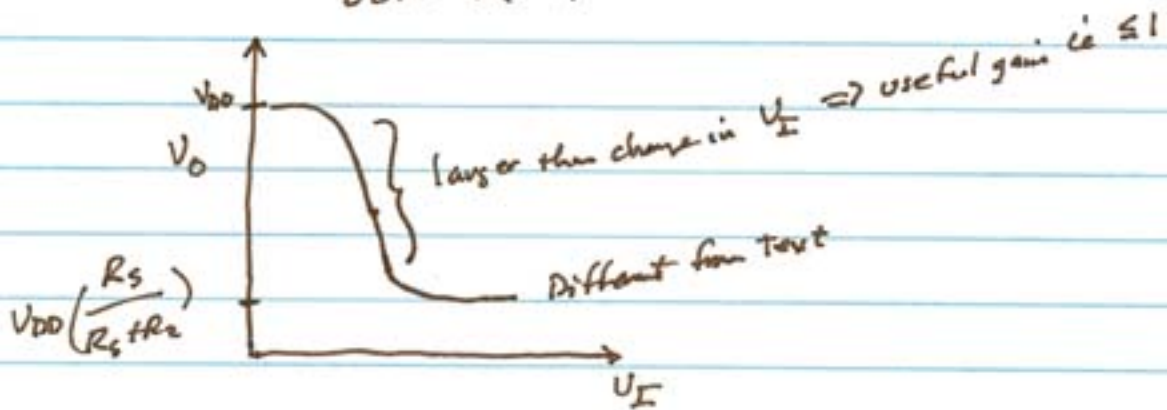
$$\text{out} = f(\text{in}) \quad \text{transfer}$$



$$V_{DD} = \underbrace{R_D I_D}_{\text{fixed}} + \underbrace{R_S I_D}_{\text{increase}} + \underbrace{V_{DS}}_{\text{decrease}}$$