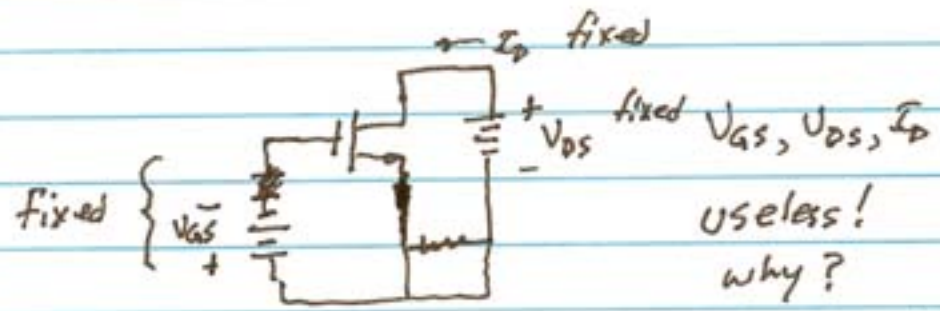


4 types MOSFETS

Voltages, currents & relation


use?



useless!  
why?


not possible input  
no possible output

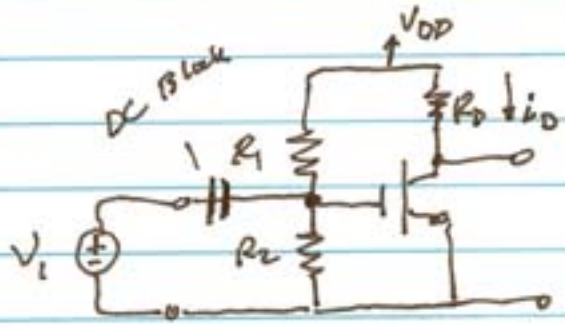must be able to vary input  $\rightarrow$  varying output








$$V_{DD} - R_D i_D = V_{DD} - R_D (I_D + \theta i_D)$$

↑  
from  $V_{GS}$

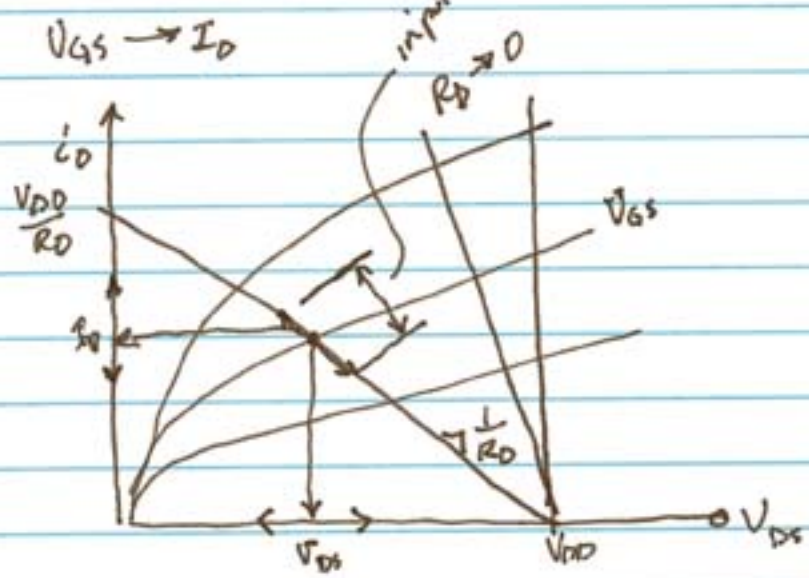

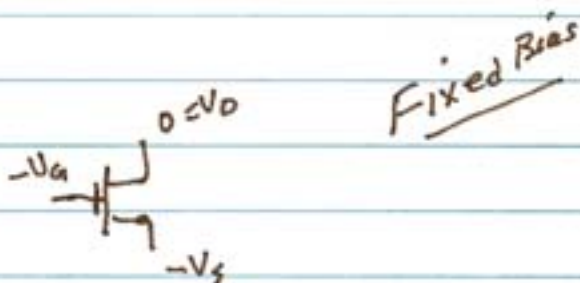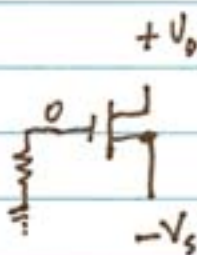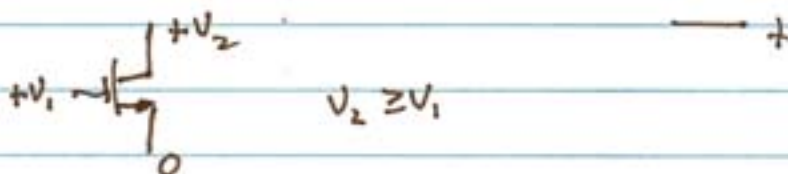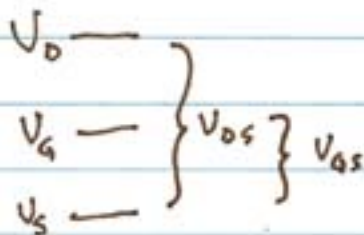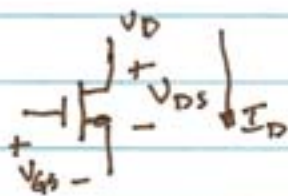
Biasing = setting of DC values that allow AC signals



Compensate for device variation  
"feedback"

SELF BIAS

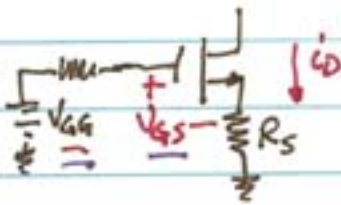for  $V_{GS}$  fixed,  $i_D$  is  $>$  or  $<$  design value




Case 1  $i_D <$  design

$$V_{GS} = V_{GG} - R_S i_D$$

↑  
too small  
increase

$$V_{GS} = V_{GG} - R_S i_D$$


↑  
too large  
reduce

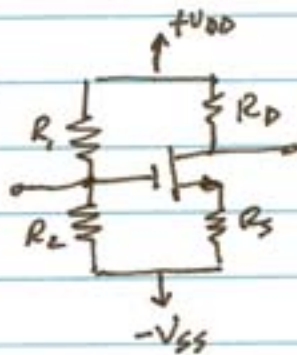

$V_{DD}, -V_{SS}$  can be  $= 0$  (anytime)

Current source bias

Current mirror

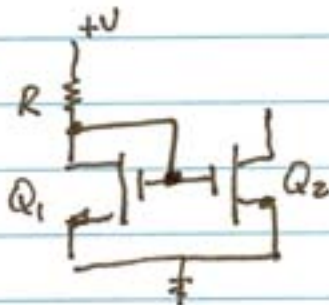

$$V_{GS1} = V_{GS2}$$

$$I_{D1} = I_{D2} \text{ given that } V_{DS1} = V_{DS2}$$

$Q_1 \cong Q_2$

$$V - R I_{D1} = V_{GS1} = V_{GS2}$$

↑  
specify