


10/1/07 4/4

$$dz = \left(\frac{\partial z}{\partial x} \right) dx + \left(\frac{\partial z}{\partial y} \right) dy$$

$$i_D = \left(\frac{\partial i_D}{\partial v_{GS}} \right) \delta v_{GS} + \left(\frac{\partial i_D}{\partial v_{DS}} \right) \delta v_{DS}$$


Want a linear world!!

linear \equiv plane, tangent to surface

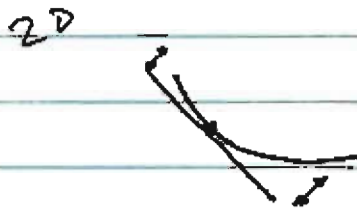


linear \rightarrow Small signal model \leftarrow

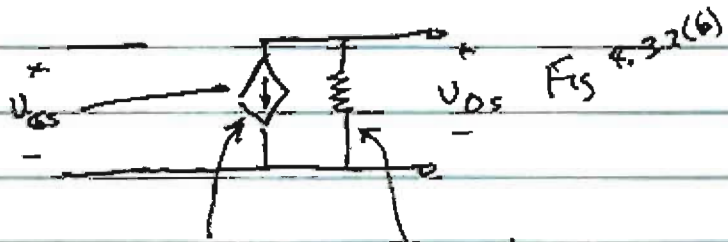non-linear \rightarrow large signal model



$$\frac{\left(\frac{\partial i_D}{\partial v_{GS}} \right) \delta v_{GS}}{i_D} = \frac{1}{\frac{\left(\frac{\partial i_D}{\partial v_{DS}} \right) \delta v_{DS}}{i_D}} = \frac{1}{r_o = r_D}$$




P 289

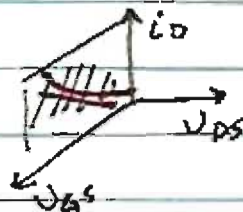

10/1/07 2/4

$$z = \frac{V}{I}$$

$$= \frac{\partial V}{\partial i} \Big|_{\text{const}} \rightarrow \frac{V}{I} \quad \text{linear, sinusoidal}$$

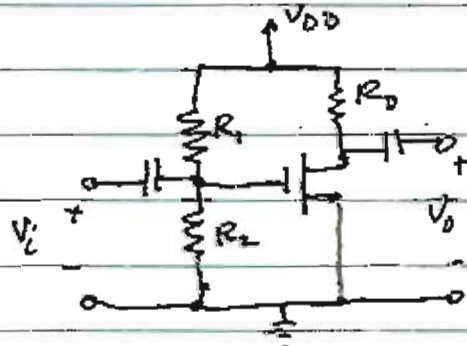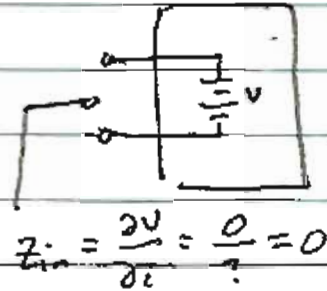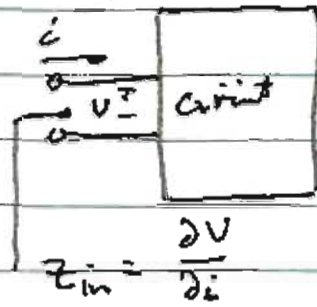


Small-signal analysis
 Δ Variable is small and
 the only constant.



$$R_G = R_1 \parallel R_2$$

$$V_i = V_{GS}$$

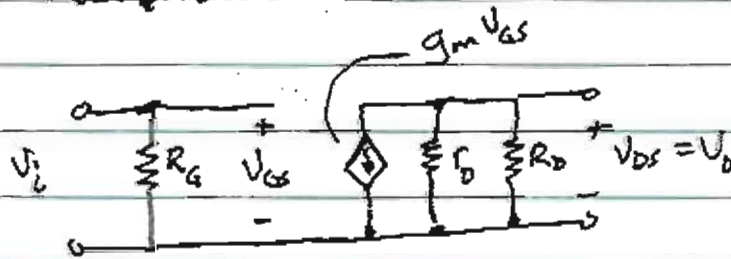


Voltage gain = $A_v \equiv \frac{V_o}{V_i}$

$V_o = -g_m V_{GS} (r_o \parallel R_D)$


$= -g_m V_i (r_o \parallel R_D)$

$\frac{V_o}{V_i} = A_v = -g_m (r_o \parallel R_D)$

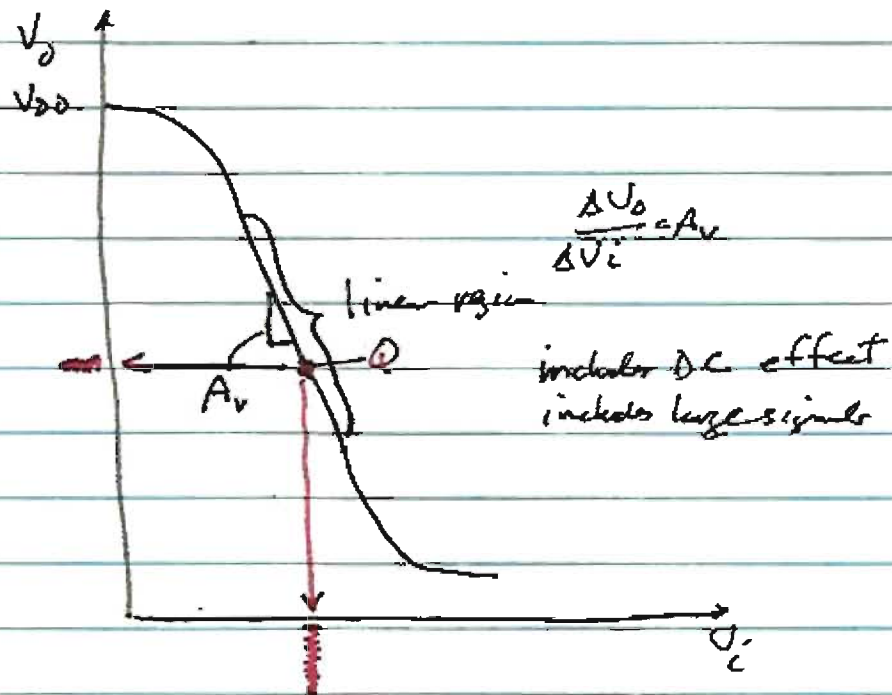
alternative method = transfer characteristic



Know into Table 8.3, Pp 302-303

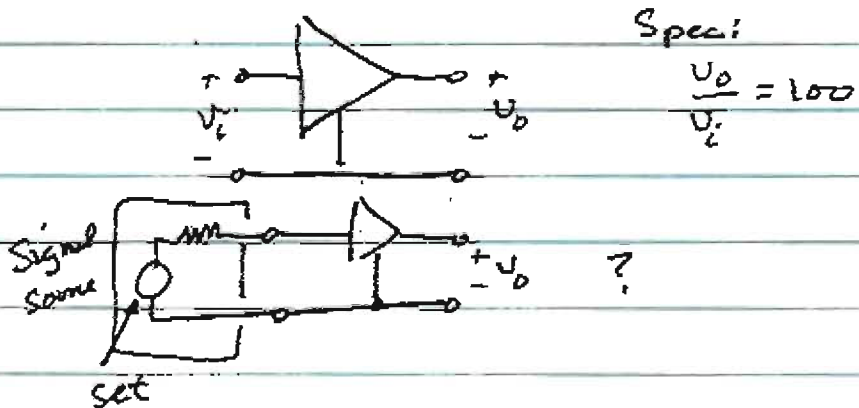

Speci
 $\frac{V_o}{V_i} = 100$

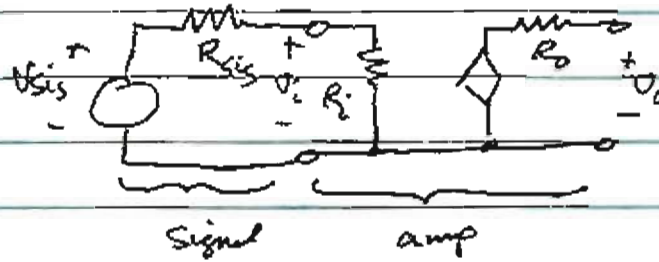

Source

$$V_i = \left(\frac{R_i}{R_{sis} + R_i} \right) V_{sis} \quad V_{sis}, R_{sis} \text{ unknown}$$


$$V_o = 100 V_i$$

G overall gain
A actual gain


Common Source, Common Gate, Common Drain



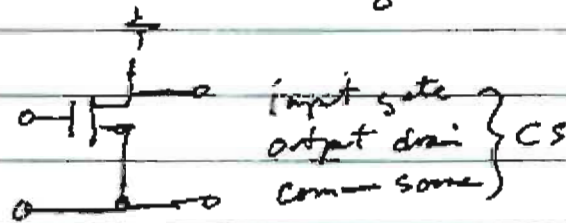
- 1st lead input
- 2nd lead output
- 3rd lead common



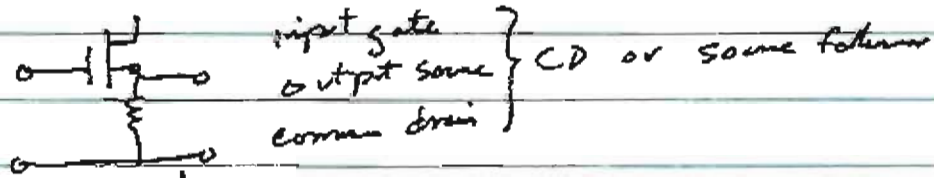input gate
output drain
common source } CS



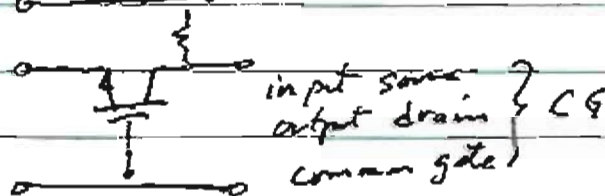input gate
output source
common drain } CD or source follower



input source
output drain
common gate } CG