
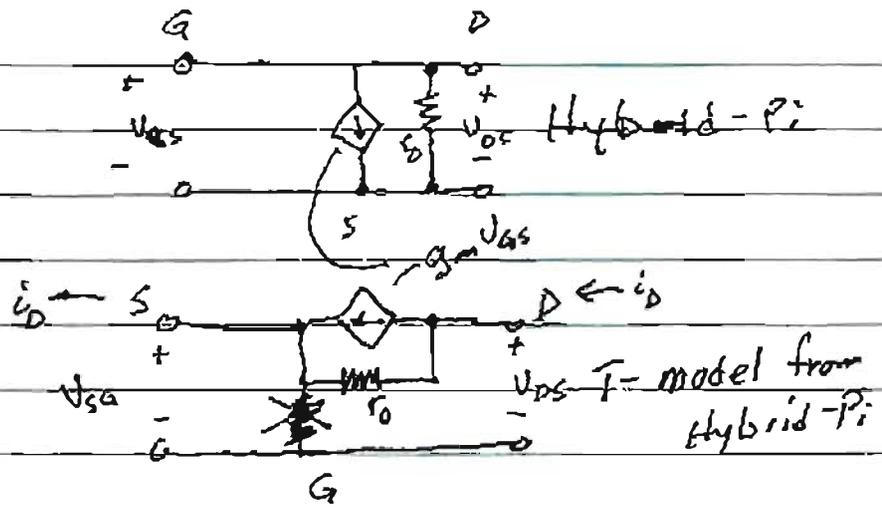


10/18/07 1/7

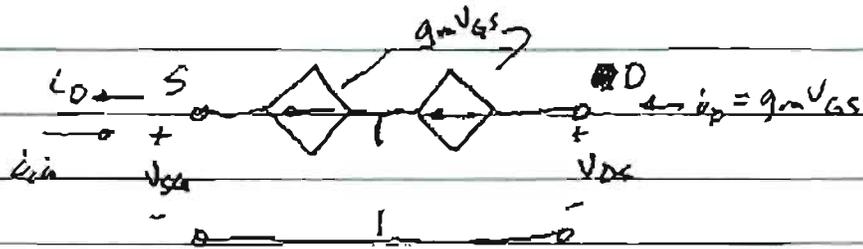



temp remove  $r_0$



$$R_{in} = \frac{-V_{GS}}{-i_D} \quad (i_{in} = -i_D)$$
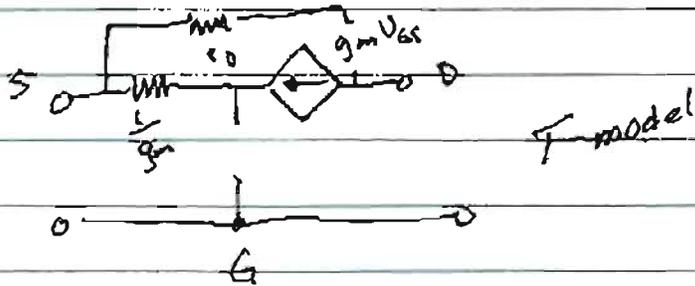
$$= \frac{-V_{GS}}{-g_m V_{GS}} = \frac{1}{g_m} \quad \text{Wow!}$$




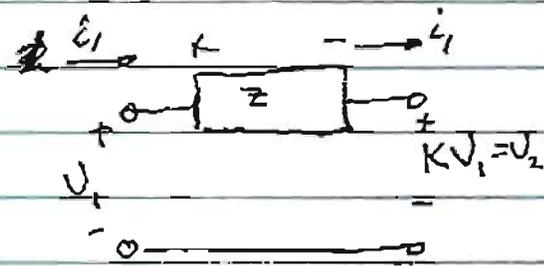

$Z_{in} = \frac{V_1}{i_1}$


$i_1 = (V_1 - V_2) \left( \frac{1}{Z} \right)$

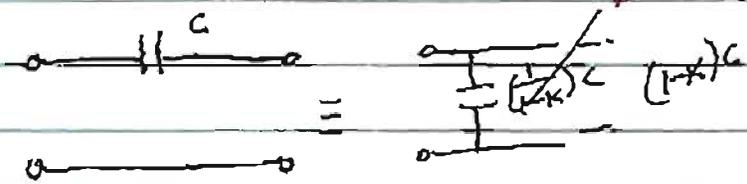$Z_{in} = \frac{V_1}{V_1 - KV_1} \cdot \frac{1}{\frac{1}{Z}} = \left( \frac{1}{1-K} \right) Z$




C is multiplied by  $\frac{1}{1-K}$  (1-K)

"Miller Effect"

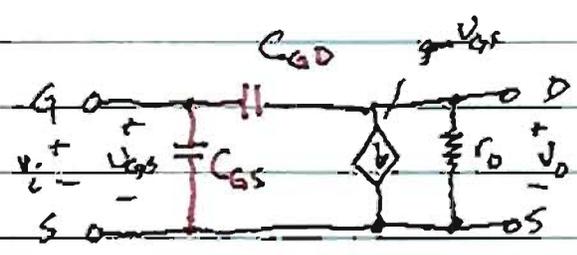


Cross-section


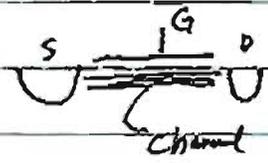


$V_D = -g_m(r_o || R_D) \gg 1 \approx -K$

effective  $C_{in} = C_{GS} + (1 + g_m(r_o || R_D)) C_{GD}$

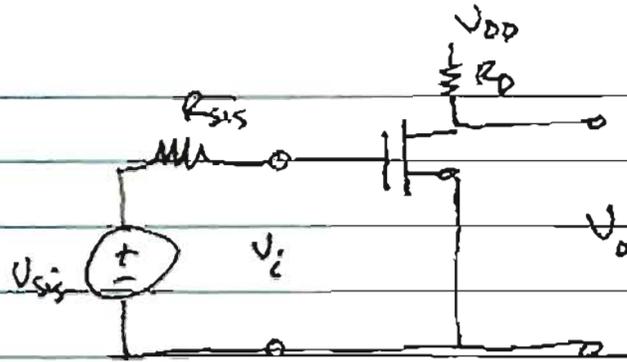


Assume bias is OK

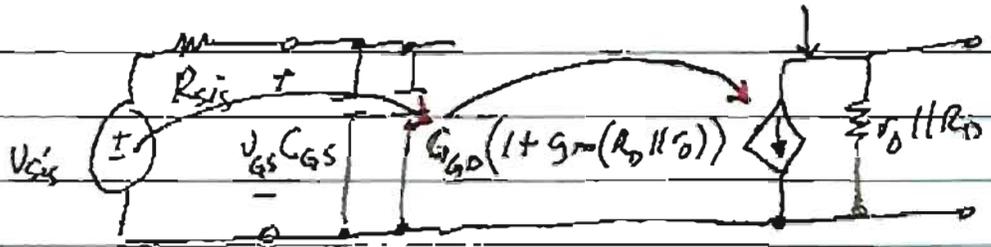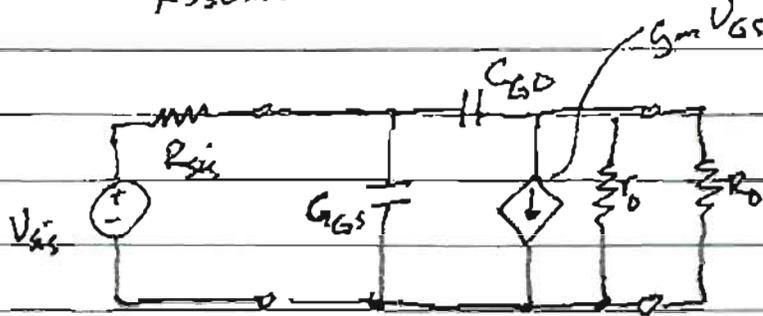

typical numbers:

$$C_{GS} = 2 \text{ pF}, C_{GD} = 3 \text{ pF}$$


$$(A \cdot g_m)(R_{eq}) = 70$$

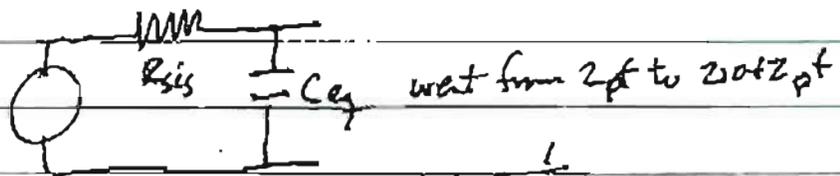

$$\omega_0 = \frac{1}{R C_{eq}}$$


$$(\text{Gain})(\text{Bandwidth}) = \text{const}$$

10/8/07 4/7

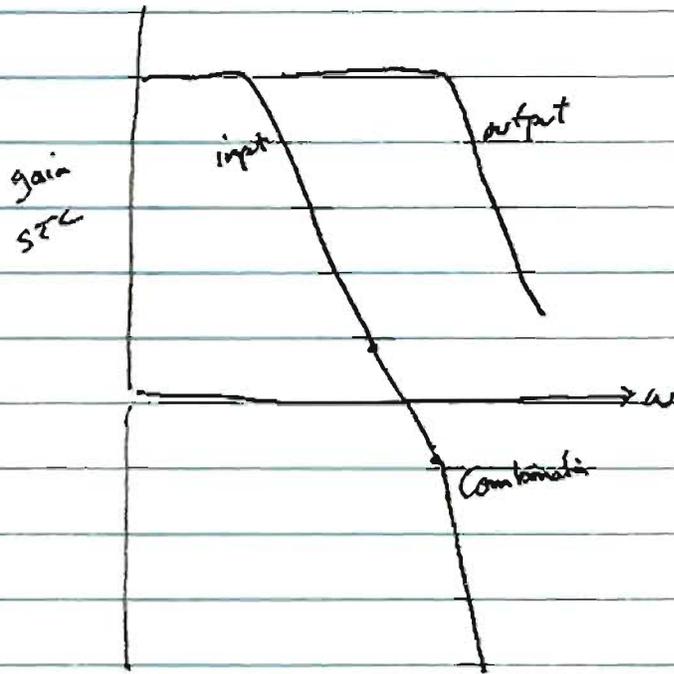

CS, CG, CD

going back

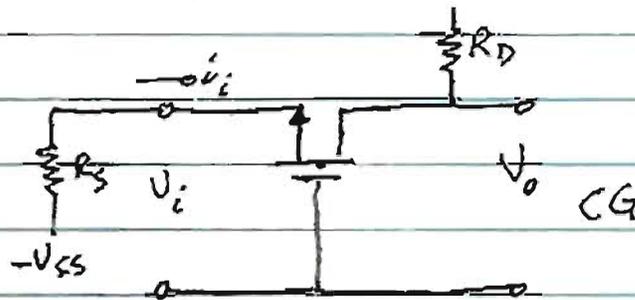


Any  $v$  or  $i$  is combination of ac + dc  
arrows show net direction

Small input R



Unity current gain

large output R

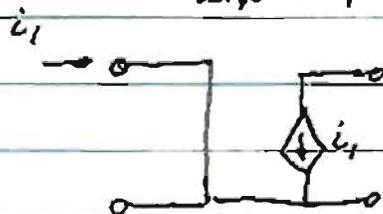


impedance transformer

10/8/07 5/7

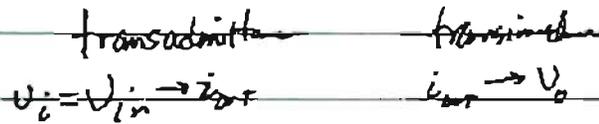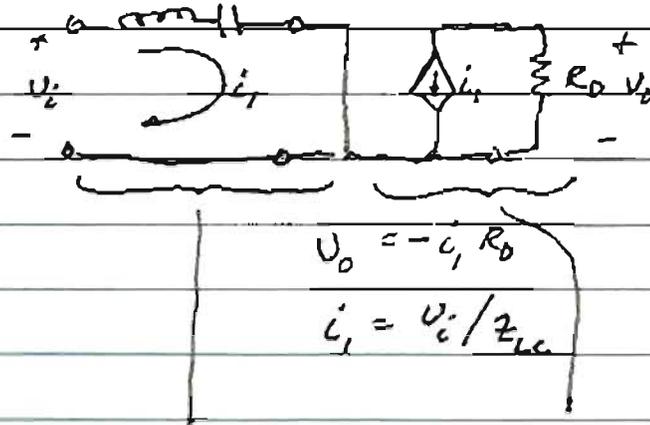

overall gain  $A_v = Y_T \cdot Z_T = \text{whatever (no dimm)} \text{ (pure gain)}$


CD  $\equiv$  Source Follower

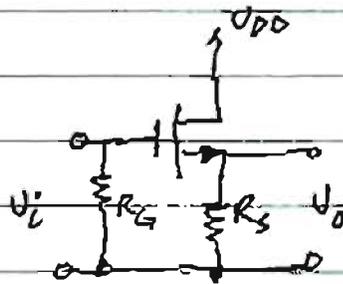

large input R ( $R_G \parallel \infty$ )

unity voltage gain

small output R

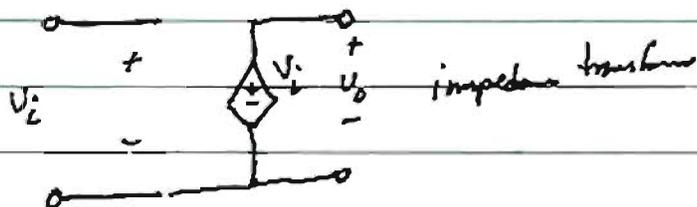

10/8/07 6/7

