


Diode "ON"

$$V_o = V_c$$

$$V_o = V_c - V_D \quad (\text{pretend } V_D \text{ constant})$$

$$i_L = \frac{V_o}{R}$$


$$i_D = i_c + i_L$$

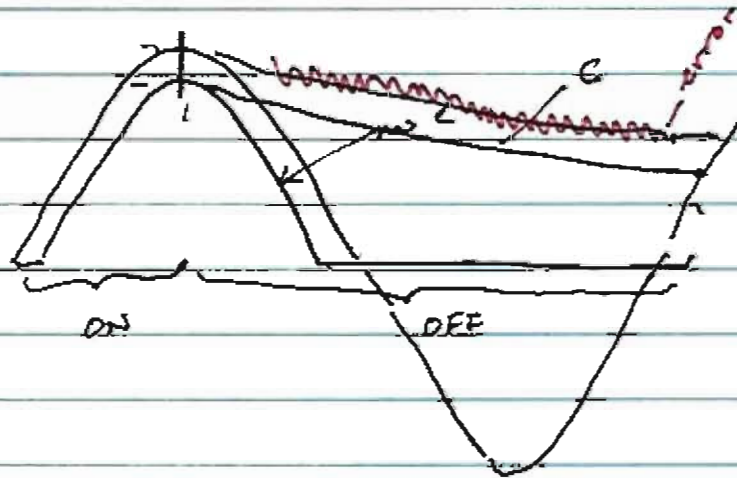



just after turn-off $-i_c = i_L$

Diode "OFF"


just before turn-on $-i_c = i_L$

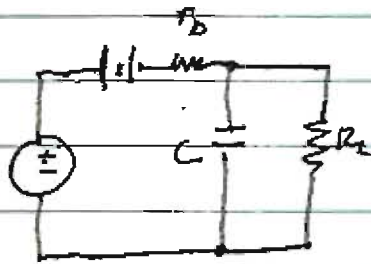

Question

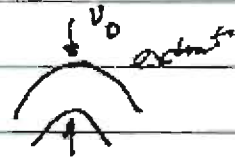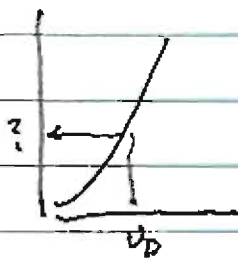 ζ mean for graph

Graphical integration

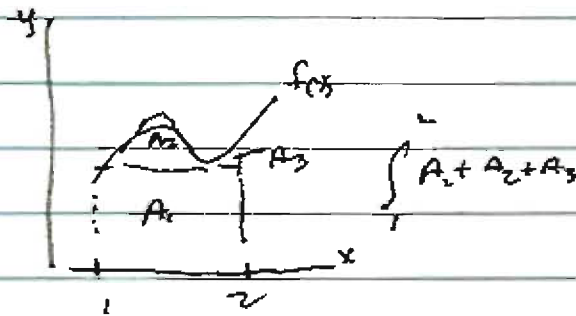


$$\text{Avg over } T = \frac{1}{T} \int_{x_1}^{x_2} f(x) dx$$

$$\text{Avg over } x = \frac{1}{x_2 - x_1} \int_{x_1}^{x_2} f(x) dx$$

$$= \frac{A_1 + A_2 + A_3}{x_2 - x_1} \checkmark$$




10/10/07

4/6

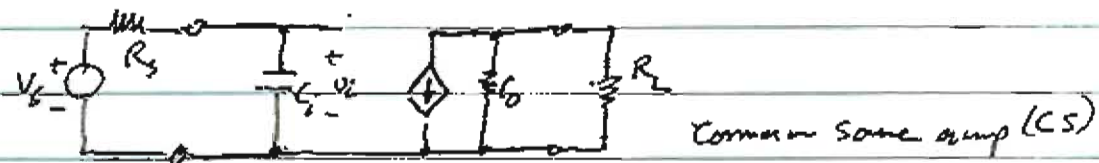

Suppose $R_s = 0$

Miller Effect

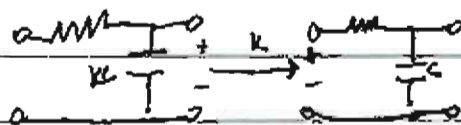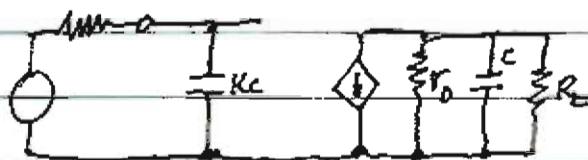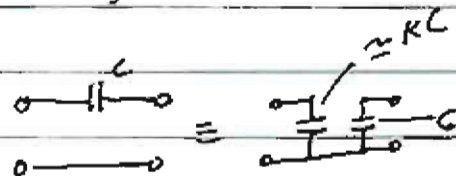


ω_D for STL is $\frac{1}{RC}$

cutoff ω @ input is approx K times lower than at output



IGNORE OUTPUT CUTOFF

10/10/07 5/6

Schematic to Linear Equivalent

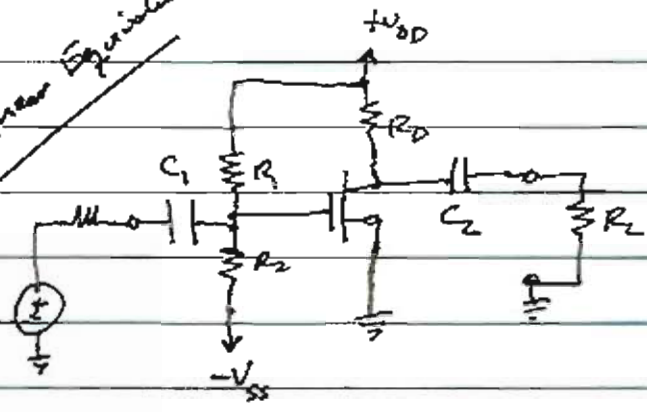

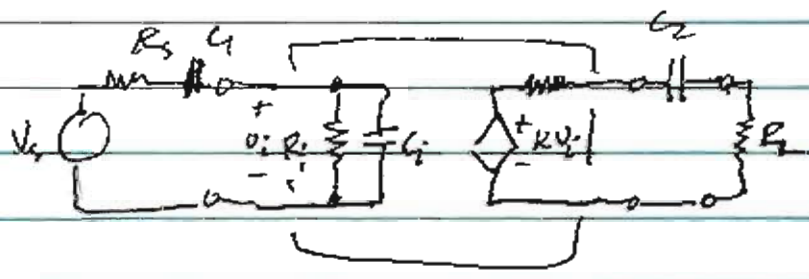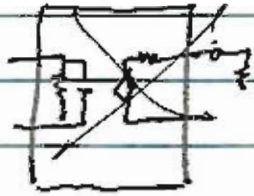1. Remove DC supplies
2. Determine freq of analysis



3. Draw appropriate equivalent circuit
 coupling caps determine LF cutoff
 parasitic caps (drain) determine HF cutoff

4. Perform Analysis
 both input & output affect LF cutoff

10/10/07 6/6



Use Thevenin or Norton models @ input & output

4 permutations

voltage output: open circuit output gain

current output: short circuit output gain

refer to table in text

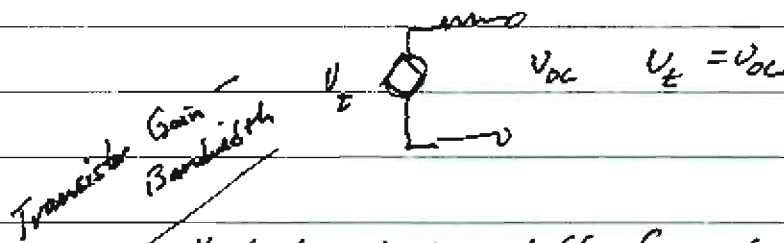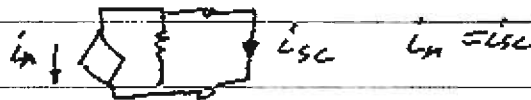

"Short-circuit cutoff freq for a transistor

$$f_T \quad f_{\beta}$$

measure of bandwidth of transistor (refer to text)