

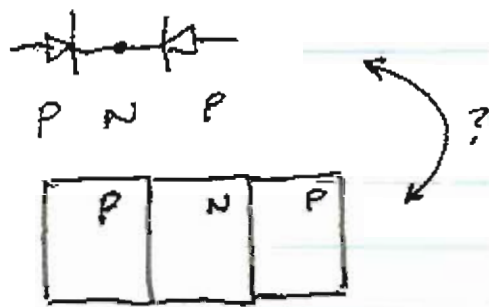


10/15/02 1/6

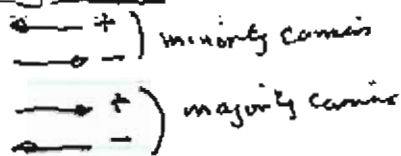

→ for very very thin

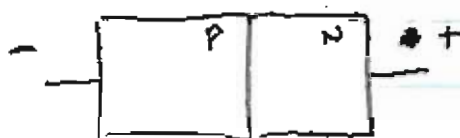


~~Net type~~
 Net type
 n majority
 p minority
 Net type
 p majority
 n minority





now reverse-biased
 minority carrier current
small


Suppose we inject minority carriers
 into either type material.

"Controlled breakdown"

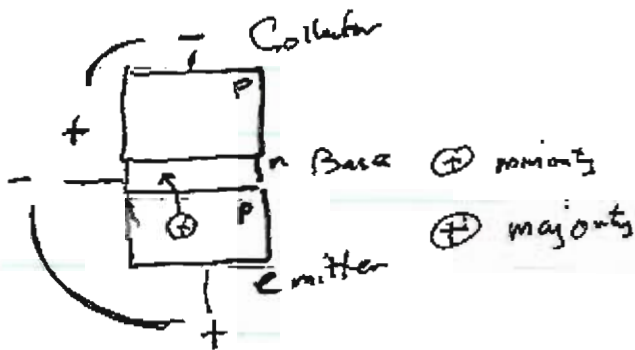

10/15/07 2/6

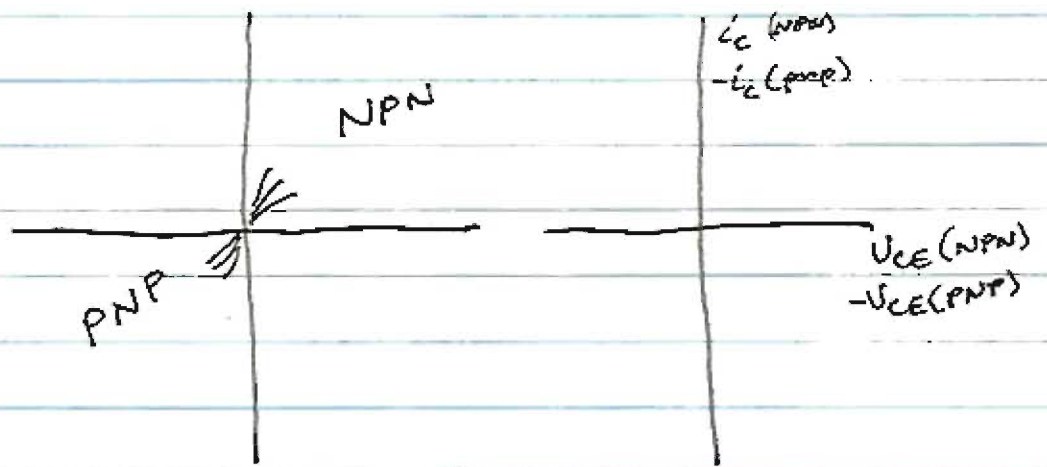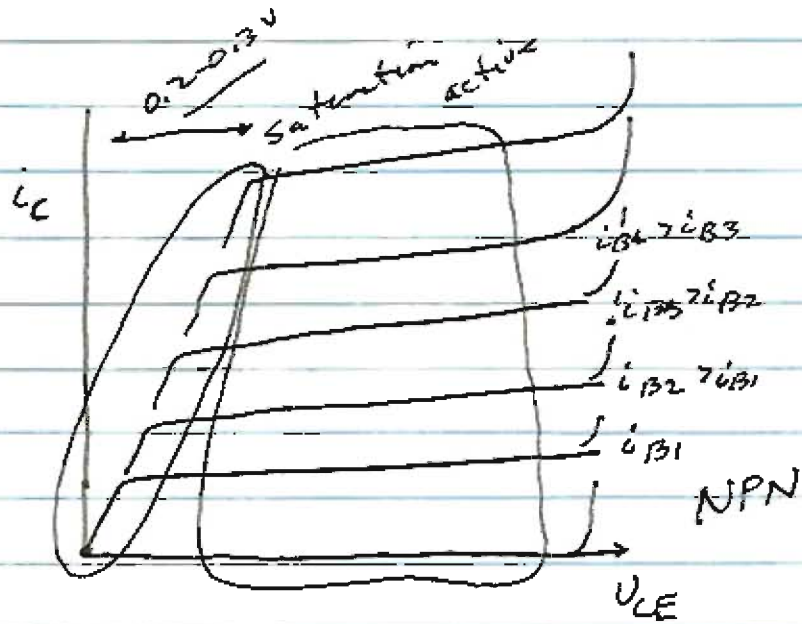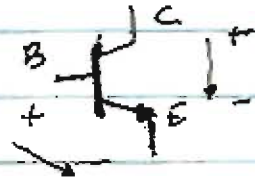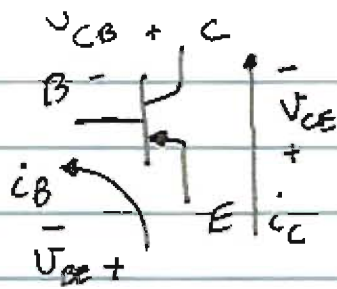


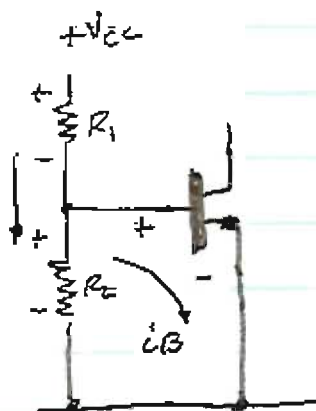

$$V_{R2} \approx V_{BE}$$

Problem


1. knee of exponential curve

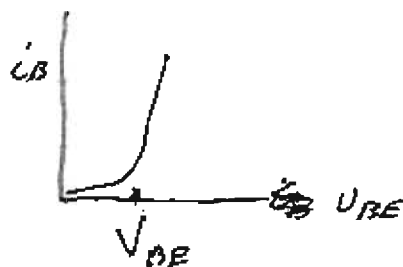

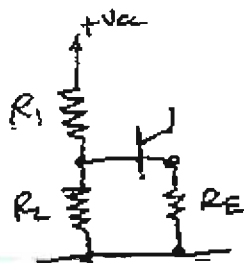
2. $I_C/I_B = \beta_{DC}$ varies widely
 $20 \leq \beta_{DC} \leq 400$


Fixed-bias unworkable unless "tuned".

Self-bias or combination of fixed & self req'd



$$V_{R2} = V_{BE} + (I_C + I_B)R_E$$

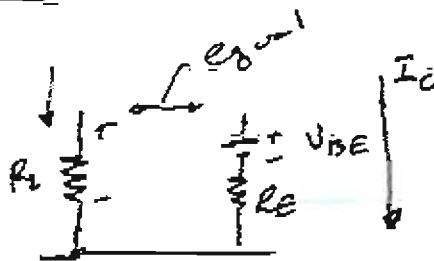

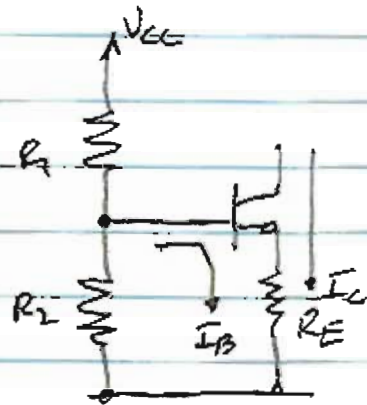

V_B (open)

$$\left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = V_{BB}$$

$$\frac{R_1 R_2}{R_1 + R_2} = R_{BB}$$

$$I_C = \beta_{DC} I_B$$

loop equation

$$-V_{BB} + R_{BB} I_B + V_{BE} + \underbrace{(I_B + I_C)}_{(1 + \beta_{DC}) I_B} R_E = 0$$

$$\left[R_{BB} + (1 + \beta_{DC}) R_E \right] I_B = V_{BB} - V_{BE}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_{BB} + (1 + \beta_{DC}) R_E}$$

observe that if $R_{BB} \ll (1 + \beta_{DC}) R_E$


$$I_B \approx \frac{V_{BB} - V_{BE}}{(1 + \beta_{DC}) R_E}$$

In practice make $R_{BB} \approx R_E$

$$I_C = \beta_{DC} I_B = \frac{(V_{BB} - V_{BE}) \beta_{DC}}{R_{BB} + (1 + \beta_{DC}) R_E}$$

If β_{DC} is large
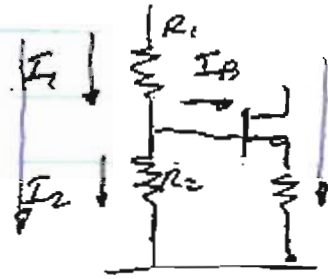
$$I_C = \frac{V_{BB} - V_{BE}}{R_E} = \frac{V_E}{R_E} \text{ (ohm's law)}$$



$I_1 = I_2 + I_B$
 If $I_B \ll I_2$
 $I_1 \approx I_2$ simple voltage divider
 β_{DC} is large

$$I_1 \approx I_2 = I_C = \beta_{DC} I_B$$


$$I_B = \frac{I_1}{\beta_{DC}}$$

$\therefore I_B$ is negligible if

$$I_1 = I_2 = I \approx I_C$$

"Gordon Rule"

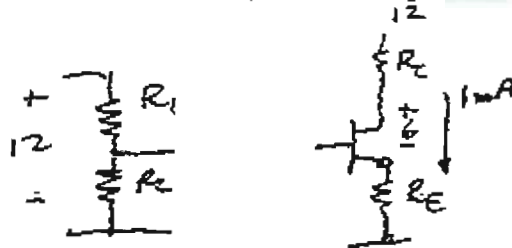Example: $I_C = 1 \text{ mA}$, $V_{CE} = 6 \text{ V}$, $V_{CC} = 12 \text{ V}$



Drop across $(R_E + R_C)$ is $12 - 6 = 6$

Assume $V_E = 2 \Rightarrow V_{RC} = 4 \text{ V}$

$$I_C R_E = 2 \Rightarrow R_E = \frac{2}{10^{-3}} = \underline{\underline{2 \text{ K}}}$$

$$V_B = V_{BE} + V_{RE} = 2.7$$

$$\left(\frac{R_2}{R_1 + R_2} \right) 12 = 2.7 \quad \left. \begin{array}{l} \frac{12}{R_1} = \frac{2.7}{2 \text{ K}} \\ R_1 = \frac{24 \text{ K}}{2.7} = \underline{\underline{8.9 \text{ K}}} \end{array} \right\}$$

10/15/01 6/6

$$V_c = V_{cc} - R_c I_c$$
$$8V = 12 - R_c \cdot 10^{-3}$$

$$R_c = R_c$$

$$R_c = 4K$$

$$V_c = 12 - (6+2)$$
$$= 4$$

