
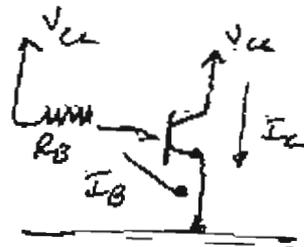


10/24/07

4/7

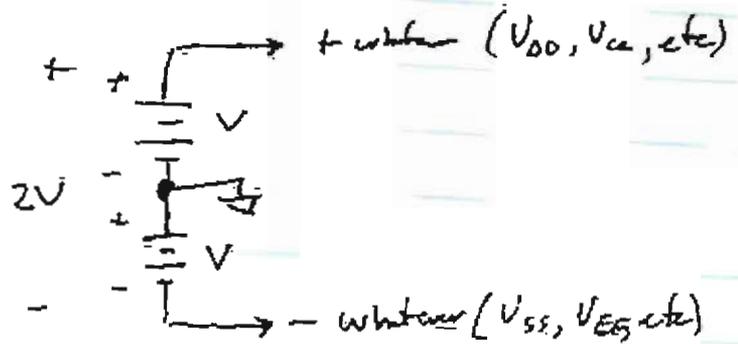

DC values

V_{CE} specified

I_C specified

β_{dc} device parameter

$$\beta_{dc} = \frac{I_C}{I_B}$$

"typical value"

$$I_B = \frac{I_C}{\beta_{dc}}$$

$$\beta_{dc} = 100$$

$$20 \leq \beta_{dc} \leq 400$$

measure I_C @ fixed I_B

eg, I_B = 10 μA


$$V_{CC} = R_{TB} I_B + V_{BE} ; V_{BE} \approx 700mV$$

$$\frac{V_{CC} - V_{BE}}{I_B} = R_{TB}$$

Measure I_C to determine actual value of β_{dc}

10/24/07

2/7

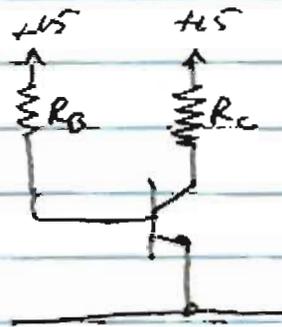

$R_B = 1.4M, I_B \approx 10\mu A$
 if $\beta_{dc} = 100, I_C = 1mA$


Choose $V_C = 10V$

$R_C = \frac{5}{10^{-3}} = 5K$

$V_C = V_{CC} - I_C R_C$

$15 - 5K I_C$

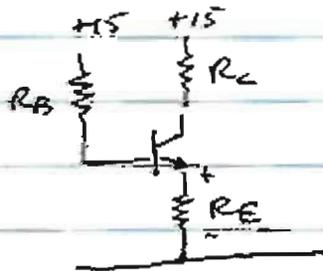if $I_C \rightarrow 3I_C$, then $V_C = 15 - 15 = 0$
 not working



$V_{CC} = R_B I_B + (I_B + I_C) R_E + V_{BE}$

$I_C = \beta_{dc} I_B$





$V_{CC} = R_B I_B + (1 + \beta_{dc}) R_E I_B + V_{BE} = 0$

$V_{CC} - V_{BE} = R_B I_B + (1 + \beta_{dc}) R_E I_B$

$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta_{dc}) R_E}$

$I_C = \beta_{dc} I_B = \frac{(V_{CC} - V_{BE}) \beta_{dc}}{R_B + (1 + \beta_{dc}) R_E}$

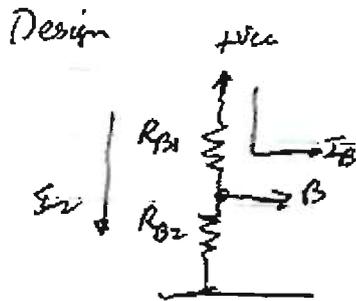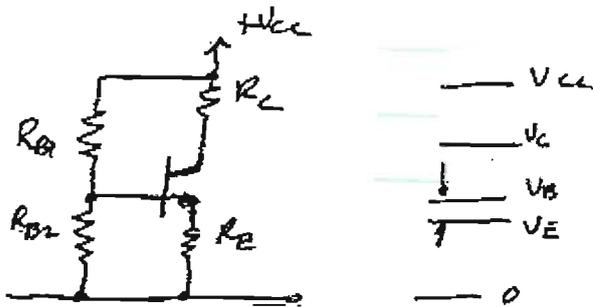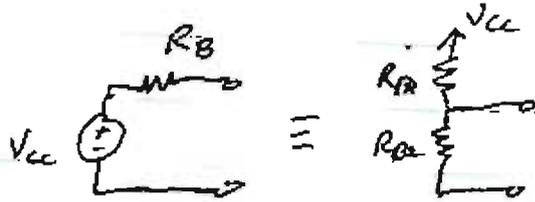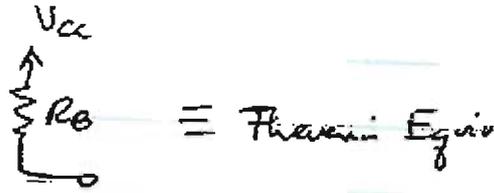$I_C \approx \frac{V_{CC} - V_{BE}}{R_E}$ if $\beta_{dc} \gg 1, R_B \approx R_E$



$$V_B = \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right) V_{CC} \quad \text{assume } I_B = 0$$

But for BJT $I_B \neq 0$. Next best thing negligible I_B w.r.t I_E .

$$\beta_{DC} I_B = I_C \quad \text{if } I_C \approx I_E$$

$$I_E = \beta_{DC} I_B, \text{ but } \beta_{DC} \gg 1. \text{ Works!}$$


$$I_E \approx I_C$$

$$\frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = R_E \quad \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right) V_{CC} = V_B$$

$$\frac{V_{CC}}{R_{B1} + R_{B2}} \approx I_E$$

10/24/07 9/7

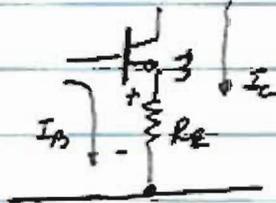Suppose $V_{CC} = 15$, $V_{CE} = 5$, $V_E = 3 \Rightarrow V_C = 8$
 $I_C = 10 \text{ mA}$



$$3 = V_E = R_E (1 + \beta) I_B$$

$$V_B = V_{BE} + V_E = 0.7 + 3 = 3.7$$

$$\text{Approx } R_E \frac{I_C}{\beta} \approx V_E$$

$$R_E \approx \frac{3}{10^{-2}} = 300 \Omega$$

$$R_B = 300 \Omega$$

$$\frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = 300$$

$$R_{B1} + R_{B2}$$


$$\frac{R_{B2}}{R_{B1} + R_{B2}} = \frac{V_B}{V_{CC}} = \frac{3.7}{15} = 0.246$$

$$R_{B1} = \frac{300}{0.246} \approx 1200 \Omega = 1.2 \text{ k}$$


$$R_{B2} = \frac{300 R_{B1}}{R_{B1} - 300} = \frac{(300)(1.2 \text{ k})}{1200 - 300} = 400 \Omega$$

$$R_{B1} R_{B2} = 300 R_{B1} + 300 R_{B2}$$


$$(R_{B1} - 300) R_{B2} = 300 R_{B1}$$

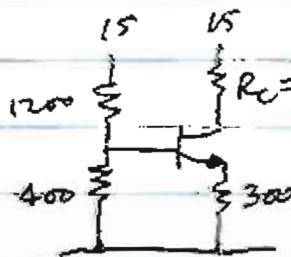

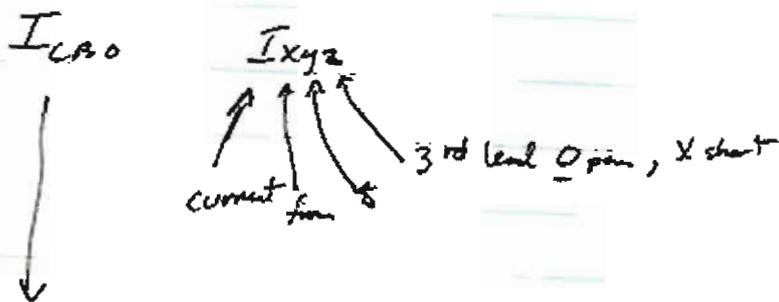
$$R_C = \frac{15 - 8}{10^{-2}} = 700 \Omega$$



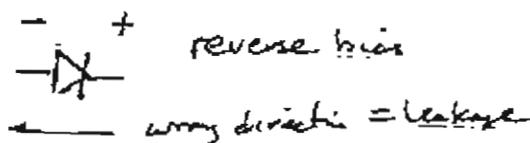Current from Collector to Base with emitter open



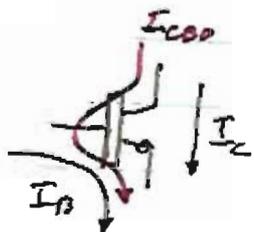
I_{CBO} is very temperature sensitive. Dramatic increase with increasing temperature.



I_B larger than designed by adding I_{CBO}

Circuit takes care of this too,

Suppose BJT is biased. For CE

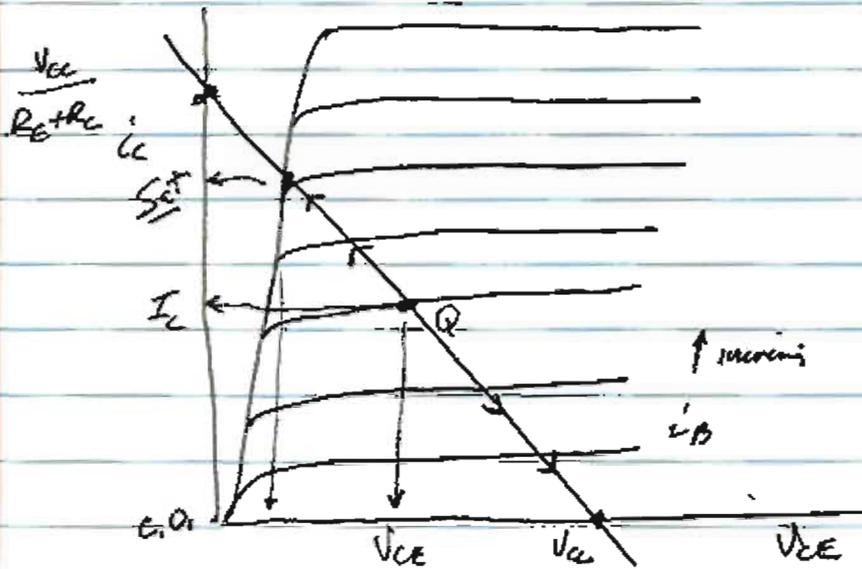

load line equation


$$V_{CC} = \underbrace{R_C I_C}_{R_C \text{ drop}} + \underbrace{R_E (1 + \beta I_C)}_{R_E \text{ drop}} + V_{CE}$$


$$\frac{1 + \beta I_C}{\beta I_C} \approx 1$$

$$V_{CC} = (R_C + R_E) I_C + V_{CE} \in \text{load line}$$

at saturation $V_{CC} = I_C (R_C + R_E) + 0$; $V_{CE} = 0$

at c.o. $V_{CE} = V_{CC}$; $I_C = 0$

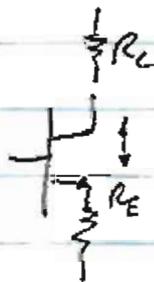

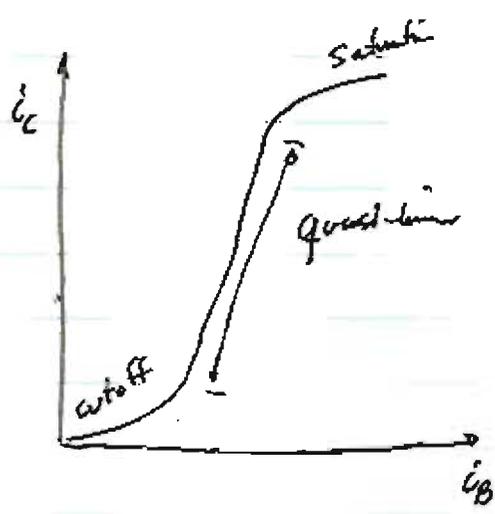

From prior plot

need small-signal parameters