

10/29/07 4/6

$\left. \begin{matrix} \log & \ln \\ 10^x & e^x \end{matrix} \right\} \text{math}$




$\left. \begin{matrix} \log \rightarrow \ln \\ \log_{10} \rightarrow \log \end{matrix} \right\} \text{pspic}$

$dB(V(RL:2)/V(RL:1))$





$$R_{in} = \frac{V_{in}}{I_{in}}$$

$$R_{out} = \frac{V_{out}}{I_{out}}$$

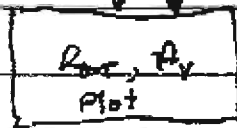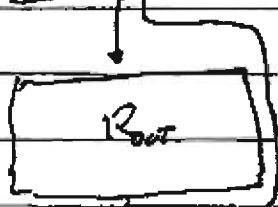
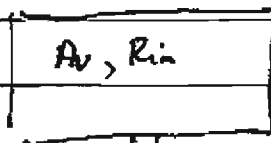




RL1 $V(RL:1)$ -
RL2 $V(RL:2)$ -

10/29/07 2/6

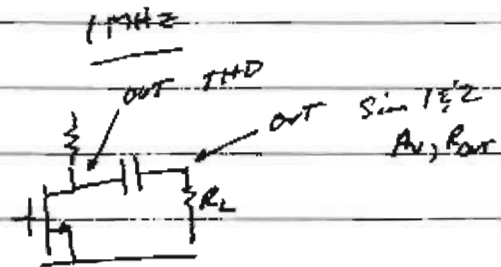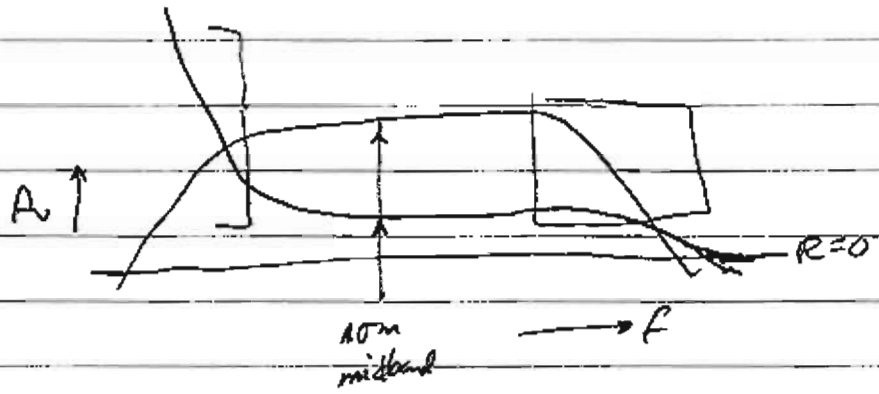

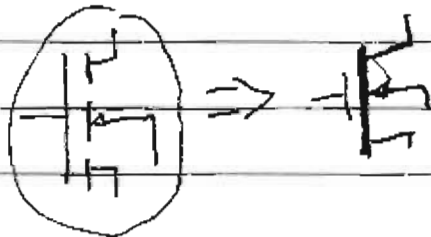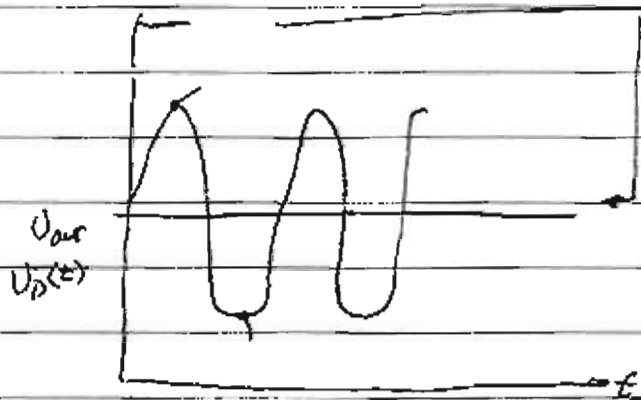DC component of $V_D(f) \equiv$ bias value




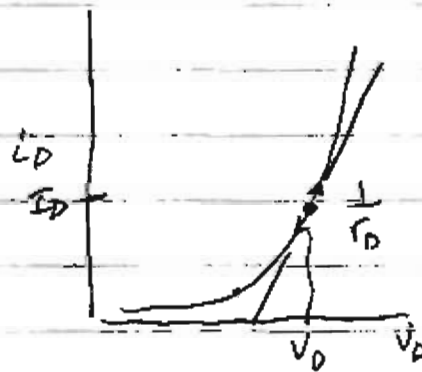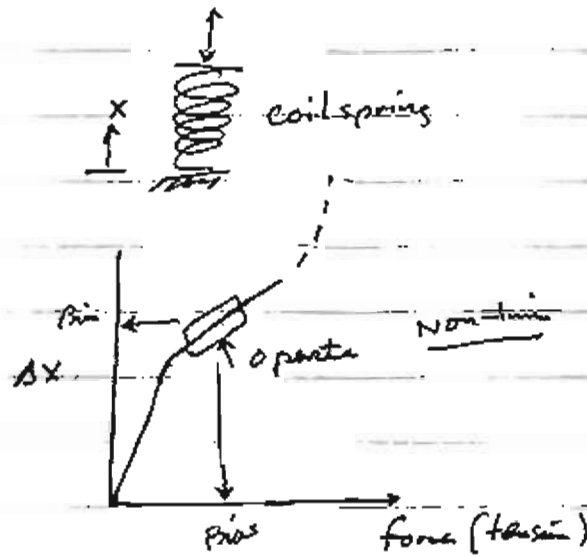

1. Bias calculation (dc) \rightarrow Q Point
2. determine linear portion @ Q Point
3. analysis via linear circuit theory

10/29/07

4/6

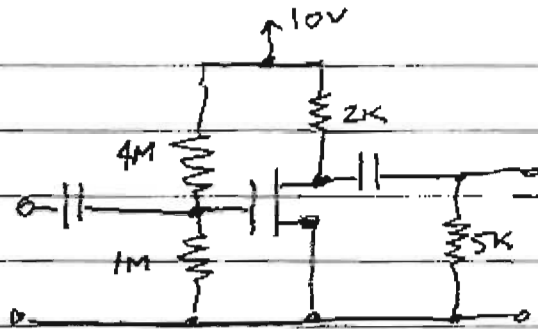


Bias: $I_G = 0$

$$V_G = \frac{1}{5} \cdot 10 = 2V, \quad I_{RG} = \frac{10}{500k} = 20\mu A$$

$$I_D = f(V_G)$$


$$V_D = V_{CC} - R_D I_D$$

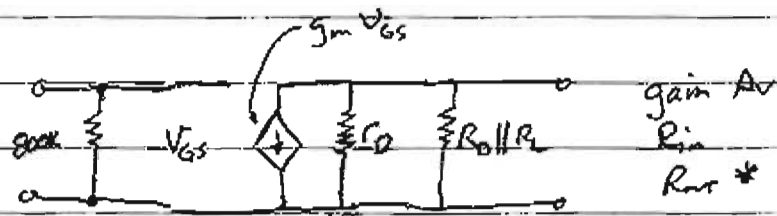

gain A_v
 R_{in}
 R_{out}^*



$$g_m = f(I_D, V_{GS}) \approx f(I_D)$$

$$@ ac \quad R = \frac{\partial V}{\partial I} = \frac{\partial V}{\partial I} \Big|_{dV=0}$$

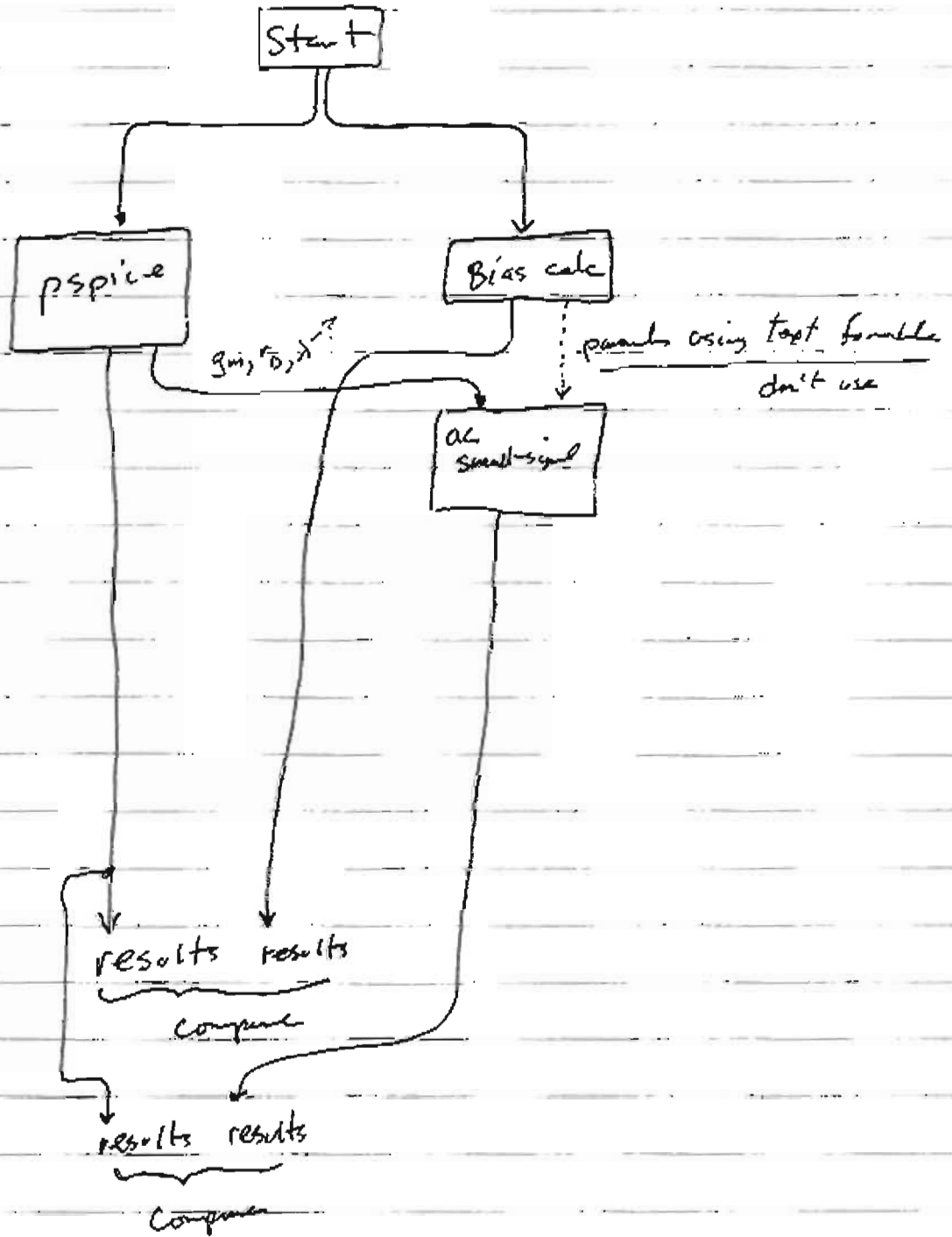

10/29/07

6/6

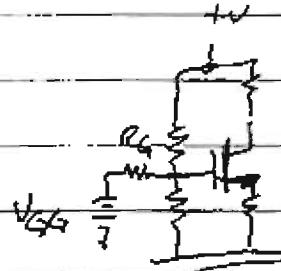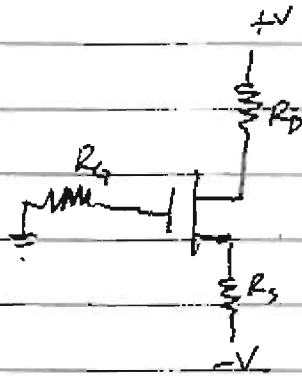

$V_G, V_S \Rightarrow V_{GS}$
 $V_{GS} \Rightarrow I_D \Rightarrow V_{DS}$

