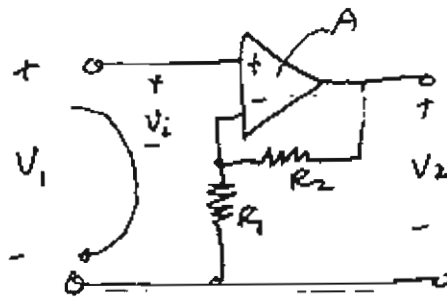


$$\frac{V_2}{V_1} = \frac{-\left(\frac{R_2}{R_1}\right)A}{1 + \left(\frac{R_2}{R_1+R_2}\right)A} \quad \text{finite } A$$

Limit  $A \rightarrow \infty \left[ \left(\frac{R_2}{R_1+R_2}\right)A \gg 1 \right]; \frac{V_2}{V_1} = -\frac{R_2}{R_1}$  inverting configuration



$$-V_1 + V_2 + \left(\frac{R_1}{R_1+R_2}\right)V_2 = 0; \quad V_1 = \frac{V_2}{A}$$


$$V_2 \left( \frac{1}{A} + \frac{R_1}{R_1+R_2} \right) = V_1$$

$$\frac{V_2}{V_1} = \frac{1}{\frac{1}{A} + \frac{R_1}{R_1+R_2}} \quad \text{non-inverting configuration}$$

Limit  $A \rightarrow \infty \quad \frac{V_2}{V_1} = \frac{R_1+R_2}{R_1} \geq 1$

Notice:

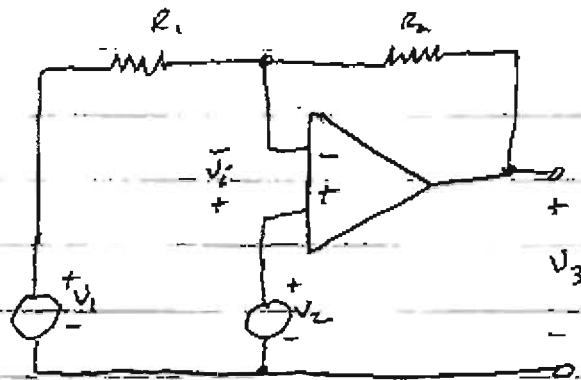For  $R_1=R_2$  inverting gain =  $-1 = \frac{1}{2} \cdot (-2) = -1$   
 non-inverting gain =  $2 = 1 \cdot (2) = 2$




By Superposition:

with  $A \rightarrow \infty$

$$V_3 = -V_1 \left( \frac{R_2}{R_1} \right) + V_2 \left( \frac{R_1 + R_2}{R_1} \right)$$

Virtual Ground

$$V_i = 0$$

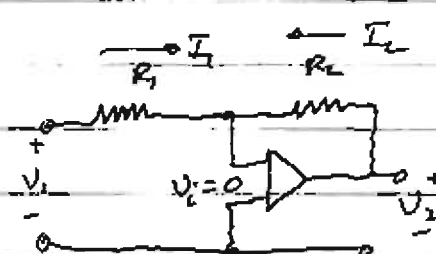

$$\frac{V_1}{R_1} = I_1, \quad \frac{V_2}{R_2} = I_2, \quad I_1 = -I_2$$


$$\frac{V_1}{R_1} = -\frac{V_2}{R_2} \Rightarrow \frac{V_2}{V_1} = -\frac{R_2}{R_1} \text{ Same as before}$$

Finite  $\neq 0$  value for  $V_2$

$$V_i = \frac{V_2}{A}, \quad A \rightarrow \infty, \quad V_i \rightarrow 0 \text{ but}$$

never ever = 0.

weighted sums

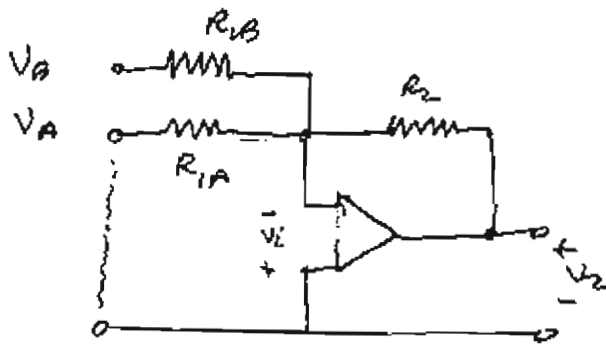

$$V_A = 0, V_B \neq 0, V_i \text{ across } R_{1A} \Rightarrow i_{1A} = 0$$

$$\frac{V_2}{V_B} = -\frac{R_2}{R_{1B}}$$

$$\frac{V_2}{V_A} = -\frac{R_2}{R_{1A}}$$


$$V_2 = -\left[ \left(\frac{R_2}{R_{1A}}\right)V_A + \left(\frac{R_2}{R_{1B}}\right)V_B + \dots + \left(\frac{R_2}{R_{1n}}\right)V_n \right]$$

negative gain (inverting) weighted summer


Ex

$$V_2 = -[2V_A + 3V_B + 5V_C]$$


Resistors make a non-unit summer

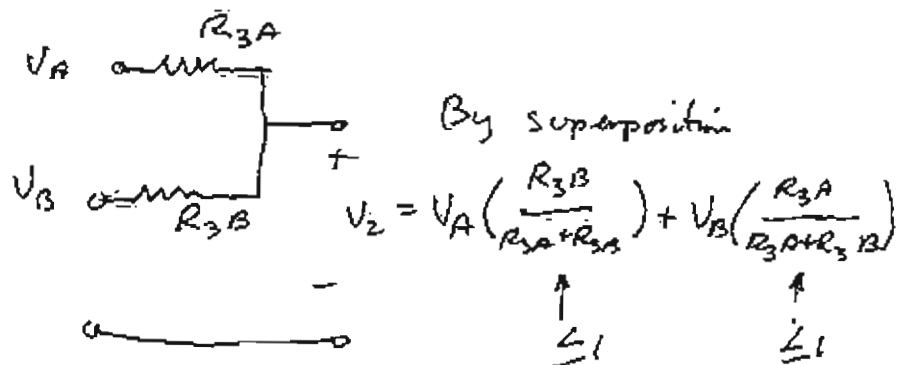
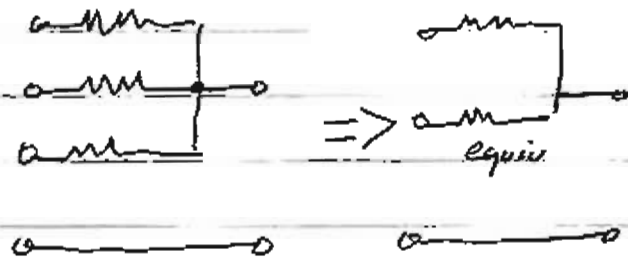
$$V_2 = \frac{1}{2}V_A + \frac{1}{2}V_B = \frac{1}{2}(V_A + V_B)$$



any number of branches

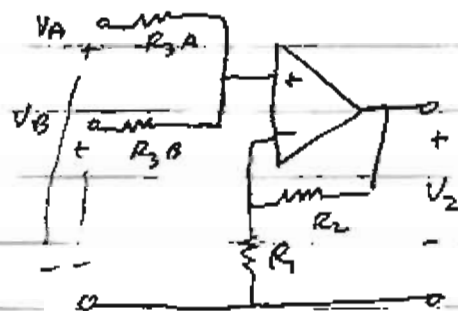


$$V_2 = \left( \frac{R_1 + R_2}{R_1} \right) \left[ \left( \frac{R_3B}{R_3A + R_3B} \right) V_A + \left( \frac{R_3A}{R_3A + R_3B} \right) V_B \right]$$


↑ overall gain  
 ↑ determine proportion

$$V_2 = 6V_A + 9V_B$$
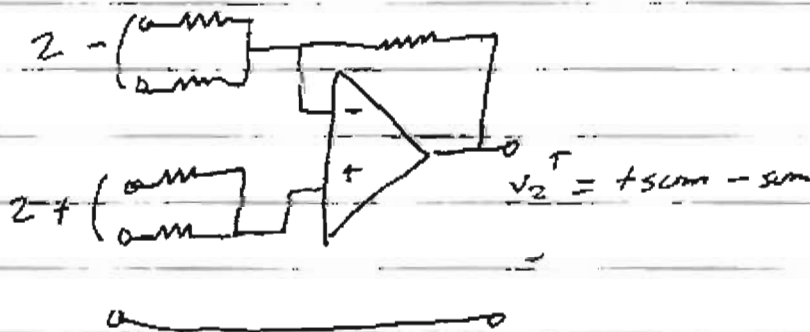
$$= (9) \left[ \frac{2}{3} V_A + V_B \right]$$



New Concept:

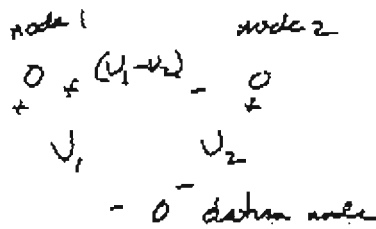


Propose

$$V_1 = V_{cm} + \frac{V_{diff}}{2}$$

$$V_2 = V_{cm} - \frac{V_{diff}}{2}$$

$V_{cm}$  = common-mode voltage

$V_{diff}$  = differential-mode voltage


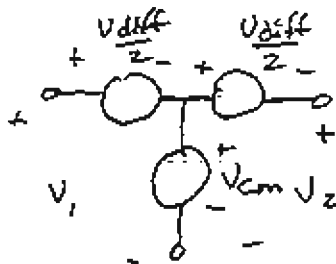


$$V_1 = V_{cm} + \frac{V_{diff}}{2}$$

$$V_2 = V_{cm} - \frac{V_{diff}}{2}$$



$$V_1 - V_2 = V_{diff}$$

Balanced vs Unbalanced connection

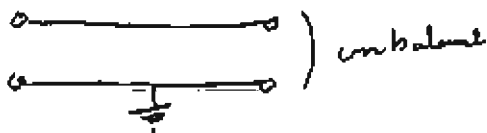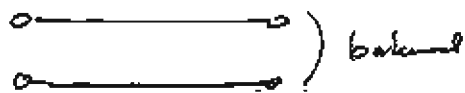


Unbalanced connection: power 120VAC

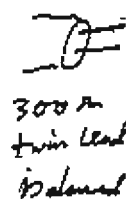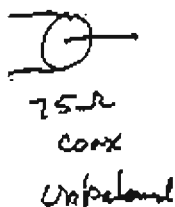balanced connection: telephone twisted pair, 300Ω twin lead



balun  
balanced-unbalanced

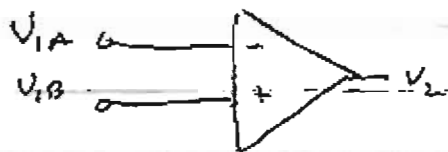

$$V_{1A} = V_{cm} + \frac{V_{diff}}{2}$$

$$V_{1B} = V_{cm} - \frac{V_{diff}}{2}$$

$V_2 = ?$  Ideally,

$$V_2 = K V_{diff} \quad \text{Reality}$$

$$V_2 = \underbrace{K_1 V_{cm}}_{\text{reject}} + \underbrace{K_2 V_{diff}}_{\text{preserve}}$$

measure of goodness:

good  
bad


0 ———  $\infty$   
bad ——— good

Common-mode Rejection Ratio (CMRR)

$$\frac{\text{differential gain}}{\text{common mode gain}}$$

Typically (1000 to 10,000)

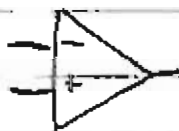differential amplifier vs. difference amplifier



inputs identical



inputs are not identical

11/19/07


7/B

Refer to gain expressions:

$$\frac{V_2}{V_1} = \frac{-\left(\frac{R_2}{R_1+R_2}\right)A}{1 + \left(\frac{R_1}{R_1+R_2}\right)A} \quad \text{vs} \quad \frac{V_2}{V_1} = \frac{A}{1 + \left(\frac{R_1}{R_1+R_2}\right)A}$$

(denominators same)

Block Diagram

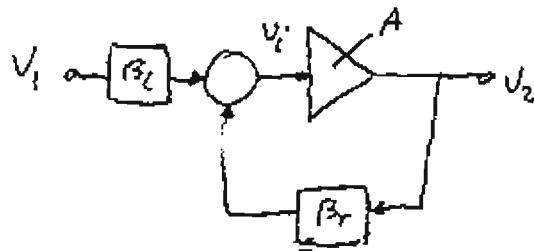


$$\frac{V_2}{V_1} = \frac{A\beta_i}{1 + A\beta_r}$$

inverting  $\beta_i = -\left(\frac{R_2}{R_1+R_2}\right)$

non-inverting  $\beta_i = +\left(1\right)$

$$\beta_r = \frac{R_1}{R_1+R_2}$$

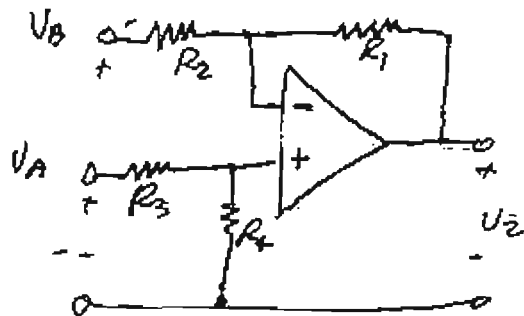

$$V_2 = \frac{A[\beta_i V_B + \beta_r V_A]}{1 + \beta_r A}$$

$$V_2 = A \left[ \frac{\beta_i V_B + \beta_r V_A}{1 + \beta_r A} \right]$$

want  $V_2 = K(V_A - V_B)$

Establish amp gain with  $R_1$  &  $R_2$   
compensate for gain with  $R_3$  &  $R_4$

Example  $R_1 = R_2 = R_3 = R_4$

$$\begin{aligned}V_2 &= V_B \left( \frac{-1}{1} \right) + V_A \left( \frac{1}{2} \right) (2) \\ &= V_A - V_B \quad \text{difference amp}\end{aligned}$$