

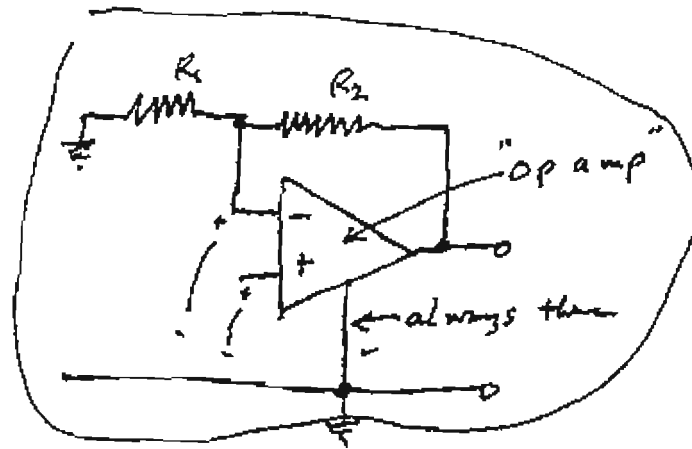
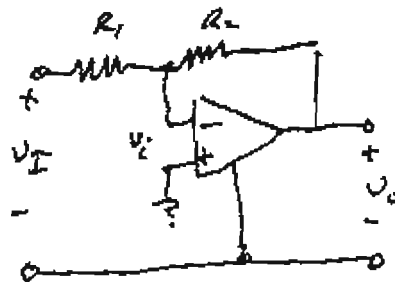


11/26/07 1/8

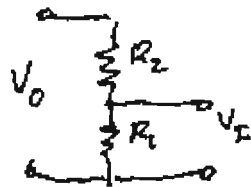


amplifier circuit

power supplies = 'rails'

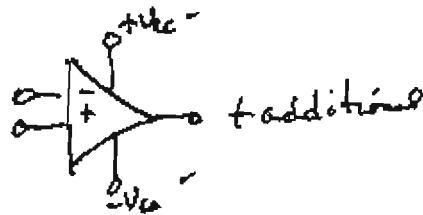

$$\left[\left(\frac{R_2}{R_1 + R_2} \right) V_i + \left(\frac{R_1}{R_1 + R_2} \right) V_o \right] A = V_o$$
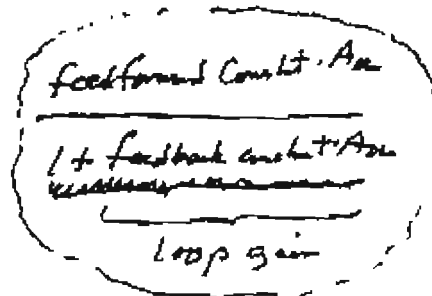
$$\Rightarrow \frac{V_o}{V_i} = - \frac{\left(\frac{R_2}{R_1 + R_2} \right) A}{1 + \left(\frac{R_1}{R_1 + R_2} \right) A}$$




closed loop gain

A_{ol} = open-loop gain

11/26/07

2/8

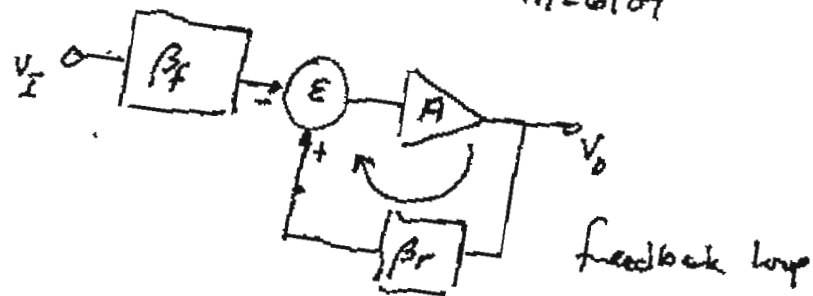

- β_f = feedforward constant
 β_r = feedback constant
 A_{ol} = open-loop gain (op amp) "A"
 $-\beta_f A$ = open-loop gain (circuit)
 $\beta_r A$ = loop gain
 $\frac{V_O}{V_I} = \frac{-\beta_f A}{1 + \beta_r A}$ = closed loop gain

$$\text{Closed-loop gain} = \frac{\text{open loop gain}}{1 + \text{loop gain}}$$

Non-inverting gain by inspection (no diagram)

$$\Rightarrow \frac{V_O}{V_I} = \frac{A}{1 + \left(\frac{R_1}{R_1 + R_2}\right)A}$$

$$\lim_{A \rightarrow \infty} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$

Finite gain

inverting $A \rightarrow 0$ $\frac{V_O}{V_I} \rightarrow 0$
 limit

non-inverting $A \rightarrow 0$ $\frac{V_O}{V_I} \rightarrow 0$
 limit



$\beta_r A \gg 1$, then $A \rightarrow \infty$

$\beta_r A \approx 1$, < 1 , then use formula

Other derivations

4/26/07 3/8

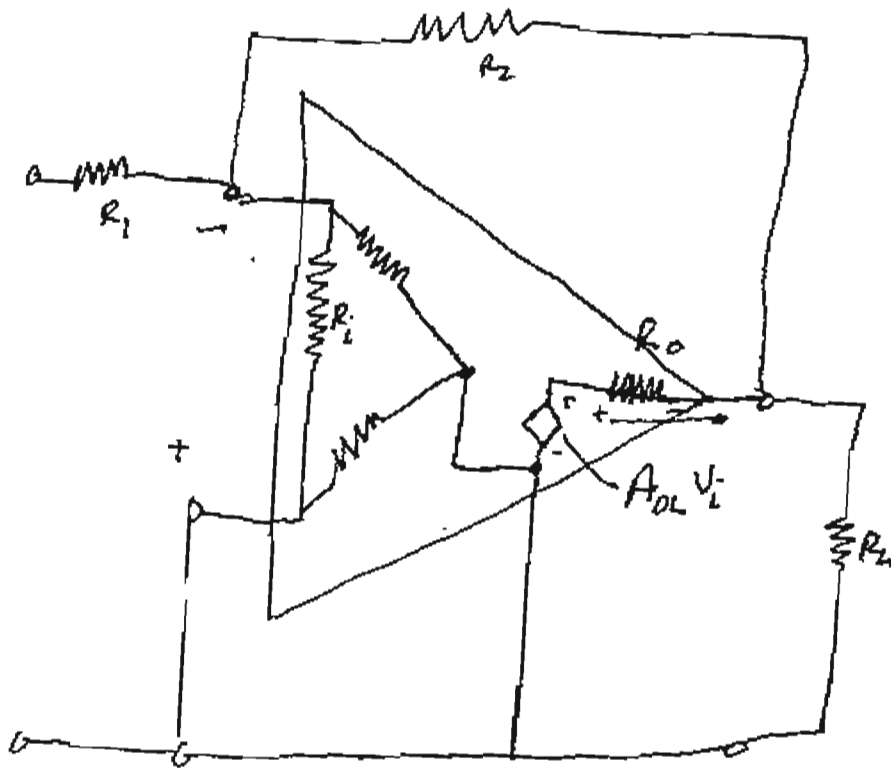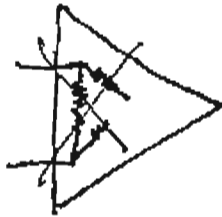
- ✓ 1. finite input resistance
- ✓ 2. non-zero output resistance
- 3. finite bandwidth
- ✓ 4. finite gain
- 5. other bias considerations




11/26/07

4/8

gain-bandwidth product = constant

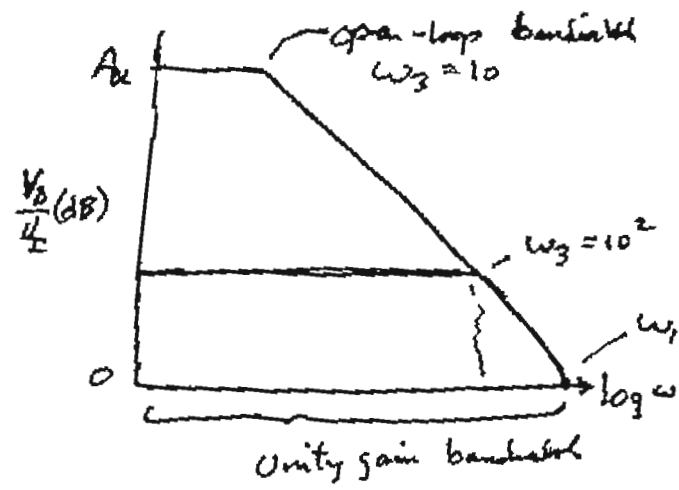


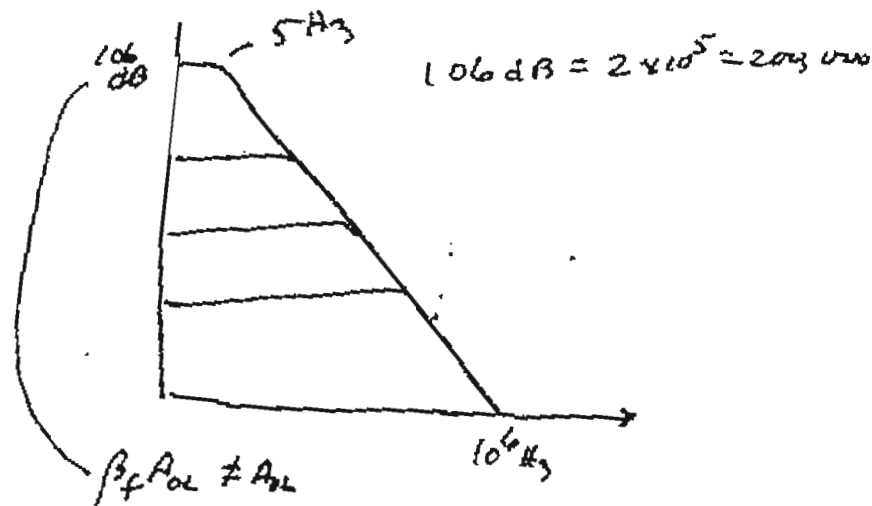$A_{OL} = 10^3$
 $\omega_1 = 10^5 > 10^4$
 $\omega_3 = 10$
 closed loop gain = $100 = 10^2$
 $\omega_3 = 100$



open loop gain = $A(s) = \frac{A_0}{1 + s/\omega_0} = \frac{A_0 \omega_0}{s + \omega_0}$

"dc gain" = low freq limit gain = A_0

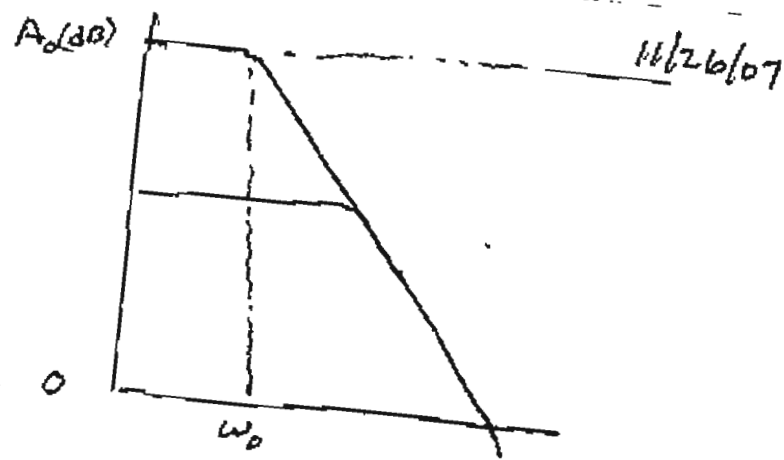

5/8

$$\begin{aligned} \frac{V_o}{V_i} &= \frac{A(s)}{1 + \frac{R_1}{R_1 R_2} A(s)} = \frac{A_0 \omega_0}{s + \omega_0} \cdot \frac{1}{1 + \beta_r \frac{A_0 \omega_0}{s + \omega_0}} \\ &= \frac{A_0 \omega_0}{(s + \omega_0) + \beta_r A_0 \omega_0} = \frac{A_0 \omega_0}{s + (1 + \beta_r A_0) \omega_0} \\ &= \frac{A_0 \omega_0}{s + \underbrace{(1 + \beta_r A_0) \omega_0}_{\text{new BW}}} \end{aligned}$$

new band width = old bandwidth $(1 + \beta_r A_0)$

$$\text{new dc gain} = \text{old dc gain} = \frac{A_0}{1 + \beta_r A_0}$$

dc went down by $1 + \beta_r A_0$

bandwidth up by $1 + \beta_r A_0$

gain-bandwidth product = constant

$$\text{inverting gain } R_i' = R_i / (1 + \beta_r A)$$

$$R_o' = R_o / (1 + \beta_r A)$$

$$\text{non-inverting gain } R_i' = R_i (1 + \beta_r A)$$

$$R_o' = R_o / (1 + \beta_r A)$$

Unprimed = without feedback

primed = with feedback

11/26/07

6/8

$$R_0 = 200 \Omega$$

$$A_{OL} = 200,000$$


$$A_{CL} = 10$$


$$\text{Loop gain} \approx 20,000$$

$$R_0' = \frac{200}{20,000} = \underline{\underline{0.01 \Omega}}$$


$$R_i \approx 20,000 \Omega$$
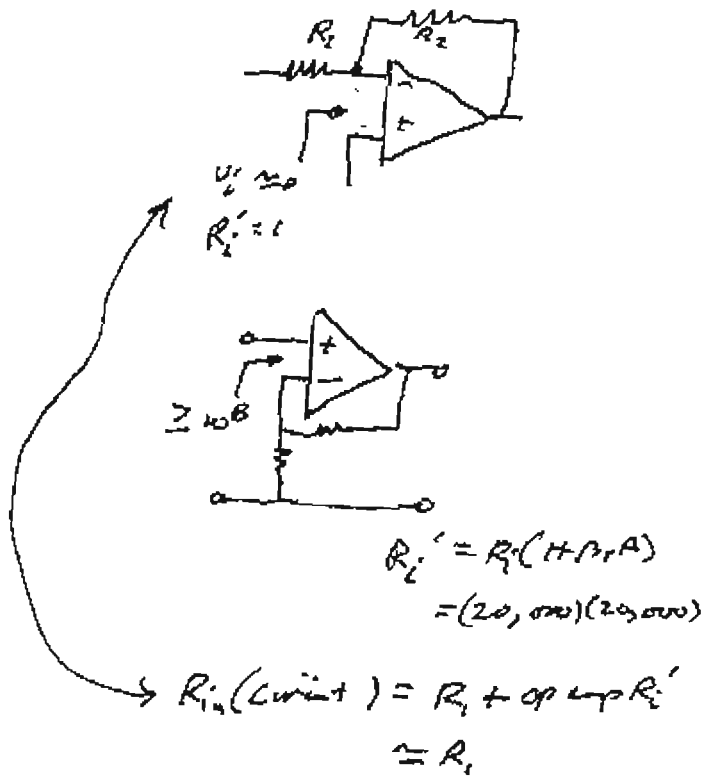
$$R_i' = \frac{20,000}{20,000} = 1 \Omega$$



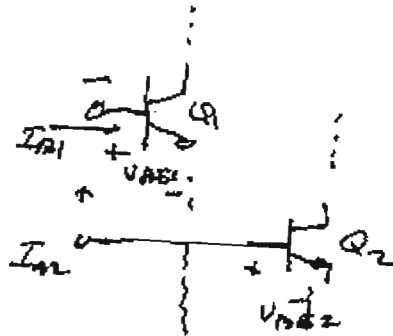

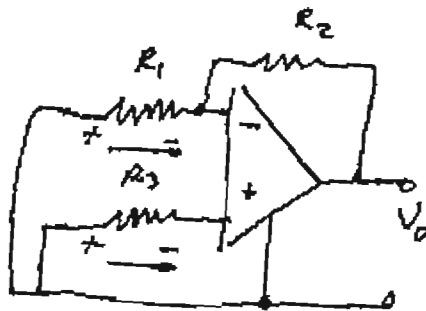$I_{B1} \neq I_{B2}$
 ~~$V_{BE1} \neq V_{BE2}$~~
 $V_{BE1} \neq V_{BE2}$
 $\therefore I_{C1} \neq I_{C2}$



Adjust \$R_1, V, R_3\$ to give \$V_o = 0\$

Drop \$R_1 \ge R_3\$ or \$R_1 \le R_3\$ \$V_o\$ goes + or -


equivalent input offset (includes both \$V, I\$)

$$V_{os} = \frac{V_o}{A_{ol}} \text{ with no input}$$

Integrator

operation in Op-amp Amplifier





first

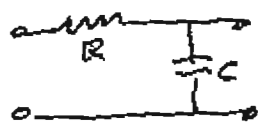

$$V_c = R i + \int i dt \quad i = I_0 e^{-t/RC}$$

$\underbrace{\hspace{1.5cm}}_{V_o}$

last

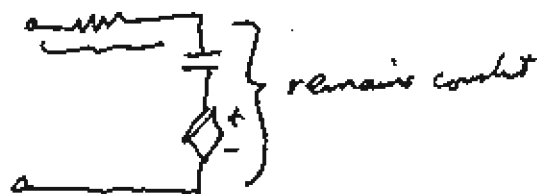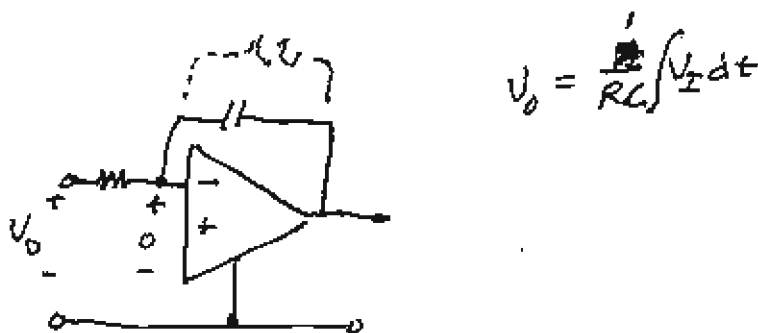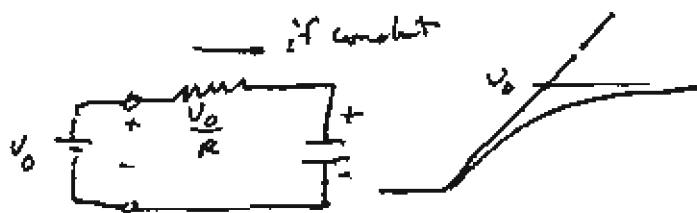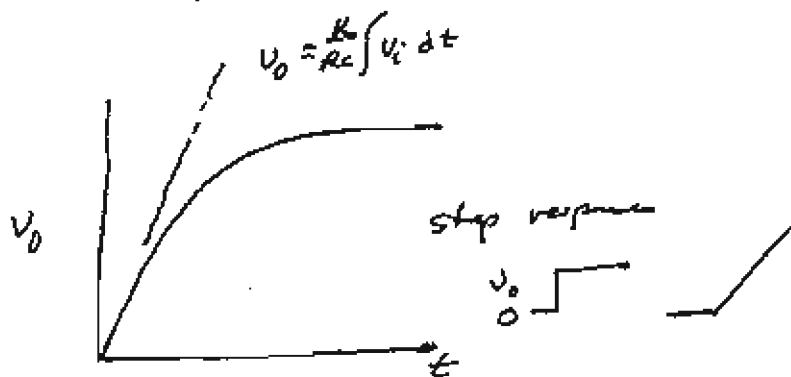

Analog Computer