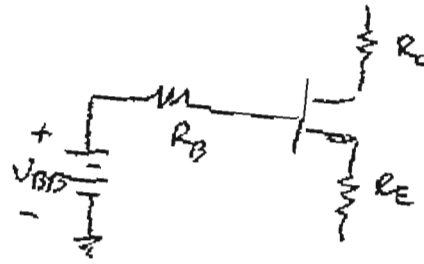


12/5/07

1/2




$$I_B = \frac{V_{BB} - V_{BE}}{R_B + (1 + \beta)R_E}$$

$$I_C = \beta I_B$$

$$I_C = \frac{(V_{BB} - V_{BE})\beta}{R_B + (1 + \beta)R_E}$$
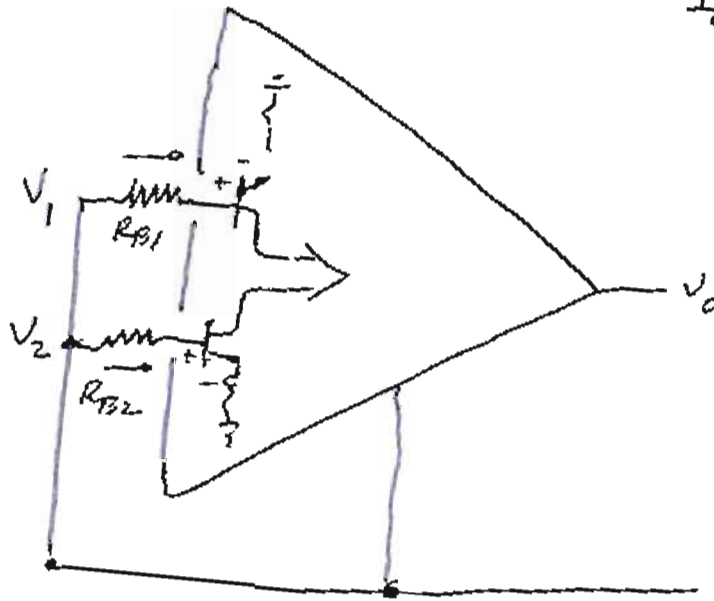
$$I_C (V_{BB} \beta) = I_C (V_{BE}) \beta$$



$$I_{C1} = \frac{(V_{BB} - V_{BE1})\beta_1}{D}$$

$$I_{C2} = \frac{V_{BB} - V_{BE2}}{D}$$

$$I_{C1} = I_{C2}$$

0 V in \rightarrow 0 V out

$$V_{BE1} = V_{BE2}$$

$$\beta_1 = \beta_2$$

or

$$V_{BE1} = V_{BE2}$$


$$I_{B1} = I_{B2}$$

not in reality

12/5/07


2/2

V_o



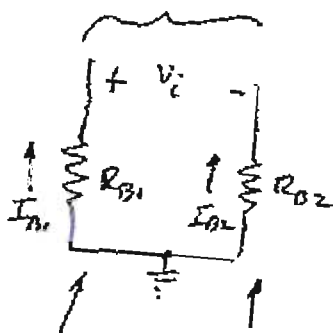


If $V_o \neq 0$ with inputs grounded then it appears that there is an input.

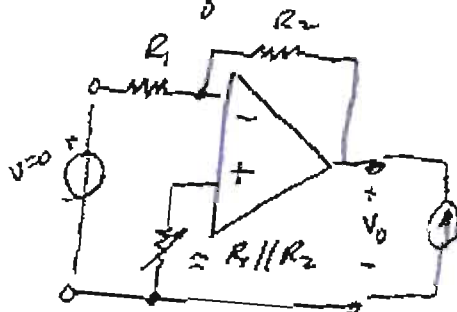adjust create a $-V_i$ to counteract the equivalent $+V_i$ that cause offset.



$$V_o = K V_i + K_2 \frac{E}{2}$$

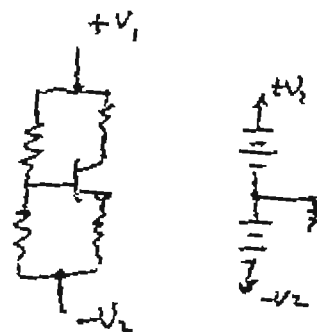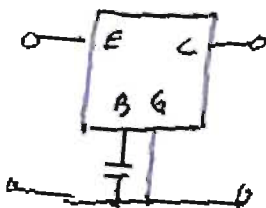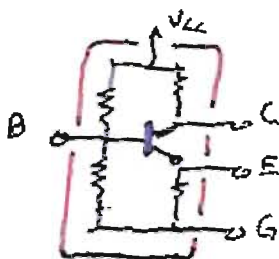

$$V_1 = 12, V_2 = 3, V_1 - V_2 = 15$$

$$\left. \begin{array}{l} V_B = 5 \\ V_E = 4.3 \\ V_C = 9 \end{array} \right\} 0 \text{ to } 15$$

$$\left. \begin{array}{l} V_B = 2 \\ V_E = 1.3 \\ V_C = 6 \end{array} \right\} -3 \text{ to } 12$$

$$+5 \rightarrow +3 \Delta = 12$$

$$\left. \begin{array}{l} V_B = -7 \\ V_E = -7.57 \\ V_C = -3 \end{array} \right\} -12 \text{ to } +3$$