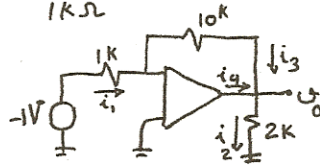


2.16

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \Rightarrow V_o = -1 \times \frac{10 \text{ k}\Omega}{1 \text{ k}\Omega} = 10 \text{ V}$$

$$i_2 = \frac{V_o}{2 \text{ k}\Omega} = 5 \text{ mA}$$

$$i_1 = i_3 = \frac{V_o}{10 \text{ k}\Omega} = 1 \text{ mA}$$



$$i_4 = i_2 - i_3 = 4 \text{ mA} \quad \text{This additional current comes from the output of the op-amp.}$$

2.17

$$|\text{Gain}| = \frac{R_2}{R_1} = \frac{R_2 (1 + \frac{x}{100})}{R_1 (1 + \frac{x}{100})} \approx \frac{R_2}{R_1} (1 \pm \frac{2x}{100})$$

$\Rightarrow 2x\%$ is the tolerance on the closed loop gain (G).

$$G = -100 \text{ V/V}, x = 5 \Rightarrow -110 < G < -90$$

or more precisely: $-100 \times \frac{105}{95} < G < -100 \times \frac{95}{105}$
 $-110.5 < G < -90.5$

2.18

$$G = \frac{V_o}{V_i} = -\frac{R_2}{R_1} \Rightarrow \frac{R_2}{R_1} = \frac{5}{15}$$

$$V_i = 0 \text{ V}, V_2 = V_o = 5 \text{ V}$$

$$\text{For } \pm 1\% \text{ on } R_1, R_2: R_1 = 15 \pm 0.15 \text{ k}\Omega$$

$$R_2 = 5 \pm 0.05 \text{ k}\Omega$$

$$V_o = V_i \frac{R_2}{R_1} = 15 \frac{R_2}{R_1} \Rightarrow 15 \times \frac{4.95}{15.15} \leq V_o \leq 15 \times \frac{5.05}{14.85}$$

$$\Rightarrow 4.9 \text{ V} \leq V_o \leq 5.1 \text{ V}$$

$$\text{For } V_i = -15 \pm 0.15 \text{ V} \quad \frac{14.85 \times 4.95}{15.15} \leq V_o \leq \frac{15.15 \times 5.05}{14.85}$$

$$\Rightarrow 4.85 \text{ V} \leq V_o \leq 5.15 \text{ V}$$

2.19

$$V_i = -\frac{V_o}{A} = -\frac{V_o}{200}$$


$$\frac{V_o}{V_i} = 50 \text{ V/V}$$

$$\frac{V_i - (-\frac{V_o}{A})}{R_1} = \frac{(-\frac{V_o}{A} - V_o)}{100 \text{ k}\Omega} \Rightarrow R_1 = 100 \text{ k}\Omega \times \frac{\frac{V_o}{200} - V_o}{-\frac{V_o}{200} - V_o}$$

$$\Rightarrow R_1 = 100 \text{ k}\Omega \times \frac{3}{201} = 1.49 \text{ k}\Omega$$

$$\text{shunt Resistor } R_a: R_a \parallel 2 \text{ k}\Omega = 1.49 \text{ k}\Omega$$
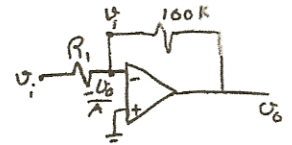
$$\frac{R_a \times 2}{R_a + 2} = 1.49 \Rightarrow R_a = 5.84 \text{ k}\Omega$$




2.20

a)

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \Rightarrow -100 \text{ V/V} = -\frac{R_2}{1 \text{ k}\Omega} \Rightarrow R_2 = 100 \text{ k}\Omega$$

$$\text{b) } A = 1000 \text{ V/V}$$

$$V_i = -\frac{V_o}{A}$$

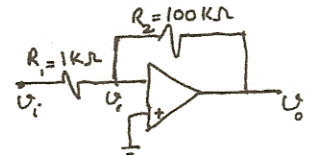

$$\frac{V_i - V_i}{R_1} = \frac{V_i - V_o}{R_2}$$

$$\frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + (1 + \frac{R_2}{R_1})/A} = \frac{-100}{1 + \frac{101}{1000}} = -90.8 \text{ V/V}$$

$$\Rightarrow \frac{V_o}{V_i} = 90.8 \text{ V/V}$$

$$\text{c) Assume } R'_1 = R_x \parallel R_1 \text{ when } R_1 = 1 \text{ k}\Omega$$

$$\frac{V_o}{V_i} = 100 \text{ V/V}$$

$$\frac{V_i - V_i}{R'_1} = \frac{V_i - V_o}{R_2} \Rightarrow R'_1 = R_2 \times \left(\frac{V_o}{100} - \frac{V_o}{1000} \right) / \left(-\frac{V_o}{1000} - V_i \right)$$

$$R'_1 = \frac{1 - 0.1}{1.001} = 0.899 \text{ k}\Omega = \frac{R_1 R_x}{R_1 + R_x} = \frac{R_x}{1 + R_x}$$

$$\Rightarrow R_x = 8.9 \text{ k}\Omega \approx 8.87 \text{ k}\Omega \pm 1\%$$

2.21

Voltage of the inverting input terminal

Cont.

2.27

$$|G| = \frac{R_2/R_1}{1 + \frac{1 + R_2/R_1}{A}} \quad \begin{matrix} A \rightarrow A(1 - \frac{x}{100}) \\ G \rightarrow G' \end{matrix}$$

$$|G'| = \frac{R_2/R_1}{1 + \frac{1 + R_2/R_1}{A(1 - \frac{x}{100})}}$$

$$\text{For } |G'| = |G| (1 - \frac{x}{100})$$

$$\frac{R_2/R_1}{1 + \frac{1 + R_2/R_1}{A(1 - \frac{x}{100})}} = \frac{R_2/R_1}{1 + \frac{1 + R_2/R_1}{A}} (1 - \frac{x}{100})$$

$$1 + \frac{1 + R_2/R_1}{A(1 - \frac{x}{100})} = (1 + \frac{1 + R_2/R_1}{A}) (1 - \frac{x}{100})$$

$$1 - \frac{x}{100} + \frac{1 + R_2/R_1}{A} \frac{1 - x/100}{1 - x/100} = 1 + \frac{1 + R_2/R_1}{A}$$

$$\frac{1 + R_2/R_1}{A} \frac{1 - x/100 - 1 + x/100}{1 - x/100} = \frac{x}{100}$$

$$A = \frac{1 + K}{1 - \frac{x}{100}} (1 + R_2/R_1) = (\frac{K-1}{1 - \frac{x}{100}}) (1 + \frac{R_2}{R_1})$$

$$\text{For } \frac{R_2}{R_1} = 100, x = 50, K = 100: A = \frac{99}{0.5} \times 101 = 19998$$

$$A \approx 2 \times 10^4 V/V$$

Thus for $A = 2 \times 10^4 V/V$, a reduction of 50% results in only 0.5% reduction of the closed loop gain whose nominal value is $\frac{R_2}{R_1} (100)$.

2.28

From the results of example 2.2, the gain of the circuit in fig. 2.8 is given by:

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} (1 + \frac{R_4}{R_2} + \frac{R_4}{R_3})$$

$$\text{For } R_1 = R_2 = R_4 = 1M\Omega \Rightarrow \frac{V_o}{V_i} = -(1 + 1 + \frac{1}{R_3})$$

$$a) \frac{V_o}{V_i} = -10 V/V \Rightarrow 10 = 2 + \frac{1}{R_3} \Rightarrow R_3 = \frac{1}{8} M\Omega = 125 K\Omega$$

$$b) \frac{V_o}{V_i} = -100 V/V \Rightarrow 100 = 2 + \frac{1}{R_3} \Rightarrow R_3 = \frac{1}{98} M\Omega = 10.2 K\Omega$$

$$c) \frac{V_o}{V_i} = -2 V/V \Rightarrow 2 = 2 + \frac{1}{R_3} \Rightarrow R_3 = \infty: \text{eliminate } R_3.$$

2.29

$$R_2/R_1 = 1000, R_2 = 100K\Omega \Rightarrow R_1 = 100\Omega$$

$$a) R_{in} = R_1 = 100\Omega$$

$$b) \frac{V_o}{V_i} = -\frac{R_2}{R_1} (1 + \frac{R_4}{R_2} + \frac{R_4}{R_3}) = -1000$$

$$\text{If } R_2 = R_1 = R_4 = 100K \Rightarrow R_3 = \frac{100K}{1000-2} \approx 100\Omega$$

$$R_{in} = R_1 = 100K\Omega$$

2.30

$$V_x = 0 - i_1 R_2, i_1 = \frac{V_i}{R_1} \Rightarrow V_x = -V_i \frac{R_2}{R_1}$$

$$\frac{V_x}{V_i} = -\frac{R_2}{R_1}$$

$$V_x = V_o \frac{R_2 || R_3}{R_2 || R_3 + R_4} = V_o \frac{R_2 R_3}{R_2 R_3 + R_4 R_2 + R_4 R_3}$$

$$\frac{V_o}{V_x} = \frac{R_2 R_3 + R_2 R_4 + R_3 R_4}{R_2 R_3} = 1 + \frac{R_4}{R_3} + \frac{R_4}{R_2}$$

$$\frac{V_o/V_x}{V_i/V_x} = \frac{V_o}{V_i} = \frac{(1 + R_4/R_3 + R_4/R_2)}{-R_1/R_2} \Rightarrow$$

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} (1 + \frac{R_4}{R_3} + \frac{R_4}{R_2})$$

2.31

$$a) R_1 = R$$

$$R_2 = R || R + \frac{R}{2} = \frac{R}{2} + \frac{R}{2} = R$$

$$R_3 = R_2 || R + \frac{R}{2} = R || R + \frac{R}{2} = R$$

$$R_4 = R_3 || R + \frac{R}{2} = R || R + \frac{R}{2} = R$$

$$b) V_i R I = R I_1 \Rightarrow I_1 = I$$


$$I_{12} = I + I = 2I \Rightarrow V_1 + 2I \times \frac{R}{2} = R I_2$$

$$R I + R I = R I_2 \Rightarrow I_2 = 2I$$

$$I_3 = I_2 + I_{12} = 4I \Rightarrow V_2 + 4I \times \frac{R}{2} = R I_3$$

$$R \times 2I + 4I \times \frac{R}{2} = R I_3 \Rightarrow I_3 = 4I, I_4 = -(4I + 4I)$$

$$I_4 = -8I$$

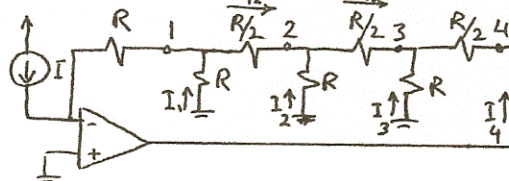

Cont.

$$c) V_1 = I_1 R = IR$$

$$V_2 = I_2 R = 2IR$$

$$V_3 = -I_3 R = -4IR$$

$$V_4 = -I_1 R + I_4 \frac{R}{2} = -4IR - 8I \frac{R}{2} = -8IR$$

2.32

$$a) I_1 = \frac{1V}{10k\Omega} = 0.1mA$$

$$I_2 = I_1 = 0.1mA, I_2 \times 10k\Omega = I_3 \times 100\Omega \Rightarrow I_3 = 10^{-4}A$$

$$V_x = 10mA \times 100\Omega = 1V$$

$$b) V_x = R_L I_L + V_0, I_L = I_2 + I_3 = 10.1mA$$

$$1V = R_L \times 10.1mA + V_0$$

$$R_L = \frac{1-V_0}{10.1} \Rightarrow R_{Lmax} = \frac{1-V_{0min}}{10.1} = \frac{14}{10.1}$$

$$c) 100\Omega \leq R_L \leq 1k\Omega$$

$$I_L \text{ stays fixed at } 10.1mA$$


$$V_0 = V_x - R_L I_L = 1 - R_L \times 10.1 \Rightarrow -9.1V \leq V_0 \leq -0.01V$$

2.33

$$a) \frac{i_L}{i_I} = 20 \Rightarrow i_L = 20i_I$$

$$-10k\Omega \times i_I = R(i_I - i_L)$$
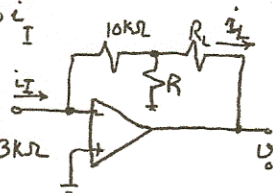
$$R = \frac{10k\Omega \times i_I}{20i_I - i_I} = 0.53k\Omega$$



$$b) R_L = 1k\Omega, -12V \leq V_0 \leq 12V$$

$$V_0 = R_L i_L + 10k\Omega \times i_I = i_I (1k\Omega \times \frac{i_L}{i_I} + 10k\Omega)$$

$$V_0 = i_I (1 \times 20 + 10) = 30i_I$$


$$i_I = \frac{V_0}{30} \Rightarrow \frac{-12}{30} \leq i_I \leq \frac{12}{30} \Rightarrow -0.4mA \leq i_I \leq 0.4mA$$

$$c) R_I = \frac{V_I}{i_I} = \frac{0}{i_I} = 0$$

$$V_- = 0 \Rightarrow i = 0$$

$$\Rightarrow i_I = 1mA$$
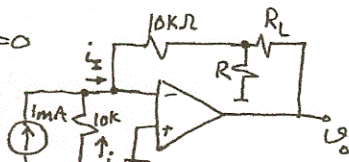
$$\text{From part a: } i_L = 20 \times i_I = 20mA$$



2.34

$$R_2 \gg R_3, \text{ if we ignore the current across } R_2: V_A = \frac{V_0 R_3}{R_3 + R_4}$$

$$\frac{V_I}{R_1} = \frac{0 - V_A}{R_2} \Rightarrow V_A = -\frac{R_2 V_I}{R_1}$$

$$V_0 \frac{R_3}{R_3 + R_4} = -\frac{R_2}{R_1} \times V_I \Rightarrow \frac{V_0}{V_I} = -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_3}\right)$$

Now if we recalculate V_A considering that there is a voltage divider between R_4 and $R_3 \parallel R_2$:

$$V_A = V_0 \frac{R_3 \parallel R_2}{R_4 + R_3 \parallel R_2} = V_0 \frac{R_3 R_2}{R_4 (R_3 + R_2) + R_3 R_2}$$

$$V_A = V_0 \frac{R_2 R_3}{R_4 R_3 + R_2 R_4 + R_2 R_3}$$

$$V_A = V_0 \frac{1}{R_4/R_2 + R_4/R_3 + 1}$$

$$V_A = -\frac{R_2}{R_1} \times V_I \Rightarrow \frac{V_0}{V_I} = -\frac{R_2}{R_1} \left(\frac{R_4}{R_2} + \frac{R_4}{R_3} + 1\right)$$

Same as example 2.2.

2.35

$$R_I = 100k\Omega, -10 \leq \frac{V_0}{V_I} \leq -1 \frac{V}{V}$$

$$R_I = R_1 = 100k\Omega$$

$$\frac{V_0}{V_I} = -\frac{R_2}{R_1} \left(\frac{R_4}{R_3} + \frac{R_4}{R_2} + 1\right)$$

$$R_4 = 0 \Rightarrow \frac{V_0}{V_I} = -\frac{R_2}{R_1} = -1 \Rightarrow R_2 = 100k\Omega$$

$$R_4 = 10k\Omega \Rightarrow \frac{V_0}{V_I} = -10 = -1 \times \left(\frac{10k\Omega}{R_3} + \frac{10k\Omega}{100k\Omega} + 1\right)$$

$$+10 = \left(\frac{10}{R_3} + 1.1\right) \Rightarrow R_3 = 1.12k\Omega$$

$$\text{Potentiometer in the middle: } \frac{V_0}{V_I} = -1 \left(\frac{5}{5+R_3} + \frac{5}{100}\right)$$

$$\frac{V_0}{V_I} = -1.87V/V$$

2.36

According to eq. 2.7:

$$U_o = -\left(\frac{R_F}{R_1} U_1 + \frac{R_F}{R_2} U_2 + \frac{R_F}{R_n} U_n\right)$$

$$U_o = -\left(\frac{50k}{100k} U_1 + \frac{50k}{100k} U_2 + \frac{50k}{100k} U_3\right)$$

$$U_o = -(U_1 + U_2) \quad U_1 = 3, U_2 = -3 \Rightarrow U_o = -1.5V$$

2.37

we choose the weighted Sommer configuration

$$U_o = -\left[4U_1 + \frac{U_2}{3}\right]$$

$$i_1 = \frac{U_1}{R_1} \quad i_2 = \frac{U_2}{R_2}$$

$$i_1, i_2 \leq 0.1 \text{ mA for } U_1, U_2 = 1V$$

$$R_1, R_2 \geq 10k\Omega$$

$$\frac{R_F}{R_1} = 4, \text{ if } R_1 = 10k\Omega \Rightarrow R_F = 40k\Omega$$

$$\frac{R_F}{R_2} = \frac{1}{3} \Rightarrow R_2 = 120k\Omega$$

2.38

$$U_o = -(2U_1 + 4U_2 + 8U_3)$$

$$R_1, R_2, R_3 \geq 10k\Omega$$

$$\frac{R_F}{R_1} = 2, \frac{R_F}{R_2} = 4, \frac{R_F}{R_3} = 8$$

$$R_3 = 10k\Omega \Rightarrow R_F = 80k\Omega$$

$$R_2 = 20k\Omega$$

$$R_1 = 40k\Omega$$

2.39

$$a) U_o = -(U_1 + 2U_2 + 3U_3)$$


$$\frac{R_F}{R_1} = 1 \Rightarrow R_1 = 10k\Omega, \frac{R_F}{R_2} = 2 \Rightarrow R_2 = 5k\Omega$$

$$\frac{R_F}{R_3} = 3 \Rightarrow R_3 = \frac{10}{3}k\Omega$$

$$R_{I1} = 10k\Omega$$

$$R_{I2} = 5k\Omega$$

$$R_{I3} = 3.3k\Omega$$

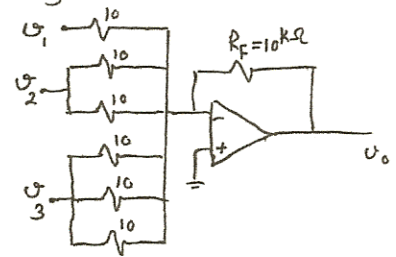

$$b) U_o = -(U_1 + U_2 + 2U_3 + 2U_4)$$

$$\frac{R_F}{R_1} = 1 \Rightarrow R_1 = 10k\Omega$$

$$\frac{R_F}{R_2} = 1 \Rightarrow R_2 = 10k\Omega$$

$$\frac{R_F}{R_3} = 2 \Rightarrow R_3 = \frac{10}{2}k\Omega$$

$$\frac{R_F}{R_4} = 2 \Rightarrow R_4 = \frac{10}{2}k\Omega$$

$$R_{I1} = R_{I2} = 10k\Omega$$

$$R_{I3} = R_{I4} = 5k\Omega$$

$$c) U_o = -(U_1 + 5U_2)$$

$$R_1 = 10k\Omega$$

$$R_2 = \frac{10k}{5}$$




$$R_{I1} = 10k\Omega$$

$$R_{I2} = 2k\Omega$$

$$d) U_o = -6U_1$$

$$R_1 = \frac{10k}{6}$$


$$R_{I1} = 1.67k\Omega$$

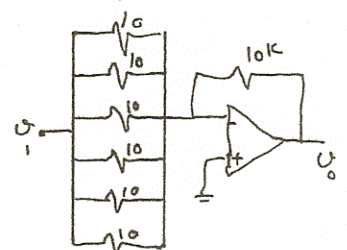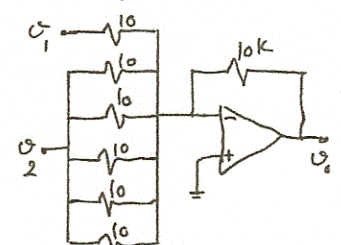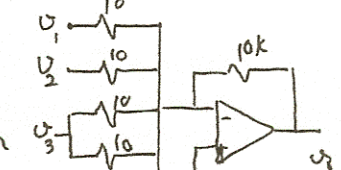


suggested configurations:

$$U_o = -(2U_1 + 2U_2 + 2U_3)$$

$$U_o = -(3U_1 + 3U_2)$$

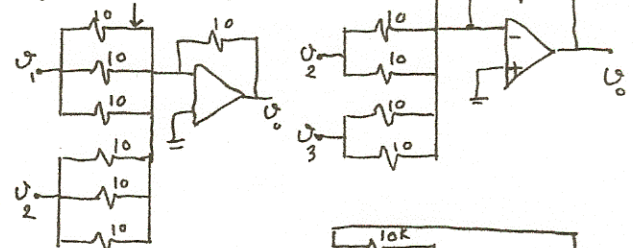

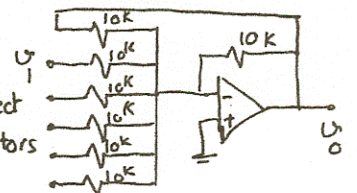In order to have coefficient = 0.5, connect one of the input resistors to U_o . $\frac{U_o}{U_1} = 0.5$



2.40

The output signal should be:



$$V_o = -5 \sin \omega t - 5$$

if we assume: $V_1 = 5 \sin \omega t$
 $V_2 = 2V$ } $V_o = -V_1 + 2.5V_2$

In a weighted summer configuration:

$$\frac{R_F}{R_1} = +1 \quad \frac{R_F}{R_2} = 2.5$$
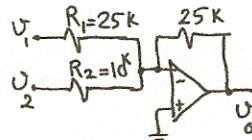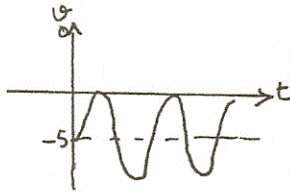
$$R_2 = 10k\Omega \Rightarrow R_F = 25k\Omega = R_1$$



we want to have: $V_o = 10V_1 - 10V_2$


we use the circuit in Fig. 2.11.

According to Eq. 2.8:

$$V_o = V_1 \frac{R_a}{R_1} \frac{R_c}{R_b} - V_2 \frac{R_c}{R_3}$$

$$\frac{R_a}{R_1} \frac{R_c}{R_b} = 10, \quad \frac{R_c}{R_3} = 10, \quad \text{if } R_3 = 10k\Omega \Rightarrow R_c = 100k\Omega$$
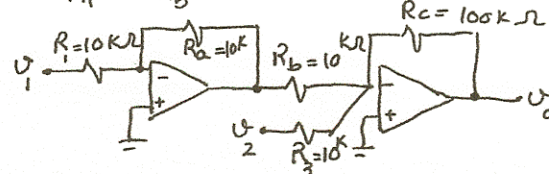
$$\Rightarrow \frac{R_a}{R_1} \times \frac{100k\Omega}{R_b} = 10 \Rightarrow R_a = R_1 = R_b = 10k\Omega$$



$$V_o = 10V_1 - 10V_2 = 10 \times 0.02 \sin 2\pi \times 1000t$$

$$V_o = 0.2 \sin(2\pi \times 1000t) \quad -0.2 \leq V_o \leq 0.2$$

2.41

$$V_o = V_1 + 2V_2 - 3V_3 - 4V_4 \quad \text{Consider Fig. 2.11.}$$

According to eq. 2.8 For a weighted summer

$$V_o = V_1 \frac{R_a}{R_1} \frac{R_c}{R_b} + V_2 \frac{R_a}{R_2} \frac{R_c}{R_b} - V_3 \frac{R_c}{R_3} - V_4 \frac{R_c}{R_4}$$


$$\frac{R_a}{R_1} \frac{R_c}{R_b} = 1, \quad \frac{R_a}{R_2} \frac{R_c}{R_b} = 1, \quad \frac{R_c}{R_3} = 3, \quad \frac{R_c}{R_4} = 4$$

assume:

$$R_4 = 10k\Omega \Rightarrow R_c = 40k\Omega \Rightarrow R_3 = \frac{40}{3} = 13.3k\Omega$$

$$\frac{R_a}{R_1} \times \frac{40}{R_b} = 1 \quad \frac{R_a}{R_2} \times \frac{40}{R_b} = 1$$
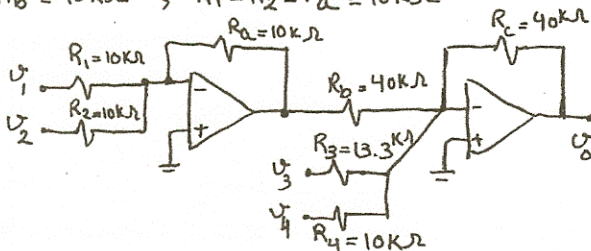
$$R_b = 40k\Omega, \quad R_1 = R_2 = R_a = 10k\Omega$$



2.43

This is a weighted summer circuit:

$$V_o = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 + \frac{R_F}{R_4} V_4 \right)$$

$$\text{we may write: } V_1 = 5V \times a_1, \quad V_2 = 5V \times a_2, \quad V_3 = 5V \times a_3, \quad V_4 = 5V \times a_4$$

$$V_o = -R_F \left(\frac{5a_1}{80k} + \frac{5a_2}{40k} + \frac{5a_3}{20k} + \frac{5a_4}{10k} \right)$$

$$V_o = -R_F \left(\frac{a_1}{16} + \frac{a_2}{8} + \frac{a_3}{4} + \frac{a_4}{2} \right)$$

$$V_o = - \frac{R_F}{16} (2a_1 + 2a_2 + 2a_3 + 2a_4)$$

$$-12V \leq V_o \leq 0 \Rightarrow \frac{R_F}{16} (2 \times 1 + 2 \times 1 + 2 \times 1 + 2 \times 1) =$$

$$= \frac{15R_F}{16} = 12 \quad \text{when } a_1 = a_2 = a_3 = a_4 = 1 \text{ we have the peak value at } V_o.$$

$$\Rightarrow R_F = 12.8k\Omega$$

2.42

$$V_1 = 3 \sin(2\pi \times 60t) + 0.01 \sin(2\pi \times 1000t)$$

$$V_2 = 3 \sin(2\pi \times 60t) - 0.01 \sin(2\pi \times 1000t)$$

2.44


$$a) \frac{V_o}{V_1} = 1 = 1 + \frac{R_2}{R_1} \Rightarrow R_2 = 0, R_1 = 10k\Omega$$

$$b) \frac{V_o}{V_1} = 2 = 1 + \frac{R_2}{R_1} \Rightarrow R_1 = R_2 = 10k\Omega$$

Cont.

c) $\frac{U_o}{U_i} = 101 \text{ V/V} = 1 + \frac{R_2}{R_1} \Rightarrow \text{if } R_1 = 10 \text{ k}\Omega \Rightarrow R_2 = 1 \text{ M}\Omega$
d) $\frac{U_o}{U_i} = 100 \text{ V/V} = 1 + \frac{R_2}{R_1} \Rightarrow \text{if } R_1 = 10 \text{ k}\Omega \Rightarrow R_2 = 990 \text{ k}\Omega$

2.45

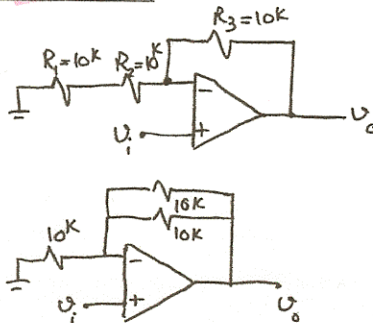

short-circuit R_2 :

$$\frac{U_o}{U_i} = 2$$

short circuit R_3 :

$$\frac{U_o}{U_i} = 1$$

2.46

$U_+ = U_- = V = R \times i$, $i = 100 \mu\text{A}$ when $V = 10 \text{ V}$
 $\Rightarrow R = \frac{10}{0.1 \text{ mA}} = 100 \text{ k}\Omega$

As indicated, i only depends on R and V and the meter resistance does not affect i .

2.47

Refer to the circuit in P2.47:

a) using superposition, we first set $U_{P1} = U_{P2} = \dots = 0$
The output voltage that results in response to $U_{N1}, U_{N2}, \dots, U_{Nn}$ is:

$$U_{ON} = -\left[\frac{R_F}{R_{N1}} U_{N1} + \frac{R_F}{R_{N2}} U_{N2} + \dots + \frac{R_F}{R_{Nn}} U_{Nn} \right]$$


Then we set $U_{N1} = U_{N2} = \dots = 0$, then:

$$R_N = R_{N1} \parallel R_{N2} \parallel R_{N3} \parallel \dots \parallel R_{Nn}$$

The circuit simplifies to:

$$U_{Op} = \left(1 + \frac{R_F}{R_N} \right) \times$$
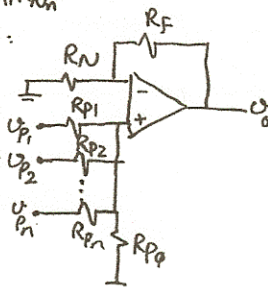
$$\left(U_{P1} \frac{1/R_{P1}}{1/R_{P1} + 1/R_{P2} + \dots + 1/R_{Pn}} + U_{P2} \frac{1/R_{P2}}{1/R_{P1} + 1/R_{P2} + \dots + 1/R_{Pn}} + \dots + U_{Pn} \frac{1/R_{Pn}}{1/R_{P1} + 1/R_{P2} + \dots + 1/R_{Pn}} \right)$$



$$U_{Op} = \left(1 + \frac{R_F}{R_N} \right) \left(U_{P1} \frac{R_P}{R_{P1}} + U_{P2} \frac{R_P}{R_{P2}} + \dots + U_{Pn} \frac{R_P}{R_{Pn}} \right)$$

where:


$$R_P = R_{P1} \parallel R_{P2} \parallel \dots \parallel R_{Pn}$$

when all inputs are present:

$$U_o = U_{ON} + U_{Op} = -\left(\frac{R_F}{R_{N1}} U_{N1} + \frac{R_F}{R_{N2}} U_{N2} + \dots \right) + \left(1 + \frac{R_F}{R_N} \right) \left(\frac{R_P}{R_{P1}} U_{N1} + \frac{R_P}{R_{P2}} U_{N2} + \dots \right)$$

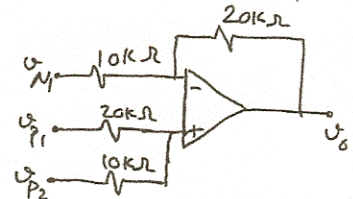b) $U_o = -2U_{N1} + U_{P1} + 2U_{P2}$
 $\frac{R_F}{R_{N1}} = 2$ $R_{N1} = 10 \text{ k}\Omega \Rightarrow R_F = 20 \text{ k}\Omega$
 $\left(1 + \frac{R_F}{R_N} \right) \left(\frac{R_P}{R_{P1}} \right) = 1 \Rightarrow 3 \frac{R_P}{R_{P1}} = 1 \Rightarrow R_{P2} = \frac{R_{P1}}{2}$
 $\left(1 + \frac{R_F}{R_N} \right) \left(\frac{R_P}{R_{P2}} \right) = 2 \Rightarrow 3 \frac{R_P}{R_{P2}} = 2 \Rightarrow R_{P2} = \frac{R_{P1}}{2}$
where $R_P = \frac{R_{P1} \times R_{P2}}{R_{P1} + R_{P2}}$ (ignoring R_{P0})

Note that if the results from the last 2 constraints differ, we would use an additional resistor connected from the positive input to ground. (R_{P0})



2.48

$$U_o = U_{I1} + 3U_{I2} - 2(U_{I3} + 3U_{I4})$$

Refer to P2.47.

$$\frac{R_F}{R_{N3}} = 2 \text{ if } R_{N3} = 10 \text{ k}\Omega \Rightarrow R_F = 20 \text{ k}\Omega$$

$$\frac{R_F}{R_{N4}} = 6 \Rightarrow R_{N4} = \frac{20}{6} = 3.3 \text{ k}\Omega$$

$$R_N = R_{N3} \parallel R_{N4} = 10 \text{ k}\Omega \parallel 3.3 \text{ k}\Omega = 2.48 \text{ k}\Omega$$

$$\left(1 + \frac{R_F}{R_N} \right) \frac{R_P}{R_{P2}} = 1 \Rightarrow \left(1 + \frac{20}{2.48} \right) \frac{R_P}{R_{P2}} = 1 \Rightarrow 9.06 R_P' = R_{P2}$$

$$R_P = R_{P1} \parallel R_{P2} \parallel R_{P0} \Rightarrow R_P = \frac{1}{\frac{1}{R_{P1}} + \frac{1}{R_{P2}} + \frac{1}{R_{P0}}}$$

$$\left(1 + \frac{R_F}{R_N} \right) \frac{R_P}{R_{P2}} = 3 \Rightarrow 9.06 \frac{R_P}{R_{P2}} = 3 \Rightarrow R_{P2} = 3 R_P$$

$$R_{P1} \parallel R_{P2} = \frac{9 \times 3 R_P}{9 + 3} = 2.25 R_P, R_P = 2.25 R_P \parallel R_{P0}$$


Cont.

$$2.25 R_p + R_{p0} = 2.25 R_{p0} \Rightarrow R_{p0} = 1.8 R_p$$

$$\text{if } R_p = 10 \text{ k}\Omega \Rightarrow R_{p0} = 18 \text{ k}\Omega$$

$$R_{p1} = 9 \times 10 \text{ k} = 90 \text{ k}\Omega$$
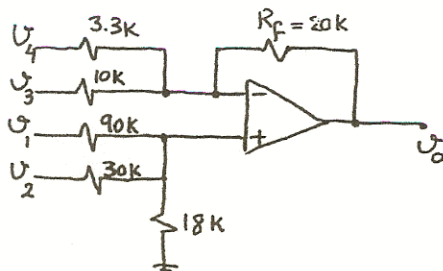
$$R_{p2} = 3 \times 10 \text{ k} = 30 \text{ k}\Omega$$



2.49

$$U_+ = U_I \frac{R_4}{R_3 + R_4} = U$$

$$\frac{U_-}{R_1} = \frac{U_2 - U_-}{R_2} \Rightarrow U_o = U_- (1 + \frac{R_2}{R_1})$$

from the two above equations :

$$\frac{U_o}{U_I} = (1 + \frac{R_2}{R_1}) (\frac{R_4}{R_3 + R_4}) = \frac{1 + R_2/R_1}{1 + R_3/R_4}$$

2.50

Refer to Fig. 2.50. Setting $U_2 = 0$, we obtain the output component due to U_1 as:

$$U_{o1} = -20V$$

Setting $U_1 = 0$, we obtain the output component due to U_2 as:

$$U_{o2} = U_2 (1 + \frac{20R}{R}) (\frac{20R}{20R + R}) = 20 U_2$$

The total output voltage is :

$$U_o = U_{o1} + U_{o2} = 20 (U_2 - U_1)$$

$$\text{For } U_1 = 10 \sin 2\pi \times 60t - 0.1 \sin(2\pi \times 1000t)$$

$$U_2 = 10 \sin 2\pi \times 60t + 0.1 \sin(2\pi \times 1000t)$$

$$U_o = 4 \sin(2\pi \times 1000t)$$

2.51

$$\frac{U_o}{U_I} = 1 + \frac{R_2}{R_1} = 1 + \frac{(1-x)}{x} = 1 + \frac{1}{x} - 1 = \frac{1}{x}$$

$$0 \leq x \leq 1 \Rightarrow 1 \leq \frac{U_o}{U_I} \leq \infty$$

if we add a resistor on the ground path:

$$\frac{U_o}{U_I} = 1 + \frac{(1-x) \times 10K}{x \times 10K + R}$$


$$\text{Gain}_{\max} = 21 \text{ when}$$

$$x=0 \Rightarrow 21 = 1 + \frac{10K}{R}$$

$$\Rightarrow R = \frac{10K}{20} = 0.5 \text{ k}\Omega$$



2.52

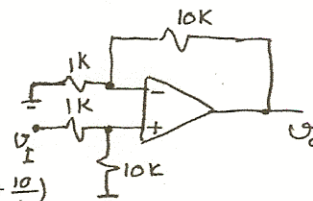

$$U_o = U_I \frac{10}{1+10} (1 + \frac{10}{1})$$

$$U_o = 10 U_I$$


2.53

a) Source is connected directly.

$$U_o = 10 \times \frac{1}{101} = 0.099V$$

$$i_L = \frac{U_o}{1K} = \frac{0.099}{1} = 0.099 \text{ mA}$$

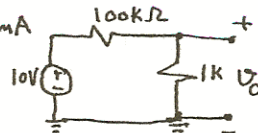current supplied by the source is 0.099 mA.



b) inserting a buffer


$$U_o = 10V$$

$$i_L = \frac{10V}{1K} = 10 \text{ mA}$$

current supplied by the

source is 0.

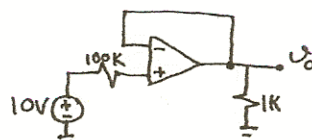The load current i_L comes from the power supply of the op-amp.



2.54


$$U_o = U_i - \frac{U_o}{A}$$

$$\frac{U_o}{U_i} = \frac{1}{1 + \frac{1}{A}}$$

error of Gain magnitude

$$\left| \frac{U_o}{U_i} - 1 \right| = - \frac{1}{A+1}$$

$A (V/V)$	1000	100	10
$\frac{U_o}{U_i} (V/V)$	0.999	0.990	0.909
Gain Error	-0.1%	-1%	-9.1%

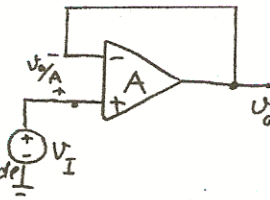

2.55

for an inverting amplifier:

$$R_i = R_1, \quad G = -\frac{R_2}{R_1}$$

for a non-inverting amplifier:

$$R_i = \infty, \quad G = 1 + \frac{R_2}{R_1}$$

Case	Gain V/V	R_{in}	R_1	R_2
a	-10	10K	10K	100K
b	-1	100K	100K	100K
c	-2	50K	50K	100K
d	+1	∞	10K	10K
e	+2	∞	10K	10K
f	+11	∞	10K	100K
g	-0.5	10K	10K	5K

2.56


$$A = 50 V/V, \quad 1 + \frac{R_2}{R_1} = 10 V/V$$

$$\text{if } R_1 = 10K\Omega \Rightarrow R_2 = 90K$$

According to Eq. 2.11: $G = \frac{U_o}{U_i} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A}}$

$$G = \frac{1 + \frac{90}{10}}{1 + \frac{1}{50}} = \frac{10}{1.02} = 9.8 V/V$$

In order to compensate the gain drop,

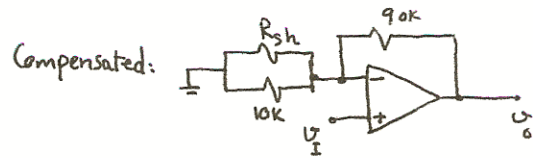we can shunt a resistor with R_1 .

$$R_{sh}: 10 = \frac{1 + \left(\frac{90}{10} + \frac{90}{R_{sh}} \right)}{1 + \frac{1}{1 + \frac{90}{10} + \frac{90}{R_{sh}}}}$$

$$10 \times (50R_{sh} + 90R_{sh} + 900) = 50 \times (10R_{sh} + 90R_{sh} + 900)$$

$$100R_{sh} = 3600 \Rightarrow R_{sh} = 36K\Omega$$

if $A = 100$ then:

$$G_{uncompensated} = \frac{1 + \frac{90}{10}}{1 + \frac{1}{100}} = \frac{10}{1.01} = 9.9 V/V$$

$$G_{compensated} = \frac{1 + \frac{90}{10} + \frac{90}{36}}{1 + \frac{1}{100}} = \frac{12.5}{1.01} = 12.4 V/V$$

2.57

$$G = \frac{G_o}{1 + \frac{G_o}{A}}, \quad \frac{G_o - G}{G_o} \times 100 = \frac{G_o/A \times 100}{1 + \frac{G_o}{A}}$$

$$\text{or } 1 + \frac{G_o}{A} \geq \frac{100}{x} \Rightarrow \frac{A}{G_o} \geq \left(\frac{100}{x} - 1 \right)$$

$$\Rightarrow A \geq G_o F \text{ where } F = \frac{100}{x} - 1 \leq \frac{100}{x}$$

x	0.01	0.1	1	10
F	10^4	10^3	10^2	10

Thus for:

$x = 0.01$	$G_o (V/V)$	1	10	10^2	10^3	10^4
	$A (V/V)$	10^4	10^5	10^6	10^7	10^8

too high to be practical

$x = 0.1$	$G_o (V/V)$	1	10	10^2	10^3	10^4
	$A (V/V)$	10^3	10^4	10^5	10^6	10^7

$x = 1$	$G_o (V/V)$	1	10	10^2	10^3	10^4
	$A (V/V)$	10^2	10^3	10^4	10^5	10^6

$x = 10$	$G_o (V/V)$	1	10	10^2	10^3	10^4
	$A (V/V)$	10	10^2	10^3	10^4	10^5

2.58

for non-inverting amplifier, Eq. 2.11:

$$G = \frac{G_0}{1 + \frac{G_0}{A}}, \quad \varepsilon = \frac{G_0 - G}{G_0} \times 100$$

for inverting amplifier, Eq. 2.5:

$$G = \frac{G_0}{1 + \frac{1 - G_0}{A}}, \quad \varepsilon = \frac{G_0 - G}{G_0} \times 100$$

Case	$G_0 (V/V)$	$A (V/V)$	$G (V/V)$	$\varepsilon \%$
a	-1	10	-0.83	16
b	1	10	0.91	9
c	-1	100	-0.98	2
d	10	10	5	50
e	-10	100	-9	10
f	-10	1000	-9.89	1.1
g	+1	2	0.67	33

2.59

Refer to Fig. P2.59, when potentiometer is set to the bottom:

$$V_0 = V_+ = -15 + \frac{30 \times 20}{20 + 100 + 20} = -10.714 \text{ V}$$

$$\text{when set to the top: } V_0 = -15 + \frac{30 \times 120}{20 + 100 + 20} = 10.714 \text{ V}$$

$$\Rightarrow -10.714 \leq V_0 \leq 10.714$$

$$\text{pot has 20 turn, each turn: } \Delta V_0 = \frac{2 \times 10.714 - (-10.714)}{20}$$

2.60

Refer to Fig. 2.16. Notice that similar to eq. 2.15 we have: $\frac{R_4}{R_3} = \frac{R_2}{R_1} = \frac{100}{10}$. therefore according to 2.16:

$$V_0 = \frac{R_2}{R_1} V_{Id} \Rightarrow A = \frac{R_2}{R_1} = 10 \text{ V/V}$$

According to 2.20: $R_{id} = 2R_1 = 20 \text{ k}\Omega$

If $\frac{R_2}{R_1}$, $\frac{R_4}{R_3}$ were different by $i\%$:

$$\frac{R_2}{R_1} = 0.99 \frac{R_4}{R_3}$$

Refer to eq. 2.19: $A_{cm} = \frac{R_4}{R_4 + R_3} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right)$

$$A_{cm} = \frac{100}{100 + 10} (1 - 0.99) = 0.009$$

$$CMRR = 20 \log \frac{|A_d|}{|A_{cm}|}, \text{ so let's calculate } A_d$$

$$A_d = \frac{V_0}{V_{Id}} \text{ if we apply superposition:}$$

$$V_{01} = -\frac{R_2}{R_1} V_{I1} \quad V_{02} = V_{I2} \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right)$$

$$V_0 = V_{02} + V_{01} = V_{I2} \frac{R_4/R_3}{1 + \frac{R_4}{R_3}} \left(1 + \frac{R_2}{R_1}\right) - \frac{R_2}{R_1} V_{I1}$$

$$\text{Replace } \frac{R_2}{R_1} = 0.99 \frac{R_4}{R_3} \Rightarrow \frac{R_2}{R_1} = 0.99 \times \frac{100}{10} = 9.9$$

$$V_0 = V_{I2} \frac{10}{1 + 10} (1 + 9.9) - V_{I1} 9.9 = 9.9 (V_{I2} - V_{I1})$$

$$\frac{V_0}{V_{Id}} = 9.9 = A_d \Rightarrow CMRR = 20 \log \frac{9.9}{0.009} = 60.8$$

$$CMRR = 60.8$$

2.61

If we assume $R_3 = R_1$, $R_4 = R_2$, then

$$\text{eq. 2.20: } R_{id} = 2R_1 \Rightarrow R_1 = \frac{20}{2} = 10 \text{ k}\Omega$$

(Refer to Fig. 2.16)

$$\text{a) } A_d = \frac{R_2}{R_1} = 1 \text{ V/V} \Rightarrow R_2 = 10 \text{ k}\Omega$$

$$R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$$

$$\text{b) } A_d = \frac{R_2}{R_1} = 2 \text{ V/V} \Rightarrow R_2 = 20 \text{ k}\Omega = R_4$$

$$R_1 = R_3 = 10 \text{ k}\Omega$$

$$\text{c) } A_d = \frac{R_2}{R_1} = 100 \text{ V/V} \Rightarrow R_2 = 1 \text{ M}\Omega = R_4$$

$$R_1 = R_3 = 10 \text{ k}\Omega$$


$$\text{d) } A_d = \frac{R_2}{R_1} = 0.5 \text{ V/V} \Rightarrow R_2 = 5 \text{ k}\Omega = R_4$$

$$R_1 = R_3 = 10 \text{ k}\Omega$$


2.62

Refer to Fig P2.62:


Cont.

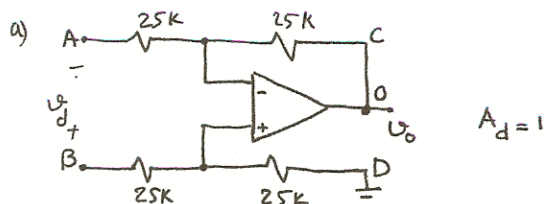


b) $\frac{V_o}{V_i} = -1 \frac{V}{V}$
i)

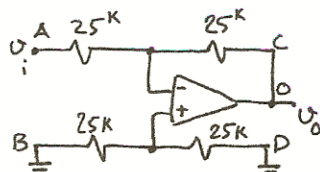

ii) $\frac{V_o}{V_i} = +1 \frac{V}{V}$

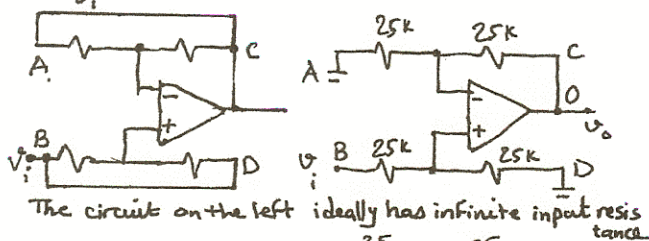


iii) $\frac{V_o}{V_i} = +2 \frac{V}{V}$

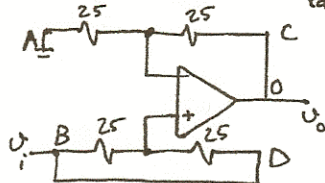


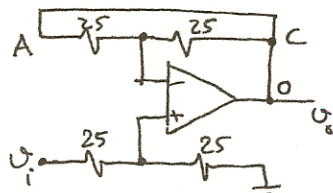iv) $\frac{V_o}{V_i} = +\frac{1}{2} \frac{V}{V}$

$V_A = \frac{V_i}{2} = \frac{V_o}{2}$
 $\Rightarrow \frac{V_o}{V_i} = \frac{1}{2}$



2.72

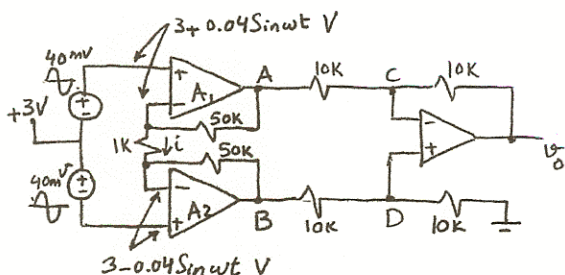

$i = \frac{3 + 0.04 \sin \omega t - (3 - 0.04 \sin \omega t)}{10k} = 0.08 \sin \omega t, \text{mA}$

$V_A = 3 + 0.04 \sin \omega t + 50k \times i = 3 + 4.04 \sin \omega t, \text{V}$

$V_B = 3 - 0.04 \sin \omega t - 50k \times i = 3 - 4.04 \sin \omega t, \text{V}$

$V_C = V_D = \frac{1}{2} V_B = 1.5 - 2.02 \sin \omega t, \text{V}$

$V_o = V_B - V_A = -8.08 \sin \omega t, \text{V}$

2.73

Refer to Fig. 2.20.a.

The gain of the first stage is: $(1 + \frac{R_2}{R_1}) = 101$

If the opamps of the first stage saturate at $\pm 14 \text{V}$:

$-14 \leq V_{i1} \leq +14 \text{V} \Rightarrow -14 \leq 101 V_{iCM} \leq +14$
 $\Rightarrow -0.14 \leq V_{iCM} \leq 0.14$

As explained in the text, the disadvantage of circuit in Fig. 2.20.a is that V_{iCM} is amplified by a gain equal to $V_{id} (1 + \frac{R_2}{R_1})$ in the first stage and therefore a very small V_{iCM} range is acceptable to avoid saturation.

b) In Fig. 2.20.b, when V_{iCM} is applied, V_{id} for both A_1 & A_2 is the same and therefore no current flows through $2R_1$. This means V_{id} at the output of A_1 and A_2 is the same as V_{iCM} .

$-14 \leq V_o \leq +14 \Rightarrow -14 \leq V_{iCM} \leq +14$

This circuit allows for bigger range of V_{iCM} .

2.74

$V_{i1} = V_{CM} - V_d/2$

$V_{i2} = V_{CM} + V_d/2$

Refer to Fig. 2.20.a.

output of the first stage: $(1 + \frac{R_2}{R_1})(V_{CM} - V_d/2)$

$V_{o1} = (1 + \frac{R_2}{R_1})(V_{CM} - V_d/2)$

$V_{o2} = (1 + \frac{R_2}{R_1})(V_{CM} + V_d/2)$

$V_{o2} - V_{o1} = (1 + \frac{R_2}{R_1}) V_d \Rightarrow A_d(1) = 1 + \frac{R_2}{R_1}$

$\frac{V_{o2} + V_{o1}}{2} = (1 + \frac{R_2}{R_1}) V_{CM} \Rightarrow A_{CM}(1) = 1 + \frac{R_2}{R_1}$

$CMRR = 20 \log \left| \frac{A_d}{A_{CM}} \right| = 0 \quad (\text{First stage})$

Now Consider Fig. 2.20.b

$V_{o1} = V_{i1} + R_2 \times \frac{(V_{i1} - V_{i2})}{2R_1}$

$V_{o1} = V_{CM} - V_d/2 + \frac{R_2}{2R_1} (-V_d)$

Cont.


2.78

Refer to Fig. P.2.78.a.

Since the inputs of the op-amp don't draw any current, V_I appears across R :

$$i_o = \frac{V_I}{R}$$

Fig. P2.78.B

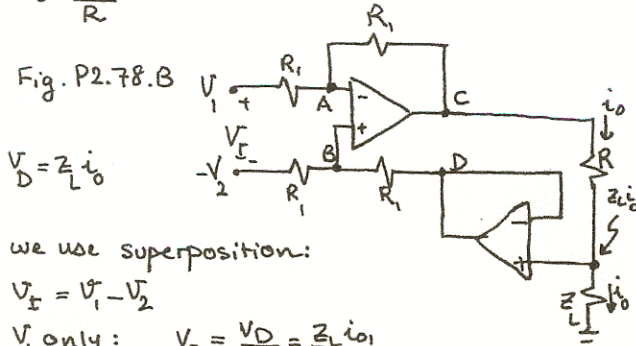

$$V_D = Z_L i_o$$

we use superposition:

$$V_I = V_1 - V_2$$

$$V_1 \text{ only: } V_B = \frac{V_D}{2} = \frac{Z_L i_o}{2}$$

$$\frac{V_1 - \frac{Z_L i_o}{2}}{R_1} = \frac{\frac{Z_L i_o}{2} - i_o (Z_L + R)}{R_1}$$

$$\rightarrow V_I = i_o R \Rightarrow i_o = \frac{V_I}{R}$$

Now if only $(-V_2)$ is applied:

$$V_B = \frac{-V_2 + Z_L i_o}{2}, \quad V_A = \frac{i_o (R + Z_L)}{2}$$

$$V_A = V_B \Rightarrow -V_2 + Z_L i_o = i_o R + i_o Z_L$$

$$-V_2 = i_o R \Rightarrow i_o = \frac{-V_2}{R}$$

The total current due to both sources is:

$$i_o = i_{o1} + i_{o2} = \frac{V_1}{R} - \frac{V_2}{R} = \frac{V_I}{R}$$

The circuit in Figure P2.78(a) has ideally infinite input resistance, and it requires that both terminals of Z_L be available, while the other circuit has finite input resistance with one side of Z_L grounded.

2.79

A_o	f_b (Hz)	f_t (Hz)
10^5	10^2	10^7
10^6	1	10^6
10^5	10^3	10^8
10^7	10^{-1}	10^6
2×10^5	10	2×10^6

eq. 2.28:

$$\omega_t = A_o \omega_b$$

$$\Rightarrow f_t = A_o f_b$$

2.80

$$\text{Eq. 2.25: } A = \frac{A_o}{1 + j\omega/\omega_b} \Rightarrow |A| = \frac{|A_o|}{\sqrt{1 + (\frac{f}{f_b})^2}}$$

$$A_o = 86 \text{ dB}, \quad A = 40 \text{ dB @ } f = 100 \text{ kHz}$$

$$20 \log \sqrt{1 + (\frac{f}{f_b})^2} = 20 \log \frac{|A_o|}{|A|} = 20 \log A_o - 20 \log A$$

$$= 86 - 40 = 46 \text{ dB}$$

$$1 + (\frac{100 \text{ kHz}}{f_b})^2 = (199.5)^2 \Rightarrow f_b = 0.501 \text{ kHz}$$


$$f_b = 501 \text{ Hz}$$

$$f_t = A_o f_b = \underbrace{1.995 \times 10^4}_{86 \text{ dB}} \times 501 = 9.998 \text{ MHz} \approx 10 \text{ MHz}$$

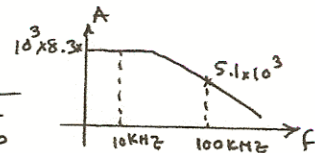2.81

$$A_o = 8.3 \times 10^3 \text{ V/V}$$

$$\text{Eq. 2.25: } A = \frac{A_o}{1 + j\frac{f}{f_b}}$$



$$f_t = A_o f_b$$

$$5.1 \times 10^3 = \frac{8.3 \times 10^3}{\sqrt{1 + (\frac{100 \text{ kHz}}{f_b})^2}} \Rightarrow 1 + (\frac{100 \text{ kHz}}{f_b})^2 = 2.65$$

$$f_b = 60.7 \text{ kHz}$$

$$f_t = A_o f_b = 8.3 \times 10^3 \times 60.7 = 503 \text{ MHz}$$

2.82

we have:

$$A_o = 20 \text{ dB} + A_{(db)} \quad 20 \text{ dB} = 20 \log 10 \Rightarrow A_o = 10 \text{ A}$$

$$a) A_o = 10 \times 3 \times 10^5 = 3 \times 10^6 \text{ Hz V/V}$$

$$A = \frac{A_o}{1 + j\frac{f}{f_b}} \Rightarrow |1 + j\frac{f}{f_b}| = \frac{A_o}{A} = 10 \Rightarrow \frac{6 \times 10^2}{f_b} = \sqrt{99}$$

$$\Rightarrow f_b = 60.3 \text{ Hz}$$

$$f_t = A_o f_b = 3 \times 10^6 \times 60.3 = 180.9 \text{ MHz}$$

$$b) A = 50 \times 10^5 \text{ V/V} \Rightarrow A_o = 10 \times 50 \times 10^5 = 50 \times 10^6 \text{ V/V}$$

$$|1 + j\frac{f}{f_b}| = \frac{A_o}{A} = 10 \Rightarrow \frac{10^8}{f_b} = \sqrt{99} \Rightarrow f_b = 1 \text{ Hz}$$

$$f_t = A_o f_b = 50 \text{ MHz}$$

$$c) A = 1500 \text{ V/V} \Rightarrow A_o = 15000 \text{ V/V}$$

Cont.

$$\left|1 + \frac{jf}{f_b}\right| = 10 \Rightarrow \frac{0.1 \times 10^6}{f_b} = \sqrt{99} \Rightarrow f_b = 10 \text{ kHz}$$

$$f_c = 15000 \times 10^3 = 150 \text{ MHz}$$

d) $A_0 = 10 \times 100 = 1000 \text{ V/V}$

$$\left|1 + \frac{jf}{f_b}\right| = 10 \Rightarrow \frac{0.1 \times 10^4}{f_b} = \sqrt{99} \Rightarrow f_b = 10 \text{ MHz}$$

$$f_c = 1000 \times 10^3 \text{ MHz} = 1000 \text{ MHz}$$

e) $A_0 = 25 \text{ V/V} \times 10 = 25 \times 10^4 \text{ V/V}$

$$\left|1 + \frac{jf}{f_b}\right| = 10 \Rightarrow \frac{25 \text{ kHz}}{f_b} = \sqrt{99} \Rightarrow f_b = 2.51 \text{ kHz}$$

$$f_c = A_0 f_b = 25 \times 10^4 \times 2.51 \times 10^3 = 627.5 \text{ MHz}$$

2.83

$$G_{nom} = -\frac{R_2}{R_1} = -20 \quad A_0 = 10^4 \text{ V/V} \quad f_c = 10^6 \text{ Hz}$$

Eq. 2.35: $\omega_{3db} = \frac{\omega_c}{1 + R_2/R_1} = \frac{2\pi \times 10^6}{1 + 20} = 2\pi \times 47.6 \text{ kHz}$

$$f_{3db} = 47.6 \text{ kHz}$$

Eq. 2.34: $\frac{V_o}{V_i} \approx \frac{-R_2/R_1}{1 + \frac{s}{\omega_c/(1 + R_2/R_1)}} = \frac{-20}{1 + \frac{21.5}{2\pi \times 10^6} s}$

$$f = 0.1 f_{3db} \Rightarrow \left|\frac{V_o}{V_i}\right| = \frac{-20}{\sqrt{1 + (0.1)^2}} = +19.9 \text{ V/V}$$

$$f = 10 f_{3db} \Rightarrow \left|\frac{V_o}{V_i}\right| = \frac{-20}{\sqrt{1 + 100}} = 1.99 \text{ V/V}$$

2.84

$$1 + \frac{R_2}{R_1} = 100 \text{ V/V}, \quad f_c = 20 \text{ MHz}$$

$$f_{3db} = \frac{f_c}{1 + \frac{R_2}{R_1}} = 200 \text{ kHz}$$

$$\angle G(j\omega) = \frac{100}{1 + j f/f_{3db}} \Rightarrow \phi = -\tan^{-1} \frac{f}{f_{3db}} =$$

$$\phi = -6^\circ \Rightarrow f = f_{3db} \times \tan 6^\circ = 21 \text{ kHz}$$

$$\phi = -84^\circ \Rightarrow f = f_{3db} \times \tan 84^\circ = 1.9 \text{ MHz}$$

2.85

a) $-\frac{R_2}{R_1} = -100 \text{ V/V}, \quad f_{3db} = 100 \text{ kHz}$

Eq. 2.35: $\omega_c = \omega_{3db} (1 + \frac{R_2}{R_1}) \Rightarrow f_c = 100 \text{ kHz} \times 101 = 10.1 \text{ MHz}$

b) $1 + \frac{R_2}{R_1} = 100 \text{ V/V} \quad f_{3db} = 100 \text{ kHz}$

$$f_c = f_{3db} (1 + \frac{R_2}{R_1}) = 10 \text{ MHz}$$

c) $1 + \frac{R_2}{R_1} = 2 \text{ V/V} \quad f_{3db} = 10 \text{ MHz}$

$$f_c = 10 \text{ MHz} \times 2 = 20 \text{ MHz}$$

d) $-\frac{R_2}{R_1} = -2 \text{ V/V} \quad f_{3db} = 10 \text{ MHz}$

$$f_c = 10 \text{ MHz} (1 + 2) = 30 \text{ MHz}$$

e) $-\frac{R_2}{R_1} = -1000 \text{ V/V} \quad f_{3db} = 20 \text{ kHz}$

$$f_c = 20 \text{ kHz} (1 + 1000) = 20.02 \text{ MHz}$$

f) $1 + \frac{R_2}{R_1} = 1 \text{ V/V} \quad f_{3db} = 1 \text{ MHz}$

$$f_c = 1 \text{ MHz} \times 1 = 1 \text{ MHz}$$

g) $-\frac{R_2}{R_1} = -1 \quad f_{3db} = 1 \text{ MHz}$

$$f_c = 1 \text{ MHz} (1 + 1) = 2 \text{ MHz}$$

2.86

$$1 + \frac{R_2}{R_1} = 100 \text{ V/V} \quad f_{3db} = 8 \text{ kHz}$$

$$f_c = 8 \times 100 = 800 \text{ kHz}$$

for $f_{3db} = 20 \text{ kHz} : G_0 = \frac{800}{20} = 40 \text{ V/V}$

2.87

$$f_{3db} = f_c = 1 \text{ MHz}$$

$$|G| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3db}}\right)^2}} = \frac{1}{\sqrt{1 + f^2}} \quad f \text{ in MHz}$$

$$|G| = 0.99 \Rightarrow f = 0.142 \text{ MHz}$$

The follower behaves like a low-pass STC circuit with a time constant $\tau = \frac{1}{\omega_{3db}}$

Thus: $\tau = \frac{1}{2\pi \times 10^6} = \frac{1}{2\pi} \mu\text{s}$

$$\tau_r = 2.2\tau = 0.35 \mu\text{s} \quad (\text{Refer to Appendix F})$$

Output distortion will be due to slew rate limitation and will occur at the frequency for which $\left. \frac{dV_o}{dt} \right|_{\max} = SR$

$$\omega_{\max} \times 5 = \frac{1}{10^{-8}} = 2 \times 10^8 \text{ rad/s} \Rightarrow f_{\max} = 31.8 \text{ KHz}$$

b) The output will distort at the value of V_i that results in $\left. \frac{dV_o}{dt} \right|_{\max} = SR$.

$$V_o = 10 V_i \sin 2\pi \times 20 \times 10^3$$

$$\left. \frac{dV_o}{dt} \right|_{\max} = 10 V_i \times 2\pi \times 20 \times 10^3$$

$$\text{Thus } V_i = \frac{1/10^{-6}}{10 \times 2\pi \times 20 \times 10^3} = 0.795 \text{ V}$$

$$c) V_i = 50 \text{ mV} \quad V_o = 500 \text{ mV} = 0.5 \text{ V}$$

Slew rate begins at the frequency for which $\omega \times 0.5 = SR$

$$\text{which gives } \omega = \frac{1/10^{-6}}{0.5} = 2 \times 10^6 \text{ rad/s or } f = 318.3 \text{ KHz}$$

However the small signal 3db frequency is

$$f_{3db} = \frac{f_c}{1 + \frac{R_2}{R_1}} = \frac{2 \times 10^6}{10} = 200 \text{ KHz}$$

Thus the useful frequency range is limited at 200 KHz.

d) for $f = 5 \text{ KHz}$, the slew rate limitation occurs at the value of V_i given by

$$\omega \times 10 V_i = SR \Rightarrow V_i = \frac{1/10^{-6}}{2\pi \times 5 \times 10^3 \times 10} = 3.18 \text{ V}$$

Such an input voltage, however would ideally result in an output of 31.8V which exceeds V_{omax} . Thus $V_{imax} = \frac{V_{omax}}{10} = 1 \text{ V peak}$.

2.100

$$V_o = V_{os} \left(1 + \frac{R_2}{R_1} \right) \Rightarrow -0.3 = V_{os} \left(1 + \frac{100}{1} \right) \approx 3 \text{ mV}$$

2.101

$$V_{os} = \pm 2 \text{ mV}$$

$$V_o = 0.01 \sin \omega t \times 200 + V_{os} \times 200 = 2 \sin \omega t \pm 0.4 \text{ V}$$

2.102

$$\text{Output DC offset, } V_{os} = 3 \text{ mV} \times 1000 = 3 \text{ V}$$


Therefore the maximum amplitude of an input sinusoid is the one that results in an output peak amplitude of $13.3 = 10 \text{ V} \Rightarrow V_i = \frac{10}{1000} = 10 \text{ mV}$

If the amplifier is capacity coupled, then:

$$V_{imax} = \frac{13}{1000} = 13 \text{ mV}$$

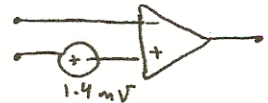2.103

$$V_{os} = \frac{1.4}{100} = 1.4 \text{ mV}$$




2.104

$$a) I_B = (I_{B1} + I_{B2})/2$$

open input:

$$V_o = V_i + R_2 I_{B1} = V_{os} + R_2 I_{B1}$$
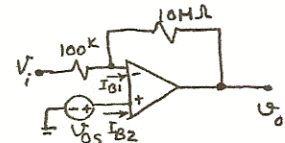
$$9.31 = V_{os} + 10000 I_{B1} \quad (1)$$



input connected to ground:

$$V_o = V_i + R_2 \left(I_{B1} + \frac{V_{os}}{R_1} \right) = V_{os} \left(1 + \frac{R_2}{R_1} \right) + R_2 I_{B1}$$

$$9.09 = V_{os} \times 101 + 10000 I_{B1} \quad (2)$$


$$(1), (2) \Rightarrow 100 V_{os} = -0.22 \Rightarrow V_{os} = -2.2 \text{ mV}$$

$$\Rightarrow I_{B1} = 930 \text{ nA}$$

$$I_B \approx I_{B1} = 930 \text{ nA}$$

$$b) V_{os} = -2.2 \text{ mV}$$

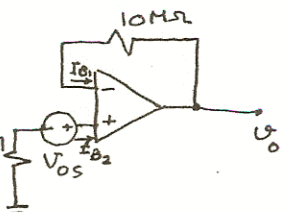c) In this case, Since R_1 is too large, we may ignore V_{os} compare to the voltage drop across R_1 .



$$V_{os} \ll R_1 I_B, \text{ Also Eq. 2.46 holds: } R_3 = R_1 \parallel R_2$$

$$\text{therefore from Eq. 2.47: } V_o = I_{os} R_2 \Rightarrow I_{os} = \frac{-0.8}{10^4}$$


$$I_{os} = -80 \text{ nA}$$

d) The phase does not change and the output still leads the input by 90°

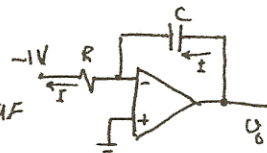2.113

$$R_{in} = R = 100k\Omega$$

$$CR = 15 \Rightarrow C = \frac{1}{100 \times 10^3} = 10nF$$




with a $-1V$ dc input applied, the capacitor charges with a constant current:

$I = \frac{-1V}{R} = 0.01mA$ and its voltage rises linearly:

$$V_o(t) = -10 + \frac{1}{C} \int_0^t I dt = -10 + \frac{I}{C} t = -10 + \frac{t}{RC}$$

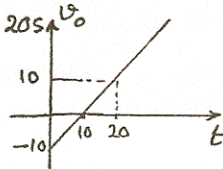the voltage reaches $0V$ at $t = 10RC = 10s$ and it reaches $10V$ at $t = 20s$



2.114

$|T| = \frac{1}{\omega RC}$ If $|T| = 100V/V$ for $f = 1kHz$, then for $|T| = 1V/V$, f has to be $1k \times 100 = 100kHz$.

$$\text{Also } RC = \frac{1}{\omega \cdot T} = \frac{1}{2\pi \times 1k \times 100} = 1.59\mu s$$

2.115

$R_{in} = R$, Thus $R = 100k\Omega$.



$$|T| = \frac{1}{\omega RC} = 1 \text{ at } \omega = \frac{1}{RC}$$

$$\omega = 1000 = \frac{1}{RC} \Rightarrow C = \frac{1}{1000 \times 100k} = 10nF$$

with a $2V-2ms$ pulse at the input, the output falls linearly until $t=2ms$ at which

$$V_o = V_i, \quad V_o = \frac{-I}{C} t = \frac{-2}{RC} t = -2t \text{ Volts where } t \text{ in ms}$$

$$\text{Thus } V_i = -4V$$

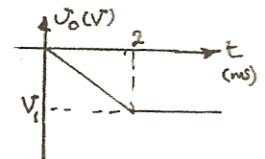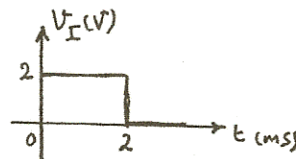

with $V_i = 2\sin 1000t$ applied at the input,

$$V_o(t) = 2 \times \frac{1}{1000 \times 10^{-3}} \sin(1000t + 90^\circ)$$

$$V_o(t) = 2 \sin(1000t + 90^\circ)$$

2.116



$$R_{in} = R = 20k\Omega$$

$$|T| = \frac{1}{\omega RC} = 1 \text{ at } \omega = 2\pi \times 10^4 \text{ Hz} \Rightarrow C = \frac{1}{2\pi \times 10^4 \times 20k} = 0.796nF$$

Refer to discussion in page 110:

$\frac{V_o}{V_i} = \frac{R_F/R}{1 + sCR_F}$ and the finite dc gain is $\frac{-R_F}{R}$. Therefore for 40db gain or equivalently $100V/V$ we have: $\frac{-R_F}{R} = -100V/V \Rightarrow R_F = 100 \times 20k = 2M\Omega$

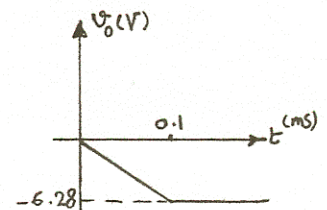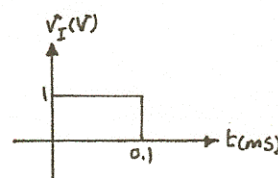The corner frequency $\frac{1}{C R_F}$ is: $\frac{1}{0.796n \times 2M} = 628 \text{ Hz}$



a) when no R_F

$$V_o(t) = \frac{-1}{RC} \int_0^t 1 \cdot dt = -62.8t \quad 0 \leq t \leq 0.1ms$$


$$V_o(0.1) = -6.28V$$

b) with R_F : $V_o(t) = V_o(\infty) (1 - e^{-t/CR_F})$

(Refer to pg. 112)


$$V_o(\infty) = -I \times R_F = -\frac{1V}{20k} \times 2M = -100V$$

$$V_o(t) = -100(1 - e^{-t/1.5})$$

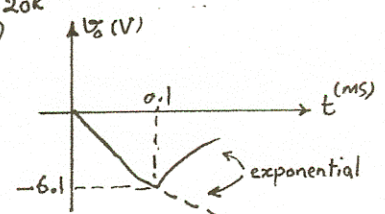

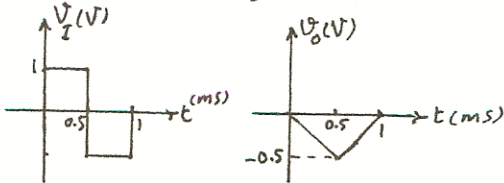2.117

For $0 \leq t \leq 0.5 \text{ ms}$: $V_o(t) = V_o(0) - \frac{1}{RC} \int_0^t V_I dt$
 $V_o(t) = 0 - \frac{t}{RC} = -\frac{t}{1 \text{ ms}}$
 $V_o(0.5) = -0.5 \text{ V}$




For $0.5 \leq t \leq 1 \text{ ms}$: $V_o(t) = V_o(0.5) - \frac{1}{RC} \int_{0.5}^t -1 dt$
 $V_o(t) = -0.5 + \frac{1}{RC} (t - 0.5)$
 $V_o(1 \text{ ms}) = -0.5 + \frac{0.5}{1} = 0 \text{ V}$

Another way of thinking about this circuit is as follows:

For $0 \leq t \leq 0.5 \text{ ms}$ a current $I = \frac{V}{R}$ flows through R and C in the direction indicated on the diagram. At time t we write:
 $I \cdot t = -C \frac{dV_o(t)}{dt} \Rightarrow V_o(t) = -\frac{I}{C} t = -\frac{1}{RC} t$
 which indicates that the output voltage is linearly decreased, reaching -0.5 V at $t = 0.5 \text{ ms}$.

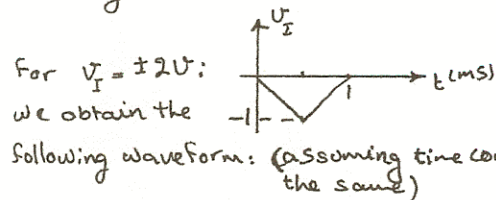Then for $0.5 \leq t \leq 1 \text{ ms}$, the current flows in the opposite direction and V_o rises linearly reaching 0 V at $t = 1 \text{ ms}$.




If RC is also doubled, then the waveform becomes the same as the first case where $V_I = \pm 1 \text{ V}$ and $RC = 1 \text{ ms}$.

2.118

Each pulse lowers the output voltage by:

$$\Delta V_o = \frac{1}{RC} \int_0^{10 \text{ ms}} 1 \cdot dt = \frac{10 \mu\text{s}}{RC} = \frac{10 \mu\text{s}}{1 \text{ ms}} = 10 \text{ mV}$$

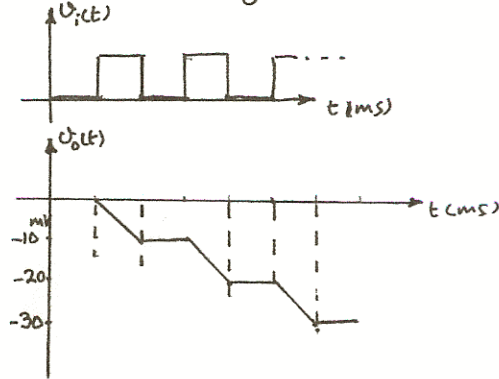Therefore a total of 100 pulses are required to cause a change of 1 V in $V_o(t)$.



2.119

Refer to Fig. P2.119.

$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1} = -\frac{Y_1}{Y_2} = -\frac{\frac{1}{R_1}}{\frac{1}{R_2} + sC} = -\frac{R_2/R_1}{1 + sCR_2}$$

which is an STC LP circuit with a dc gain of $-\frac{R_2}{R_1}$ and a 3-db frequency $\omega_0 = \frac{1}{CR_2}$.


The input resistance equal to R_1 . So for:

$R_1 = 1 \text{ k} \Rightarrow R_1 = 1 \text{ k}\Omega$ and for dc gain of 20 dB or


$$10 : \frac{R_2}{R_1} = 10 \Rightarrow R_2 = 10 \text{ k}\Omega$$

for 3db frequency of 4 kHz: $\omega_0 = 2\pi \times 4 \times 10^3 = \frac{1}{CR_2}$
 $\Rightarrow C = 4 \text{ nF}$

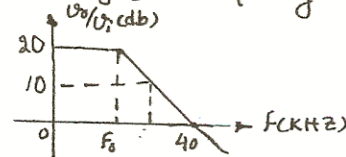the unity gain frequency is (0db) is 40 kHz



2.120

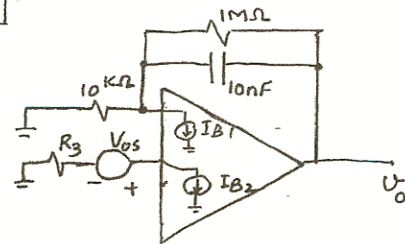

Cont.