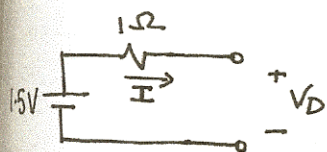


CHAPTER 3 - PROBLEMS

3.1



The diode can be reverse-biased and thus no current would flow, or forward-biased where current would flow.

a) Reverse biased $I = 0A$ $V_D = 1.5V$

b) Forward biased $I = 1.5A$ $V_D = 0V$

3.2

a) Diode is conducting and thus has a 0V drop across it. Consequently

$$V = -3V \checkmark$$

$$I = \frac{3 - (-3)}{10k\Omega} = 0.6mA \checkmark$$

b) Diode is cut off.

$$V = 3V \checkmark \quad I = 0A \checkmark$$

c) Diode is conducting

$$V = 3V \checkmark$$


$$I = \frac{3 - (-3)}{10k\Omega} = 0.6mA \checkmark$$

(d) Diode is cut off.


$$V = -3V \checkmark \quad I = 0A \checkmark$$

3.3

(a)

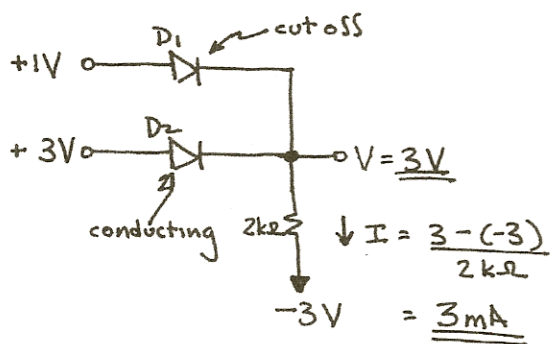


(b)

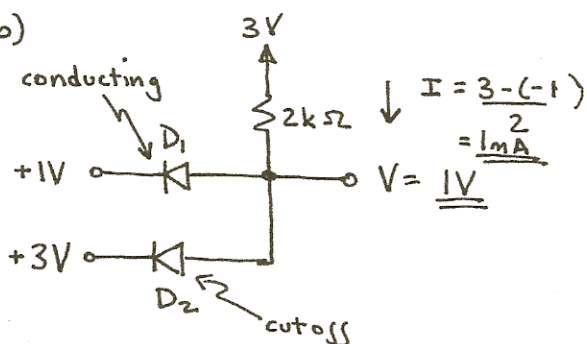

3.4


(a)

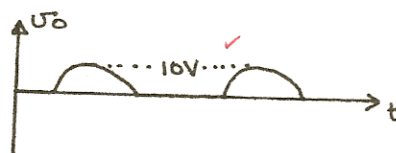

$$V_{pr} = 10V \checkmark \quad V_{p-} = 0V \checkmark$$


$$f = 1kHz$$

CHAPTER 3 PROBLEMS

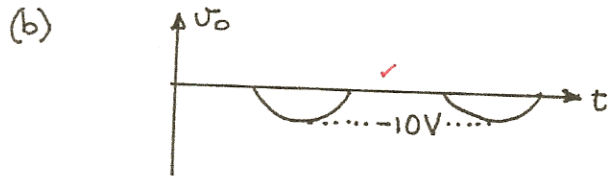


$$V_{p+} = \underline{0V} \quad V_{p-} = \underline{-10V}$$

$$f = 1\text{kHz}$$

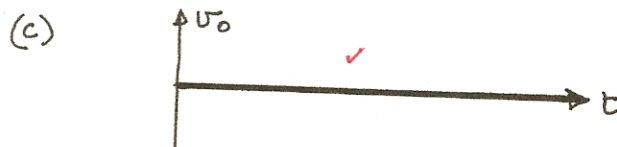


$$v_o = \underline{0V}$$

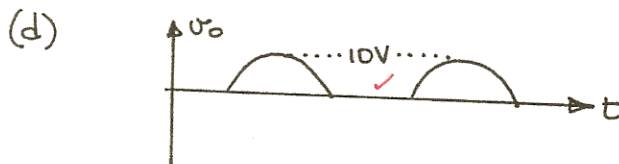Neither D_1 nor D_2 conducts so there is no output.




$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{0V} \quad f = 1\text{kHz}$$

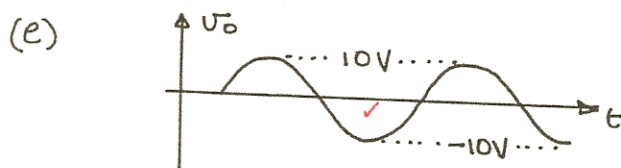Both D_1 and D_2 conduct when $v_i > 0$ just like (a)




$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{-10V} \quad f = 1\text{kHz}$$

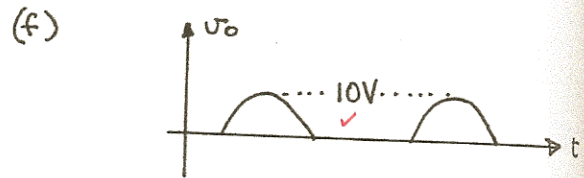D_1 conducts when $v_i > 0$ and D_2 conducts when $v_i < 0$. Thus the output follows the input.




$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{0V} \quad f = 1\text{kHz}$$

$-D_1$ is cutoff when $v_i < 0$

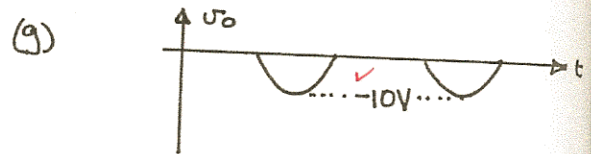


$$V_{p+} = \underline{0V} \quad V_{p-} = \underline{-10V} \quad f = 1\text{kHz}$$

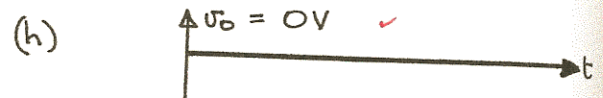D_1 shorts to ground when $v_i > 0$ and is cut off when $v_i < 0$ where the output follows v_i .



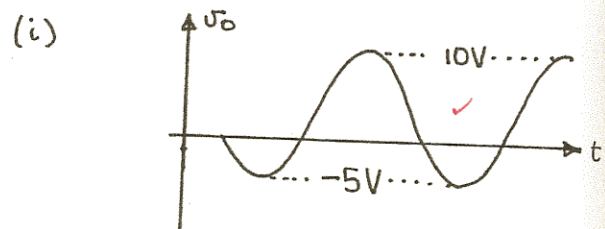$v_o = \underline{0V}$ The output is always shorted to ground as D_1 conducts when $v_i > 0$ and D_2 conducts when $v_i < 0$.




$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{-5V} \quad f = 1\text{kHz}$$

-When $v_i > 0$, D_1 is cutoff and v_o follows v_i .


When $V_I < 0$, D_1 is conducting and the circuit becomes a voltage divider where the negative peak is
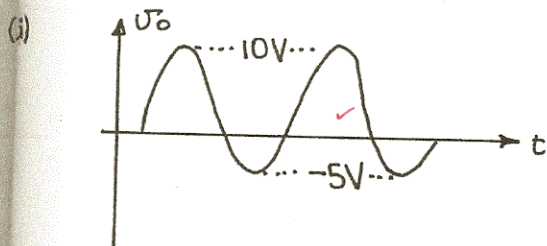
$$\frac{1k\Omega}{1k\Omega + 1k\Omega} \cdot -10V = -5V \checkmark$$



$$V_{p+} = 10V \checkmark \quad V_{p-} = -5V \checkmark \quad f = 1kHz$$

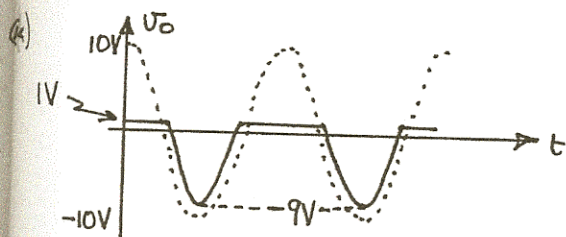When $V_I > 0$, the output follows the input as D_1 is conducting.
When $V_I < 0$, D_1 is cut off and the circuit becomes a voltage divider. ✓



$$V_{p+} = 1V \checkmark \quad V_{p-} = -9V \checkmark \quad f = 1kHz$$



When $V_I > 0$, D_1 is cut off and D_2 is conducting. The output becomes $1V$. ✓

When $V_I < 0$, D_1 is conducting and D_2 is cut off. The output becomes :-

$$V_O = V_I + 1V \checkmark$$

CHAPTER 3 PROBLEMS

3.5

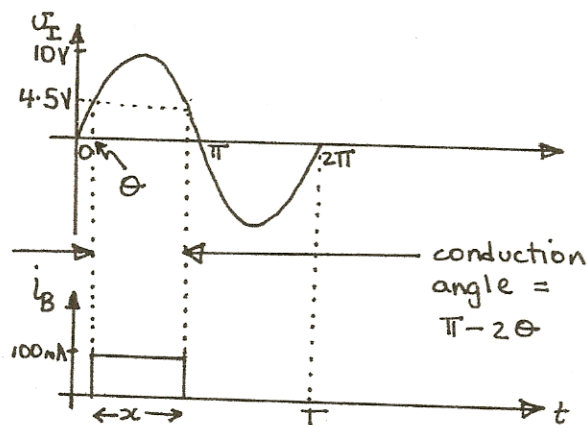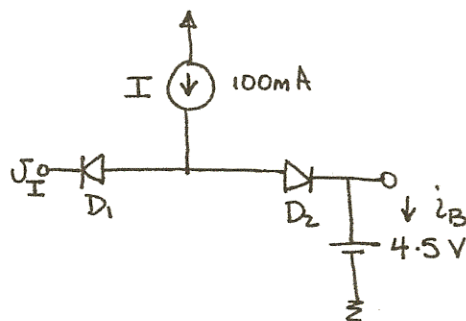

- When $V_I < 4.5V$ D_1 conducts and D_2 is cut off so $i_B = 0A$. For $V_I > 4.5V$ D_2 conducts and D_1 is cut off thus disconnecting the input V_I . All of the current then flows through the battery.

$$10 \sin \theta = 4.5V$$

$$\theta = \sin^{-1}(4.5/10)$$

$$\text{conduction angle} = \pi - 2\theta$$

Fraction of cycle that $i_B = 100mA$ is given by :-

$$x = \frac{\pi - 2\theta}{2\pi} = 0.35$$

3.19

$$i_1 = I_s e^{0.7/V_T} = 10^{-3}$$

$$i_2 = I_s e^{0.5/V_T}$$

$$\frac{i_2}{i_1} = \frac{i_2}{10^{-3}} = e^{\frac{0.5-0.7}{0.025}}$$

$$i_2 = \underline{\underline{0.335 \mu A}}$$

3.20

$$i = I_s e^{V/nV_T} = I_s e^{0.7/0.025} = 5(10^{-3})$$

$$I_s = 5(10^{-3}) e^{-0.7/0.025} = \underline{\underline{3.46 \times 10^{-5} A}}$$

V	i
0.71 V	7.46 mA ✓
0.8 V	273.21 mA ✓
0.69 V	3.35 mA ✓
0.6 V	91.65 μA ✓

$$\text{Let } i_1 = I_s e^{V_1/0.025}$$

$$i_2 = 10 i_1 = I_s e^{V_2/0.025}$$

$$\frac{i_2}{i_1} = 10 = e^{\frac{V_2 - V_1}{0.025}}$$

$$\therefore \Delta V = V_2 - V_1 = \underline{\underline{57.56 mV}}$$

3.21

To calculate I_s use

$$I_s = I e^{-V/nV_T} = I e^{-V/n \times 0.025}$$

To calculate the voltage of the measured current

$$i_2 = 0.01 i_1 \quad \text{so,}$$

$$\frac{i_2}{i_1} = 0.01 = e^{\frac{V_2 - V_1}{nV_T}}$$

$$V_2 = V_1 + nV_T \ln 0.01$$

$$= V + n(0.025) \ln(0.01)$$

V	I	$n=1$ [A]	I_s $n=2$ [A]	V [V]
0.7	1 A	6.91×10^{-13}	8.32×10^{-7}	0.5
0.650	1 mA	5.11×10^{-15}	2.26×10^{-9}	0.55
0.650	10 μA	5.11×10^{-17}	2.26×10^{-11}	0.55
0.7	10 mA	6.91×10^{-15}	8.32×10^{-9}	0.55

3.22

$$\text{Let } I_1 = I_s e^{V_1/nV_T} \quad \text{and}$$

$$I_2 = I_s e^{V_2/nV_T}$$

Calculate n by :-

$$\frac{I_2}{I_1} = e^{\frac{V_2 - V_1}{nV_T}}$$

$$n = \frac{1}{V_T} \left[\frac{V_2 - V_1}{\ln I_2/I_1} \right] = \frac{1}{0.025}$$

Calculate I_s by :-

$$I_s = I_1 e^{-V_1/nV_T}$$

Calculate the diode voltage by :- $V_3 = nV_T \ln \frac{10I_1}{I_s}$

To calculate the voltage at 1% of the measured current use

$$i_2 = 0.01 i_1 \quad \text{so,}$$

$$\frac{i_2}{i_1} = 0.01 = e^{\frac{V_2 - V_1}{n V_T}}$$

$$V_2 = V_1 + n V_T \ln 0.01 \\ = V + n(0.025) \ln(0.01)$$

V [V]	I [A]	$n=1$ [A]	$n=2$ [A]	V [V]	V [V]
0.7	1 A	6.91×10^{-13}	8.32×10^{-7}	0.585	0.470
0.650	1 mA	5.11×10^{-15}	2.26×10^{-9}	0.535	0.420
0.650	10 μ A	5.11×10^{-17}	2.26×10^{-11}	0.535	0.420
0.7	10 mA	6.91×10^{-15}	8.32×10^{-9}	0.584	0.470

3.22

Let $I_1 = I_s e^{V_1/n V_T}$ and

$$I_2 = I_s e^{V_2/n V_T} = I_1/10$$

Calculate n by :-

$$\frac{I_2}{I_1} = e^{\frac{V_2 - V_1}{n V_T}}$$

$$n = \frac{1}{V_T} \left[\frac{V_2 - V_1}{\ln I_2/I_1} \right] = \frac{1}{0.025} \left[\frac{V_2 - V_1}{\ln 0.1} \right]$$

Calculate I_s by :-

$$I_s = I_1 e^{-V_1/n V_T}$$


Calculate the diode voltage at $10I_1$ by :- $V_3 = n V_T \ln \frac{10I_1}{I_s}$

I	V_1 [V]	V_2 [V]	n	I_s [A]	V_3 [V]
10 mA	0.7	0.6	1.737	10^{-9}	0.8
1 mA	0.7	0.6	1.737	10^{-10}	0.8
10 A	0.8	0.7	1.737	10^{-7}	0.9
1 mA	0.7	0.58	2.085	1.47×10^{-9}	0.82
10 μ A	0.7	0.64	1.042	2.15×10^{-17}	0.7

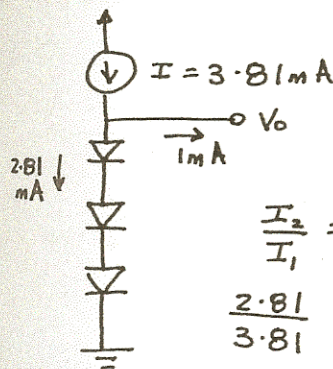3.23

The voltage across each diode is $V_0/3$


$$I = I_s e^{\frac{V_0/3}{n V_T}} = 10^{-14} e^{\frac{2/3}{0.025}} \\ = 3.81 \text{ mA}$$



$$\frac{I_2}{I_1} = e^{\frac{(V_2 - V_1)/3}{0.025}} \\ \frac{2.81}{3.81} = e^{\frac{(V_2 - 2)/3}{0.025}}$$

$$\Delta V = V_2 - 2 = -22.8 \text{ mV}$$

3.24

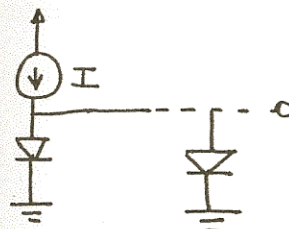

With one diode the current

$$\therefore i_D = i_{D2} = i_{D1} e^{\frac{V_{D2} - V_{D1}}{nV_T}}$$


$$= 1 \times e^{\frac{0.75 - 0.7}{1 \times 0.025}}$$

$$= 7.389 \text{ mA}$$

$$\therefore R = \frac{10 - 3}{i_D} = \frac{10 - 3}{7.389} = \underline{\underline{0.947 \text{ k}\Omega}}$$

3.37

Piecewise linear model:

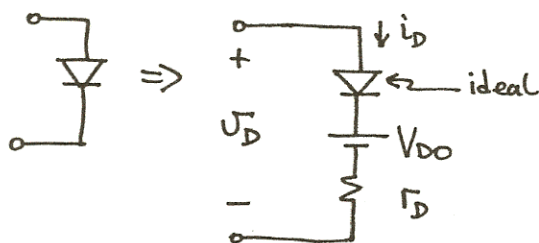

Given $n=2$, $V_D = 0.7 \text{ V}$, $i_D = 1 \text{ mA}$

The current through the diode ^{model} is given by:

$$i_D = \frac{V_D - V_{D0}}{r_D} \quad \text{~ need to find the parameters } V_{D0} \text{ and } r_D$$

Using the exponential model to find the diode voltage at 10 mA

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{V_{D2} - V_{D1}}{nV_T}}$$

$$V_{D2} = nV_T \ln\left(\frac{i_{D2}}{i_{D1}}\right) + V_{D1}$$

$$= 0.815 \text{ V}$$

FINDING V_{D0} & r_D using the given facts:

$$i_D = \frac{0.7 - V_{D0}}{r_D} = 1 \text{ mA} \quad \textcircled{1}$$

$$i_D = \frac{0.815 - V_{D0}}{r_D} = 10 \text{ mA} \quad \textcircled{2}$$

$$\textcircled{2} / \textcircled{1} \Rightarrow \frac{0.815 - V_{D0}}{0.7 - V_{D0}} = 10$$

$$V_{D0} = 0.687 \text{ V}$$

$$r_D = \frac{0.7 - V_{D0}}{1} = \underline{\underline{12.8 \Omega}}$$

Using the piecewise linear ^{model}

$$i_D = \frac{V_D - 0.687}{12.8} \Rightarrow V_D = 0.687 + 12.8 i_D$$

Using the exponential model

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{V_{D2} - 0.7}{0.05}} \Rightarrow V_{D2} = 0.7 + 0.05 \ln\left(\frac{i_{D2}}{i_{D1}}\right)$$

i_D (mA)	PIECEWISE LINEAR V_D (V)	EXPONENTIAL V_D (V)	Error (mV)
0.5	0.693 ✓	0.655	28.0 ✓
5	0.751 ✓	0.780 ✓	-29.5 ✓
14	0.866 ✓	0.832 ✓	34.0 ✓

3.38

Looking at the copy of Fig 3.12 below we see at

$$i_D = 1 \text{ mA} \rightarrow V_D = 0.7 \text{ V}$$

$$i_D = 10 \text{ mA} \rightarrow V_D = 0.8 \text{ V}$$

$$\therefore \text{slope} = \frac{1}{r_D} = \frac{10 - 1}{0.8 - 0.7} = 90 \frac{\text{mA}}{\text{V}}$$

$$\therefore r_D = \frac{1}{90 \times 10^{-3}} = \underline{\underline{11.1 \Omega}}$$

3.64

$$(a) V_z = V_{z0} + r_z I_{zT}$$

$$10 = 9.6 + r_z \times 50 \times 10^{-3}$$

$$r_z = \underline{8 \Omega}$$

Power rating:

$$V_z = V_{z0} + r_z \times 2I_{zT}$$

$$= 9.6 + 8 \times 100 \times 10^{-3}$$

$$= 10.4 \text{ V}$$

$$P = 10.4 \times 100 \times 10^{-3} = \underline{1.04 \text{ W}}$$

$$(b) V_z = V_{z0} + r_z I_{zT}$$

$$9.1 = V_{z0} + 30 \times 10 \times 10^{-3}$$

$$V_{z0} = \underline{8.8 \text{ V}}$$

$$V_z = 8.8 + 30 \times 20 \times 10^{-3} = 9.4 \text{ V}$$

$$P = 9.4 \times 20 \times 10^{-3} = \underline{188 \text{ mW}}$$

$$(c) 6.8 = 6.6 + 2 \times I_{zT}$$

$$I_{zT} = \underline{100 \text{ mA}}$$

$$V_z = 6.6 + 2 \times 200 \times 10^{-3} = 7 \text{ V}$$

$$P = 7 \times 200 \times 10^{-3} = \underline{1.4 \text{ W}}$$

$$(d) 18 = 17.2 + r_z \times 5 \times 10^{-3}$$

$$r_z = \underline{160 \Omega}$$

$$V_z = 17.2 + 160 \times 10 \times 10^{-3} = 18.8 \text{ V}$$

$$P = 18.8 \times 10 \times 10^{-3} = \underline{188 \text{ mW}}$$

$$(e) 7.6 = V_{z0} + 1.5 \times 200 \times 10^{-3}$$

$$V_{z0} = \underline{7.2 \text{ V}}$$

$$V_z = 7.2 + 1.5 \times 400 \times 10^{-3} = 7.8 \text{ V}$$

$$P = 7.8 \times 400 \times 10^{-3} = \underline{3.12 \text{ W}}$$

3.65

(a) Three 6.8 V zeners provide $3 \times 6.8 = 20.4 \text{ V}$ with $3 \times 10 = 30 \Omega$ resistance. Neglecting R , we have


$$\text{Load Regulation} = \underline{-30 \text{ mV/mA}}$$

(b) For 5.1 V zeners we use 4 diodes to provide 20.4 V with $4 \times 30 = 120 \Omega$ resistance.

$$\text{Load regulation} = \underline{-120 \text{ mV/mA}}$$

3.66

Small signal model for line regulation:

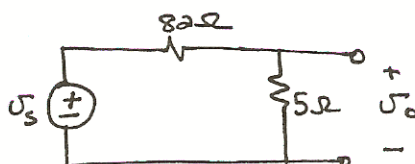

$$\frac{\Delta V_o}{\Delta V_s} = \frac{5}{5 + 82}$$

$$V_o = 5I + V_z$$

$$V_o + \Delta V_o = 5(I + \Delta I) + V_z$$

$$\Delta V_o = 5\Delta I$$


$$= \left(\frac{5}{87}\right) \Delta V_s$$

$$\Delta V_o = \frac{5}{87} \times \Delta V_s$$

$$= \frac{5}{87} \times 1.3$$

$$= \underline{74.7 \text{ mV}}$$

⇒ START HERE

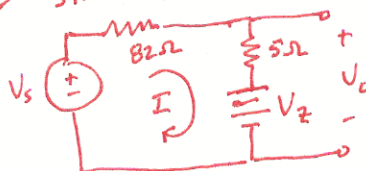


$$V_s = 82I + 5I + V_z$$

$$V_s + \Delta V_s = 82(I + \Delta I) + 5(I + \Delta I) + V_z$$


$$\Delta V_s = 82\Delta I + 5\Delta I$$

$$\Delta I = \frac{\Delta V_s}{87}$$



3.72

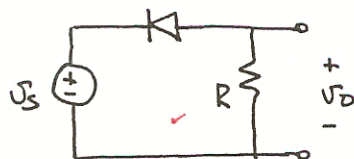

Using the constant voltage drop model:

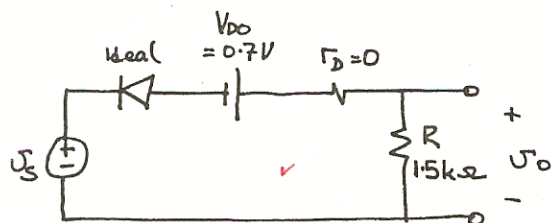

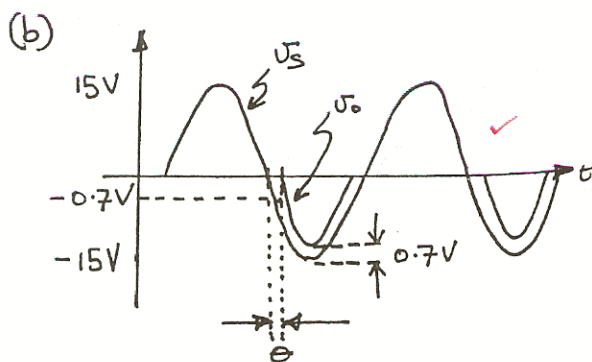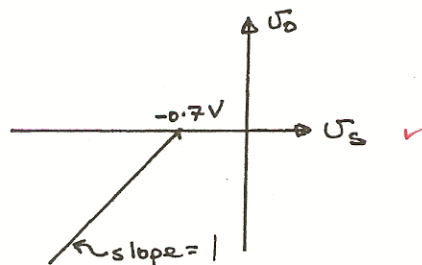- (a) $U_o = U_s + 0.7V$, for $U_s \leq -0.7V$
 $U_o = 0$, for $U_s \geq -0.7V$



- (c) The diode conducts at an angle
 $\theta = \sin^{-1} \frac{0.7}{15} = 2.67^\circ$ & stops
at $\pi - \theta = 177.33^\circ = 3.095 \text{ rad}$
 $\theta = 0.0466 \text{ rad}$ CONT.

Thus the conduction angle is $\pi - 2\theta$
 $= 174.66^\circ$ or 3.05 rad .

$$U_{o, \text{avg}} = \frac{-1}{2\pi} \int_{\theta}^{\pi-\theta} 15 \sin \phi - 0.7 \, d\phi$$

$$= \frac{-1}{2\pi} \left[-15 \cos \phi - 0.7 \phi \right]_{\theta}^{\pi-\theta}$$

$$\cos(\pi - \theta) = -\cos(\theta)$$

$$= \frac{-1}{2\pi} \left[15 \times 2 \cos \theta - 0.7 (\pi - 2\theta) \right]$$

$$= -4.43V$$

- (d) Peak current in diode is:

$$\frac{15 - 0.7}{1.5 \times 10^3} = 9.5 \text{ mA}$$



- (e) PIV occurs when U_s is at its
the peak and $U_o = 0$.

$$\text{PIV} = 15V$$


$$U_o = U_s$$

$$= U_s$$

3.74

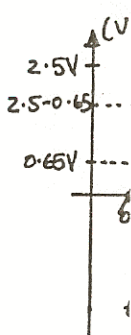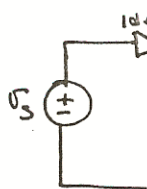

3.73

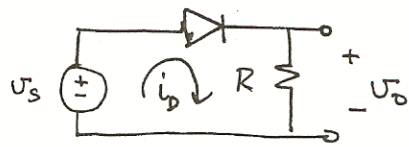

$$i_D = I_S e^{U_D / nV_T}$$

$$\frac{i_D}{i_D(1 \text{ mA})} = e^{\frac{U_D - U_D(\text{at } 1 \text{ mA})}{nV_T}}$$

$$U_D = U_D(\text{at } 1 \text{ mA}) + nV_T \ln(i_D / 10^{-3})$$

$$= " + nV_T \ln\left(\frac{U_D / R}{10^{-3}}\right)$$

$$= " + nV_T \ln(U_D / R) \text{ in } k\Omega$$

find t_1

$$\frac{2.5}{T/4}$$

$$t_2 = T/2$$

$$U_o / \text{avg} =$$

$$=$$

$$=$$

$$=$$