

$$r_{DS} = \frac{V_{DS}}{i_D} = \frac{1}{K'_n \frac{W}{L} V_{OV}} = \frac{1}{126.5 \times 10^{-6} \times \frac{16}{0.8} V_{OV}} = 1000$$

$$\Rightarrow V_{OV} = 0.4V$$

$$V_{GS} = V_{OV} + V_t = 0.4 + 0.7 = 1.1V$$

4.7

$$K'_n = \mu_n C_{ox} = \mu_n \frac{\epsilon_{ox}}{t_{ox}} = 650 \times 10 \times \frac{3.45 \times 10^{-11}}{20 \times 10^{-9}} = 112.1 \mu A/V^2$$

a) triode region: $V_{DS} < V_{GS} - V_t$

$$i_D = K'_n \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$i_D = 112.1 \times 10^{-6} \times 10 \times \left[(5 - 0.8) \times 1 - \frac{1}{2} \times 1^2 \right] = 4.15 mA$$

b) edge of saturation region: $V_{DS} = V_{GS} - V_t$

$$i_D = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2 = \frac{1}{2} \times 112.1 \times 10^{-6} \times 10 \times (1.2)^2 = 0.8 mA$$

c) triode region: $V_{DS} < V_{GS} - V_t$


$$i_D = 112.1 \times 10^{-6} \times 10 \times \left[(5 - 0.8) \times 0.2 - \frac{1}{2} \times 0.2^2 \right] = 0.92 mA$$

d) Saturation region: $V_{DS} > V_{GS} - V_t$

$$i_D = \frac{1}{2} \times 112.1 \times 10^{-6} \times 10 \times (5 - 0.8)^2 = 9.9 mA$$

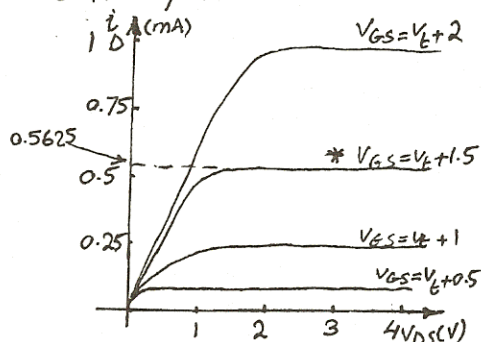4.8

Refer to Fig. 4.11b, $i_D \propto \frac{W}{L}$ so if W is halved, then i_D would also be halved. The vertical axis, i_D , has to be divided by 2:




For $V_{OV} = 1.5V$, by looking at the corresponding curve, $V_{GS} = V_t + 1.5$, we observe that:

$$i_D = 0.5625 mA$$

4.9

4.10

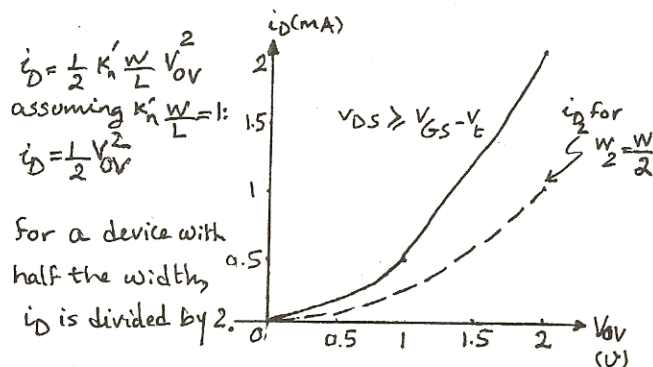

For a device with half the width, i_D is divided by 2.

This graph is not dependent on V_t , while Fig. 4.12 is dependent on V_t .

4.11

$$\text{Eq. 4.13: } r_{DS} = \left[K'_n \frac{W}{L} (V_{GS} - V_t) \right]^{-1} \text{ therefore:}$$

$$\frac{r_{DS1}}{r_{DS2}} = \frac{V_{GS2} - V_t}{V_{GS1} - V_t} \Rightarrow \frac{1000}{200} = \frac{V_{GS2} - 1}{1.5 - 1} \Rightarrow V_{GS2} = 3.5V$$

Now for a device with twice the width:

Cont.

$$\frac{r_{DS1}}{r_{DS2}} = \frac{W_2 (V_{GS2} - V_t)}{W_1 (V_{GS2} - V_t)}$$

for $V_{GS} = 1.5V$ $\frac{r_{DS1}}{r_{DS2}} = 2 \Rightarrow r_{DS2} = \frac{1000}{2} = 500\Omega$
 for $V_{GS} = 3.5V$ $\frac{r_{DS2}}{r_{DS1}} = \frac{200}{2} = 100\Omega$

4.12

$$i_D = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2 \Rightarrow 0.2 \times 10^{-3} = \frac{1}{2} \times 0.1 \times 10^{-3} (V_{GS} - 1)^2$$

$$V_{GS} - 1 = 2 \Rightarrow V_{GS} = 3V$$

$$V_{DSmin} = V_{GS} - V_t = 3 - 1 = 2V$$

for $i_D = 0.8mA$: $0.8 = \frac{1}{2} \times 0.1 (V_{GS} - 1)^2$

$$V_{GS} - 1 = 4 \Rightarrow V_{GS} = 5V$$

$$V_{DSmin} = V_{GS} - V_t = 5 - 1 = 4V$$

4.13

$V_{GS} = V_{DS}$ indicates operation in saturation mode:

$$i_D = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2$$

$$4 = \frac{1}{2} K'_n \frac{W}{L} (5 - V_t)^2$$

$$1 = \frac{1}{2} K'_n \frac{W}{L} (3 - V_t)^2 \Rightarrow 4 = \frac{(5 - V_t)^2}{(3 - V_t)^2}$$

$$(5 - V_t) = 2(3 - V_t) \Rightarrow V_t = 1V, K'_n \frac{W}{L} = 0.5 mA/V^2$$

4.14

$$i_D = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2 \Rightarrow 0.8 = \frac{1}{2} \times 50 \times 10^{-6} \frac{W}{L} (5 - 1)^2$$

$$\frac{W}{L} = 2 \Rightarrow W = 2 \times 2 = 4\mu m$$

4.15

In triode region: $i_D = K'_n \frac{W}{L} [(V_{GS} - V_t)V_{DS} - \frac{V_{DS}^2}{2}]$

$$\frac{i_{D1}}{i_{D2}} = \frac{60\mu A}{160\mu A} = \frac{(2 - V_t)0.1 - 0.01/2}{(4 - V_t)0.1 - 0.04/2} \Rightarrow V_t = 0.75V$$

if $K'_n = 50 \mu A/V^2$: $60 = 50 \frac{W}{L} [(2 - 0.75)0.1 - \frac{0.01}{2}]$

$$\frac{W}{L} = 10$$

If $V_{GS} = 3V, V_{DS} = 0.15V$ then $i_D = 50 \times 10^{-6} [2.25 \times 0.15 - \frac{0.15^2}{2}]$

$$i_D = 163.125 \mu A$$

If $V_{GS} = 3V$, the channel reach pinchoff at $V_{DS} = V_{GS} - V_t = 3 - 0.75 = 2.25V$ for which:

$$i_D = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times 2.25^2 = 1.3mA$$

$$i_D = 1.3mA$$

4.16

For the channel to remain continuous:

$$V_{DS} \leq V_{GS} - V_t \Rightarrow V_{DSmax} = 1.5 - 0.8 = 0.7V$$

4.17

Eq. 4.15: $r_{DS} = [K'_n \frac{W}{L} V_{OV}]^{-1} = \frac{1}{50 \times \frac{100}{5} (V_{GS} - 1)} m\Omega$

$$r_{DS} = \frac{1}{V_{GS} - 1} k\Omega$$

$$V_{GS} = 1.1V \Rightarrow r_{DS} = 10k\Omega$$

$$V_{GS} = 11V \Rightarrow r_{DS} = 100\Omega \Rightarrow 100\Omega \leq r_{DS} \leq 10k\Omega$$

- a) $r_{DS} \propto \frac{1}{W}$ so if W is halved, r_{DS} is doubled:
 $200\Omega \leq r_{DS} \leq 20k\Omega$
- b) $r_{DS} \propto L$ so if L is halved, r_{DS} is also halved: $50\Omega \leq r_{DS} \leq 5k\Omega$
- c) $r_{DS} \propto \frac{L}{W}$ so if both W and L are halved, $\frac{W}{L}$ stays unchanged and so does r_{DS} .
 $100\Omega \leq r_{DS} \leq 10k\Omega$

4.18

According to eq. 4.17: $V_{GD} \leq V_t$ for saturation region. Since V_{GD} is zero in Fig. P4.18, then the device is always in saturation region:

$$i_D = i = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2$$

if we replace V_{GS} by V and $K' = \frac{1}{2} K'_n$

$$i = K' \frac{W}{L} (V - V_t)^2$$

$$r = \left(\frac{\partial i}{\partial V} \right)^{-1} = \frac{1}{2K' \frac{W}{L} (V - V_t)} = \frac{1}{K' \frac{W}{L} V_{OV}} \text{ where } V_{OV} = |V_t| + V_{OV}$$

4.19

$$r_o = \frac{\Delta V_{DS}}{\Delta i_D}$$

to calculate

$$V_A + 4 = 2m$$

$$\lambda = \frac{1}{V_A}$$

4.20

Eq. 4.26

$$r_o = \frac{\Delta V_{DS}}{\Delta i_D}$$

$$i_D = 0.1mA$$

$$i_D = 1mA$$

4.21

$$V_A = V_A' L$$

depend

desired

increas

In orde

has to

$$W = 4\mu m$$

$$V_A = 0$$

$$V_A = 4$$

4.22

$$\lambda = 0.0$$

$$V_A = V$$

Now we calculate R_{Smax} , assuming that the voltage drop across the current source is at least $2V$:

a) $V_1 = 8V$ then $V_{GS} = 3V \Rightarrow V_S = 8 - 3 = 5V$

$$R_{Smax} = \frac{5}{2} = 2.5 k\Omega$$

b) $V_2 = -9 + 2 = -7V$, $V_S = 1 - |V_{GS}| = -2V$

$$R_{Smax} = \frac{-2 - (-7)}{2} = 2.5 k\Omega$$

c) $V_3 = 10 - 2 = 8V$, $V_S = 0 + |V_{GS}| = 3V$

$$R_{Smax} = \frac{8 - 3}{2} = 2.5 k\Omega$$

d) $V_4 = -5 + 2 = -3V$, $V_S = -3 + |V_{GS}| = 0V$

$$R_{Smax} = \frac{5}{2} = 2.5 k\Omega$$

4.34

$$I_D = \frac{V_{DD} - V_D}{R_D} \Rightarrow \frac{5 - 0}{R_D} = 1 mA \Rightarrow R_D = 5 k\Omega \checkmark$$

$$V_D = V_G \Rightarrow \text{saturation}$$

therefore: $i_D = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2$
 $1 = \frac{1}{2} \times 60 \times 10^{-3} \times \frac{100}{3} (V_{GS} - 1)^2 \checkmark$

$$\Rightarrow V_{GS} = 2V \Rightarrow V_S = -2V \checkmark$$

$$R_S = \frac{-2 - (-5)}{1} = 3 k\Omega \checkmark$$

4.35


a) $i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$

$$i_{D1} = 0.2 = \frac{1}{2} \times 200 \times 10^{-6} \times \frac{8}{0.8} (V_{GS1} - 0.6)^2$$

$$V_{GS1} - 0.6 = \sqrt{0.2}$$

$$V_{GS1} = 1.05V$$
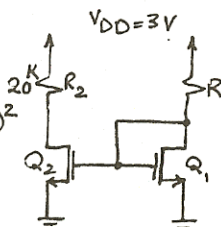
$$R = \frac{3 - 1.05}{0.2} = 9.75 k\Omega$$



b) For Q_2 to conduct $0.5mA$:

$$R_2 = \frac{3 - 1}{0.5} = 4 k\Omega$$

Since the gates are connected together, both transistors have the same V_{GS} and hence same i_D . In order to conduct $0.5mA$ or multiply i_D by 5: $\frac{W_2}{W_1} = 5 \Rightarrow W_2 = 5 \times 8$

$$W_2 = 40 \mu m$$

4.36

Refer to Fig. P4.36.

$$R = \frac{3.5}{0.115} = 3.04 k\Omega$$

$$0.115 = \frac{1}{mA} \times 60 \times 10^{-3} \times \frac{W}{0.8} (-1.5 - (-0.7))^2 \Rightarrow W = 4.8 \mu m$$

4.37

Refer to Fig. P4.37

$$V_{GS1} = 1.5V, 120 \mu A = \frac{1}{2} \times 120 \times \frac{W_1}{1} (1.5 - 1)^2$$

$$\Rightarrow W_1 = 8 \mu m$$

$$V_{GS2} = 3.5 - 1.5 = 2V, 120 = \frac{1}{2} \times 120 \times \frac{W_2}{1} (2 - 1)^2$$

$$\Rightarrow W_2 = 2 \mu m$$

$$R = \frac{5 - 3.5}{0.120} = 12.5 k\Omega$$

4.38

Refer to Fig. P4.38.

$$V_{GS1} = 1.5V, 120 \mu A = \frac{1}{2} \times 120 \times \frac{W_1}{1} (1.5 - 1)^2 \Rightarrow W_1 = 8 \mu m$$

$$V_{GS2} = 2V, 120 \mu A = \frac{1}{2} \times 120 \times \frac{W_2}{1} (2 - 1)^2 \Rightarrow W_2 = 2 \mu m$$

$$V_{GS3} = 1.5V, W_3 = 8 \mu m$$

4.39

Refer to Fig. 4.23a. $V_{GS} = 5 - 6I_D \Rightarrow$

$$I_D = \frac{1}{2} \times 2 \times (5 - 6I_D - 2)^2 \Rightarrow 36I_D^2 - 37I_D + 9 = 0$$

$$\Rightarrow I_D = 0.395 mA \text{ or } 0.633 mA$$

$I_D = 0.633 mA$ is not acceptable, because it results in $V_{GS} = 1.2V$ which is lower than $V_t = 2V$

Therefore $I_D = 0.395 mA \approx 0.4 mA$

$$V_D = 10 - 6I_D = 7.6V$$

These results show that although V_t and $K'_n \frac{W}{L}$ are doubled, I_D is only decreased by 20% and V_D is only increased by 8.5%. Therefore the conclusion is Cent

$$V_{GS} = 1.61V \Rightarrow V_T = 1.61V \quad V_O = 1.61 - 1 = 0.61V$$

Point B: $V_{OB} = 0.61V \quad V_{IB} = 1.61V$

$$b) I_Q = \frac{1}{2} \times 1 \times 0.5^2 = 0.125mA$$

$$V_{OQ} = 5 - 24 \times 0.125 = 2V$$

$$V_{IQ} = V_{GS} = V_{OV} + V_t = 0.5 + 1 = 1.5V$$

Now to calculate the incremental gain

A_v at this bias point, From equation 4.41,

we have: $A_v = -2V_{RD}/V_{OV} = -2(V_{DD} - V_{OQ})/V_{OV}$

$$A_v = -\frac{2(5-2)}{0.5} = -12V/V$$

c) $V_{IQ} = 1.5V$, $V_t = 1V$, $V_{IB} = 1.61V$. Thus the largest amplitude of a sine wave that can be applied to the input while the transistor remains in saturation is: $1.61 - 1.5 = 0.11V$

The amplitude of the output voltage signal that results is approximately equal to $V_{OQ} - V_{OB} = 2 - 0.61 = 1.39V$. The gain implied by this amplitudes is:

$$\text{gain} = \frac{-1.39}{0.11} = -12.64V/V$$

This gain is 5.3% different from the incremental gain calculated in part (b). This difference is due to the fact that the segment of the voltage transfer curve considered here is not perfectly linear.

4.50

$$V_{DS} = 1V = V_{OQ} \Rightarrow I_D = \frac{V_{DD} - V_{OQ}}{R} = \frac{10 - 1}{18} = 0.5mA$$

$$I_D = 0.5 = \frac{1}{2} \times 1 \times V_{OV}^2 \Rightarrow V_{OV} = \sqrt{2I_D} = 1V$$

$$V_{OV} = V_{GS} - V_t \Rightarrow V_{GS} = 2V$$

$$A_v = \frac{-2V_{RD}}{V_{OV}} = \frac{-2 \times 18 \times 0.5}{1} = -18V/V$$

$$V_o^+ = V_{DD} - V_{OQ} = 10 - 1 = 9V$$

$$V_o^- = V_{OQ} - V_{OB}$$

In order to find V_{OB} where $V_{DS} = V_{GS} - V_t$ or

$$V_{OB} = V_{IB} - V_t : V_o = V_{DD} - R_D I_D$$

$$V_{OB} = 10 - 18 \times \frac{1}{2} \times 1 \times V_{OB}^2 \Rightarrow 9V_{OB}^2 + V_{OB} - 10 = 0 \Rightarrow V_{OB} = 1V$$

$$V_o^- = V_{OQ} - V_{OB} = 1 - 1 = 0$$

Using the same formulas we can calculate the

rest of the values for $V_{DS} = 2, 3, \dots, 10V$

V_{DS} (V)	I_D (mA)	V_{OV} (V)	V_{GS} (V)	A_v (V/V)	V_o^+ (V)	V_o^- (V)
1	0.5	1	2	18	9	0
2	0.44	0.94	1.94	17.62	8	1
3	0.39	0.88	1.88	15.9	7	2
4	0.33	0.81	1.81	14.8	6	3
5	0.28	0.75	1.75	13.3	5	4
6	0.22	0.66	1.66	12.1	4	5
7	0.17	0.58	1.58	10.3	3	6
8	0.11	0.47	1.47	8.5	2	7
9	0.06	0.35	1.35	5.7	1	8
10	0	0	1V	0	0	0

4.51

$$R_D = 20k\Omega, V_{RD} = 2V \Rightarrow I_D = 0.1mA$$

$$A_v = -\frac{2V_{RD}}{V_{OV}} \Rightarrow -10 = -\frac{2 \times 2}{V_{OV}} \Rightarrow V_{OV} = 0.4V$$

$$V_{GS} = 1.2V \Rightarrow V_t = 1.2 - 0.4 = 0.8V$$

$$I_D = \frac{1}{2} K'_n \frac{W}{L} V_{OV}^2 \Rightarrow 0.1 = \frac{1}{2} \times 50 \times 10^{-3} \frac{W}{L} 0.4^2$$

$$\Rightarrow \frac{W}{L} = 25$$

4.52

$$\text{Eq. 4.41 : } A_v = -\frac{2(V_{DD} - V_{OQ})}{V_{OV}}$$

$$a) A_{vmax} = -\frac{2(V_{DD} - 0)}{V_{OVmin}} = -\frac{2 \times 5}{0.2} = -50V/V$$

b)

Remove this problem from the assignment.

c)

4.5

From F
Assuming

$$A_v = -\frac{V_o}{V_i}$$

$$A_v = -\frac{V_o}{V_i}$$

$$-A_v V_o + \hat{V}_o = \frac{A_v V_o}{1}$$

$$\hat{V}_o = \frac{A_v V_o}{1}$$

$$V_{DS}(V)$$

$$1$$

$$1.5$$

$$2$$

$$2.5$$

$$I_D = \frac{1}{2}$$

$$R_D = 1$$

4.5

$$i_{D1} = 1$$

Note t

$$\Rightarrow \left(\frac{W}{L}\right)$$

$$\sqrt{\left(\frac{W}{L}\right) / 1}$$

$$V_o = V_{DS}$$

$$\text{If } \left(\frac{W}{L}\right)$$

then:

$$A_v = \frac{\partial V_o}{\partial V_i}$$

4.55

$$I_D = 2.1$$

$$V_{GS} =$$

4.53

From Figure 4.26(c) we have: $\hat{V}_o = V_{DS} - V_{OB}$
Assuming linear operation around the bias point:

$$A_v = -\frac{\hat{V}_o}{V_{IB} - V_{IQ}} = -\frac{\hat{V}_o}{V_{OB} + V_t - V_{IQ}} = -\frac{\hat{V}_o}{V_{OB} + V_t - (V_{OV} + V_t)}$$

$$A_v = -\frac{\hat{V}_o}{V_{OB} - V_{OV}} = -\frac{\hat{V}_o}{V_{OB} - V_{DS} + V_{DS} - V_{OV}} = -\frac{\hat{V}_o}{-\hat{V}_o + V_{DS} - V_{OV}}$$

$$-A_v \hat{V}_o + A_v (V_{DS} - V_{OV}) = -\hat{V}_o \Rightarrow \hat{V}_o (1 - A_v) = -A_v (V_{DS} - V_{OV})$$

$$\hat{V}_o = \frac{A_v (V_{DS} - V_{OV})}{A_v - 1} \Rightarrow \hat{V}_o = \frac{V_{DS} - V_{OV}}{1 - \frac{1}{A_v}}$$

$V_{DS} (V)$	$A_v (\%)$	$\hat{V}_o (V)$	$\hat{V}_i (V)$
1	-16	0.47	0.029
1.5	-14	0.93	0.066
2	-12	1.38	0.12
2.5	-10	1.81	0.18

$$I_D = \frac{1}{2} \times 1 \times (0.5)^2 = 0.125 \text{ mA}$$

$$R_D = \frac{V_{DD} - V_{DS}}{I_D} = \frac{5 - 1}{0.125} = 32 \text{ k}\Omega$$

4.54

$$i_{D1} = i_{D2} \Rightarrow \frac{1}{2} K'_n \left(\frac{W}{L}\right)_1 (V_{GS1} - V_t)^2 = \frac{1}{2} K'_n \left(\frac{W}{L}\right)_2 (V_{GS2} - V_t)^2$$

Note that $V_{GS1} = V_I$

$$V_{GS2} = V_{DD} - V_o$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 (V_I - V_t)^2 = \left(\frac{W}{L}\right)_2 (V_{DD} - V_o - V_t)^2$$

$$\sqrt{\left(\frac{W}{L}\right)_1 / \left(\frac{W}{L}\right)_2} (V_I - V_t) = V_{DD} - V_o - V_t$$

$$V_o = V_{DD} - V_t + \sqrt{\left(\frac{W/L}{W/L}\right)_1} V_t - \sqrt{\left(\frac{W/L}{W/L}\right)_1} V_I$$

$$\text{If } \left(\frac{W}{L}\right)_1 = \frac{50}{0.5} = 100 \quad \left(\frac{W}{L}\right)_2 = \frac{5}{0.5} = 10$$

then:

$$A_v = \frac{\partial V_o}{\partial V_I} = -\sqrt{\frac{100}{10}} = -3.16 \text{ V/V}$$

4.55

$$I_D = 2 \text{ mA} = \frac{1}{2} \times 80 \times 10^{-3} \times \frac{240}{6} \times (V_{GS} - 1.2)^2 \Rightarrow V_{GS} = 2.32 \text{ V} \quad \text{Refer to Fig. 4.30c}$$

$$R_D I_D = \frac{15}{3} = 5 \text{ V} \Rightarrow R_D = \frac{5}{2 \text{ mA}} = 2.5 \text{ k}\Omega$$

$$R_S I_D = 5 \text{ V} \Rightarrow R_S = \frac{5}{2} = 2.5 \text{ k}\Omega$$

$$V_G = 5 + V_{GS} = 7.32 \text{ V}$$

$$\frac{15}{R_{G1} + R_{G2}} \times R_{G2} = 7.32 \quad R_{G1} = 22 \text{ M}\Omega \Rightarrow R_{G2} = 20.97 \text{ M}\Omega$$

$$V_{DS} = 5 \text{ V}$$

at the edge of saturation $V_{DS} = V_{GS} - V_t$ or $V_{DS} = 2.32 - 1.2 = 1.12 \text{ V}$. So V_{DS} is $5 - 1.12 = 3.88 \text{ V}$ away from the edge of saturation.

4.56

Refer to Fig. 4.30e

$$I_D = 2 \text{ mA} = \frac{1}{2} K'_n \frac{W}{L} V_{OV}^2 \Rightarrow 2 = \frac{1}{2} \times 50 \times 10^{-3} \times \frac{200}{4} V_{OV}^2$$

$$V_{OV} = 1.26 \text{ V}$$

$$V_{DS} = V_{OV} \text{ edge of triode}$$

Midway of cutoff ($V_{DS} = V_{DD}$) and beginning of triode operation ($V_{DS} = V_{OV}$) is when $V_{DS} = \frac{30 + 1.26}{2}$

$$V_{DS} = 15.63 \text{ V}$$

$$V_{GS} = 2.32 \text{ V} \Rightarrow V_S = -2.32 \text{ V} \Rightarrow R_S = \frac{-2.32 + 15}{2}$$

$$R_S = 6.34 \text{ k}\Omega$$

$$V_D = V_S + V_{DS} = -2.32 + 15.63 = 13.31 \text{ V} \Rightarrow R_D = \frac{15 - 13.31}{2}$$

$$R_D = 0.85 \text{ k}\Omega$$

4.57

$$V_G = 12 \times \frac{2.2}{2.2 + 5.6} = 3.4 \text{ V}$$

$$K'_n \frac{W}{L} = 220 \text{ to } 380 \text{ } \mu\text{A/V}^2$$

$$V_t = 1.3 \text{ to } 2.4 \text{ V}$$

$$I_D = \frac{1}{2} \times K'_n \frac{W}{L} (3.4 - V_t)^2$$

$$I_{Dmin} = \frac{1}{2} \times 220 (3.4 - 2.4)^2 = 110 \text{ } \mu\text{A}$$

$$I_{Dmax} = \frac{1}{2} \times 380 (3.4 - 1.3)^2 = 838 \text{ } \mu\text{A}$$

to limit I_{Dmax} to $150 \text{ } \mu\text{A}$:

$$150 = \frac{1}{2} \times 380 (3.4 - 0.15 R_S - 1.3)^2$$

$$R_S = 8.1 \text{ k}\Omega$$


$$\text{Select } R_S = 8.2 \text{ k}\Omega$$

$$I_{Dmax} = \frac{1}{2} \times 380 \times (3.4 - I_{Dmax} \times 8.2 - 1.3)^2$$

$$I_{Dmax} = 0.15 \text{ mA or } 0.44 \text{ mA}$$

The second answer results in negative V_{GS}

Cont.

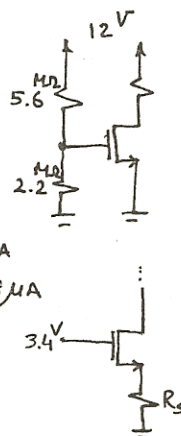


and therefore it is not acceptable.

$$I_{Dmin} = \frac{1}{2} \times 0.22 \times (3.4 - 8.2 I_{Dmin} - 2.4)^2$$

$$I_{Dmin} = 0.04 \text{ mA}$$

4.58

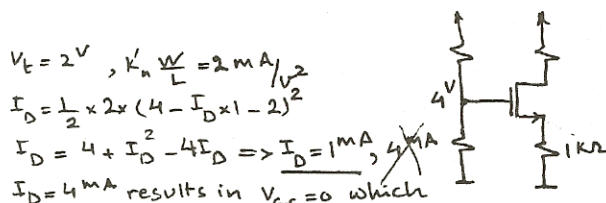

$$V_t = 2V, K_n \frac{W}{L} = 2 \text{ mA/V}^2$$

$$I_D = \frac{1}{2} \times 2 \times (4 - I_D \times 1 - 2)^2$$

$$I_D = 4 + I_D^2 - 4I_D \Rightarrow I_D = 1 \text{ mA}$$

$I_D = 4 \text{ mA}$ results in $V_{GS} = 0$ which

is not acceptable, therefore $I_D = 1 \text{ mA}$.

For $K_n \frac{W}{L}$ 50% larger, i.e. $K_n \frac{W}{L} = 3 \text{ mA/V}^2$

$$I_D = \frac{1}{2} \times 3 \times (4 - I_D - 2)^2 \Rightarrow I_D = 1.13 \text{ mA}$$

I_D increases by 13%.

4.59

Refer to Fig. 4.30.c

$$V_{GS} = 5 - 2 = 3V, I_D = \frac{V_S}{R_S} = \frac{2}{1} = 2 \text{ mA}$$

$$I_D = 2 = \frac{1}{2} \times 2 \times (3 - V_t)^2 \Rightarrow 1.41 = 3 - V_t \Rightarrow V_t = 1.59V$$

For a device with $V_t = 1.59 - 0.5 = 1.09V$:

$$I_D = \frac{1}{2} \times 2 \times (5 - I_D \times 1 - 1.09)^2 \Rightarrow I_D = 2.37 \text{ mA}$$

$$V_S = 2.37V$$

4.60

To maximize gain, we design for

the lowest possible V_D consistent

with allowing a 2V p-p signal

swing. $V_{Dmin} = V_D - 1$ ✓


$$V_{Dmin} = V_G - V_t = 0 - 2$$
 ✓

$$V_D - 1 = -2 \Rightarrow V_D = -1V \Rightarrow R_D = \frac{10 - (-1)}{1 \text{ mA}} = 11 \text{ k}\Omega$$
 ✓

$$I_D = \frac{1}{2} \times 2 \times [0 - (-10 + 1 \times R_S) - 2]^2 = 1 \Rightarrow 1 = (8 - R_S)^2$$

$$R_S = 7 \text{ k}\Omega$$

V_{GS}

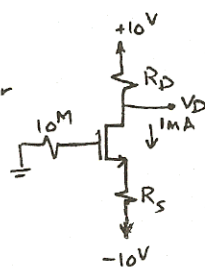

4.61

For P-channel MOSFET to be 1V from the edge

of saturation: $V_{DS} = V_{GS} - V_t - 1$. Since $V_D = 3V$

and $I_D = 1 \text{ mA}$: $R_D = \frac{3}{1} = 3 \text{ k}\Omega$, $R_1 + R_2 = \frac{10V}{10 \mu A} = 1 \text{ M}\Omega$

$$a) |V_t| = 1V, K_p \frac{W}{L} = 0.5 \text{ mA/V}^2$$

$$I_D = 0.5 \times \frac{1}{2} \times (V_{GS} + 1)^2 = 1 \Rightarrow V_{GS} = -3V$$

$$V_{DS} = -3 + 1 - 1 = -3V$$

$$V_S = 6V, V_G = 3V, R_S = \frac{10 - 6}{4 \mu A} = 1 \text{ k}\Omega$$

$$\frac{R_2}{R_1 + R_2} = \frac{3}{10} \Rightarrow R_1 = 0.7 \text{ M}\Omega, R_2 = 0.3 \text{ M}\Omega$$

$$b) |V_t| = 2V, K_p \frac{W}{L} = 1.25 \text{ mA/V}^2$$

$$1 = \frac{1}{2} \times 1.25 \times (V_{GS} + 2)^2 \Rightarrow V_{GS} = -3.26V \text{ or } -0.74V$$

the second answer is not acceptable $|V_{GS}| < |V_t|$

$$V_{GS} = -3.26V$$

$$V_{DS} = -3.26 + 2 - 1 = -2.26V$$

$$V_S = 3 + 2.26 = 5.26V$$

$$V_G = 2V$$

$$R_S = \frac{10 - 5.26}{4 \mu A} = 1.18 \text{ k}\Omega, R_D = 3 \text{ k}\Omega$$

$$\frac{R_2}{R_1 + R_2} = \frac{2}{10} \Rightarrow R_2 = 0.2 \text{ M}\Omega, R_1 = 0.8 \text{ M}\Omega$$

4.62

$$K = \frac{1}{2} K_n \frac{W}{L}$$

$$a) I_D = \frac{1}{2} K_n \frac{W}{L} (V_{GS} - V_t)^2$$

$$I_D = K (V_{GS} - V_t)^2$$

$$\frac{\partial I_D}{\partial K} = (V_{GS} - V_t)^2 + 2K(V_{GS} - V_t)(-R_S) \frac{\partial I_D}{\partial K}$$

$$\frac{\partial I_D}{\partial K} = \frac{I_D}{K} - 2R_S \sqrt{\frac{I_D}{K}} K \frac{\partial I_D}{\partial K}$$

$$\frac{\partial I_D}{\partial K} (1 + 2\sqrt{K I_D} R_S) = \frac{I_D}{K} \Rightarrow S_{I_D}^K = \frac{\partial I_D}{\partial K} \frac{K}{I_D} = \frac{1}{1 + 2\sqrt{K I_D} R_S}$$

$$b) K = 100 \mu A/V^2, \frac{\Delta K}{K} = \pm 10\%, V_t = 1V, I_D = 100 \mu A$$

$$\frac{\Delta I_D}{I_D} = \pm 1\%$$


$$S_{I_D}^K = \frac{\partial I_D / I_D}{\partial K / K} = \frac{1}{10} = 0.1 = \frac{1}{1 + 2\sqrt{100 \times 10^{-3} \times 100 \times 10^{-3}} R_S}$$

$$\Rightarrow R_S = 45 \text{ k}\Omega$$

Cont.

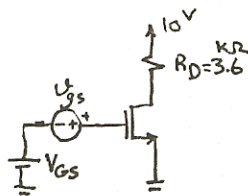4.69

$$\begin{aligned} a) I_D &= \frac{1}{2} \times 1 \times (4-2)^2 = 2 \text{ mA} \\ V_D &= V_{DD} - R_D I_D = 10 - 2 \times 3.6 \\ V_D &= 2.8 \text{ V} \end{aligned}$$



$$\begin{aligned} b) g_m &= k'_n \frac{W}{L} V_{ov} = 1 \times (4-2) = 2 \text{ mA/V} \\ c) A_v &= \frac{V_D}{V_{GS}} = -g_m R_D = -2 \times 3.6 = -7.2 \text{ V/V} \end{aligned}$$


$$\begin{aligned} d) r_o &\approx \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 2} = 50 \text{ k}\Omega \\ A_v &= \frac{V_D}{V_{GS}} = -g_m (R_D || r_o) = -2(3.6 || 50) = -6.7 \text{ V/V} \end{aligned}$$

4.70

$$g_m R_D = 5 \Rightarrow g_m = \frac{5}{50 \text{ k}\Omega} = 0.1 \text{ mA/V}$$

For 0.5V output signal and

$$\text{a gain of } 5 \text{ V/V}, V_{GS} = \frac{0.5}{5} = 0.1 \text{ V}$$

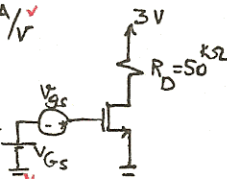So we can write $V_{DS} - 0.5 \gg V_{GS} + 0.1 - V_t$

$$\text{or } V_{DS} \gg V_{GS} + 0.6 - 0.8 \Rightarrow V_{DS} \gg V_{GS} - 0.2$$

Also, from the other side: $V_{DS} + 0.5 \leq V_{DD}$

$$\text{or } V_{DS} \leq 3 - 0.5 \Rightarrow V_{DS} \leq 2.5 \text{ V}$$

We design the circuit for lowest possible V_{DS} that guarantees the device operation in saturation: $V_{DS} = V_{GS} - 0.2$

$$V_{DS} = V_{DD} - R_D I_D \Rightarrow V_{GS} - 0.2 = 3 - (50 \times I_D)$$

$$\Rightarrow I_D = \frac{3.2 - V_{GS}}{50}$$

$$\text{Also, from eq. 4.71: } g_m = \frac{2 I_D}{V_{GS} - V_t} = 0.1$$

$$g_m = 0.1 = \frac{2}{V_{GS} - 0.8} \times \frac{3.2 - V_{GS}}{50}$$

$$\Rightarrow V_{GS} = 1.49 \text{ V}, I_D = 0.034 \text{ mA}$$

$$V_{DS} = 1.49 - 0.2 = 1.29 \text{ V}, V_{ov} = 1.49 - 0.8 = 0.69 \text{ V}$$

$$\frac{W}{L} = \frac{I_D}{\frac{1}{2} k'_n V_{ov}^2} = \frac{0.034 \times 10^{-3}}{\frac{1}{2} \times 100 \times 0.69^2} = 1.43$$

$$\frac{W}{L} = 1.43$$

both num & denom $\times 10^6$

4.71

$$\begin{aligned} A_v &= -g_m R_D \\ g_m &= \frac{2 I_D}{V_{ov}} \quad \text{eq. 4.71} \end{aligned} \Rightarrow A_v = -\frac{2 R_D I_D}{V_{ov}} = -\frac{2(V_{DD} - V_D)}{V_{ov}}$$

Minimum V_{DS} for edge of saturation:

$$V_{DS} \geq V_{GS} - V_t \quad \text{or } V_{DSmin} = V_{GSmax} - V_t$$

$$V_{DS} - |A_v| \hat{V}_i = V_{GS} + \hat{V}_i - V_t$$

If we replace A_v with ①:

$$V_D - \frac{2(V_{DD} - V_D)}{V_{ov}} \hat{V}_i = V_{GS} + \hat{V}_i$$

$$\Rightarrow V_D (1 + \frac{2 \hat{V}_i}{V_{ov}}) = V_{ov} + \hat{V}_i + \frac{2 V_{DD} \hat{V}_i}{V_{ov}}$$

$$V_D = \frac{V_{ov} + \hat{V}_i + 2 V_{DD} (\hat{V}_i / V_{ov})}{1 + 2 (\hat{V}_i / V_{ov})}$$

$$V_{DD} = 3 \text{ V}, \hat{V}_i = 20 \text{ mV}, m = 10 = \frac{V_{ov}}{V_t} \Rightarrow V_{ov} = 0.2 \text{ V}$$

$$V_D = \frac{0.2 + 0.02 + 2 \times 3 \times 0.01}{1 + 2 \times 0.1} = 0.68 \text{ V}$$

$$A_v = -\frac{2(3 - 0.68)}{0.2} = -23.2 \text{ V/V}$$

If $I_D = 100 \mu\text{A} = 0.1 \text{ mA}$:

$$A_v = -\frac{2 R_D I_D}{V_{ov}} \Rightarrow 23.2 = \frac{2 \times R_D \times 0.1}{0.2}$$

$$R_D = 23.2 \text{ k}\Omega$$

$$\begin{aligned} I_D &= \frac{1}{2} k'_n \frac{W}{L} V_{ov}^2 \Rightarrow 0.1 = \frac{1}{2} \times 100 \times 10^{-8} \frac{W}{L} 0.2^2 \\ \Rightarrow \frac{W}{L} &= 50 \end{aligned}$$

4.72

$$k'_n = \mu_n C_{ox} = 500 \times 10^8 \times 0.4 \times 10^{-15} = 20 \text{ mA/V}^2, k'_p = 10 \text{ mA/V}^2$$

Case	Type	I_D (mA)	$ V_{GS} $ (V)	$ V_t $ (V)	V_{ov} (V)	W (μm)	L (μm)	$\frac{W}{L}$	$\frac{W}{L}$ (mA/V ²)	g_m (mA/V)
a	N	1	3	2	1	100	1	100	2	2
b	N	1	1.2	0.7	0.5	50	$\frac{1}{8}$	400	8	4
c	N	10	?	?	2	250	1	250	5	10
d	N	0.5	?	?	0.5	?	?	200	4	2
e	N	0.1	?	?	1.41	10	2	5	0.1	0.14
f	N	0.1	1.8	0.8	1	40	4	10	0.2	0.2
g	P	1	?	?	2	?	?	25	0.25	1
h	P	1	3	1	2	?	?	50	0.5	1
i	P	10	?	?	1	4000	2	2000	20	20

Cont.

Case Type

j P
k P
l P


4.73

Eq. 4.7C

$$\frac{W}{L} = \frac{1}{2 \times \dots}$$

$$g_m = \frac{2}{\dots}$$

4.74

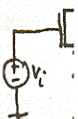

$$\frac{V_o}{V_i} = \dots$$

$$\frac{V_o}{V_i} = \dots$$

4.7

$$r_o \approx \frac{V_A}{I_D}$$

$$g_m = \frac{2}{V_{ov}}$$

$$g_m = \dots$$

$$\frac{V_o}{V_i} = \dots$$

$$\frac{V_o}{V_i} = \dots$$

$$\frac{V_o}{V_i} = \dots$$

4.78

$i_D = \frac{1}{2} K'_n \frac{W}{L} v_{ov}^2$
 The equation for the tangent line passing from point A (v_{ov}, i_D) can be written as:

$$(i_D - I_D) = \left. \frac{\partial i_D}{\partial v_{ov}} \right|_{v_{ov}=V_{ov}} (v_{ov} - V_{ov})$$

$$\left. \frac{\partial i_D}{\partial v_{ov}} \right|_{i_D=I_D} = K'_n \frac{W}{L} v_{ov}$$

$$\Rightarrow i_D - I_D = K'_n \frac{W}{L} v_{ov} (v_{ov} - V_{ov})$$

$$i_D - \frac{1}{2} K'_n \frac{W}{L} v_{ov}^2 = K'_n \frac{W}{L} v_{ov} (v_{ov} - V_{ov})$$

The tangent intersects the v_{ov} axis at $i_D = 0$

$$0 - \frac{1}{2} K'_n \frac{W}{L} v_{ov}^2 = K'_n \frac{W}{L} v_{ov} (v_{ov} - V_{ov})$$

$$-\frac{v_{ov}}{2} = v_{ov} - V_{ov} \Rightarrow v_{ov} = \frac{V_{ov}}{2}$$

The slope of the tangent is g_m and it is

$$\text{equal to: } g_m = \frac{\Delta i_D}{\Delta v_{ov}} = \frac{I_D}{v_{ov} - \frac{v_{ov}}{2}} = \frac{I_D}{\frac{v_{ov}}{2}} = \frac{2I_D}{v_{ov}}$$

4.79

For this common-source amplifier we have:

$$g_m = \frac{2 \text{ mA}}{V} , r_o = 50 \text{ k}\Omega , R_D = 10 \text{ k}\Omega$$

$$R_G = 10 \text{ M}\Omega , R_{sig} = 0.5 \text{ M}\Omega \text{ and } R_L = 20 \text{ k}\Omega$$

From equation 4.82 we have:

$$G_v = - \frac{R_G}{R_G + R_{sig}} g_m (r_o \parallel R_D \parallel R_L) = - \frac{10 \times 2}{10 + 0.5} (50 \parallel 10 \parallel 20) \checkmark$$

$$G_v = -11.2 \text{ V/V} \checkmark$$

4.80

a) $A_{v_o} = -2 \frac{(V_{DD} - V_D)}{V_{ov}} = -2 \frac{(10 - 2.5)}{1} = -15 \text{ V/V}$

b) If V_{ov} is halved ($V_{ov} = 0.5$) then I_D is divided by 4, i.e. $I_D = \frac{0.5}{4} = 0.125 \text{ mA}$

Since V_D is kept unchanged at 2.5 V then:

$$R_D = \frac{10 - 2.5}{0.125} = 60 \text{ k}\Omega , g_m = \frac{2I_D}{V_{ov}} = \frac{0.5 \text{ mA}}{V}$$

$$r_o = \frac{V_A}{I_D} \Rightarrow r_o = 4 \times r_{o1} = 4 \times \frac{75}{0.5} = 600 \text{ k}\Omega$$

$$A_{v_o} = -15 \times 2 = -30 \text{ V/V (without } r_o)$$

c) If we take r_o into account:

$$A_{v_o} = -g_m (r_o \parallel R_D) = -0.5 (600 \parallel 60 \text{ k}) = -27.3 \text{ V/V}$$

$$R_{out} = R_D \parallel r_o = 60 \text{ k} \parallel 60 \text{ k} = 30 \text{ k}\Omega$$

d) $R_{in} = R_G = 4.7 \text{ M}\Omega$

$$R_o = R_{out} = 30 \text{ k}\Omega$$

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_{v_o} \frac{R_L}{R_L + R_o} = \frac{4.7}{4.7 + 0.1} \times \frac{27.3 \times 15}{15 + 30}$$

$$G_v = 5.77 \text{ V/V}$$

e) As we can see by reducing V_{ov} to half of its value or equivalently multiplying drain current by 4, A_{v_o} is almost doubled, while R_{out} is multiplied by 4.

As a result G_v which is proportional to both

A_{v_o} and $\frac{1}{R_{out}}$ is only slightly reduced.

(G_v was -7 V/V before and it is 5.8 V/V now)

4.81

For an NMOS common-gate amplifier with

$g_m = 5 \text{ mA/V}$, $R_D = 5 \text{ k}\Omega$, $R_L = 2 \text{ k}\Omega$, $R_{sig} = 200 \Omega$ we have:

$$R_{in} = \frac{1}{g_m} = \frac{1}{5} = 0.2 \text{ k}\Omega = 200 \Omega$$

From Eq. 4.96b we know that the overall

voltage gain of this amplifier is:

$$G_v = \frac{g_m (R_D \parallel R_L)}{1 + g_m R_{sig}} = \frac{5 (5 \parallel 2 \text{ k})}{1 + 5 \times 0.2} = 3.57 \text{ V/V}$$

If we increase the bias current by a factor of 4, while maintaining the other parameter constant (assuming linear operation), we have:

$$g_m = \sqrt{2 K'_n \frac{W}{L} I_D} \Rightarrow \frac{g_{m2}}{g_{m1}} = \sqrt{\frac{I_{D2}}{I_{D1}}} = \sqrt{4} = 2$$

$$g_m = 2 \times 5 = 10 \text{ mA/V}$$

$$R_{in} = \frac{1}{g_m} = 0.1 \text{ k}\Omega = 100 \Omega$$

$$G_v = g_m \frac{R_D \parallel R_L}{1 + g_m R_{sig}} = 10 \frac{(5 \parallel 2 \text{ k})}{1 + 10 \times 0.2} = 4.76 \text{ V/V}$$

4.82

Refer

 $G_{v1} = -$ $\frac{G_{v2}}{G_{v1}}$

4.83

Eq. 4

 $G_{v1} = -$ $\frac{G_{v1}}{G_{v2}}$ $g_m = 1$

In or

 $\frac{G_{v1}}{G_{v2}}$

4.84

 $A_{v_o} = 0$

Eq. 4.1

 $g_m = 1$

Eq. 4.

 $\Rightarrow r_o$

4.8

we h

Eq. 4.

 $A_{v_o} = 1$
From

with

 $\Rightarrow A_v$

4.82

Refer to Eq. 4.90: $G_v = \frac{R_G}{R_G + R_{S,ig}} \frac{g_m (R_D \parallel R_L)}{1 + g_m R_S}$ $G_{v1} = -16 V/V$ reduced by factor of 4:

$$\frac{G_{v2}}{G_{v1}} = \frac{1}{1 + g_m R_S} \Rightarrow \frac{1}{4} = \frac{1}{1 + 2R_S} \Rightarrow R_S = 1.5 k\Omega$$

4.83

$$\text{Eq. 4.90: } G_v = \frac{R_G}{R_G + R_{S,ig}} \frac{g_m (R_D \parallel R_L)}{1 + g_m R_S}$$

 $G_v = -10 V/V$ for $R_S = 1 k\Omega$ and $G_v = -20 V/V$ for $R_S = 0$

$$\frac{G_{v1}}{G_{v2}} = \frac{1 + g_m R_{S2}}{1 + g_m R_{S1}} \Rightarrow \frac{10}{20} = \frac{1 + g_m \times 0}{1 + g_m \times 1} \Rightarrow 1 + g_m = 2$$

$$g_m = 1 \text{ mA/V}$$

In order to have $G_v = -8 V/V$:

$$\frac{G_{v1}}{G_{v3}} = \frac{20}{8} = \frac{1 + g_m R_{S3}}{1 + 0} \Rightarrow 1 + R_{S3} = 2.5 \Rightarrow R_{S3} = 1.5 k\Omega$$

4.84

 $A_{v0} = 0.98 V/V$ and $A_v = \frac{0.98}{2} = 0.49 V/V$ for $R_L = 500 \Omega$

$$\text{Eq. 4.102a: } A_v = \frac{R_L}{R_L + \frac{1}{g_m}} \Rightarrow 0.49 = \frac{0.5}{0.5 + \frac{1}{g_m}} \Rightarrow$$

$$g_m = 1.92 \text{ mA/V}$$

$$\text{Eq. 4.103: } A_{v0} = \frac{r_o}{r_o + \frac{1}{g_m}} \Rightarrow 0.98 = \frac{r_o}{r_o + 0.52}$$

$$\Rightarrow r_o = 25.5 k\Omega$$

4.85

we have $g_m = 5 \text{ mA/V}$ and $r_o = 20 k\Omega$. From

$$\text{Eq. 4.103 we know: } A_{v0} = \frac{r_o}{r_o + \frac{1}{g_m}} = \frac{20}{20 + \frac{1}{5}} = 0.99 V/V$$

$$A_{v0} = 0.99 V/V$$

$$\text{From Eq. 4.105: } R_{out} = \frac{1}{g_m} \parallel r_o = \frac{1}{5} \parallel 20^k = 198 \Omega$$

$$R_{out} \leq 200 \Omega$$

With $R_L = 1 k\Omega$ we have:

$$A_v = \frac{R_L \parallel r_o}{(R_L \parallel r_o) + \frac{1}{g_m}} = \frac{1k \parallel 20^k}{(1k \parallel 20^k) + \frac{1}{5}}$$

$$\Rightarrow A_v = 0.83 V/V$$

4.86

$$R_{i2} = \frac{1}{g_{m2}} = 50 \Omega \Rightarrow g_{m2} = \frac{1}{0.05} = 20 \text{ mA/V}$$

if Q_1 is biased the same as Q_2 , then $g_{m1} = g_{m2}$

$$i_{D1} = g_{m1} V_i = 20 \times 5 \text{ mV} = 100 \mu\text{A} = 0.1 \text{ mA}$$

$$V_{D1} = i_{D1} \times 50 \Omega = 0.5 \text{ V}$$

In order to have $V_{D2} = V_{D1} = 1 \text{ V}$:

$$V_{D2} = I_D R_D \Rightarrow 1 = 0.1 \times R_D \Rightarrow R_D = 10 k\Omega$$

4.87

$$\text{a) } I_D = 0.1 = \frac{1}{2} \times 0.8 \times V_{OV}^2 \Rightarrow V_{OV} = 0.5 \text{ V}$$

$$\Rightarrow V_{GS} = 0.5 + 1 = 1.5 \text{ V}$$

$$V_G = 0 \Rightarrow V_S = -1.5 \text{ V}$$

$$R_S = \frac{-1.5 - (-5)}{0.1} = 35 k\Omega$$


$$V_{DS} = 5 - R_D \times 0.1$$

Largest possible R_D is achieved for V_{DSmin}

$$V_{DS} \geq V_{GS} - V_t \Rightarrow V_{DSmin} = V_{OV} \Rightarrow V_{DS} - 1 = V_{OV}$$

$$\Rightarrow V_{DS} = 1 + 0.5 = 1.5 \text{ V} \Rightarrow R_D = \frac{5 - 1.5}{0.1} = 35 k\Omega$$

$$R_G = 10 \text{ M}\Omega \leftarrow \text{arbitrary}$$

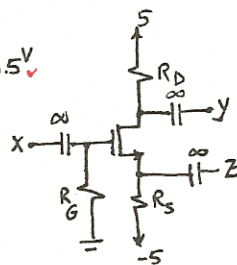 $V_{O,peak} = 1$ 

$$\text{b) } g_m = \frac{2 I_D}{V_{OV}} = \frac{2 \times 0.1}{0.5} = 0.4 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{40}{0.1} = 400 k\Omega$$

 $\leftarrow \text{not correct approach}$ c) IF Z is grounded then the circuit becomes a common-source configuration. The voltage gain according to Eq. 4.82:

$$G_v = - \frac{R_G}{R_G + R_{S,ig}} g_m (r_o \parallel R_D \parallel R_L) \quad \text{overall}$$

$$G_v = \frac{10 \text{ M}}{10 \text{ M} + 1 \text{ M}} \times 0.4 \times (400^k \parallel 35^k \parallel 40^k) = 6.5 V/V$$

$$G_v = 6.5 V/V$$

d) IF y is grounded, then the circuit becomes a source follower configuration.

$$\text{Eq. 4.103: } A_{v0} = \frac{r_o}{r_o + \frac{1}{g_m}} = \frac{400}{400 + \frac{1}{0.4}} = 0.99 V/V$$

$$R_{out} = \frac{1}{g_m} \parallel r_o = \frac{1}{0.4} \parallel 400 = 2.48 k\Omega$$

$$R_{out} = 2.48 k\Omega \quad \text{Correct if } R_S \text{ considered to be the load otherwise}$$

$$R_{out} = \frac{1}{g_m} \parallel r_o \parallel R_S = 2.31 k\Omega$$

Cont.

e) If x is grounded, the circuit becomes a common-gate configuration.

$$R_{in} = \frac{1}{g_m} \parallel R_s = 35k \parallel \frac{1}{0.4} = 2.33k\Omega \quad (\text{ignores } r_o)$$

$$\text{Eq. 4.98: } i_i = i_{sig} \frac{R_{sig}}{R_{sig} + R_{in}} \Rightarrow$$

$$i_i = 10\mu A \frac{100k}{100k + 2.33k} = 9.77\mu A$$

$$V_y = R_D \times i_i = 35 \times 9.77\mu A = 0.34V$$

4.88

a) Fig. P4.88a is a source follower:

$$\text{Eq. 4.103: } A_{v_0} = \frac{r_o}{r_o + \frac{1}{g_m}}, \quad r_o \gg \frac{1}{g_m} \Rightarrow A_{v_0} \approx \frac{1}{V_{ov}}$$

$$R_{out} = \frac{1}{g_m} = \frac{1}{5} = 0.2k\Omega$$

b) Fig. P4.88b is a common-gate configuration:

$$R_{in} = \frac{1}{g_m} = \frac{1}{5} = 0.2k\Omega$$

$$\text{Eq. 4.94: } A_v = g_m (R_D \parallel R_L) = 5 (5k \parallel 2k) = 7.1 V/V$$

c) If we connect both stages together, then:

$$\text{for the first stage: } A_v = A_{v_0} \frac{R_L}{R_L + R_{out}}$$

where R_L is in fact R_{in} of the second stage

$$\text{Therefore: } A_{v_1} = 1 \times \frac{0.2k}{0.2 + 0.2} = 0.5 V/V$$

$$\text{For the second stage: } A_{v_2} = 7.1 V/V$$

$$\text{Overall gain } A_v = A_{v_1} A_{v_2} = 7.1 \times 0.5 = 3.55 V/V$$

4.89

4.90

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$k'_n = \mu_n C_{ox}$$

$$I_D = 100\mu A$$

$$V_{DS} = 1.5V$$

$$g_m = \frac{2I_D}{V_{ov}}$$

$$\chi = \frac{Y}{2\sqrt{ZC}}$$

$$g_{mb} = \chi$$

$$C_{ov} = Wl$$

$$C_{gs} = \frac{2}{3}$$

$$C_{gd} = C_{ov}$$

$$C_{sb} = \frac{C_{gs}}{\sqrt{1}}$$

$$C_{db} = \frac{C}{\sqrt{1}}$$

4.91

$$g_m = \frac{2}{V_{ov}}$$

$$f_T = \frac{g_m}{2\pi C_{gs}}$$

4.92

$$f_T = \frac{1}{2\pi C_{gs}}$$

Also C_g

we can

g_m and

$$f_T = \frac{1}{2\pi C_{gs}}$$

Therefore,

current

the fre

size of

are ac

4.93

$$\begin{aligned} \mu_n &= \frac{3.45 \times 10^{-11}}{8 \times 10^{-9}} = 4.3 \times 10^{-3} \text{ F/m}^2 = 4.3 \text{ pF}/\mu\text{m}^2 \\ C_{ox} &= 450 \times 10^{-4} \times 4.3 \times 10^{-3} = 193.5 \text{ fF}/\mu\text{m}^2 \\ \mu_n A &= \frac{1}{2} \times 193.5 \times \frac{20}{1} V_{ov}^2 \Rightarrow V_{ov} = 0.23 \text{ V} \\ V_{ov} > V_{th} &\Rightarrow \text{Saturation} \\ I_D &= \frac{880 \text{ } \mu\text{A/V}}{0.5} \Rightarrow r_o = \frac{1}{\lambda I_D} = \frac{1}{0.05 \times 0.1} = 200 \text{ k}\Omega \\ \frac{I_D}{V_{ov}} &= \frac{0.5}{2 \sqrt{0.65+1}} = 0.19 \\ \Rightarrow g_m &= 167.2 \text{ } \mu\text{A/V} \end{aligned}$$

$$\begin{aligned} W L_{ov} C_{ox} &= 20 \times 0.05 \times 4.3 = 4.3 \text{ pF} \\ \frac{2}{3} W L_{ox} C_{ox} + C_{ov} &= \frac{2}{3} \times 20 \times 1 \times 4.3 + 4.3 = 61.6 \text{ pF} \\ C_{ov} &= 4.3 \text{ pF} \\ \frac{C_{gs}}{1 + \frac{V_{gs}}{V_o}} &= \frac{15}{1 + \frac{1}{0.7}} = 9.6 \text{ pF} \\ \frac{C_{gd}}{1 + \frac{V_{gd}}{V_o}} &= \frac{15}{1 + \frac{1+1.5}{0.7}} = 7 \text{ pF} \end{aligned}$$

$$\begin{aligned} \frac{I_D}{V_{ov}} &= \frac{2 \times 0.1}{0.25} = 0.8 \text{ mA/V} \\ f_T &= \frac{0.8 \times 10^{-3}}{2\pi(20+5) \times 10^{-15}} = 5.1 \text{ GHz} \end{aligned}$$

$$g_m = \frac{2 I_D}{V_{ov}}, \quad g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$C_{gs} \approx \frac{2}{3} W L C_{ox}$, if $C_{gs} \gg C_{gd}$ then we can ignore C_{gd} . If we replace C_{gs} and C_{gs} in the f_T formula, we have:

$$\frac{\frac{2}{3} \mu_n C_{ox} \frac{W}{L} I_D}{\frac{2}{3} W L C_{ox}} = \frac{1.5}{\pi L} \sqrt{\frac{\mu_n I_D}{2 C_{ox} W L}}$$

there we can see that the higher the I_D , then the higher is the f_T . Also frequency is reverse proportional to the size of the device, i.e. higher frequencies are achievable for smaller devices.

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})} \quad (1)$$

For $C_{gs} \gg C_{gd}$ and the overlap capacitance of C_{gs} negligibly small: $C_{gs} \approx \frac{2}{3} W L C_{ox}$
Also $g_m = \frac{2 I_D}{V_{ov}} = K'_n \frac{W}{L} V_{ov}$

If we substitute g_m and C_{gs} in (1) from the above formulas: $f_T = K'_n \frac{W}{L} V_{ov} \frac{1}{2\pi \times \frac{2}{3} W L C_{ox}}$
 $\Rightarrow f_T = \frac{3 \mu_n V_{ov}}{4\pi L^2}$

Therefore, for a given device f_T is proportional to V_{ov} . $f_T \propto V_{ov}$

For $L = 1 \mu\text{m}$, $V_{ov} = 0.25$:

$$f_T = \frac{3 \times 450 \times 10^{-4} \times 0.25}{4 \times \pi \times 1 \times 10^{-12}} = 2.7 \text{ GHz}$$

For $V_{ov} = 0.5 \text{ V}$: $\frac{f_{T1}}{f_{T2}} = \frac{V_{ov1}}{V_{ov2}} \Rightarrow \frac{f_{T1}}{f_{T2}} = \frac{2.7 \times 0.5}{0.25}$
 $f_T = 5.4 \text{ GHz}$

4.94

$A_M = -27 \text{ V/V}$, $C_{gs} = 0.3 \text{ pF}$, $C_{gd} = 0.1 \text{ pF}$
Common-Source configuration.

Eq. 4.127: $C_{in} = C_{gs} + C_{gd}(1 + g_m R'_L)$.

Also $A_M = -g_m R'_L$, therefore:

$$C_{in} = 0.3 + 0.1 \times (1 + 27) = 3.1 \text{ pF}$$

Now to find the range of R_{sig} that results in 3-dB frequencies over 10 MHz, we use

eq. 4.132: $f_H = \frac{1}{2\pi C_{in} R'_{sig}}$

If we neglect R_G effect then $R'_{sig} \approx R_{sig}$.

$$f_H \geq 10 \text{ MHz} \Rightarrow \frac{1}{2\pi \times 3.1 \times 10^{-12} \times R_{sig}} \geq 10 \text{ MHz}$$

$$\Rightarrow R_{sig} \leq 5.1 \text{ k}\Omega$$

4.95

$$R_{sig} = 100 \text{ k}\Omega, R_{in} = 100 \text{ k}\Omega, C_{gs} = 1 \text{ pF}, C_{gd} = 0.2 \text{ pF} \checkmark$$

Cont.

$$A_M = -\frac{R_G}{R_G + R_{sig}} g_m (r_o \parallel R_D \parallel R_L) \quad (\text{Eq. 4.119})$$

Also $R_{in} = 100 \text{ k}\Omega = R_G$

$$A_M = \frac{-100}{100 + 100} 3(50 \text{ k} \parallel 8 \text{ k} \parallel 10 \text{ k}) = -6.1 \text{ V/V}$$

$$f_H = \frac{1}{2\pi C_{in} R'_{sig}} \quad (\text{Eq. 4.132})$$

$$R'_{sig} = R_{sig} \parallel R_G = 100 \parallel 100 = 50 \text{ k}\Omega$$

$$C_{in} = C_{gs} + C_{gd}(1 + g_m R'_L)$$

$$R'_L = r_o \parallel R_D \parallel R_L = 4.1 \text{ k}\Omega$$

$$C_{in} = 1 + 0.2(1 + 3 \times 4.1) = 3.66 \text{ pF}$$

Now we can calculate f_H :

$$f_H = \frac{1}{2\pi \times 3.66 \times 10^{-12} \times 50 \times 10^3} = 870 \text{ kHz}$$

In order to double f_H , we have to either decrease C_{in} (by reducing R_{out}) or reduce R'_{sig} by reducing R_{in} .

If we reduce $R_{out} = R_D \parallel r_o$:

$$\frac{f_{H2}}{f_{H1}} = \frac{C_{in1}}{C_{in2}} \Rightarrow 2 = \frac{3.66 \text{ pF}}{1 + 0.2(1 + 3 \times R'_L)}$$

$$\Rightarrow R'_L = 1.27 \text{ k}\Omega \quad R'_L = R_{out} \parallel R_L = R_{out} \parallel 10 \text{ k}$$

$$\Rightarrow R_{out} = 1.45 \text{ k}\Omega$$

Therefore in order to double f_H to $870 \times 2 = 1.74 \text{ MHz}$, we have to reduce $R_{out} = r_o \parallel R_D$ to $1.45 \text{ k}\Omega$ or equivalently reducing R_D to $1.5 \text{ k}\Omega$. The new midband gain would be:

$$\frac{A_{M2}}{A_{M1}} = \frac{R'_{L2}}{R'_{L1}} \Rightarrow A_{M2} = -6.1 \times \frac{1.27}{4.1} = -1.9 \text{ V/V}$$

Gain is almost reduced by a factor of 3.

If we reduce $R_{in} = R_G$:

$$\frac{f_{H2}}{f_{H1}} = \frac{R'_{sig1}}{R'_{sig2}} \Rightarrow 2 = \frac{50 \text{ k}}{R'_{sig2}} \Rightarrow R'_{sig2} = 25 \text{ k}\Omega$$

$$\Rightarrow 25 \text{ k}\Omega = 100 \text{ k} \parallel R_G \Rightarrow R_G = 33 \text{ k}\Omega = R_{in}$$

Therefore in order to double f_H , R_{in} is reduced by a factor of 3, from $100 \text{ k}\Omega$ to $33 \text{ k}\Omega$.

The new midband gain would be:

$$\frac{A_{M2}}{A_{M1}} = \frac{R_{G2}}{R_{G1}} \frac{R_{G1} + R_{sig}}{R_{G2} + R_{sig}} \Rightarrow A_{M2} = -6.1 \times \frac{1}{3} \times \frac{100 + 100}{33 + 100}$$

$$A_{M2} = 3.06 \text{ V/V}$$

Gain is almost reduced by a factor of 2.

4.96

$$R_{in} = 2 \text{ M}\Omega, g_m = 4 \text{ mA/V}, r_o = 100 \text{ k}\Omega$$

$$C_{gs} = 2 \text{ pF}, C_{gd} = 0.5 \text{ pF}, R_{sig} = 500 \text{ }\Omega$$

a) using Eq. 4.119 and noting that we have:

$$A_M = -\frac{R_G}{R_G + R_{sig}} g_m (r_o \parallel R_D \parallel R_L) = -15.2 \text{ V/V}$$

b) Eq. 4.132: $f_H = \frac{1}{2\pi C_{in} R'_{sig}}$ where

$$C_{in} = C_{gs} + C_{gd}(1 + g_m (r_o \parallel R_D \parallel R_L))$$

$$C_{in} = 2 + 0.5(1 + 4 \times (100 \text{ k} \parallel 10 \text{ k} \parallel 10 \text{ k})) = 12.2 \text{ pF}$$

$$R'_{sig} = 0.5 \text{ M} \parallel 2 \text{ M} = 0.4 \text{ M}\Omega = 400 \text{ k}\Omega$$


$$f_H = \frac{1}{2\pi \times 12.2 \times 10^{-12} \times 400 \times 10^3} = 33.1 \text{ kHz}$$

4.97

If we write KCL

at node D:
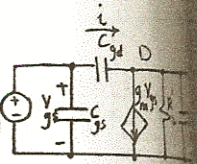
$$i = g_m v_{gs} + \frac{v_o}{R'_L} + v_o C_L$$



$$\text{then: } v_{sig} = i \times \frac{1}{C_{gd} s} + v_o$$

$$v_{sig} = (g_m v_{gs} + \frac{v_o}{R'_L} + v_o C_L s) \frac{1}{C_{gd} s} + v_o$$

$$v_{sig} (1 - \frac{g_m}{C_{gd} s}) = v_o (1 + \frac{1}{R'_L C_{gd} s} + \frac{C_L s}{C_{gd} s})$$

$$\frac{v_o}{v_{sig}} = -g_m R'_L \frac{(1 - S(C_{gd}/g_m))}{R'_L C_{gd} s + 1 + R'_L C_L s}$$

$$\frac{v_o}{v_{sig}} = -g_m R'_L \frac{1 - S C_{gd}/g_m}{1 + S(C_L + C_{gd}) R'_L}$$

$$\text{If } (g_m/C_{gd}) \gg \omega \Rightarrow \frac{v_o}{v_{sig}} = \frac{-g_m R'_L}{1 + S(C_L + C_{gd}) R'_L}$$

$$\text{For } C_{gd} = 0.5 \text{ pF}, C_L = 2 \text{ pF}, g_m = 4 \text{ mA/V}, R'_L = 10 \text{ k}\Omega$$

$$\frac{v_o}{v_{sig}} = \frac{A_M}{1 + S/\omega_H} \Rightarrow \begin{cases} A_M = -g_m R'_L = -4 \times 10 = -40 \\ f_H = \frac{1}{2\pi(C_L + C_{gd}) R'_L} \end{cases}$$

$$\Rightarrow f_H = \frac{10^{12}}{2\pi \times (2 + 0.5) \times 5 \times 10^3}$$

$$f_H = 12.7 \text{ MHz}$$

$$g_m/C_{gd} = \frac{4}{0.5} = 8 \text{ } \frac{\text{mA/V}}{\text{pF}} = 8 \text{ } \frac{\text{Grad/s}}{\text{pF}}$$

4.103

$$A_M = -\frac{R_G}{R_G + R_{sig}} g_m (r_o \parallel R_D \parallel R_L) = -\frac{2 \times 3}{2 + 0.5} (20^k \parallel 10^k) \checkmark$$

$$A_M = -16V/V \checkmark$$

using equations 4.134, 4.136 and 4.138 we have:

$$f_{P1} = \frac{1}{2\pi C_{c1} (R_G + R_{sig})} \Rightarrow 3^{Hz} = \frac{1}{2\pi \times C_{c1} (2 + 0.5) \times 10^6} \checkmark$$

$$\Rightarrow C_{c1} = 21.2 \text{ nF} \checkmark$$

$$f_{P2} = \frac{g_m}{2\pi C_{c2}} \Rightarrow 50^{Hz} = \frac{3 \times 10^{-3}}{2\pi \times C_{c2}} \Rightarrow C_{c2} = 9.6 \mu F \checkmark$$

$$f_{P3} = \frac{1}{2\pi C_{c2} (R_D + R_L)} \Rightarrow 10^{Hz} = \frac{1}{2\pi C_{c2} (10^k + 20^k)}$$

$$\Rightarrow C_{c2} = 0.5 \mu F \checkmark$$

$$f_L = 50^{Hz} \checkmark \text{ (Highest of the 3 poles)}$$

4.104

Refer to Fig. P4.104.

$$f_{P1} = \frac{1}{2\pi C_{c1} R_{in}} = 1^{Hz} \quad (\text{a decade lower than } 10^{Hz})$$

$$f_{P2} = \frac{1}{2\pi C_{c2} (R_L + R_D \parallel R_o)} = 10^{Hz}$$

$$f_{P1} = 1^{Hz} = \frac{1}{2\pi C_{c1} \times 2.33 \times 10^6} \Rightarrow C_{c1} = 68.3 \text{ nF}$$

$$f_{P2} = 10^{Hz} = \frac{1}{2\pi C_{c2} (10^k + 10^k \parallel 47^k)} \Rightarrow C_{c2} = 873 \text{ nF}$$

4.105

Note that $k'_n \frac{W_n}{L_n} = k'_p \frac{W_p}{L_p}$ (matched)

a) when v_o is low: (eq. 4.140)

$$r_{DSN} = \frac{1}{k'_n \left(\frac{W_n}{L_n}\right) (V_{DD} - V_{tn})} = \frac{1}{120 \times 10^{-6} \times \frac{1.2}{0.8} \times (3 - 0.7)}$$

$$r_{DSN} = 2.4 \text{ k}\Omega$$

when v_o is high (V_{OH}): (eq. 4.141)

$$r_{DSP} = \frac{1}{k'_p \left(\frac{W_p}{L_p}\right) (V_{DD} - |V_{tp}|)} = \frac{1}{60 \times 10^{-6} \times \frac{2.4}{0.8} \times (3 - 0.7)}$$

$$r_{DSP} = 2.4 \text{ k}\Omega$$

$$b) I_{max} = k'_n \left(\frac{W_n}{L_n}\right) (V_{DD} - V_{tn})$$

$$I_{max} = 120 \times 10^{-6} \times \frac{1.2}{0.8} \times (3 - 0.7)$$

$$c) \text{ Eq. 4.148: } V_{IH} = \frac{1}{8} (5V_D)$$

$$V_{IH} = \frac{1}{8} (5 \times 3 - 2 \times 0.7) = 1.7V$$

$$\text{Eq. 4.149: } V_{IL} = \frac{1}{8} (3V_{DD})$$

$$N_{MH} = V_{OH} - V_{IH}$$

$$N_{ML} = V_{IL} - V_{OL}$$

4.106

From the formula given in E have: $V_{th} = \frac{r(V_{DD} - |V_{tp}|) + V_{tn}}{1 + r}$

$$\text{where } r = \sqrt{\frac{k'_p \left(\frac{W_p}{L_p}\right)}{k'_n \left(\frac{W_n}{L_n}\right)}}$$

We have $V_{tn} = |V_{tp}| = 0.7V$, $V_{DD} =$

$k'_p = 60 \mu A/V^2$. Thus: for $\left(\frac{W_p}{L_p}\right)$

$$r = \sqrt{\frac{60}{120}} = 0.71$$

$$V_{th} = \frac{0.71(3 - 0.7) + 0.7}{1 + 0.71} = 1.1$$

For $\left(\frac{W_p}{L_p}\right) = 2 \left(\frac{W_n}{L_n}\right)$ (the m

we have: $r = \sqrt{\frac{60}{120} \times 2} = 1$

$$V_{th} = \frac{1 \times (3 - 0.7) + 0.7}{1 + 1} = 1.5V$$

For $\left(\frac{W_p}{L_p}\right) = 4 \left(\frac{W_n}{L_n}\right)$ we have:

$$V_{th} = \frac{1.41 \times (3 - 0.7) + 0.7}{1 + 1.41} = 1.6$$

The results are summarized table:

$$\left(\frac{W_p}{L_p}\right) = \left(\frac{W_n}{L_n}\right) \quad V_{th} = 1.36V$$

$$\left(\frac{W_p}{L_p}\right) = 2 \left(\frac{W_n}{L_n}\right) \quad V_{th} = 1.5V$$

$$\left(\frac{W_p}{L_p}\right) = 4 \left(\frac{W_n}{L_n}\right) \quad V_{th} = 1.64V$$