

SOLUTIONS MANUAL

MICROWAVE TRANSISTOR AMPLIFIERS

Analysis and Design

SECOND EDITION

Guillermo Gonzalez



PRENTICE HALL

Upper Saddle River, NJ 07458

Acquisitions Editor: *Eric Svendsen*
Project Editor: *Lorena Cerisano*
Production Manager: *Joan Eurell*
Production Coordinator: *Julia Meehan*

©1996 by Prentice-Hall, Inc.
Simon & Schuster / A Viacom Company
Upper Saddle River, New Jersey 07458

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission in writing from the publisher.

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

ISBN 0-13-271255-5

Prentice-Hall International (UK) Limited, *London*
Prentice-Hall of Australia Pty. Limited, *Sydney*
Prentice-Hall Canada Inc., *Toronto*
Prentice-Hall Hispanoamericana, S.A., *Mexico*
Prentice-Hall of India Private Limited, *New Delhi*
Prentice-Hall of Japan, Inc., *Tokyo*
Simon & Schuster Asia Pte. Ltd., *Singapore*
Editora Prentice-Hall do Brasil, Ltda., *Rio de Janeiro*

CONTENTS

CHAPTER	1	page 1
CHAPTER	2	page 19
CHAPTER	3	page 42
CHAPTER	4	page 71
CHAPTER	5	page 88

CHAPTER 1

1.1) IN (1.3.41) LET $\Gamma_0 = |\Gamma_0| e^{j\psi_0}$:

$$|V(d)| = |A_1| |1 + |\Gamma_0| e^{j(\psi_0 - 2\beta d)}|$$

THE MAXIMUM VALUE OF $|V(d)|$ OCCURS WHEN $e^{j(\psi_0 - 2\beta d)} = 1$,
AND THE MINIMUM VALUE OCCURS WHEN $e^{j(\psi_0 - 2\beta d)} = -1$.

HENCE,

$$|V(d)|_{\max} = |A_1| |1 + |\Gamma_0|| \quad \text{AND} \quad |V(d)|_{\min} = |A_1| |1 - |\Gamma_0||$$

$$= |A_1| (1 + |\Gamma_0|) \quad = |A_1| (1 - |\Gamma_0|)$$

1.2) $v(d, t) = \text{Re} [V(d) e^{j\omega t}]$

$$V(d) = 3.95 e^{j(\beta d - 63.44^\circ)} + 1.77 e^{-j\beta d}$$


$$\therefore v(d, t) = 3.95 \cos(\omega t + \beta d - 63.44^\circ) + 1.77 \cos(\omega t - \beta d)$$

$$\text{AND } i(d, t) = \frac{3.95}{50} \cos(\omega t + \beta d - 63.44^\circ) - \frac{1.77}{50} \cos(\omega t - \beta d)$$

1.3) (a) $\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(100 + j100) - 50}{(100 + j100) + 50} = 0.62 \angle 29.7^\circ$

$$Z_{IN}(\frac{\lambda}{8}) = 50 \frac{(100 + j100) \cos 45^\circ + j50 \sin 45^\circ}{50 \cos 45^\circ + j(100 + j100) \sin 45^\circ} = 40 - j70 \Omega$$

$$VSWR = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|} = \frac{1 + 0.62}{1 - 0.62} = 4.26$$

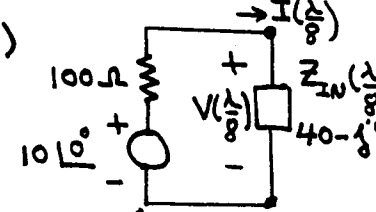(b)  $V(\frac{\lambda}{8}) = \frac{10 \angle 0^\circ (40 - j70)}{40 - j70 + 100} = 5.15 \angle -33.7^\circ$

$$I(\frac{\lambda}{8}) = V(\frac{\lambda}{8}) / Z_{IN}(\frac{\lambda}{8}) = 0.064 \angle 26.6^\circ$$

$$P(\frac{\lambda}{8}) = \frac{1}{2} \text{Re} [V(\frac{\lambda}{8}) I^*(\frac{\lambda}{8})] = 82 \text{ mW}$$

$$V(\frac{\lambda}{8}) = 5.15 \angle -33.7^\circ = A_1 e^{j\frac{\pi}{4}} [1 + 0.62 \angle 29.7^\circ e^{-j\frac{\pi}{2}}]$$

$$\therefore A_1 = 3.643 \angle -56.31^\circ$$

$$V(d) = 3.643 \angle -56.31^\circ e^{j\beta d} [1 + 0.62 \angle 29.7^\circ e^{-j2\beta d}]$$

$$V(0) = 3.643 \angle -56.31^\circ [1 + 0.62 \angle 29.7^\circ] = 5.72 \angle -45.02^\circ$$

$$I(0) = \frac{5.72 \angle -45.02^\circ}{100 + j100} = 0.04 \angle -90^\circ$$

$$P(0) = \frac{1}{2} \operatorname{Re}[V(0)I^*(0)] = 82 \text{ mW}$$

$$\text{As expected: } P\left(\frac{\lambda}{8}\right) = P(0)$$

$$1.4) \quad b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

$$\text{Letting } Z_0 = Z_{01} = Z_{02}, \text{ THEN } b_1 = \frac{V_1^-}{\sqrt{Z_0}}, b_2 = \frac{V_2^-}{\sqrt{Z_0}},$$

$$a_1 = \frac{V_1^+}{\sqrt{Z_0}}, \text{ AND } a_2 = \frac{V_2^+}{\sqrt{Z_0}}.$$

$$\therefore \frac{V_1^-}{\sqrt{Z_0}} = S_{11} \frac{V_1^+}{\sqrt{Z_0}} + S_{12} \frac{V_2^+}{\sqrt{Z_0}} \Rightarrow V_1^- = S_{11}V_1^+ + S_{12}V_2^+$$

$$\frac{V_2^-}{\sqrt{Z_0}} = S_{21} \frac{V_1^+}{\sqrt{Z_0}} + S_{22} \frac{V_2^+}{\sqrt{Z_0}} \Rightarrow V_2^- = S_{21}V_1^+ + S_{22}V_2^+$$

$$\text{With } b_1 = \sqrt{Z_0} I_1^-, b_2 = \sqrt{Z_0} I_2^-, a_1 = \sqrt{Z_0} I_1^+, a_2 = \sqrt{Z_0} I_2^+$$

$$\text{WE OBTAIN: } I_1^- = S_{11}I_1^+ + S_{12}I_2^+$$

$$I_2^- = S_{21}I_1^+ + S_{22}I_2^+$$

$$1.5) \quad \begin{cases} a_1 = T_{11}b_2 + T_{12}a_2 & (1) \\ b_1 = T_{21}b_2 + T_{22}a_2 & (2) \end{cases}$$

$$\begin{cases} b_1 = S_{11}a_1 + S_{12}a_2 & (3) \\ b_2 = S_{21}a_1 + S_{22}a_2 & (4) \end{cases}$$

FROM (3) AND (4):

$$a_1 = \frac{1}{S_{11}} b_1 - \frac{S_{12}}{S_{11}} a_2 \quad (5)$$

$$a_1 = \frac{1}{S_{21}} b_2 - \frac{S_{22}}{S_{21}} a_2 \quad (6)$$

EQUATING (5) AND (6):

$$\frac{1}{S_{11}} b_1 - \frac{S_{12}}{S_{11}} a_2 = \frac{1}{S_{21}} b_2 - \frac{S_{22}}{S_{21}} a_2$$

$$\therefore b_1 = \frac{S_{11}}{S_{21}} b_2 + \left[S_{12} - \frac{S_{22} S_{11}}{S_{21}} \right] a_2 \quad (7)$$

COMPARING (2) AND (7):

$$T_{21} = \frac{S_{11}}{S_{21}} \quad \text{AND} \quad T_{22} = S_{12} - \frac{S_{11} S_{22}}{S_{21}}$$

EQUATING (3) AND (7) GIVES

$$S_{11} a_1 + S_{12} a_2 = \frac{S_{11}}{S_{21}} b_2 + \left[S_{12} - \frac{S_{11} S_{22}}{S_{21}} \right] a_2$$

$$\therefore a_1 = \frac{1}{S_{21}} b_2 - \frac{S_{22}}{S_{21}} a_2 \quad (8)$$

COMPARING (1) AND (8):


$$T_{11} = \frac{1}{S_{21}} \quad \text{AND} \quad T_{12} = - \frac{S_{22}}{S_{21}}$$

SIMILARLY, STARTING WITH (1) AND (2), IT FOLLOWS

THAT:

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \begin{bmatrix} \frac{T_{21}}{T_{11}} & T_{22} - \frac{T_{12} T_{21}}{T_{11}} \\ \frac{1}{T_{11}} & - \frac{T_{12}}{T_{11}} \end{bmatrix}$$

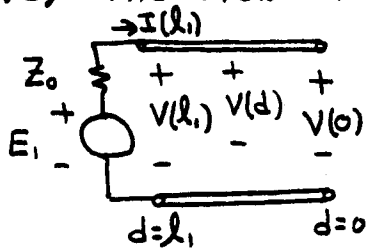1.6) THE OPEN-CIRCUIT VOLTAGE $E_{1,TH}$ IS OBTAINED AS FOLLOWS:



$$\Gamma_0 = 1$$

$$V(d) = A(e^{j\beta d} + e^{-j\beta d}) = 2A \cos \beta d$$


$$I(d) = j2 \frac{A}{Z_0} \sin \beta d$$

$$V(l_1) = 2A \cos \beta l_1 = E_1 - I(l_1) Z_0$$

$$= E_1 - j2A \sin \beta l_1$$

$$\therefore A = \frac{E_1}{2(\cos \beta l_1 + j \sin \beta l_1)} = \frac{E_1}{2} e^{-j\beta l_1}$$

$$\text{HENCE: } E_{1,TH} = V(0) = 2A = E_1 e^{-j\beta l_1}$$

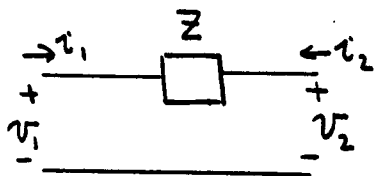1.7) (a)  $V_1 = AV_2 - Bi_2$
 $i_1 = CV_2 - Di_2$

$$A = \left. \frac{V_1}{V_2} \right|_{i_2=0} \quad \text{WITH } i_2=0 : V_1 = V_2$$

$$\therefore A = 1$$

$$B = - \left. \frac{V_1}{i_2} \right|_{V_2=0} \quad \text{WITH } V_2=0 : V_1 = i_1 Z = -i_2 Z$$

$$\therefore B = - \frac{(-i_2 Z)}{i_2} = Z$$

$$C = \left. \frac{i_1}{V_2} \right|_{i_2=0} \quad \text{WITH } i_2=0 : i_1 = -i_2 = 0$$

$$\therefore C = 0$$

$$D = \left. \frac{i_1}{-i_2} \right|_{V_2=0} \quad \text{WITH } V_2=0 : i_1 = -i_2$$

$$\therefore D = 1$$

(b) From Fig. 1.8.1:

$$S_{11} = \frac{A' + B' - C' - D'}{A' + B' + C' + D'} = \frac{1 + \frac{Z}{Z_0} - 0 - 1}{1 + \frac{Z}{Z_0} + 0 + 1} = \frac{Z}{Z + 2Z_0}$$

$$S_{12} = \frac{2(A'D' - B'C')}{A' + B' + C' + D'} = \frac{2(1 - 0)}{1 + \frac{Z}{Z_0} + 0 + 1} = \frac{2Z_0}{Z + 2Z_0}$$

$$S_{21} = \frac{2}{A' + B' + C' + D'} = \frac{2}{1 + \frac{Z}{Z_0} + 0 + 1} = \frac{2Z_0}{Z + 2Z_0}$$

$$S_{22} = \frac{-A' + B' - C' + D'}{A' + B' + C' + D'} = \frac{-1 + \frac{Z}{Z_0} - 0 + 1}{1 + \frac{Z}{Z_0} + 0 + 1} = \frac{Z}{Z + 2Z_0}$$

FOR THE SHUNT ADMITTANCE Y THE ABCD MATRIX IS :

$$A = 1, B = 0, C = Y, \text{ AND } D = 1$$

AND

$$S_{11} = \frac{A' + B' - C' - D'}{A' + B' + C' + D'} = \frac{1 + 0 - YZ_0 - 1}{1 + 0 + YZ_0 + 1} = \frac{-YZ_0}{2 + YZ_0}$$


$$S_{12} = \frac{2(A'D' - B'C')}{A' + B' + C' + D'} = \frac{2(1 - 0)}{1 + 0 + YZ_0 + 1} = \frac{2}{2 + YZ_0}$$

$$\text{ALSO: } S_{22} = S_{11} \text{ AND } S_{21} = S_{12}$$

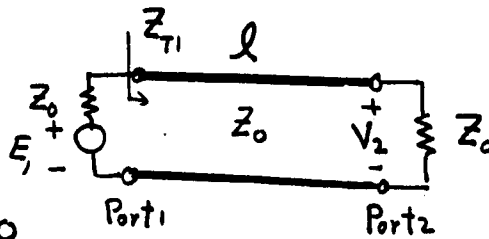1.8) IN A Z_0 SYSTEM:

$$Z_{T1} = Z_0$$

$$S_{11} = \frac{Z_{T1} - Z_0}{Z_{T1} + Z_0} = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$$



ALSO (FROM SYMMETRY): $S_{22} = 0$

$$S_{21} = 2 \frac{\sqrt{Z_0}}{\sqrt{Z_0}} \frac{V_2}{E_1} = 2 \frac{V_2}{E_1} \quad \text{Since } V(x) = \frac{E_1}{2} e^{-j\beta x}$$

$$\therefore S_{21} = \frac{2 \left(\frac{E_1}{2} e^{-j\beta l} \right)}{E_1} = e^{-j\beta l}$$

$$V_2 = V(l) = \frac{E_1}{2} e^{-j\beta l}$$

ALSO (FROM SYMMETRY): $S_{12} = e^{-j\beta l}$

AN ALTERNATE WAY OF DERIVING S_{21} IS:



$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$

SINCE b_2 IS THE WAVE AT PORT 2 AND a_1 IS THE WAVE AT PORT 1, WE HAVE:

$$b_2 = a_1 e^{-j\beta l} \quad (a_2 = 0)$$

$$\therefore S_{21} = \frac{b_2}{a_1} = e^{-j\beta l}$$
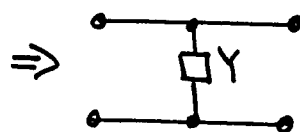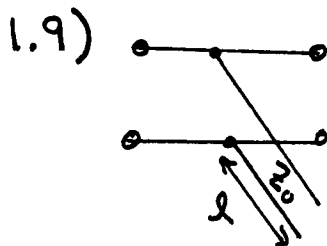
$$T = \begin{bmatrix} \frac{1}{S_{21}} & -\frac{S_{22}}{S_{21}} \\ \frac{S_{11}}{S_{21}} & S_{12} - \frac{S_{11}S_{22}}{S_{21}} \end{bmatrix} = \begin{bmatrix} e^{j\beta l} & 0 \\ 0 & e^{-j\beta l} \end{bmatrix}$$




$$Y = \frac{1}{Z_0} = \frac{1}{-jZ_0 \cot \beta l} = jY_0 \tan \beta l$$

$$S_{11} = S_{22} = \frac{-Z_0 Y}{2 + Z_0 Y} = \frac{-1}{1 - j2 \cot \beta l}$$

$$S_{12} = S_{21} = \frac{2}{2 + Z_0 Y} = \frac{2}{2 + j \tan \beta l}$$

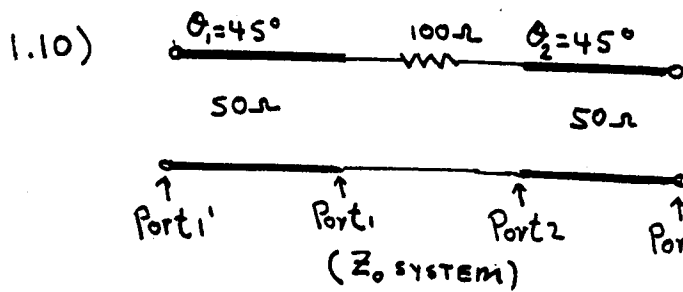USE (1.4.11) TO EVALUATE THE T PARAMETERS.



THE S PARAMETERS AT PORTS 1 AND 2 ARE:

$$S_{11} = \frac{Z}{Z + 2Z_0} = \frac{100}{100 + 2(50)} = 0.5$$


$$S_{22} = S_{11} = 0.5$$

$$S_{12} = S_{21} = \frac{2Z_0}{Z + 2Z_0} = 0.5$$

THE S PARAMETERS AT PORTS 1' AND 2' ARE OBTAINED USING (1.5.4):

$$S'_{11} = S'_{22} = S_{11} e^{-j2\theta_1} = 0.5 \angle -90^\circ = -j0.5$$
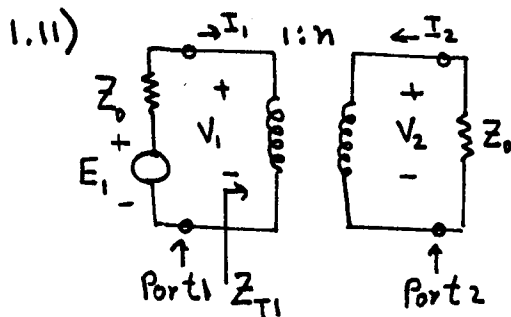
$$S'_{21} = S'_{12} = S_{21} e^{-j(\theta_1 + \theta_2)} = 0.5 \angle -90^\circ = -j0.5$$



IN THE Z₀ SYSTEM SHOWN, THE PARAMETERS S₁₁ AND S₂₁ ARE CALCULATED AS FOLLOWS:

$$I_2 = \frac{I_1}{n}, \quad V_2 = V_1 n$$

$$Z_{T1} = \frac{V_1}{I_1} = \frac{V_2}{I_2 n^2} = \frac{Z_0}{n^2}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \frac{Z_{T1} - Z_0}{Z_{T1} + Z_0} = \frac{\frac{Z_0}{n^2} - Z_0}{\frac{Z_0}{n^2} + Z_0} = \frac{1 - n^2}{1 + n^2}$$


$$S_{21} = 2 \sqrt{\frac{Z_{02}}{Z_{01}}} \frac{V_2}{E_1} = 2 \frac{V_2}{E_1} \quad (1)$$

$$V_1 = \frac{E_1 Z_{T1}}{Z_{T1} + Z_0} = \frac{E_1 \frac{Z_0}{n^2}}{\frac{Z_0}{n^2} + Z_0} = \frac{E_1}{n^2 + 1}$$

$$V_2 = n V_1 = \frac{n E_1}{n^2 + 1} \quad \text{OR} \quad \frac{V_2}{E_1} = \frac{n}{n^2 + 1} \quad (2)$$

(2) INTO (1):

$$S_{21} = \frac{2n}{n^2 + 1}$$

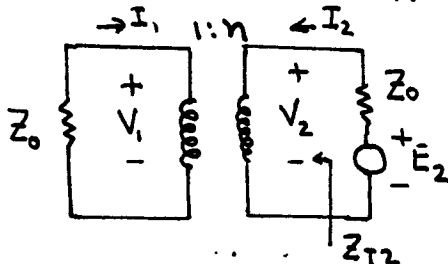

THE PARAMETERS S₂₂ AND S₁₂ ARE CALCULATED AS FOLLOWS:

$$Z_{T2} = Z_0 n^2$$

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} = \frac{Z_{T2} - Z_0}{Z_{T2} + Z_0} = \frac{n^2 Z_0 - Z_0}{n^2 Z_0 + Z_0} = \frac{n^2 - 1}{n^2 + 1}$$

$$S_{12} = 2 \frac{V_1}{E_2} \quad (3)$$

$$V_2 = \frac{E_2 Z_{T2}}{Z_{T2} + Z_0} = \frac{E_2 Z_0 n^2}{Z_0 n^2 + Z_0} = \frac{E_2 n^2}{n^2 + 1}$$

$$V_1 = \frac{V_2}{n} = \frac{E_2 n}{n^2 + 1} \quad \text{OR} \quad \frac{V_1}{E_2} = \frac{n}{n^2 + 1} \quad (4)$$


(4) INTO (3):

$$S_{12} = \frac{2n}{n^2 + 1}$$

AT PORTS 1' AND 2', WITH $\theta = \theta_1 = \theta_2$, WE OBTAIN:

$$[S'] = \begin{bmatrix} s_{11} e^{-j2\theta} & s_{12} e^{-j2\theta} \\ s_{21} e^{-j2\theta} & s_{22} e^{-j2\theta} \end{bmatrix} = e^{-j2\theta} \begin{bmatrix} \frac{1-n^2}{1+n^2} & \frac{2n}{n^2+1} \\ \frac{2n}{n^2+1} & \frac{n^2-1}{n^2+1} \end{bmatrix}$$

1.12)

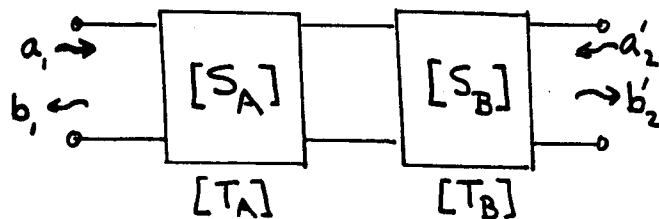

[T] AND [S]
PARAMETERS ARE
RELATED BY (1.4.11)

FROM (1.4.13):

$$\begin{bmatrix} a_1 \\ b_1 \end{bmatrix} = \begin{bmatrix} T_{11}^A & T_{12}^A \\ T_{21}^A & T_{22}^A \end{bmatrix} \begin{bmatrix} T_{11}^B & T_{12}^B \\ T_{21}^B & T_{22}^B \end{bmatrix} \begin{bmatrix} b_2' \\ a_2' \end{bmatrix}$$


OVERALL T_{11} IS: $T_{11} = T_{11}^A T_{11}^B + T_{12}^A T_{21}^B$

$$T_{11} = \frac{1}{S_A} \frac{1}{S_B} + \left(-\frac{S_{22}^A}{S_{21}^A} \right) \left(\frac{S_{11}^B}{S_{21}^B} \right)$$

$$\text{SINCE } T_{11} = \frac{1}{S_{21}} = \frac{1 - S_{22}^A S_{11}^B}{S_{21}^A S_{21}^B} \Rightarrow S_{21} = \frac{S_{21}^A S_{21}^B}{1 - S_{22}^A S_{11}^B}$$

$$1.13) (a) \Gamma_0 = \frac{100 - 50}{100 + 50} = \frac{1}{3}, \text{ VSWR} = \frac{1 + \frac{1}{3}}{1 - \frac{1}{3}} = 2$$
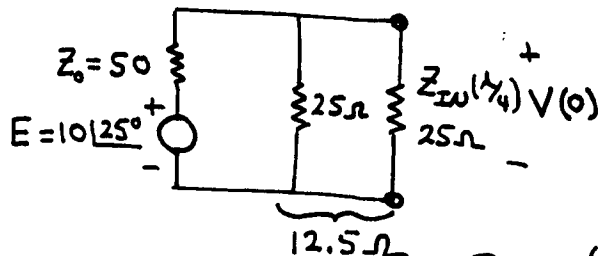
$$(b) Z_{IN}(\lambda/4) = \frac{Z_0^2}{Z_L} = \frac{50^2}{100} = 25 \Omega$$




$$V(0) = \frac{10\angle 25^\circ (12.5)}{12.5 + 50} = 2\angle 25^\circ$$

$$P_{AVS} = \frac{|E|^2}{8 Z_0} = \frac{10^2}{8(50)} = 0.25 \text{ W}$$

$$\text{THE INPUT POWER IS: } P_{IN} = \frac{(V(0)_{rms})^2}{12.5} = \frac{(\frac{2}{\sqrt{2}})^2}{12.5} = 0.16 \text{ W}$$

SINCE THE TRANSMISSION LINE IS LOSSLESS, THE POWER DELIVERED TO THE LOAD (P_L) IS THE SAME AS P_{IN} .
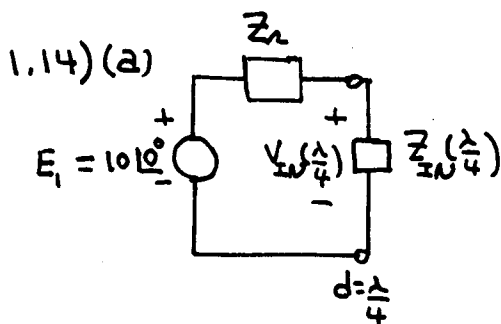
$$\therefore P_L = P_{IN} = 0.16 \text{ W}$$



$$Z_{IN}(\lambda/4) = \frac{Z_0^2}{Z_L} = \frac{50^2}{50 + j50} = 25 - j25$$

NOTE: IF Z_L IS GIVEN, THE VALUE OF Z_{IN} FOR MAXIMUM POWER IS

$$Z_{IN} = Z_L^*$$

HOWEVER, IN THIS PROBLEM Z_{IN} IS GIVEN. HENCE, THE VALUE OF Z_L FOR MAX. POWER DELIVERED TO Z_{IN} IS: $Z_L = -\text{Im}[Z_{IN}]$

$$\therefore Z_L = j25$$


$$V_{IN}(\lambda/4) = \frac{10\angle 0^\circ (25 - j25)}{j25 + (25 - j25)} = 10 - j10 = 14.14\angle -45^\circ$$

$$I_{IN}(\lambda/4) = \frac{14.14\angle -45^\circ}{25 - j25} = 0.4$$

$$P_{IN} = \frac{1}{2} \text{Re}[14.14\angle -45^\circ (0.4)] = 2 \text{ W}$$

$$P_L = P_{IN} = 2 \text{ W}$$

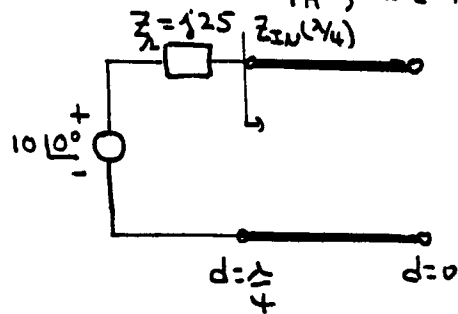(b) To FIND E_{TH} , WE FIND THE OPEN CIRCUIT VOLTAGE AT $d=0$:



$$\Gamma_o = 1, V(d) = 2A \cos \beta d$$

$$I(d) = j2 \frac{A}{Z_o} \sin \beta d \quad (1)$$

$$Z_{IN}(\frac{\lambda}{4}) = 0 \text{ (A SHORT CIRCUIT)}$$

$$\therefore I(\frac{\lambda}{4}) = \frac{10 \angle 0^\circ}{j25 + 0} = -j0.4 \quad (2)$$

FROM (1) AND (2): $-j0.4 = j2 \frac{A}{50} \sin \frac{\pi}{2} \Rightarrow A = -10$


HENCE: $V(d) = 2(-10) \cos \beta d = -20 \cos \beta d$

$$E_{TH} = V(0) = -20$$

TO FIND Z_{TH} WE SET $E_i = 0$, THEN:

$$Z_{TH} = \frac{Z_o^2}{Z_L} = \frac{50^2}{j25} = -j100$$

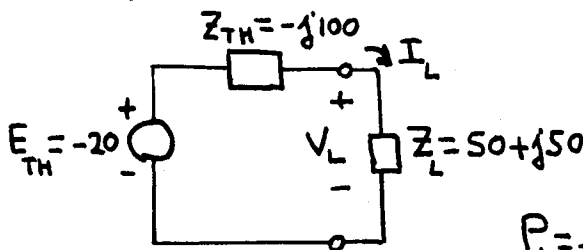THE THEVENIN'S EQUIVALENT CIRCUIT AT $d=0$ IS:



$$I_L = \frac{-20}{-j100 + 50 + j50} = 0.283 \angle -135^\circ$$

$$V_L = 0.283 \angle -135^\circ (50 + j50) = 20 \angle -90^\circ$$

$$P_L = \frac{1}{2} \text{Re}[20 \angle -90^\circ (0.283 \angle 135^\circ)] = 2 \text{ W}$$

1.15) $v_2(0) = \frac{V_2(0)}{\sqrt{Z_o}} = a_2(0) + b_2(0) = 0 + 3.54 \angle 45^\circ$

$$\therefore V_2(0) = \sqrt{50} (3.54 \angle 45^\circ) = 25.03 \angle 45^\circ$$

$$i_2(0) = \sqrt{Z_o} I_2(0) = a_2(0) - b_2(0) = 0 - 3.54 \angle 45^\circ$$

$$\therefore I_2(0) = \frac{-3.54 \angle 45^\circ}{\sqrt{50}} = 0.501 \angle -135^\circ$$

$$P_2(0) = \frac{1}{2} |I_2(0)|^2 50 = \frac{1}{2} (0.501)^2 50 = 6.27 \text{ W}$$

$$P_2(0) = \frac{1}{2} \frac{|V_2(0)|^2}{50} = \frac{1}{2} \frac{(25.03)^2}{50} = 6.27 \text{ W}$$

Also: $P_2(0) = \frac{1}{2} |a_2(0)|^2 - \frac{1}{2} |b_2(0)|^2 = \frac{1}{2} (3.54)^2 = 6.27 \text{ W}$

$$1.16) (a) Z_{IN}(d) = Z_{IN} \Big|_{d=\frac{\lambda}{8}} = 50 \frac{(150 + j150) + j50 \tan 45^\circ}{50 + j(150 + j150) \tan 45^\circ} = 23 - j65 \Omega$$

$$(b) a_1(0) = \frac{1}{2\sqrt{Z_0}} [V_1(0) + Z_0 I_1(0)] \quad , \quad V_1(0) = E_1 - Z_0 I_1(0)$$

$$\therefore a_1(0) = \frac{E_1}{2\sqrt{Z_0}} = \frac{10}{2\sqrt{50}} = 0.707$$

$$a_1\left(\frac{\lambda}{8}\right) = a_1(0) e^{-j\pi/4} = 0.707 \angle -45^\circ$$

$$b_1(0) = \frac{1}{2\sqrt{Z_0}} [V_1(0) - 50 I_1(0)] = \frac{1}{2\sqrt{50}} [10 - 50 I_1(0) - 50 I_1(0)] \quad (1)$$

$$I_1(0) = \frac{10 \angle 0^\circ}{50 + 23 - j65} = 0.102 \angle 41.68^\circ \quad (2)$$

$$(2) \text{ INTO } (1): b_1(0) = \frac{1}{2\sqrt{50}} [10 - 2(50)(0.102 \angle 41.68^\circ)] = 0.508 \angle -70.65^\circ$$

$$b_1\left(\frac{\lambda}{8}\right) = b_1(0) e^{j\pi/4} = 0.508 \angle -25.65^\circ$$

SINCE $Z_2 = Z_0$, THE OUTPUT IS MATCHED. HENCE, $a_2(0) = 0$

$$(c) V_1(0) = I_1(0) Z_{IN}(0) = 0.102 \angle 41.68^\circ (23 - j65) = 7.05 \angle -28.8^\circ$$

$$\text{OR } V_1(0) = \sqrt{Z_0} [a_1(0) + b_1(0)] = \sqrt{50} [0.707 + 0.508 \angle -70.65^\circ] = 7.05 \angle -28.8^\circ$$

$$V_1\left(\frac{\lambda}{8}\right) = \sqrt{Z_0} [a_1\left(\frac{\lambda}{8}\right) + b_1\left(\frac{\lambda}{8}\right)] = \sqrt{50} [0.707 \angle -45^\circ + 0.508 \angle -25.65^\circ] = 8.47 \angle -36.92^\circ$$

$$I_1\left(\frac{\lambda}{8}\right) = \frac{8.47 \angle -36.92^\circ}{150 + j150} = 0.04 \angle -81.92^\circ$$

$$(d), (e) P_1(0) = \frac{1}{2} \operatorname{Re}[V_1(0) I_1^*(0)] = 0.12 \text{ W}, \quad P_1\left(\frac{\lambda}{8}\right) = \frac{1}{2} \operatorname{Re}[V_1\left(\frac{\lambda}{8}\right) I_1^*\left(\frac{\lambda}{8}\right)] = 0.12 \text{ W}$$

$$\text{Also: } P_1(0) = P_1\left(\frac{\lambda}{8}\right) = \frac{1}{2} |a_1(0)|^2 - \frac{1}{2} |b_1(0)|^2 = \frac{1}{2} |a_1\left(\frac{\lambda}{8}\right)|^2 - \frac{1}{2} |b_1\left(\frac{\lambda}{8}\right)|^2 = \frac{1}{2} (0.707)^2 - \frac{1}{2} (0.508)^2 = 0.12 \text{ W}$$

$$(f) S_{11}\left(\frac{\lambda}{8}\right) = \frac{Z_{T1} - Z_0}{Z_{T1} + Z_0} = \frac{150 + j150 - 50}{150 + j150 + 50} = 0.721 \angle 19.44^\circ$$

$$S_{11}(0) = S_{11}\left(\frac{\lambda}{8}\right) e^{-j2(\pi/4)} = 0.721 \angle 19.44^\circ \angle -90^\circ = 0.721 \angle -70.56^\circ$$

$$(g) (VSWR)_{in} = \frac{1 + |S_{11}|}{1 - |S_{11}|} = 6.17, \quad (VSWR)_{out} = 1$$

$$(h) \lambda = \frac{3 \times 10^8}{10^9} = 0.3 \text{ m (OR } 30 \text{ cm)}, \quad \ell = \frac{\lambda}{8} = \frac{30}{8} = 3.75 \text{ cm}$$

$$(i) b_2\left(\frac{\lambda}{8}\right) = S_{21} a_1\left(\frac{\lambda}{8}\right) + S_{22} a_2\left(\frac{\lambda}{8}\right) = 3 \angle 60^\circ (0.707 \angle -45^\circ) = 2.12 \angle 15^\circ$$

$$P_2(0) = \frac{1}{2} |b_2(0)|^2 = \frac{1}{2} |b_2\left(\frac{\lambda}{8}\right)|^2 = \frac{1}{2} (2.12)^2 = 2.25 \text{ W}$$

$$1.17) (a) Z_{IN}(0) = Z_{IN}(\frac{\lambda}{4}) = 75 \frac{(150 + j150) + j75 \tan 45^\circ}{75 + j(150 + j150) \tan 45^\circ} = 60 - j105 \Omega$$

(b) THE VSWR IN THE $\lambda_2 = \frac{\lambda}{4}$ LINE IS UNITY, SINCE THE LINE IS MATCHED.

$$\text{IN THE } \lambda_1 = \frac{\lambda}{8} \text{ LINE: } \Gamma_0 = \frac{(150 + j150) - 75}{(150 + j150) + 75} = 0.62 \angle 29.7^\circ$$

$$\therefore \text{VSWR} = \frac{1 + 0.62}{1 - 0.62} = 4.26$$

$$(c) V_1(0) = \frac{10 \angle 0^\circ Z_{IN}(0)}{Z_{IN}(0) + Z_1} = \frac{10(60 - j105)}{60 - j105 + 100} = 6.32 \angle -26.98^\circ$$

$$I_1(0) = \frac{V_1(0)}{Z_{IN}(0)} = \frac{6.32 \angle -26.98^\circ}{60 - j105} = 0.0523 \angle 33.27^\circ$$

$$a_1(0) = \frac{1}{2\sqrt{75}} [V_1(0) + 75 I_1(0)] = 0.516 \angle -4.6^\circ$$

$$b_1(0) = \frac{1}{2\sqrt{75}} [V_1(0) - 75 I_1(0)] = 0.32 \angle -64.88^\circ$$

$$a_1(\frac{\lambda}{8}) = a_1(0) e^{-j\pi/4} = 0.516 \angle -49.6^\circ$$

$$b_1(\frac{\lambda}{8}) = b_1(0) e^{j\pi/4} = 0.32 \angle -19.8^\circ$$

$$a_2(0) = 0$$

$$(d) P_1(0) = \frac{1}{2} |a_1(0)|^2 - \frac{1}{2} |b_1(0)|^2 = \frac{1}{2} (0.516)^2 - \frac{1}{2} (0.32)^2 = 0.082 \text{ W}$$

$$P_1(\frac{\lambda}{8}) = \frac{1}{2} |a_1(\frac{\lambda}{8})|^2 - \frac{1}{2} |b_1(\frac{\lambda}{8})|^2 = \frac{1}{2} (0.516)^2 - \frac{1}{2} (0.32)^2 = 0.082 \text{ W}$$

$$(e) P_{AVS} = \frac{|E_s|^2}{8 \text{Re}[Z_s]} = \frac{(10)^2}{8(100)} = 0.125 \text{ W}$$

$$\frac{1}{2} |a_1(0)|^2 = 0.133 \text{ W}$$

SINCE $Z_1 \neq Z_0$, IT FOLLOWS THAT $P_{AVS} \neq \frac{1}{2} |a_1(0)|^2$

$$1.18) (a) V = \frac{5 \angle 30^\circ (100)}{100 + (50 + j50)} = 3.162 \angle 11.565^\circ$$

$$I = \frac{V}{Z_L} = \frac{3.162 \angle 11.565^\circ}{100} = 0.0316 \angle 11.565^\circ$$

$$a_p = \frac{1}{2\sqrt{R_n}} (V + Z_n I) = \frac{1}{2\sqrt{50}} (3.162 \angle 11.565^\circ + (50 + j50)(0.0316 \angle 11.565^\circ))$$

$$= 0.355 \angle 30.14^\circ$$

$$b_p = \frac{1}{2\sqrt{R_L}} (V - Z_L^* I) = \frac{1}{2\sqrt{50}} (3.162 \angle 11.565^\circ - (50 - j50)(0.0316 \angle 11.565^\circ))$$

$$= 0.158 \angle 56.53^\circ$$

$$V_p^+ = \frac{E_L Z_L^*}{2R_L} = \frac{5 \angle 30^\circ (50 - j50)}{2(50)} = 3.536 \angle -15^\circ$$

$$V_p^- = V - V_p^+ = 3.162 \angle 11.565^\circ - 3.536 \angle -15^\circ = 1.581 \angle 101.59^\circ$$

$$I_p^+ = \frac{E_L}{2R_L} = \frac{5 \angle 30^\circ}{2(50)} = 0.05 \angle 30^\circ$$

$$I_p^- = I_p^+ - I = 0.05 \angle 30^\circ - 0.0316 \angle 11.565^\circ = 0.022 \angle 56.52^\circ$$

$$(b) \quad V_p^+ = \frac{Z_L^*}{\sqrt{R_L}} a_p = \frac{(50 - j50)}{\sqrt{50}} 0.355 \angle 30.14^\circ = 3.54 \angle -15^\circ$$

$$(c) \quad V_p^- = \frac{Z_L}{\sqrt{R_L}} b_p = \frac{(50 + j50)}{\sqrt{50}} 0.158 \angle 56.53^\circ = 1.58 \angle 101.5^\circ$$

$$V = V_p^+ + V_p^- = 3.16 \angle 11.56^\circ$$

$$I_p^+ = \frac{a_p}{\sqrt{R_L}} = \frac{0.355 \angle 30.14^\circ}{\sqrt{50}} = 0.05 \angle 30.14^\circ$$

$$I_p^- = \frac{b_p}{\sqrt{R_L}} = \frac{0.158 \angle 56.53^\circ}{\sqrt{50}} = 0.022 \angle 56.53^\circ$$

$$I = I_p^+ - I_p^- = 0.0316 \angle 11.56^\circ$$

1.19) IN EXAMPLE 1.71: $V = 5.59 \angle -26.57^\circ$, $a_p = 0.5$, $b_p = 0$

$$(a) \quad V_p^+ = \frac{E_L Z_L^*}{2R_L} = \frac{10(100 - j50)}{2(100)} = 5.59 \angle -26.57^\circ$$

$$V_p^- = V - V_p^+ = 5.59 \angle -26.57^\circ - 5.59 \angle -26.57^\circ = 0$$

$$(b) \quad a_p = \frac{\sqrt{R_L}}{Z_L^*} V_p^+ = \frac{\sqrt{100}}{100 - j50} (5.59 \angle -26.57^\circ) = 0.5$$

$$b_p = \frac{\sqrt{R_L}}{Z_L} V_p^- = 0$$

1.20) IN EXAMPLE 1.72: $V=10$, $a_p=1.5$, $b_p=-0.5$


$$(a) \quad V_p^+ = \frac{E_n Z_n^*}{2R_n} = \frac{30(100)}{2(100)} = 15$$

$$V_p^- = V - V_p^+ = 10 - 15 = -5$$

$$(b) \quad a_p = \frac{\sqrt{R_n}}{Z_n^*} V_p^+ = \frac{\sqrt{100}}{100} (15) = 1.5$$

$$b_p = \frac{\sqrt{R_n}}{Z_n} V_p^- = \frac{\sqrt{100}}{100} (-5) = -0.5$$

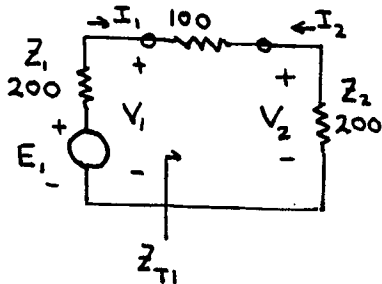1.21) WITH $E_2=0$: $Z_{T1} = 100 + 200 = 300$



$$S_{p11} = \frac{Z_{T1} - Z_1^*}{Z_{T1} + Z_1} = \frac{300 - 200}{300 + 200} = 0.2$$

$$V_1 = \frac{E_1 300}{300 + 200} = \frac{3}{5} E_1, \quad I_1 = \frac{E_1}{500}$$

$$V_2 = \frac{E_1 200}{200 + 300} = \frac{2}{5} E_1, \quad I_2 = -\frac{E_1}{500}$$

$$a_{p1} = \frac{1}{2\sqrt{200}} (V_1 + Z_1 I_1) = \frac{1}{2\sqrt{200}} \left(\frac{3}{5} E_1 + 200 \frac{E_1}{500} \right) = \frac{E_1}{2\sqrt{200}}, \quad a_{p2} = 0$$

$$b_{p2} = \frac{1}{2\sqrt{200}} (V_2 - Z_2^* I_2) = \frac{1}{2\sqrt{200}} \left(\frac{2}{5} E_1 + 200 \frac{E_1}{500} \right) = \frac{2E_1}{5\sqrt{200}}$$

$$S_{p21} = \frac{b_{p2}}{a_{p1}} \bigg|_{a_{p2}=0} = \frac{2E_1 / 5\sqrt{200}}{E_1 / 2\sqrt{200}} = \frac{4}{5}$$

FROM SYMMETRY: $S_{p22} = S_{p11}$ AND $S_{p12} = S_{p21}$

THE MAGNITUDE OF S_{p21} CAN ALSO BE CALCULATED AS FOLLOWS:


$$|S_{p21}|^2 = \frac{P_L}{P_{AVS}}, \quad P_L = \frac{1}{2} \left| E_1 \left(\frac{2}{5} \right) \right|^2, \quad P_{AVS} = \frac{|E_1|^2}{8(200)}$$

$$\therefore |S_{p21}|^2 = \frac{16}{25} \quad \text{OR} \quad |S_{p21}| = \frac{4}{5}$$

SINCE IN THIS EXAMPLE S_{p21} IS REAL, THEN $S_{p21} = \frac{4}{5}$.

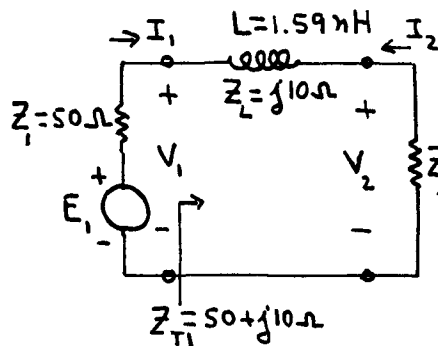1.22) (a) $f = 1 \text{ GHz}$

EVALUATION OF S_{p11} AND S_{p21} (LET $E_1 = 1 \angle 0^\circ$)



$$V_1 = \frac{E_1(50 + j10)}{100 + j10} = 0.5074 \angle 5.599^\circ$$

$$I_1 = \frac{V_1}{50 + j10} = 0.01 \angle -5.711^\circ$$

$$V_2 = \frac{E_1 50}{100 + j10} = 0.4975 \angle -5.711^\circ$$

$$I_2 = -\frac{V_2}{50} = 0.01 \angle 174.29^\circ$$

$$a_{p1} = \frac{1}{2\sqrt{R_1}}(V_1 + Z_1 I_1) = \frac{1}{2\sqrt{50}}(0.5074 \angle 5.599^\circ + 50(0.01 \angle -5.711^\circ)) = 0.0709 \angle -0.0143^\circ$$

$$b_{p1} = \frac{1}{2\sqrt{R_1}}(V_1 - Z_1^* I_1) = \frac{1}{2\sqrt{50}}(0.5074 \angle 5.599^\circ - 50(0.01 \angle -5.711^\circ)) = 0.007 \angle 85.70^\circ$$

$$a_{p2} = \frac{1}{2\sqrt{R_2}}(V_2 + Z_2 I_2) = 0$$

$$b_{p2} = \frac{1}{2\sqrt{R_2}}(V_2 - Z_2^* I_2) = \frac{1}{2\sqrt{50}}(0.4975 \angle -5.711^\circ - 50(0.01 \angle 174.29^\circ)) = 0.0705 \angle -5.711^\circ$$

$$S_{p11} = \left. \frac{b_{p1}}{a_{p1}} \right|_{a_{p2}=0} = \frac{0.007 \angle 85.7^\circ}{0.0709 \angle -0.0143^\circ} = 0.099 \angle 85.7^\circ$$

S_{p11} CAN ALSO BE CALCULATED USING:

$$S_{p11} = \frac{Z_{T1} - Z_1^*}{Z_{T1} + Z_1} = \frac{50 + j10 - 50}{50 + j10 + 50} = 0.099 \angle 84.3^\circ$$

$$S_{p21} = \left. \frac{b_{p2}}{a_{p1}} \right|_{a_{p2}=0} = \frac{0.0705 \angle -5.711^\circ}{0.0709 \angle -0.0143^\circ} = 0.994 \angle -5.7^\circ$$

(b) WITH $Z_0 = 50 \Omega$, IT FOLLOWS FROM (1.6.24) AND (1.6.25) THAT

$$S_{11} = S_{22} = \frac{Z_L}{Z_L + 2Z_0} = \frac{j10}{j10 + 100} = 0.099 \angle 84.3^\circ$$

$$S_{21} = S_{12} = \frac{2Z_0}{Z_L + 2Z_0} = \frac{100}{j10 + 100} = 0.995 \angle -5.7^\circ$$

AS EXPECTED, FOR $Z_1 = Z_2 = Z_0 = 50 \Omega$ THE S_p PARAMETERS ARE IDENTICAL TO THE S PARAMETERS.

1.23) At P: $I_1^+ = I_1^- + I_2^- + I_3^-$

AND $b_1 = S_{11} a_1 \Rightarrow \sqrt{Z_0} I_1^- = S_{11} \sqrt{Z_0} I_1^+$ OR $I_1^- = S_{11} I_1^+$

$b_2 = S_{21} a_1 \Rightarrow \sqrt{Z_0} I_2^- = S_{21} \sqrt{Z_0} I_1^+$ OR $I_2^- = S_{21} I_1^+$

$b_3 = S_{31} a_1 \Rightarrow \sqrt{Z_0} I_3^- = S_{31} \sqrt{Z_0} I_1^+$ OR $I_3^- = S_{31} I_1^+$

$\therefore I_1^+ = S_{11} I_1^+ + S_{21} I_1^+ + S_{31} I_1^+$

$S_{11} + S_{21} + S_{31} = 1$

SIMILARLY, WITH E_2 APPLIED TO PORT 2 WITH THE OTHER PORTS MATCHED GIVES

$S_{12} + S_{22} + S_{32} = 0$

WITH E_3 APPLIED TO PORT 3, WITH THE OTHER PORTS MATCHED GIVES

$S_{13} + S_{23} + S_{33} = 0$

WITH ALL THE SOURCES EQUAL TO E_0 , AS SHOWN IN FIG. 1.22b, THE CURRENTS I_1, I_2 , AND I_3 ARE EQUAL TO ZERO. HENCE,

$I_1^+ = I_1^-, I_2^+ = I_2^-, I_3^+ = I_3^-,$ AND $I_1^+ = I_2^+ = I_3^+$

FROM

$b_1 = S_{11} a_1 + S_{12} a_2 + S_{13} a_3$

OR

$I_1^- = S_{11} I_1^+ + S_{12} I_2^+ + S_{13} I_3^+ \Rightarrow S_{11} + S_{12} + S_{13} = 1$

SIMILARLY:

$I_2^- = S_{21} I_1^+ + S_{22} I_2^+ + S_{23} I_3^+ \Rightarrow S_{21} + S_{22} + S_{23} = 1$

$I_3^- = S_{31} I_1^+ + S_{32} I_2^+ + S_{33} I_3^+ \Rightarrow S_{31} + S_{32} + S_{33} = 1$

1.24) $v_1 = z_{11} i_1 + z_{12} i_2$ (1)

(2)

$v_2 = z_{21} i_1 + z_{22} i_2$ (2)

$i_1 = y_{11} v_1 + y_{12} v_2$ (3)

$i_2 = y_{21} v_1 + y_{22} v_2$ (4)

FROM (2): $i_2 = \frac{v_2}{z_{22}} - \frac{z_{21}}{z_{22}} i_1$ (5)

(5) INTO (1): $i_1 = \frac{z_{22}}{|\Delta|} v_1 - \frac{z_{12}}{|\Delta|} v_2$ (6), $|\Delta| = z_{11} z_{22} - z_{21} z_{12}$

COMPARING (6) WITH (3) GIVES: $y_{11} = \frac{z_{22}}{|\Delta|}$ AND $y_{12} = -\frac{z_{12}}{|\Delta|}$

$$(6) \text{ INTO } (2): v_2 = z_{21} \left(\frac{z_{22}}{z_1} v_1 - \frac{z_{12}}{z_1} v_2 \right) + z_{22} i_2$$

$$\text{OR } i_2 = -\frac{z_{21}}{z_1} v_1 + \frac{z_{11}}{z_1} v_2 \quad (7)$$

$$\text{COMPARING (7) WITH (4) GIVES: } y_{21} = -\frac{z_{21}}{z_1} \text{ AND } y_{22} = \frac{z_{11}}{z_1}$$

THE DERIVATION BETWEEN y AND z PARAMETERS IS SIMILAR.

$$(b) \quad v_1 = A v_2 - B i_2 \quad (8)$$

$$i_1 = C v_2 - D i_2 \quad (9)$$

$$\text{FROM (9): } v_2 = \frac{1}{C} i_1 + \frac{D}{C} i_2 \quad (10)$$

$$(10) \text{ INTO (8): } v_1 = \frac{A}{C} i_1 + \frac{AD - BC}{C} i_2 \quad (11)$$

$$\text{COMPARING (11) WITH (1) GIVES: } z_{11} = \frac{A}{C} \text{ AND } z_{12} = \frac{AD - BC}{C}$$

$$(11) \text{ INTO (8): } \frac{A}{C} i_1 + \frac{AD - BC}{C} i_2 = A v_2 - B i_2$$

$$\text{OR } v_2 = \frac{1}{C} i_1 + \frac{D}{C} i_2 \quad (12)$$

$$\text{COMPARING (12) WITH (2) GIVES: } z_{21} = \frac{1}{C} \text{ AND } z_{22} = \frac{D}{C}$$

THE DERIVATION BETWEEN z AND ABCD IS SIMILAR.

1.25)(a) FOR REAL $[Z_0]$ AND $[Y_0]$

$$[I] = [y][V]$$

$$[I^-] = [I^+] - [I]$$

$$[V^-][Y_0] = [V^+][Y_0] - [y]([V^+] + [V^-])$$

$$([Y_0] + [y])[V^-] = ([Y_0] - [y])[V^+]$$

$$[V^-] = ([Y_0] + [y])^{-1} ([Y_0] - [y])[V^+] \\ = [S][V^+]$$

$$\therefore [S] = -([Y_0] + [y])^{-1} ([y] - [Y_0]) \quad (1)$$

$$\begin{aligned}
 [Y_0] - [Y] &= [Y_0][S] + [Y][S] \\
 [Y_0]([I] - [S]) &= [Y]([I] + [S]) \\
 [Y] &= [Y_0]([I] - [S])([I] + [S])^{-1}
 \end{aligned}$$

(b) FROM (1):

$$[S] = - \left[\begin{bmatrix} Y_0 & 0 \\ 0 & Y_0 \end{bmatrix} + \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \right]^{-1} \left[\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} - \begin{bmatrix} Y_0 & 0 \\ 0 & Y_0 \end{bmatrix} \right]$$

$$[S] = - \begin{bmatrix} y_{11} + Y_0 & y_{12} \\ y_{21} & y_{22} + Y_0 \end{bmatrix}^{-1} \begin{bmatrix} y_{11} - Y_0 & y_{12} \\ y_{21} & y_{22} - Y_0 \end{bmatrix}$$

$$\begin{bmatrix} y_{11} + Y_0 & y_{12} \\ y_{21} & y_{22} + Y_0 \end{bmatrix}^{-1} = \frac{\begin{bmatrix} y_{22} + Y_0 & -y_{12} \\ -y_{21} & y_{11} + Y_0 \end{bmatrix}}{(y_{11} + Y_0)(y_{22} + Y_0) - y_{12}y_{21}}$$

$$\therefore [S] = - \frac{\begin{bmatrix} (y_{22} + Y_0)(y_{11} - Y_0) - y_{12}y_{21} & (y_{22} + Y_0)y_{12} - y_{12}(y_{22} - Y_0) \\ -y_{21}(y_{11} - Y_0) + y_{21}(y_{11} + Y_0) & -y_{12}y_{21} + (y_{11} + Y_0)(y_{22} - Y_0) \end{bmatrix}}{(y_{11} + Y_0)(y_{22} + Y_0) - y_{12}y_{21}}$$

$$[S] = \frac{1}{\Delta_2} \begin{bmatrix} (1 - y'_{11})(1 + y'_{22}) + y'_{12}y'_{21} & -2y'_{12} \\ -2y'_{21} & (1 + y'_{11})(1 - y'_{22}) + y'_{12}y'_{21} \end{bmatrix}$$

WHERE $\Delta_2 = (1 + y'_{11})(1 + y'_{22}) - y'_{12}y'_{21}$, $y'_{11} = y_{11}Z_0$, $y'_{12} = y_{12}Z_0$,
 $y'_{21} = y_{21}Z_0$, AND $y'_{22} = y_{22}Z_0$ ($Y_0 = 1/Z_0$).

1.26) STEP 1. CONVERT THE $[S]$ PARAMETERS OF THE BJT TO $[Z]$ PARAMETERS (CALLED $[Z_1]$).

STEP 2. CALCULATE THE $[Z]$ PARAMETERS OF THE INDUCTOR (CALLED $[Z_2]$).

STEP 3. ADD THE $[Z]$ PARAMETERS (I.E., $[Z_3] = [Z_1] + [Z_2]$)

STEP 4. CONVERT $[Z_3]$ TO $[S]$ PARAMETERS. THESE ARE THE $[S]$ PARAMETERS OF THE TWO-PORT NETWORK.

1.27) CONVERT THE CE S PARAMETERS TO CE y PARAMETERS (SEE FIG. 1.8.1),

THAT IS: $y_{11,e} = 0.016 + j0.034$ $y_{12,e} = 0.00141 - j0.0272(10^{-3})$

$$y_{21,e} = 0.04 - j0.036 \quad y_{22,e} = 0.00363 + j0.0079$$

USE THE RELATIONS IN FIG. 1.8.1b TO CALCULATE THE CB AND CC y PARAMETERS. THAT IS,

$$y_{11,b} = 0.061 + j0.00587 \quad y_{12,b} = -0.00503 - j0.00787$$

$$y_{21,b} = -0.0436 + j0.0281 \quad y_{22,b} = 0.00363 + j0.0079$$

AND

$$y_{11,c} = 0.016 + j0.034 \quad y_{12,c} = -0.0174 - j0.034$$

$$y_{21,c} = -0.056 + j0.002 \quad y_{22,c} = 0.061 + j0.00587$$

CONVERT FROM CB AND CC y PARAMETERS TO CB AND CC S PARAMETERS. THAT IS,

$$[S]_{CB} = \begin{bmatrix} 0.356 \angle -173.6^\circ & 0.243 \angle 35.41^\circ \\ 1.348 \angle -54.81^\circ & 1.198 \angle -32.7^\circ \end{bmatrix} \quad \text{AND} \quad [S]_{CC} = \begin{bmatrix} 0.893 \angle -62.03^\circ & 0.764 \angle 29.68^\circ \\ 1.12 \angle -35.26^\circ & 0.176 \angle 98.35^\circ \end{bmatrix}$$

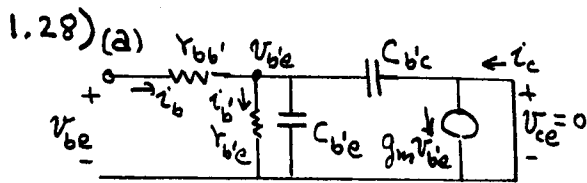


FIG. 1.11.4 WITH $v_{ce} = 0$

$$i_c = g_m v_{b'e} \quad (1)$$

$$i_{b'} = i_b \frac{\left(\frac{1}{j\omega(C_{b'e} + C_{b'c})} \right)}{r_{b'e} + \left(\frac{1}{j\omega(C_{b'e} + C_{b'c})} \right)} \quad (2)$$

$$v_{b'e} = i_{b'} r_{b'e} \quad (3)$$

FROM (1), (2), AND (3): $i_c = g_m r_{b'e} i_{b'} = \frac{g_m r_{b'e} i_b}{1 + j\omega r_{b'e} (C_{b'e} + C_{b'c})}$

DEFINE $h_{fe}(j\omega)$ AS:

$$h_{fe}(j\omega) = \frac{i_c}{i_b} \bigg|_{v_{ce}=0} = \frac{g_m r_{b'e}}{1 + j\omega r_{b'e} (C_{b'e} + C_{b'c})} = \frac{g_m r_{b'e}}{1 + j\omega/\omega_\beta}$$

WHERE

$$f_\beta = \frac{\omega_\beta}{2\pi} = \frac{1}{2\pi r_{b'e} (C_{b'e} + C_{b'c})} \approx \frac{1}{2\pi r_{b'e} C_{b'e}} \quad (\text{SINCE } C_{b'e} \gg C_{b'c})$$

f_T (THE GAIN-BANDWIDTH PRODUCT) IS THE FREQUENCY WHERE $|h_{fe}(j\omega)| = 1$, OR

$$1 = \frac{g_m r_{b'e}}{\sqrt{1 + (\omega_T/\omega_\beta)^2}} \approx g_m r_{b'e} \frac{\omega_\beta}{\omega_T} \Rightarrow f_T = g_m r_{b'e} f_\beta = \frac{g_m}{2\pi C_{b'e}}$$

(b) SIMILARLY, FOR THE FET IN FIG. 1.11.15 WE OBTAIN

$$f_T = \frac{g_m}{2\pi (C_{gs} + C_{gd})} \approx \frac{g_m}{2\pi C_{gs}} = \frac{g_m}{2\pi C_c} \quad (\text{SINCE } C_{gs} \text{ IS DENOTED BY } C_c \text{ IN FIG. 1.11.15})$$