

SOLUTIONS MANUAL

MICROWAVE TRANSISTOR AMPLIFIERS

Analysis and Design

SECOND EDITION

Guillermo Gonzalez



PRENTICE HALL
Upper Saddle River, NJ 07458

Acquisitions Editor: *Eric Svendsen*
Project Editor: *Lorena Cerisano*
Production Manager: *Joan Eurell*
Production Coordinator: *Julia Meehan*

©1996 by Prentice-Hall, Inc.
Simon & Schuster / A Viacom Company
Upper Saddle River, New Jersey 07458

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission in writing from the publisher.

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

ISBN 0-13-271255-5

Prentice-Hall International (UK) Limited, *London*
Prentice-Hall of Australia Pty. Limited, *Sydney*
Prentice-Hall Canada Inc., *Toronto*
Prentice-Hall Hispanoamericana, S.A., *Mexico*
Prentice-Hall of India Private Limited, *New Delhi*
Prentice-Hall of Japan, Inc., *Tokyo*
Simon & Schuster Asia Pte. Ltd., *Singapore*
Editora Prentice-Hall do Brasil, Ltda., *Rio de Janeiro*

CONTENTS

CHAPTER	1	page 1
CHAPTER	2	page 19
CHAPTER	3	page 42
CHAPTER	4	page 71
CHAPTER	5	page 88

$$3.1) (2) \quad G_T = \frac{P_L}{P_{AVS}}, \quad G_p = \frac{P_L}{P_{IN}}, \quad G_A = \frac{P_{AVN}}{P_{AVS}}, \quad P_{IN} = P_{AVS} M_L \quad (M_L \leq 1),$$

$$\text{AND } P_L = P_{AVN} M_L \quad (M_L \leq 1).$$

HENCE, [SEE (2.7.29)]: $G_T = G_p M_L$ OR $G_T \leq G_p$, AND

$$G_T = G_A M_L \text{ OR } G_T \leq G_A.$$

$$G_T = G_p \text{ WHEN } \Gamma_L = \Gamma_{IN}^* \text{ (OR WHEN } M_L = 1)$$

$$G_T = G_A \text{ WHEN } \Gamma_L = \Gamma_{OUT}^* \text{ (OR WHEN } M_L = 1)$$

(b) G_T IN (3.2.1) AND G_p IN (3.2.3) SHOULD BE IDENTICAL WHEN $\Gamma_L = \Gamma_{IN}^*$
(i.e., $P_{IN} = P_{AVS}$ WHEN $\Gamma_L = \Gamma_{IN}^*$). FROM (3.2.1) WITH $\Gamma_L = \Gamma_{IN}^*$:

$$G_T = \frac{1 - |\Gamma_{IN}|^2}{|1 - \Gamma_{IN} \Gamma_{IN}^*|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2} = \frac{1 - |\Gamma_{IN}|^2}{(1 - |\Gamma_{IN}|^2)^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

HENCE:

$$G_T = G_p = \frac{1}{1 - |\Gamma_{IN}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

G_T IN (3.2.2) AND G_A IN (3.2.4) SHOULD BE IDENTICAL WHEN $\Gamma_L = \Gamma_{OUT}^*$
(i.e., $P_L = P_{AVN}$ WHEN $\Gamma_L = \Gamma_{OUT}^*$). FROM (3.2.2) WITH $\Gamma_L = \Gamma_{OUT}^*$:

$$G_T = \frac{1 - |\Gamma_L|^2}{|1 - S_{11} \Gamma_L|^2} |S_{21}|^2 \frac{1 - |\Gamma_{OUT}|^2}{|1 - \Gamma_{OUT} \Gamma_{OUT}^*|^2} = \frac{1 - |\Gamma_L|^2}{|1 - S_{11} \Gamma_L|^2} |S_{21}|^2 \frac{1 - |\Gamma_{OUT}|^2}{(1 - |\Gamma_{OUT}|^2)^2}$$

HENCE:

$$G_T = G_A = \frac{1 - |\Gamma_L|^2}{|1 - S_{11} \Gamma_L|^2} |S_{21}|^2 \frac{1}{1 - |\Gamma_{OUT}|^2}$$

3.2) (a) WITH $Z_L = Z_L = Z_0$ THEN $\Gamma_L = \Gamma_L = 0$, AND FROM (3.2.1):

$$G_T = |S_{21}|^2$$

(b) FROM (3.2.5): $\Gamma_{IN} = S_{11}$ WHEN $\Gamma_L = 0$. THEREFORE, FROM (3.2.3):

$$G_p = \frac{|S_{21}|^2}{1 - |\Gamma_{IN}|^2} = \frac{|S_{21}|^2}{1 - |S_{11}|^2}$$

(c) FROM (3.2.6): $\Gamma_{OUT} = S_{22}$ WHEN $\Gamma_L = 0$. THEREFORE, FROM (3.2.4):

$$G_A = \frac{|S_{21}|^2}{1 - |\Gamma_{OUT}|^2} = \frac{|S_{21}|^2}{1 - |S_{22}|^2}$$

3.3)(a) WITH THE VALUES GIVEN IN THE PROBLEM IT FOLLOWS THAT:

FROM (3.2.5): $\Gamma_{IN} = 0.671 \angle 160.72^\circ$

FROM (3.2.6): $\Gamma_{OUT} = 0.615 \angle -82.8^\circ$

FROM (3.2.1): $G_T = 8.575$ OR 9.33 dB

FROM (3.2.3): $G_p = 9.487$ OR 9.77 dB

FROM (3.2.4): $G_A = 8.745$ OR 9.42 dB

(b) $P_{AVS} = \frac{|E_s|^2}{8 \operatorname{Re}[Z_s]} = \frac{10^2}{8(50)} = 0.25 \text{ W}$, $M_A = \frac{G_T}{G_p} = \frac{8.575}{9.487} = 0.904$

$P_{IN} = P_{AVS} M_A = 0.25(0.904) = 0.226 \text{ W}$

$P_L = G_p P_{IN} = 9.487(0.226) = 2.144 \text{ W}$

$P_{AVN} = G_A P_{AVS} = 8.745(0.25) = 2.186 \text{ W}$

3.4) $\Gamma_L = 0$ AND $\Gamma_L = 0.5 \angle 90^\circ$. HENCE:


$G_T = G_{TW} = 11.294$ OR 10.53 dB


$G_p = 22.145$ OR 13.45 dB

$G_A = 21.33$ OR 13.29 dB

3.5) OBSERVE THAT $\Gamma_{OUT} = S_{22}$ WHEN $\Gamma_L = 0$. THEREFORE, THE ORIGIN (I.E., $\Gamma_L = 0$) IS A STABLE POINT WHEN $|S_{22}| < 1$.

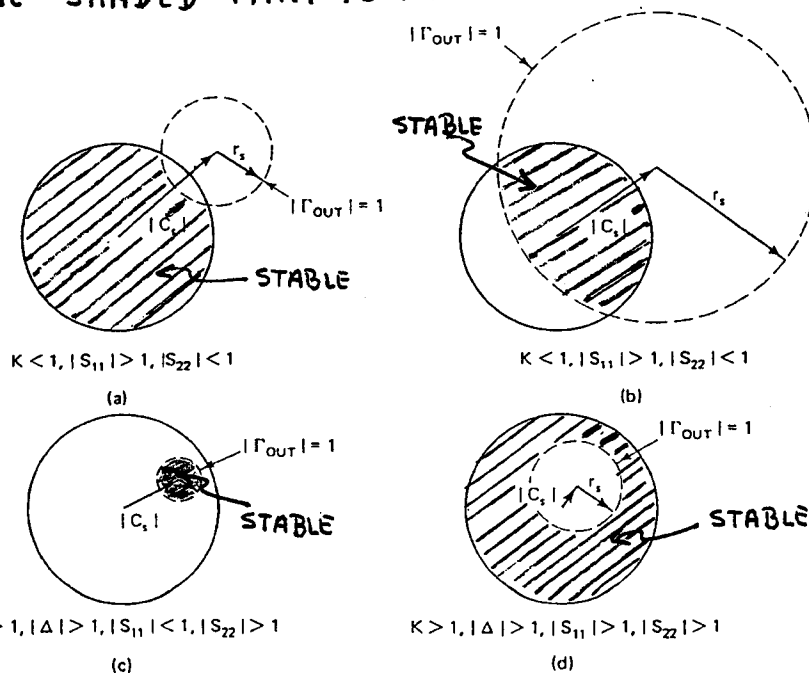
THE "SHADED" PART IS THE "STABLE REGION".



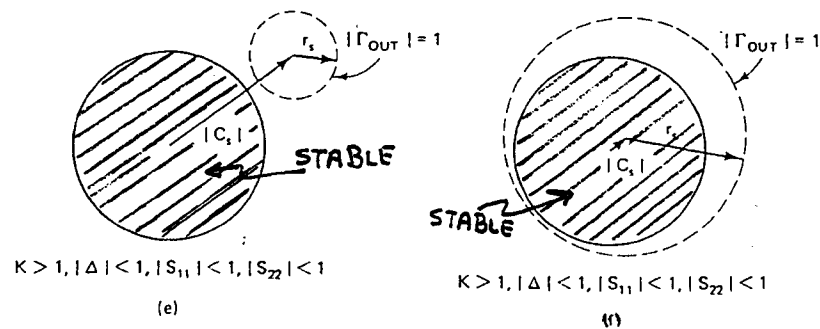

3.6) OBSERVE THAT $\Gamma_{IN} = S_{11}$ WHEN $\Gamma_L = 0$. THEREFORE, THE ORIGIN (I.E., $\Gamma_L = 0$) IS A STABLE POINT WHEN $|S_{11}| < 1$.

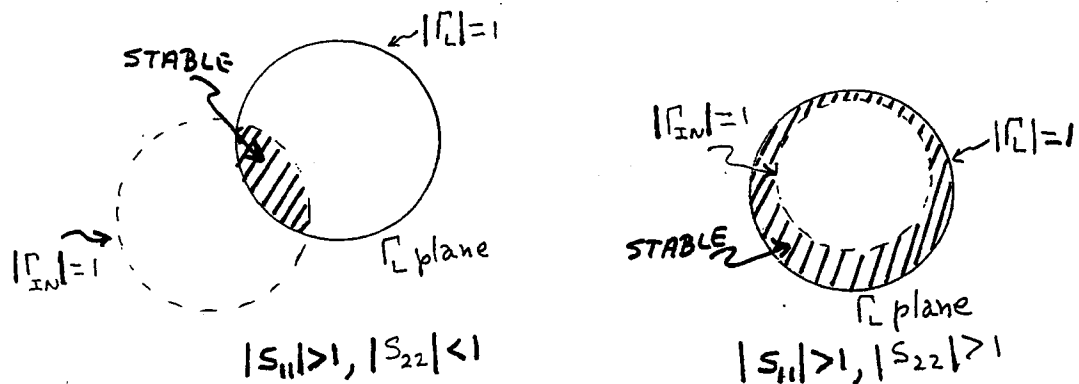THE "SHADED" PART IS THE "STABLE REGION".




3.7) (a) $K = 1.284, \Delta = 0.386 \angle 134.2^\circ \therefore$ UNCONDITIONALLY STABLE.

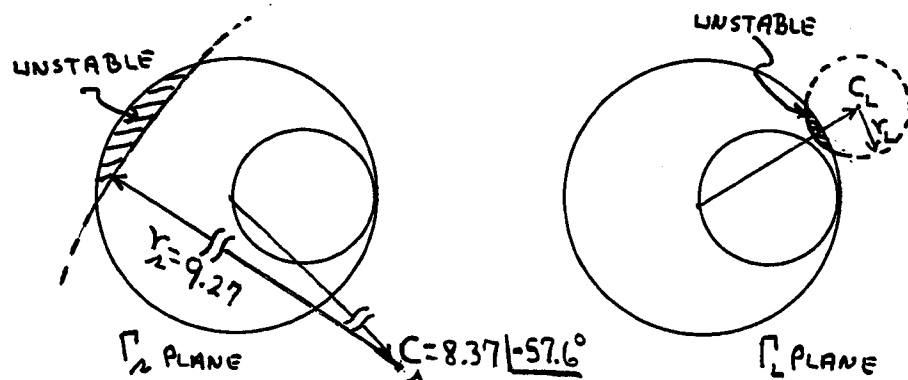(b) $K = 0.909, \Delta = 0.402 \angle -65.04^\circ \therefore$ POTENTIALLY UNSTABLE.

INPUT STABILITY CIRCLE $\begin{cases} r_L = 9.27 \\ C_L = 8.37 \angle -57.6^\circ \end{cases}$



OUTPUT STABILITY CIRCLE $\begin{cases} r_L = 0.19 \\ C_L = 1.18 \angle 29.8^\circ \end{cases}$



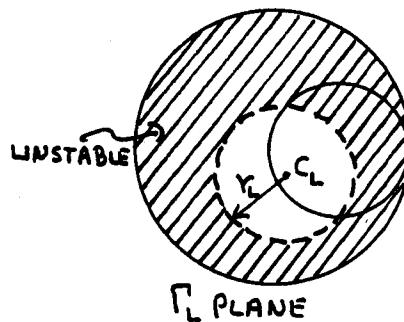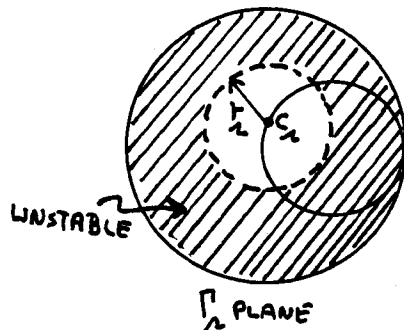(c) $K=1.202$, $\Delta=1.76 \angle 18.5^\circ$ $\therefore$ POTENTIALLY UNSTABLE



INPUT STABILITY CIRCLE $\begin{cases} \gamma_{\lambda}=0.518 \\ C_{\lambda}=0.152 \angle 82.1^\circ \end{cases}$

OUTPUT STABILITY CIRCLE $\begin{cases} \gamma_L=0.494 \\ C_L=0.239 \angle -58^\circ \end{cases}$



3.8)


f (GHz)	K	Δ	STABILITY CIRCLE	STABILITY CIRCLE
4	0.412	$0.65 \angle -90.3^\circ$	$\gamma_{\lambda}=0.444, C_{\lambda}=1.25 \angle 80.9^\circ$	$\gamma_L=3.79, C_L=4.3 \angle 91.4^\circ$
6	0.56	$0.57 \angle -131.1^\circ$	$\gamma_{\lambda}=0.604, C_{\lambda}=1.43 \angle 111.6^\circ$	$\gamma_L=6.316, C_L=6.93 \angle 107.8^\circ$
8	0.78	$0.43 \angle -174.9^\circ$	$\gamma_{\lambda}=0.789, C_{\lambda}=1.69 \angle 152.6^\circ$	$\gamma_L=7.39, C_L=8.2 \angle 126.1^\circ$
10	0.89	$0.32 \angle -114^\circ$	$\gamma_{\lambda}=0.759, C_{\lambda}=1.72 \angle -171.8^\circ$	$\gamma_L=3.49, C_L=4.41 \angle 150.1^\circ$
14	1.33	$0.17 \angle -2.4^\circ$	$\gamma_{\lambda}=0.513, C_{\lambda}=1.62 \angle -110.2^\circ$	$\gamma_L=1.87, C_L=3.08 \angle -171.7^\circ$

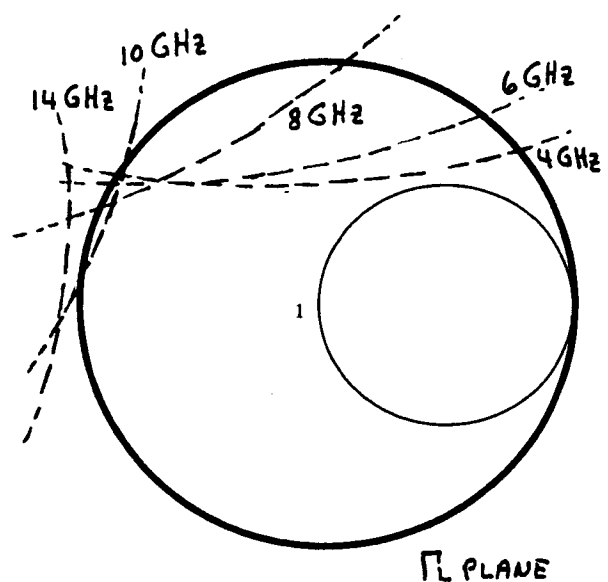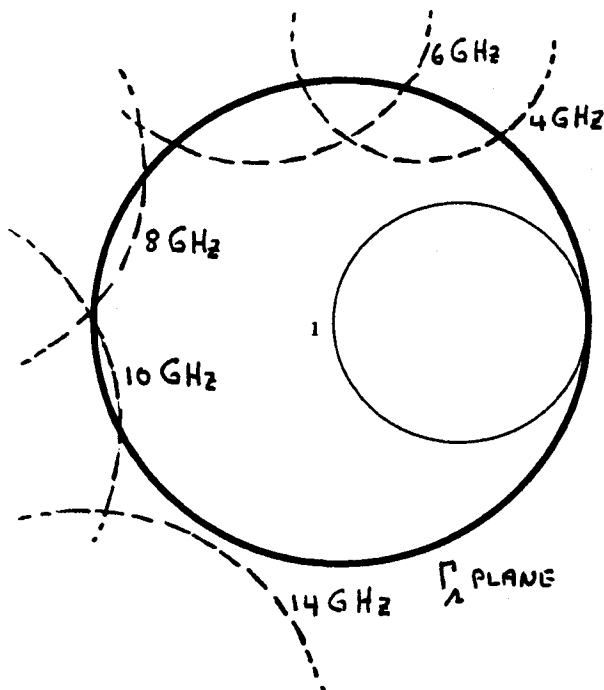

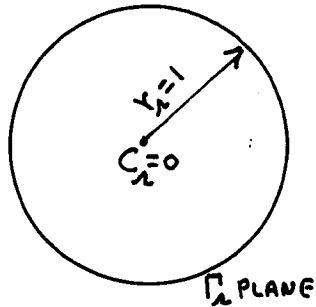3.9) (a) $K=1, \Delta=1$


INPUT
STABILITY
CIRCLE:

$$\begin{cases} \gamma_A = 1 \\ C_A = 0 \end{cases}$$




OUTPUT
STABILITY
CIRCLE:
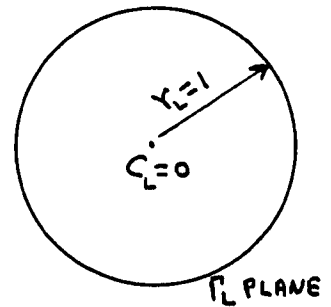
$$\begin{cases} \gamma_L = 1 \\ C_L = 0 \end{cases}$$




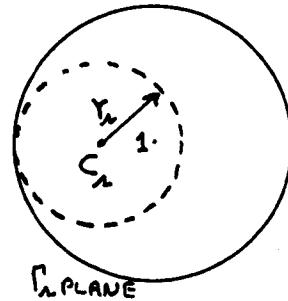(b) $K=1, \Delta=-2.414$

$$\begin{cases} \gamma_A = 0.55 \\ C_A = 0.45 \angle 180^\circ \end{cases}$$



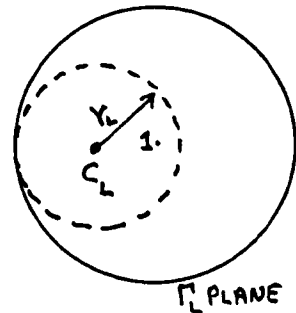
$$\begin{cases} \gamma_L = 0.55 \\ C_L = 0.45 \angle 180^\circ \end{cases}$$




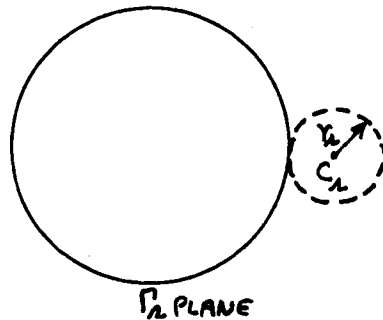(c) $K=1, \Delta=0.415$

$$\begin{cases} \gamma_A = 0.26 \\ C_A = 1.26 \end{cases}$$



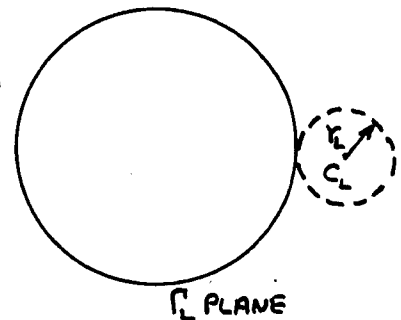
$$\begin{cases} \gamma_L = 0.26 \\ C_L = 1.26 \end{cases}$$




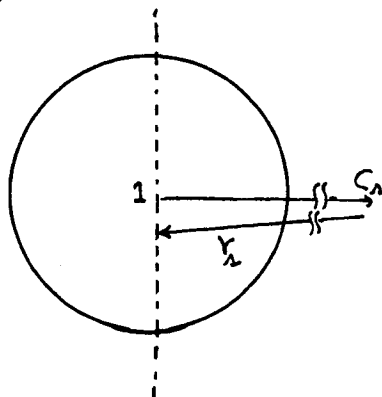(d) $K=0, \Delta=-1$

$$\begin{cases} \gamma_A = \infty \\ C_A = \infty \end{cases}$$


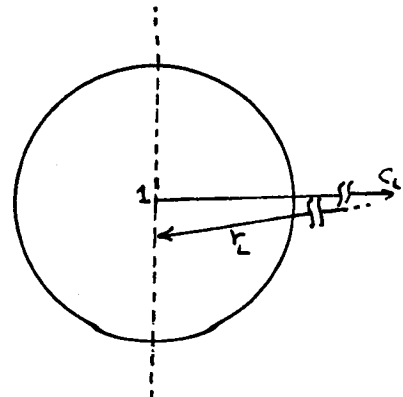
$$\begin{cases} \gamma_L = \infty \\ C_L = \infty \end{cases}$$



3.10) (a) From (3.3.7) AND (3.3.8) : $\lim_{S_{12} \rightarrow 0} \Delta = S_{11} S_{22}$. THEN,



$$\lim_{S_{12} \rightarrow 0} \gamma_L = 0$$

AND $\lim_{S_{12} \rightarrow 0} C_L = \frac{(S_{22} - S_{11} S_{22} S_{11})^*}{|S_{22}|^2 - |S_{11} S_{22}|^2} = \frac{S_{22}^* (1 - |S_{11}|^2)}{|S_{22}|^2 (1 - |S_{11}|^2)} = \frac{S_{22}^*}{|S_{22}|^2} = \frac{1}{S_{22}}$

SIMILARLY: $\lim_{S_{12} \rightarrow 0} \gamma_L = 0$ AND $\lim_{S_{12} \rightarrow 0} C_L = \frac{1}{S_{11}}$

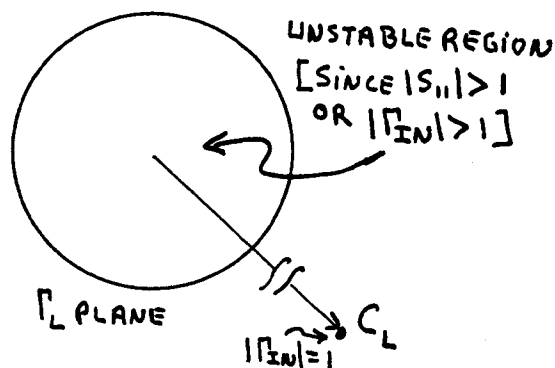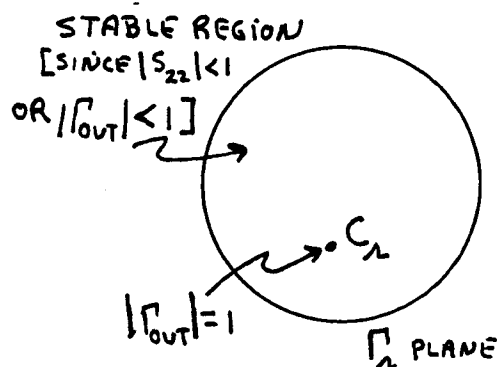(b) $\begin{cases} \gamma_L = 0 \\ C_L = \frac{1}{S_{11}} = 0.5 \angle -90^\circ \end{cases}$

$\begin{cases} \gamma_L = 0 \\ C_L = \frac{1}{S_{22}} = 10 \angle -45^\circ \end{cases}$



3.11) THE SOURCE STABILITY CIRCLE DOES NOT ENCLOSE THE CENTER OF THE SMITH CHART WHEN: $|C_L| > \gamma_L$. FROM (3.3.9) AND

(3.3.10) WE OBTAIN: $|S_{11} - \Delta S_{22}^*| > |S_{12} S_{21}|$

FROM PROBLEM 3.20: $|S_{11} - \Delta S_{22}^*|^2 = |S_{12} S_{21}|^2 + (1 - |S_{22}|^2)(|S_{11}|^2 - |\Delta|^2)$

HENCE: $|S_{12} S_{21}|^2 + (1 - |S_{22}|^2)(|S_{11}|^2 - |\Delta|^2) > |S_{12} S_{21}|^2$

OR $(1 - |S_{22}|^2)(|S_{11}|^2 - |\Delta|^2) > 0$ (1)

FROM (1): $\begin{cases} \text{If } |S_{22}| < 1 \text{ then } |\Delta| < |S_{11}| \\ \text{If } |S_{22}| > 1 \text{ then } |\Delta| > |S_{11}| \end{cases}$

SIMILARLY: $|C_L| > \gamma_L \Rightarrow |S_{22} - \Delta S_{11}^*| > |S_{12} S_{21}|$ OR
 $(1 - |S_{11}|^2)(|S_{22}|^2 - |\Delta|^2) > 0$ (2)

FROM (2): $\begin{cases} \text{If } |S_{11}| < 1 \text{ then } |\Delta| < |S_{22}| \\ \text{If } |S_{11}| > 1 \text{ then } |\Delta| > |S_{22}| \end{cases}$

3.12) THE ANSWER TO THIS PROBLEM FOLLOWS FROM THE RESULTS IN APPENDIX J. THAT IS, WITH $C_{ii}=0$ AND $\Gamma_{ii}=1$ WE OBTAIN:

$$C_{OUT} = \frac{S_{22} - \Delta S_{11}^*}{1 - |S_{11}|^2} \quad \text{AND} \quad \Gamma_{OUT} = \frac{|S_{12} S_{21}|}{1 - |S_{11}|^2}$$

ALSO, WITH $C_{00}=0$ AND $\Gamma_{00}=1$ WE OBTAIN:

$$C_{IN} = \frac{S_{11} - \Delta S_{22}^*}{1 - |S_{22}|^2} \quad \text{AND} \quad \Gamma_{IN} = \frac{|S_{12} S_{21}|}{1 - |S_{22}|^2}$$

3.13) (2) $\Delta = S_{11} S_{22} - S_{12} S_{21}$ AND $S_{11} S_{22} = \Delta + S_{12} S_{21}$

$$\therefore |\Delta| = |S_{11} S_{22} - S_{12} S_{21}| \quad \text{AND} \quad |S_{11} S_{22}| = |\Delta + S_{12} S_{21}|$$

$$\text{HENCE: } |\Delta| \leq |S_{11} S_{22}| + |S_{12} S_{21}| \quad (1) \quad |S_{11} S_{22}| \leq |\Delta| + |S_{12} S_{21}| \quad (2)$$

$$\text{FROM (3.3.13): } K > 1 \text{ OR } 1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2 > 2|S_{12} S_{21}| \quad (3)$$

$$(1) \text{ INTO (3): } 1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2 > 2|\Delta| - 2|S_{11} S_{22}| \quad (4)$$

$$(2) \text{ INTO (3): } 1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2 > 2|S_{11} S_{22}| - 2|\Delta| \quad (5)$$

$$\text{FROM (4): } (1 - |\Delta|)^2 > (|S_{11}| - |S_{22}|)^2 \quad (6)$$

$$\text{FROM (5): } (1 + |\Delta|)^2 > (|S_{11}| + |S_{22}|)^2 \quad (7)$$

$$\text{FROM (6) AND (7): } (1 - |\Delta|)^2 (1 + |\Delta|)^2 > (|S_{11}| - |S_{22}|)^2 (|S_{11}| + |S_{22}|)^2$$

$$(1 - |\Delta|^2)^2 > (|S_{11}|^2 - |S_{22}|^2)^2 \quad (8)$$

$$\text{SINCE: } B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \text{ AND } B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$\text{THEN: } B_1 B_2 = (1 - |\Delta|^2)^2 - (|S_{11}|^2 - |S_{22}|^2)^2 \quad (9), \quad B_1 + B_2 = 2(1 - |\Delta|^2) \quad (10)$$

$$\text{FROM (8) AND (9) WE HAVE: } B_1 B_2 > 0 \quad (11)$$

(b) THE RELATION $B_1 B_2 > 0$ SHOWS THAT IF $B_1 > 0$ THEN $B_2 > 0$. THEREFORE, THE CONDITIONS $K > 1$ AND $B_1 > 0$ ARE SIMILAR TO $K > 1$ AND $B_2 > 0$.

(c) IF $B_1 > 0$ THEN $B_2 > 0$. HENCE, FROM (10):

$$2(1 - |\Delta|^2) > 0$$

$$\text{OR } |\Delta| < 1$$

3.14) FOR THIS TRANSISTOR: $K = 0.532$, $\Delta = 0.617 \angle -85.4^\circ$

$$r_n = 1.96$$


$$C_n = 2.64 \angle 116.7^\circ$$

$$r_L = 0.576$$

$$C_L = 1.4 \angle 41.5^\circ$$


AT POINT A: $r = 0.25$
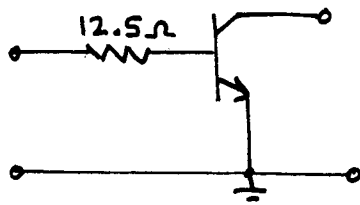
$$\therefore R = 0.25(50) = 12.5 \Omega$$




AT POINT B: $g = 1$
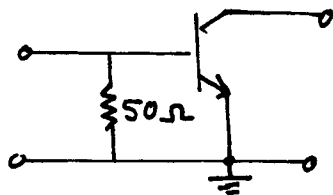
$$\therefore G = \frac{1}{50} = 20 \text{ mS (OR } 50 \Omega)$$




AT POINT C: $r = 1$

$$\therefore R = 1(50) = 50 \Omega$$

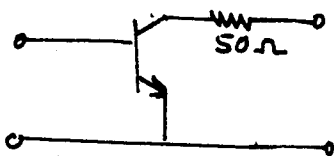

AT POINT D: $g = 0.12$
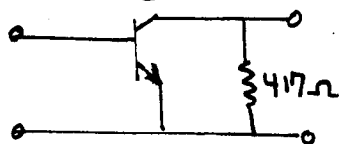
$$G = \frac{0.12}{50} = 2.4 \text{ mS (OR } 417 \Omega)$$





FOR THIS CIRCUIT IT FOLLOWS THAT: $S_{11} = 0.695 \angle -77.3^\circ$, $S_{12} = 0.03 \angle 42.5^\circ$,

$$S_{21} = 5.13 \angle 124.1^\circ \text{ AND } S_{22} = 0.665 \angle -25.8^\circ$$

HENCE, $K = 1.02$ AND $\Delta = 0.488 \angle -84.7^\circ$

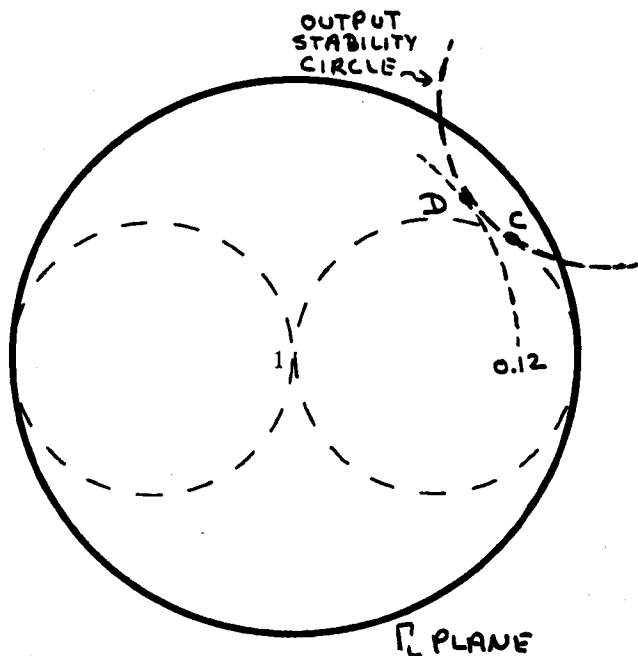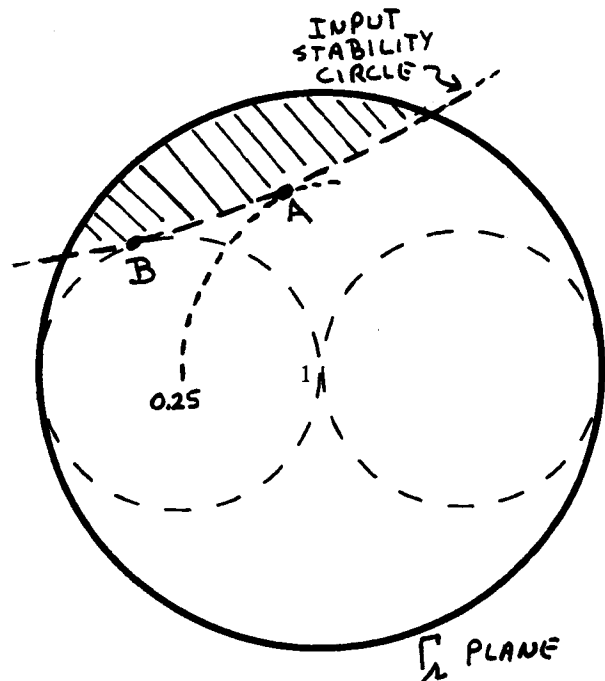AND THE CIRCUIT IS UNCONDITIONALLY STABLE.



3.15) THE MAXIMUM VALUE OF $G_i = \frac{1-|\Gamma_i|^2}{|1-S_{ii}\Gamma_i|^2}$ IS OBTAINED AS FOLLOWS:

LET $\Gamma_i = x + jy$ AND $S_{ii} = a + jb$, THEN

$$G_i = \frac{1-x^2-y^2}{(1-xa+yb)^2 + (xb+ya)^2} = \frac{1-x^2-y^2}{D}; D = (1-xa+yb)^2 + (xb+ya)^2$$

$$\begin{cases} \frac{\partial G_i}{\partial x} = \frac{-2x}{D} - \frac{(1-x^2-y^2)[-2a(1-xa+yb) + 2b(xb+ya)]}{D^2} = 0 \\ \frac{\partial G_i}{\partial y} = \frac{-2y}{D} - \frac{(1-x^2-y^2)[2b(1-xa+yb) + 2a(xb+ya)]}{D^2} = 0 \end{cases}$$

OR

$$\begin{cases} 2xD = -(1-x^2-y^2)[-2a(1-xa+yb) + 2b(xb+ya)] & (1) \\ 2yD = -(1-x^2-y^2)[2b(1-xa+yb) + 2a(xb+ya)] & (2) \end{cases}$$

DIVIDING (1) BY (2) GIVES:

$$\frac{x}{y} = \frac{-a(1-xa+yb) + b(xb+ya)}{b(1-xa+yb) + a(xb+ya)} = \frac{-a + xa^2 + xb^2}{b + yb^2 + ya^2}$$

OR

$$xb + yb^2x + ya^2x = -ay + xa^2y + xb^2y \Rightarrow x = -\frac{ay}{b} \quad (3)$$

(3) INTO (1): $-\frac{2ay}{b}(1 + \frac{a^2y}{b} + yb)^2 = -(1 - \frac{a^2y^2}{b^2} - y^2)(-2a(1 + \frac{a^2y}{b} + yb))$

OR

$$-\frac{y}{b}(1 + \frac{a^2y}{b} + yb) = 1 - \frac{a^2y^2}{b^2} - y^2 \Rightarrow y = -b \quad (4)$$

(4) INTO (3): $x = -\frac{a}{b}(-b)$ OR $x = a$ (5)

FROM (4) AND (5): $\Gamma_i = x + jy = a - jb$ OR $\Gamma_i = S_{ii}^*$.

3.16) (2) FOR $G_{TU, \max}$: $\Gamma_n = S_{11}^* = 0.706 \angle 160^\circ$ AND


$$\Gamma_L = S_{22}^* = 0.508 \angle 20^\circ$$


$$G_{n, \max} = \frac{1}{1-|S_{11}|^2} = \frac{1}{1-(0.706)^2} = 1.99 \text{ OR } 3 \text{ dB}$$

$$G_o = |S_{21}|^2 = (5.01)^2 = 25.1 \text{ OR } 14 \text{ dB}$$



$$G_{L, \max} = \frac{1}{1-|S_{22}|^2} = \frac{1}{1-(0.508)^2} = 1.35 \text{ OR } 1.3 \text{ dB}$$
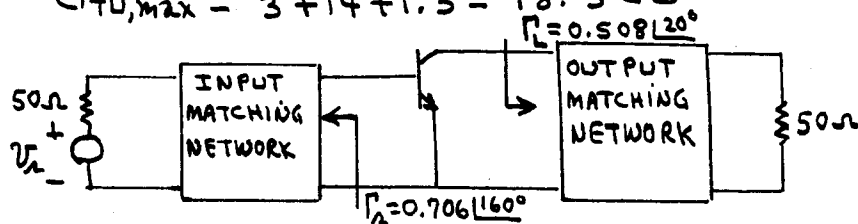
$$G_{TU, \max} = 3 + 14 + 1.3 = 18.3 \text{ dB}$$




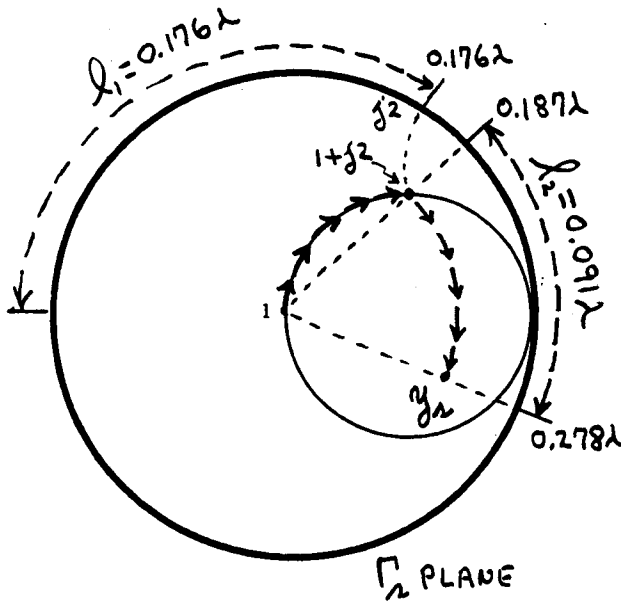

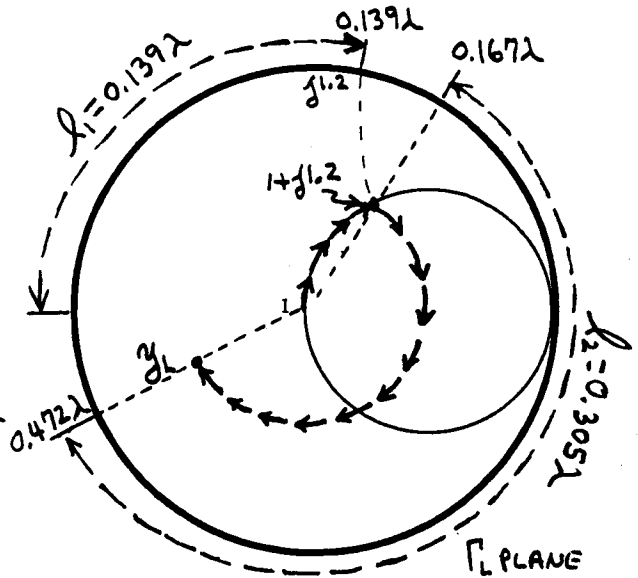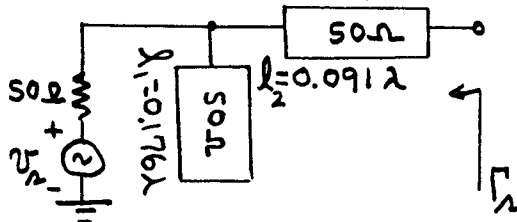
$$\Gamma_L = 0.706 \angle 160^\circ, \quad Y_L = \frac{1}{Z_L} = -2.9 - j2.8$$


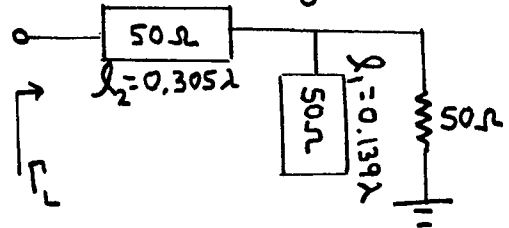
$$\Gamma_L = 0.508 \angle 20^\circ, \quad Y_L = \frac{1}{Z_L} = 0.335 - j0.157$$



(b)

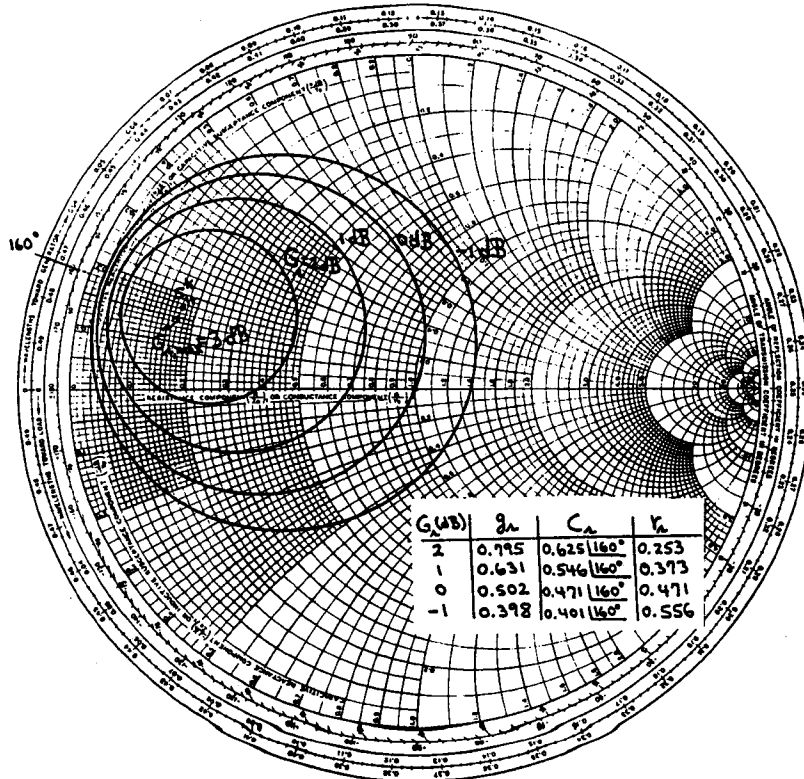

3.17) (a) THE INPUT RESISTANCE IS CALCULATED AS FOLLOWS:

$$\Gamma_{IN} = S_{11} = 2.3 \angle -135^\circ, \quad Z_{IN} = 50(-0.45 - j0.34) = -22.48 - j17.04 \Omega.$$

Z_{IN} CAN ALSO BE CALCULATED USING THE SMITH CHART.

PLOT $\frac{1}{S_{11}^*} = 0.435 \angle -135^\circ$ AND READ $Z_{IN} = 50(-0.45 - j0.34) = -22.5 - j17 \Omega$


FOR $G_n = 4 \text{ dB}$, $g_n = 2.512[1 - (2.3)^2] = -10.78$

FROM (3.4.11) AND (3.4.12): $C_n = 0.404 \angle 135^\circ$ AND $\Gamma_n = 0.24$

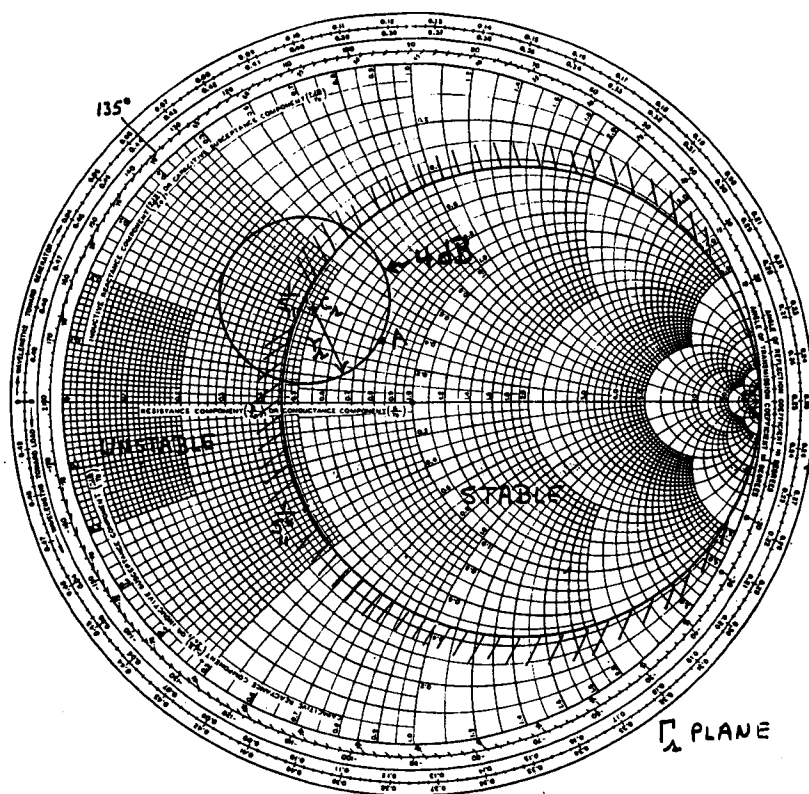
(b) AT POINT A, Γ_n HAS THE LARGEST REAL PART ON THE $G_n = 4 \text{ dB}$ CIRCLE. THAT IS,

$$\Gamma_n = 0.2 \angle 115^\circ$$

THE INPUT MATCHING CIRCUIT MUST TRANSFORM 50Ω TO $\Gamma_n = 0.2 \angle 115^\circ$.




(c) DESIGN FOR $\Gamma_n = 0.2 \angle 115^\circ$ AND $\Gamma_L = S_{22}^* = 0.8 \angle 66^\circ$. THEN,
 $G_n = 4 \text{ dB}$, $G_o = |S_{21}|^2 = 16$ (OR 12.04 dB), $G_{L, \max} = \frac{1}{1 - (0.8)^2} = 2.78$ (OR 4.4 dB)
 $\therefore G_{TW}(\text{dB}) = G_n + G_o + G_{L, \max} = 4 + 12.04 + 4.4 = 20.4 \text{ dB}$

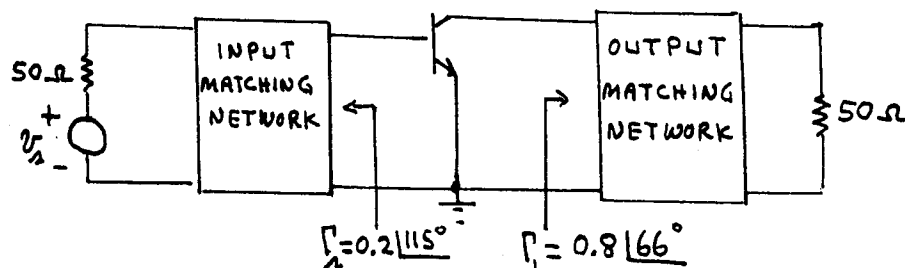

$$3.18)(a) G_{L, \max} = \frac{1}{1-(0.5)^2} = 1.33 \text{ OR } 1.25 \text{ dB}, G_{L, \max} = \frac{1}{1-(0.6)^2} = 1.563 \text{ OR } 1.94 \text{ dB}$$

$$G_0 = |S_{21}|^2 = 25 \text{ OR } 13.98 \text{ dB}, \therefore G_{T U, \max} = 1.25 + 13.98 + 1.94 = 17.2 \text{ dB}$$

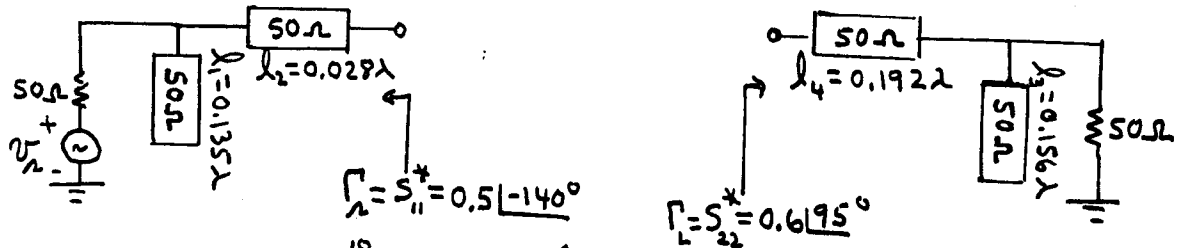(b) A MATCHING NETWORK DESIGN AT 900 MHz IS:




$$\text{AT } 900 \text{ MHz: } \lambda = \frac{3 \times 10^{10}}{9 \times 10^8} = 33.3 \text{ cm}, l_1 = 0.135\lambda = 4.496 \text{ cm}, \\ l_2 = 0.028\lambda = 0.932 \text{ cm}, l_3 = 0.156\lambda = 5.195 \text{ cm}, l_4 = 0.192\lambda = 6.394 \text{ cm}$$

$$(c) g_L = \frac{G_L}{G_{L, \max}} = \frac{1.259}{1.563} = 0.805$$

FROM (3.4.11) AND (3.4.12):

$$C_L = 0.519 \angle 95^\circ$$

$$r_L = 0.304$$

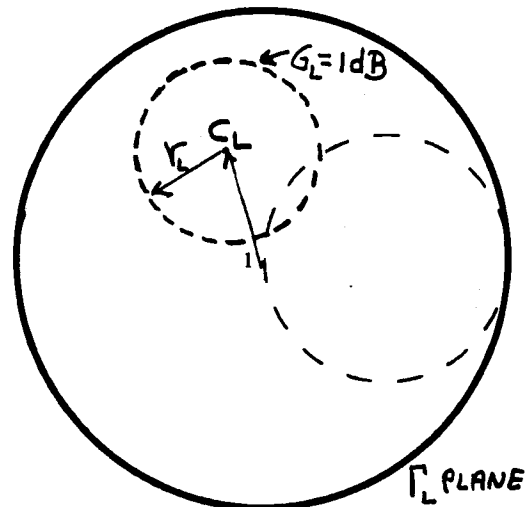


(d) LET $\lambda' = \frac{c}{f'}$ WHERE $f' = 1 \text{ GHz}$,

AND $\lambda = \frac{c}{f}$ WHERE $f = 900 \text{ MHz}$.

$$\therefore \frac{\lambda}{\lambda'} = \frac{f'}{f} \text{ OR } \lambda = \frac{f'}{f} \lambda' = \frac{10^9}{9 \times 10^8} \lambda' = 1.11\lambda'$$
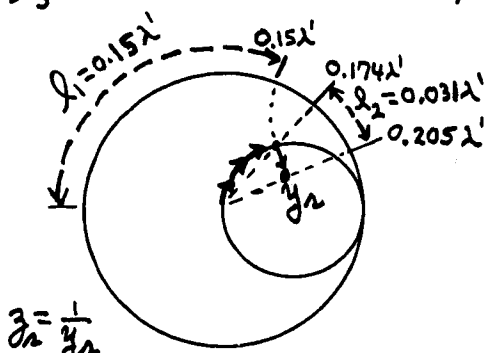
$$l_1 = 0.135\lambda = 0.135(1.11\lambda') = 0.15\lambda', l_2 = 0.028(1.11\lambda') = 0.031\lambda', \\ l_3 = 0.156(1.11\lambda') = 0.173\lambda', l_4 = 0.192(1.11\lambda') = 0.213\lambda'$$



$$z_n = \frac{1}{y_n}$$

$$y_n = 1.79 + j1.58, \Gamma_n = 0.55 \angle -146^\circ$$

$$\therefore G_{T U} = \frac{1 - (0.55)^2}{|1 - 0.48 \angle 137^\circ (0.55 \angle -146^\circ)|^2} (4.6)^2$$

$$z_L = \frac{1}{y_L}$$

$$y_L = 0.28 - j0.72, \Gamma_L = 0.693 \angle 74.4^\circ$$

$$\frac{1 - (0.693)^2}{|1 - 0.57 \angle -99^\circ (0.693 \angle 74.4^\circ)|^2} = 31.97 \text{ OR } 15.05 \text{ dB}$$

$$3.19) (a) \Gamma_{M\Lambda}^* = S_{11} + \frac{S_{12} S_{21} \Gamma_{ML}}{1 - S_{22} \Gamma_{ML}} = \frac{S_{11} - \Delta \Gamma_{ML}}{1 - S_{22} \Gamma_{ML}} \quad (1)$$

$$\Gamma_{ML}^* = S_{22} + \frac{S_{12} S_{21} \Gamma_{M\Lambda}}{1 - S_{11} \Gamma_{M\Lambda}} = \frac{S_{22} - \Delta \Gamma_{M\Lambda}}{1 - S_{11} \Gamma_{M\Lambda}} \quad (2)$$

SOLVING (2) FOR $\Gamma_{M\Lambda}$ GIVES: $\Gamma_{M\Lambda} = \frac{\Gamma_{ML}^* - S_{22}}{S_{11} \Gamma_{ML}^* - \Delta} \quad (3)$

EQUATING (1) AND (3): $\frac{S_{11} - \Delta \Gamma_{ML}}{1 - S_{22} \Gamma_{ML}} = \frac{\Gamma_{ML} - S_{22}}{S_{11} \Gamma_{ML}^* - \Delta}$

$$|S_{11}|^2 \Gamma_{ML} - S_{11} \Delta^* - \Delta S_{11}^* \Gamma_{ML}^2 + |\Delta|^2 \Gamma_{ML} = \Gamma_{ML} - S_{22}^* - S_{22} \Gamma_{ML}^2 + |S_{22}|^2 \Gamma_{ML}$$

$$\Gamma_{ML}^2 (S_{22} - \Delta S_{11}^*) - \Gamma_{ML} (1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2) + S_{22}^* - S_{11} \Delta^* = 0$$

OR $\Gamma_{ML}^2 - \Gamma_{ML} \frac{B_2}{C_2} + \frac{C_2^*}{C_2} = 0$ WHERE $\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta S_{11}^* \end{cases}$

THE SOLUTIONS ARE:

$$\Gamma_{ML} = \frac{\frac{B_2}{C_2} \pm \sqrt{\left(\frac{B_2}{C_2}\right)^2 - 4 \frac{C_2^*}{C_2}}}{2} = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$$

SIMILARLY, SOLVING (1) FOR $\Gamma_{M\Lambda}$ AND EQUATING THE RESULT TO (2) GIVES: $\Gamma_{M\Lambda} = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$ WHERE $\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta S_{22}^* \end{cases}$

(b) FOR $S_{12} \rightarrow 0$ IT FOLLOWS FROM (3.6.3) AND (3.6.4) THAT

$$\Gamma_{M\Lambda} = \left(S_{11} + \frac{S_{12} S_{21} \Gamma_{ML}}{1 - S_{22} \Gamma_{ML}} \right)^* \approx S_{11}^*$$

AND

$$\Gamma_{ML} = \left(S_{22} + \frac{S_{12} S_{21} \Gamma_{M\Lambda}}{1 - S_{11} \Gamma_{M\Lambda}} \right)^* \approx S_{22}^*$$

$$3.20) (a) |C_1|^2 = |S_{11} - \Delta S_{22}^*|^2 = (S_{11} - \Delta S_{22}^*)(S_{11}^* - \Delta^* S_{22})$$

$$= |S_{11}|^2 - S_{11} S_{22}^* \Delta^* - S_{11}^* S_{22} \Delta + |\Delta S_{22}|^2$$

$$= |S_{11}|^2 - |S_{11} S_{22}|^2 + S_{11} S_{22}^* S_{12}^* S_{21}^* - |S_{11} S_{22}|^2 + S_{11}^* S_{22}^* S_{12} S_{21} + |\Delta S_{22}|^2 \quad (1)$$

$$\text{SINCE } |\Delta|^2 = (S_{11} S_{22} - S_{12} S_{21})(S_{11}^* S_{22}^* - S_{12}^* S_{21}^*)$$

$$= |S_{11} S_{22}|^2 - S_{11} S_{22}^* S_{12}^* S_{21}^* - S_{11}^* S_{22}^* S_{12} S_{21} + |S_{12} S_{21}|^2$$

$$\text{THEU: } |S_{11} S_{22}|^2 - S_{11} S_{22}^* S_{12}^* S_{21}^* - S_{11}^* S_{22}^* S_{12} S_{21} = |\Delta|^2 - |S_{12} S_{21}|^2 \quad (2)$$

$$(2) \text{ INTO } (1): |C_1|^2 = |S_{11}|^2 - |\Delta|^2 + |S_{12} S_{21}|^2 - |S_{11} S_{22}|^2 + |\Delta|^2 |S_{22}|^2$$

$$= |S_{12} S_{21}|^2 + |S_{11}|^2 (1 - |S_{22}|^2) - |\Delta|^2 (1 - |S_{22}|^2)$$

$$= |S_{12} S_{21}|^2 + (1 - |S_{22}|^2) (|S_{11}|^2 - |\Delta|^2)$$

$$\text{SIMILARLY: } |C_2|^2 = |S_{12} S_{21}|^2 + (1 - |S_{11}|^2) (|S_{22}|^2 - |\Delta|^2)$$


3.21) $K = 1.03$ AND $\Delta = 0.324 \angle -64.8^\circ \therefore$ UNCONDITIONALLY STABLE

FROM (3.6.5): $\Gamma_{M_A} = 0.73 \angle 135^\circ$


FROM (3.6.6): $\Gamma_{M_L} = 0.95 \angle 33.8^\circ$

FROM (3.6.10): $G_{T, \max} = 19.08$ OR 12.8 dB

A DESIGN USING LUMPED ELEMENTS IS:

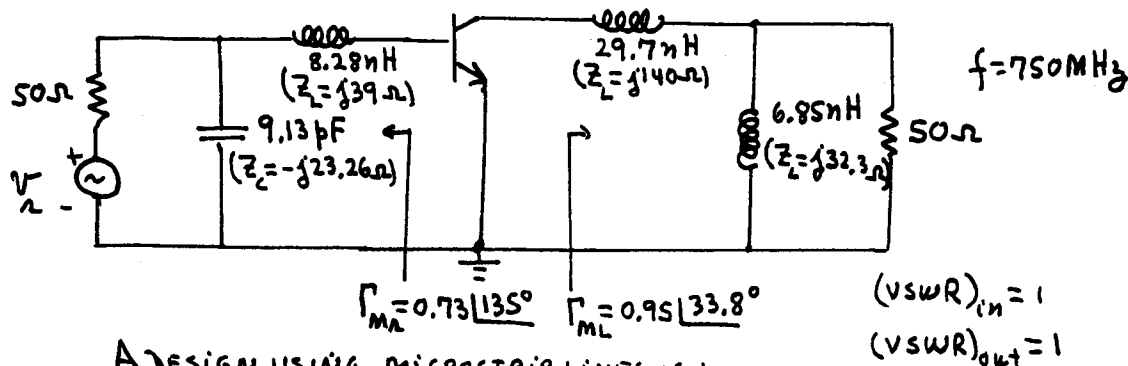

A DESIGN USING MICROSTRIP LINES IS:

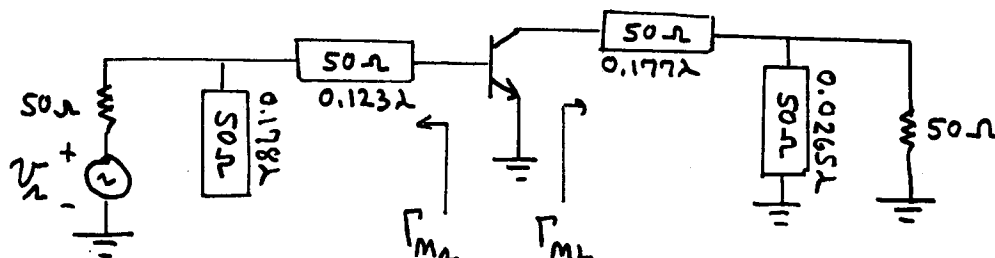

3.22) (a) THE ADMITTANCE OF THE 70Ω STUB IS: $y_{oc} = j$ OR $Y_{oc} = \frac{j}{70}$

THE ADMITTANCE OF THE TWO PARALLEL STUBS IS:

$$Y_{oc, \text{TOTAL}} = \frac{1}{70} + \frac{1}{70} = \frac{2j}{70} = \frac{j}{35} = j29 \text{ mS}$$

THE ADMITTANCE OF THE 50Ω LOAD PLUS $Y_{oc, \text{TOTAL}}$ IS (CALLED Y_x):


$$Y_x = \frac{1}{50} + \frac{j}{35} = 20 + j29 \text{ mS}$$

NORMALIZING Y_x WITH $Y_{o1} = \frac{1}{Z_{o1}} = \frac{1}{40}$ ($y_x = 0.8 + j1.16$)

AND ROTATING IN THE SMITH CHART

A DISTANCE $l = 0.25\lambda$ GIVES
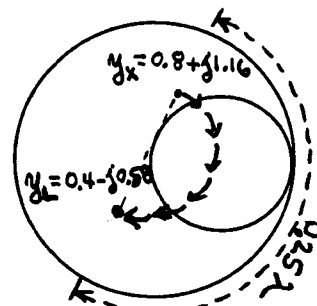
$$Z_L = \frac{1}{y_L} = 0.8 + j1.16 \therefore \Gamma_L = \Gamma_{M_L} = 0.55 \angle 67^\circ$$



(b) FROM FIG. 2.5.4 (WITH $\epsilon_r = 10$ AND $h = 30 \text{ mils}$):

$W = 28.5 \text{ mils}$ AND $\epsilon_{\text{eff}} = 6.68$, $\lambda_0 = \frac{3 \times 10^{10}}{2 \times 10^9} = 15 \text{ cm}$.

$$\therefore l_1 = 0.25\lambda = \frac{0.25\lambda_0}{\sqrt{\epsilon_{\text{eff}}}} = \frac{0.25(15)}{\sqrt{6.68}} = 1.45 \text{ cm}.$$

3.23) THE OUTPUT IS MATCHED WITH $\Gamma_{ML} = \Gamma_{OUT}^* = 0.718 \angle 103.9^\circ$.

THEREFORE, $\Gamma_x = 0$ (OR $Z_x = 50 \Omega$) AND $(VSWR)_{out} = 1$.


NOTE: THIS IS THE OUTPUT MATCHING NETWORK IN FIG. 3.6.4 (SEE FIG. 3.6.3b). IT IS SIMPLE TO VERIFY THAT $\Gamma_x = 0$ USING FIG. 3.6.3b. THAT IS, PLOT $y_{out} = y_{ML}^* = 0.414 + j1.19$ IN THE SMITH CHART AND FIND y_x , WHICH WILL BE $y_x = 1$ ($Z_x = 50 \Omega$ OR $\Gamma_x = 0$).

3.24) (a) SINCE $K = 1.19$ AND $\Delta = 0.399 \angle 126.5^\circ$ (I.E., $|\Delta| < 1$) THE BJT IS UNCONDITIONALLY STABLE AT 3.5 GHz. THEREFORE, IT CAN BE DESIGNED FOR A SIMULTANEOUS CONJUGATE MATCH.

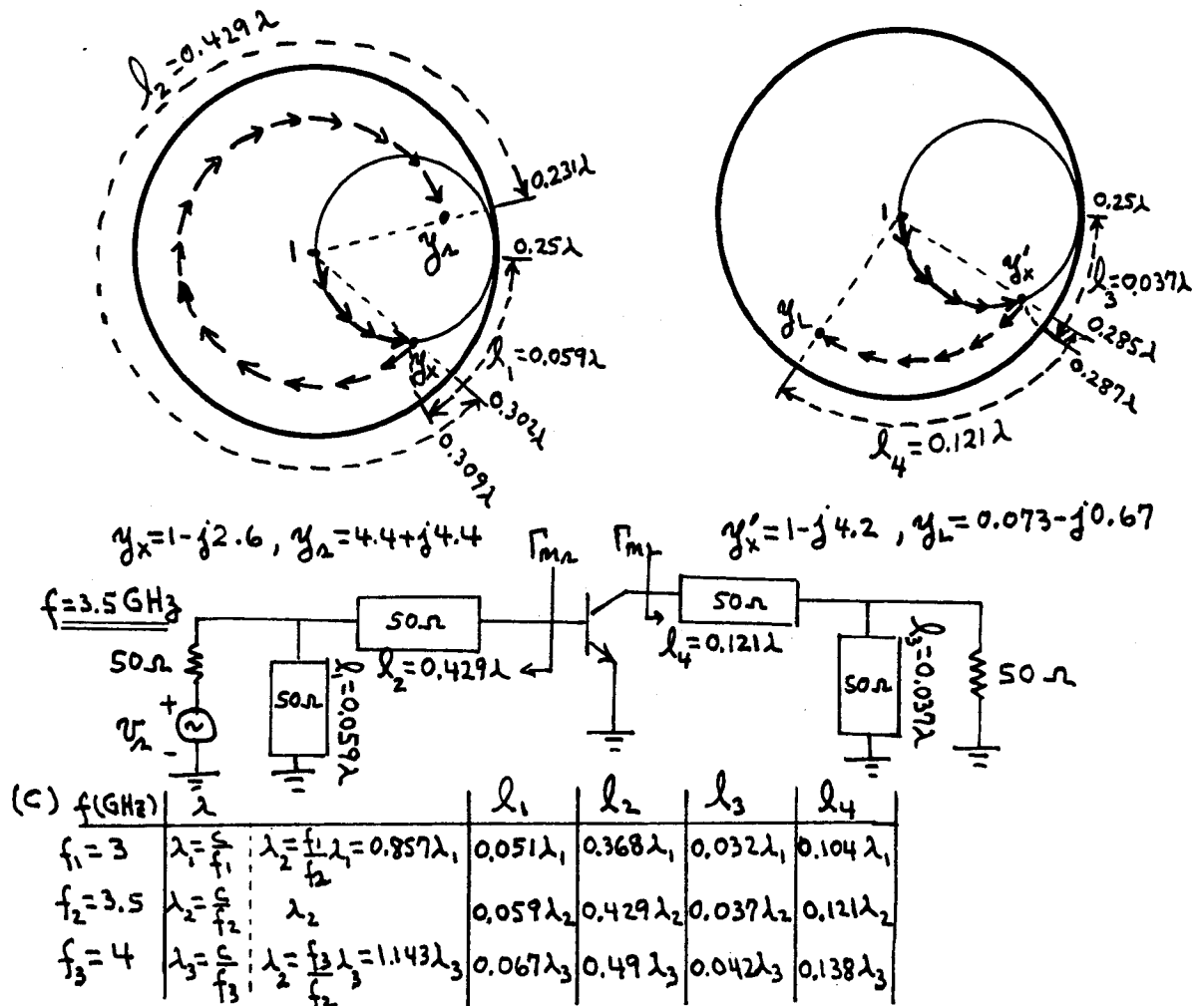(b) FROM (3.6.5) AND (3.6.6): $\Gamma_{ML} = 0.798 \angle -166.9^\circ$, $\Gamma_M = 0.904 \angle 68^\circ$

FROM (3.6.10): $G_{T,max} = 23.06$ OR 13.63 dB.

A DESIGN FOR THE AMPLIFIER AT 3.5 GHz IS:



USING THE SMITH CHART IT IS SIMPLE TO FIND THE VALUES OF Γ_L AND Γ_L AT f_1 AND f_3 . THE VALUES OF G_T ARE CALCULATED USING (3.2.1). THE RESULTS ARE:

$f(\text{GHz})$	Γ_L	Γ_L	G_T
3	$0.833 \angle -118.5^\circ$	$0.934 \angle 82.2^\circ$	0.944 OR -0.25 dB
3.5	$0.798 \angle -166.9^\circ$	$0.904 \angle 68^\circ$	23.06 OR 13.63 dB
4	$0.749 \angle 145.6^\circ$	$0.878 \angle 51.5^\circ$	2.257 OR 3.54 dB

3.25) (a) THE TRANSISTOR IS UNCONDITIONALLY STABLE ($K=1.033$, $\Delta=0.324 \angle -64.8^\circ$)

WITH $g_p = \frac{G_p}{|S_{21}|^2} = \frac{10}{(1.92)^2} = 2.713$, WE OBTAIN FROM (3.7.4) AND (3.7.5):

$$C_p = 0.781 \angle 33.85^\circ \quad \text{AND} \quad \gamma_p = 0.214$$

THE $G_p=10\text{dB}$ GAIN CIRCLE IS DRAWN IN THE SMITH CHART. SELECTING Γ_L AT POINT "A": $\Gamma_L = 0.567 \angle 33.85^\circ$, GIVES

$$\Gamma_L = \Gamma_{IN}^* = 0.276 \angle 93.33^\circ$$

AND

$$\Gamma_{OUT} = 0.86 \angle -33.85^\circ$$


FROM (2.8.3): $|\Gamma_a| = 0$ (SINCE $\Gamma_L = \Gamma_{IN}^*$)

$$\text{HENCE: } (VSWR)_{in} = 1$$

FROM (2.8.6): $|\Gamma_b| = 0.572$

$$\text{HENCE: } (VSWR)_{out} = \frac{1+0.572}{1-0.572} = 3.67$$

A DESIGN IS:

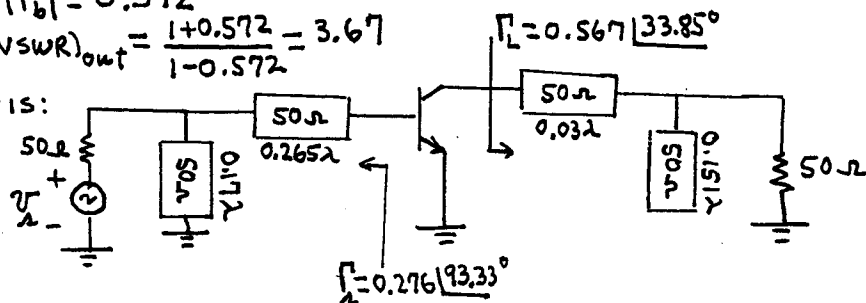

(b) $G_{p,max} = G_{T,max} = 19.08$ OR 12.8 dB

THE $G_{p,max}$ GAIN CIRCLE (i.e., a point) OCCURS AT:

$$g_{p,max} = \frac{G_{p,max}}{|S_{21}|^2} = \frac{19.08}{(1.92)^2} = 5.176, \quad C_{p,max} = 0.95 \angle 33.8^\circ, \quad \gamma_{p,max} = 0.$$

OBSERVE (SEE PROBLEM 3.21) THAT: $\Gamma_{ML} = C_{p,max} = 0.95 \angle 33.8^\circ$

AND $\Gamma_L = \Gamma_{IN}^* = 0.73 \angle 135^\circ$ IS IDENTICAL TO Γ_{ML} .

3.26) FOR THIS TRANSISTOR: $K=1.053$ AND $\Delta=0.576 \angle -85.4^\circ$.
THEREFORE, IT IS UNCONDITIONALLY STABLE.

$$G_{p,\max} = G_{T,\max} = 77.12 \text{ OR } 18.87 \text{ dB}$$


$$G_p = 10 \text{ dB CIRCLE: } g_p = 0.977, C_p = 0.306 \angle 39.45^\circ, \gamma_p = 0.693$$

THE $G_p = 10 \text{ dB}$ CONSTANT-GAIN CIRCLE
IS SHOWN IN THE SMITH CHART. THE Γ_L
SELECTED IS SHOWN AS "A": $\Gamma_L = 0.85 \angle 89^\circ$.

$$\text{THEN: } \Gamma_L = \Gamma_{IN}^* = 0.793 \angle 64.2^\circ, \Gamma_{OUT} = 0.798 \angle 42.3^\circ$$

$$|\Gamma_L| = 0, (VSWR)_{in} = 1$$

$$|\Gamma_L| = 0.9, (VSWR)_{out} = 18.9$$

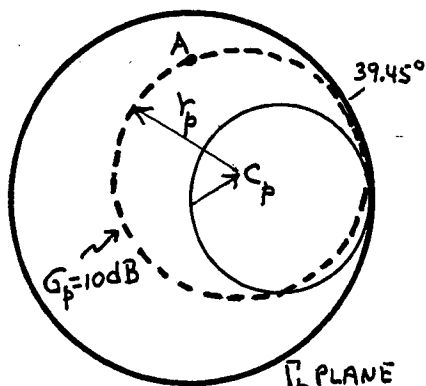

3.27) (a) $K=0.53$, $\Delta=0.524 \angle -142.9^\circ$; IT IS POTENTIALLY UNSTABLE.

OUTPUT STABILITY CIRCLE [(3.3.7) AND (3.3.8)]:

$$C_L = 1.47 \angle 76.6^\circ \text{ AND } \gamma_L = 0.668$$

$$G_p = 10 \text{ dB CONSTANT-GAIN CIRCLE [(3.7.4) AND (3.7.5)]: } g_p = \frac{10}{(2.43)^2} = 1.694,$$

$$C_p = 0.41 \angle 76.6^\circ \text{ AND } \gamma_p = 0.641$$

(b) THE $G_p = 10 \text{ dB}$ GAIN CIRCLE IS DRAWN ON THE SMITH CHART. THREE
VALUES OF Γ_L ARE DENOTED BY "a", "b", AND "c". THEN,

	Γ_L	$\Gamma_L = \Gamma_{IN}^*$	Γ_{OUT}	$ \Gamma_L $	$(VSWR)_{in}$	$(VSWR)_{out}$
"a"	$0.59 \angle 0^\circ$	$0.687 \angle 106.11^\circ$	$0.84 \angle -70.73^\circ$	0.889	1	17
"b"	$0.24 \angle -90^\circ$	$0.757 \angle 100.35^\circ$	$0.83 \angle -76.22^\circ$	0.891	1	17.3
"c"	$0.67 \angle 145^\circ$	$0.851 \angle 97.7^\circ$	$0.84 \angle -83.74^\circ$	0.889	1	17

THE 3 VALUES OF Γ_L ARE IN THE STABLE REGION, SINCE $C_L = 1.3 \angle 115.7^\circ$ AND $\gamma_L = 0.46$.

$$(c) \text{ FOR } G_p = 15 \text{ dB: } g_p = \frac{10^{1.5}}{(2.43)^2} = 5.355, C_p = 0.81 \angle 76.6^\circ, \gamma_p = 0.402$$

$$\text{FOR } G_p = 20 \text{ dB: } g_p = \frac{10^2}{(2.43)^2} = 16.94, C_p = 1.17 \angle 76.6^\circ, \gamma_p = 0.457$$

$$\text{FOR } G_p = 40 \text{ dB: } g_p = \frac{10^4}{(2.43)^2} = 1,694, C_p = 1.46 \angle 76.6^\circ, \gamma_p = 0.665$$

THE $G_p = 15 \text{ dB}$, 20 dB , AND 40 dB GAIN CIRCLES ARE ALSO DRAWN
ON THE SMITH CHART. THE $G_p = 40 \text{ dB}$ CIRCLE ALMOST COINCIDES WITH
THE OUTPUT STABILITY CIRCLE.

3.28) OUTPUT STABILITY CIRCLE: $|\Gamma_L - C_L|^2 = \gamma_L^2$

OR $|\Gamma_L|^2 - \Gamma_L C_L^* - \Gamma_L^* C_L + |C_L|^2 = \gamma_L^2$ (1)

(1) INTERSECTS THE SMITH CHART WHEN $|\Gamma_L| = 1$; THEN

$$1 - \Gamma_L C_L^* - \Gamma_L^* C_L + |C_L|^2 = \gamma_L^2$$

LET $\Gamma_L = U_L + jV_L$ AND $C_L = \text{Re}[C_L] + j\text{Im}[C_L]$:

$$-(U_L + jV_L)(\text{Re}[C_L] - j\text{Im}[C_L]) - (U_L - jV_L)(\text{Re}[C_L] + j\text{Im}[C_L]) = \gamma_L^2 - |C_L|^2 - 1$$

$$2U_L \text{Re}[C_L] + 2V_L \text{Im}[C_L] = 1 + |C_L|^2 - \gamma_L^2$$

OR $V_L = -\frac{\text{Re}[C_L]}{\text{Im}[C_L]} U_L + \frac{1 + |C_L|^2 - \gamma_L^2}{2 \text{Im}[C_L]}$ (2)

(2) IS THE EQUATION OF A STRAIGHT LINE WITH SLOPE $m_L = -\frac{\text{Re}[C_L]}{\text{Im}[C_L]}$ AND INTERCEPT $b_L = \frac{1 + |C_L|^2 - \gamma_L^2}{2 \text{Im}[C_L]}$. THIS LINE INTERSECTS THE SMITH CHART

(I.E., $|\Gamma_L| = 1$) AT TWO POINTS.

SIMILARLY, THE POWER GAIN CIRCLE INTERSECTS $|\Gamma_L| = 1$ AT TWO POINTS DETERMINED BY: (LET $C_p = \text{Re}[C_p] + j\text{Im}[C_p]$)

$$V_L = -\frac{\text{Re}[C_p]}{\text{Im}[C_p]} U_L + \frac{1 + |C_p|^2 - \gamma_p^2}{2 \text{Im}[C_p]} = -m_p U_L + b_p$$

THE POINTS OF INTERSECTION DETERMINED BY (2) AND (3) ARE EQUAL IF $m_L = m_p$ AND $b_L = b_p$.

$$m_L = -\frac{\text{Re}[C_L]}{\text{Im}[C_L]} = -\frac{\text{Re}[S_{22}^* - \Delta^* S_{11}]}{\text{Im}[S_{22}^* - \Delta^* S_{11}]}$$

$$m_p = -\frac{\text{Re}[C_p]}{\text{Im}[C_p]} = -\frac{\text{Re}[C_2^*]}{\text{Im}[C_2^*]} = -\frac{\text{Re}[S_{22}^* - \Delta^* S_{11}]}{\text{Im}[S_{22}^* - \Delta^* S_{11}]}$$

$$\therefore m_L = m_p$$



IT ALSO FOLLOWS THAT $b_L = b_p$.

3.29) (a) $K = 1.032$, $\Delta = 1.65 \angle 78.1^\circ$ $\therefore$ POTENTIALLY UNSTABLE

FROM (3.3.7) TO (3.3.10):

$$\text{INPUT STAB. CIRCLE} \begin{cases} C_1 = 0.285 \angle -161.1^\circ \\ r_1 = 0.65 \end{cases}$$
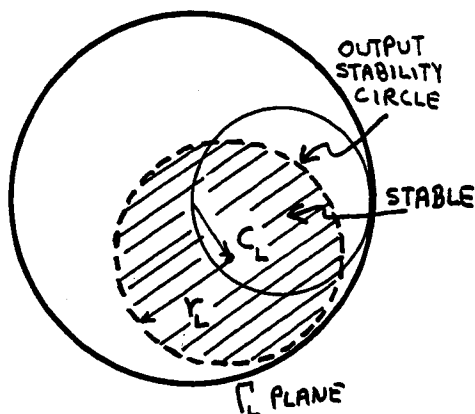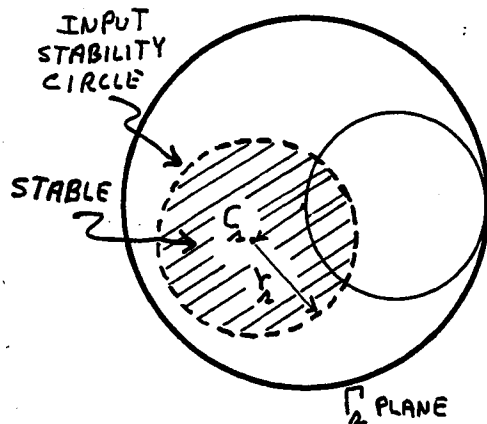
$$\text{OUTPUT STAB. CIRCLE} \begin{cases} C_L = 0.315 \angle -61.5^\circ \\ r_L = 0.627 \end{cases}$$



(b) FROM (3.2.3) WITH $\Gamma_L = 0$: (AND $\Gamma_{IN} = S_{11}$ WHEN $\Gamma_L = 0$)

$$G_p = \frac{|S_{21}|^2}{1 - |S_{11}|^2} = \frac{4^2}{1 - (0.5)^2} = 21.33 \text{ OR } 13.3 \text{ dB}$$

(c) G_p CAN BE INFINITE, BECAUSE IT IS POTENTIALLY UNSTABLE.
AS Γ_L APPROACHES THE STABILITY CIRCLE, $G_p \rightarrow \infty$.

3.30) FROM EXAMPLE 3.8.1: $G_{A, \max} = 9.66 \text{ dB}$, $G_A = 9.66 - 2 = 7.66 \text{ dB}$.

FROM (3.7.15) AND (3.7.16), FOR THE $G_A = 7.66 \text{ dB}$ GAIN CIRCLE:

$$g_a = \frac{10^{0.766}}{(2.3)^2} = 1.103, \quad C_a = 0.503 \angle -40.45^\circ, \quad r_a = 0.436$$

THE VALUES OF Γ_L ON THE 7.6 dB CIRCLE ARE GIVEN BY:

$$\Gamma_L = C_a + r_a e^{j\theta_1} = 0.503 \angle -40.45^\circ + 0.436 e^{j\theta_1}$$

LETTING $\theta_1 = 0, \frac{\pi}{2}, \pi$, AND $\frac{3\pi}{2}$ WE OBTAIN THE VALUES OF Γ_L SHOWN IN THE TABLE. THE ASSOCIATED VALUES OF Γ_{OUT} ARE ALSO SHOWN.


FOR $(VSWR)_{out} = 1.5$ (OR $|\Gamma_b| = 0.2$), USING (3.8.7) AND (3.8.8), THE CENTER AND RADIUS OF THE $(VSWR)_{out} = 1.5$ CIRCLE ARE CALCULATED.

THE VALUES OF Γ_L ON THE $(VSWR)_{out} = 1.5$ CIRCLE ARE GIVEN BY:

$\Gamma_L = C_v + r_v e^{j\theta_2}$. LETTING $\theta_2 = 0, \frac{\pi}{2}, \pi$, AND $\frac{3\pi}{2}$, FOUR VALUES OF Γ_L ON THE $(VSWR)_{out} = 1.5$ CIRCLE ARE CALCULATED, AS SHOWN IN THE TABLE. THE ASSOCIATED VALUES OF Γ_{IN} , $|\Gamma_a|$, AND $(VSWR)_{in}$ ARE ALSO SHOWN.

Γ_L	Γ_{OUT}	(VSWR) _{out} CIRCLE	Γ_L	Γ_{IN}	$ \Gamma_a $	(VSWR) _{in}
($\theta_1 = 0^\circ$) 0.881 $\angle -21.73^\circ$	0.451 $\angle 176.74^\circ$	$C_V = 0.437 \angle -176.74^\circ$ $\Gamma_V = 0.161$	0.276 $\angle -174.8^\circ$ ($\theta_2 = 0$) 0.457 $\angle 162.7^\circ$ ($\theta_2 = \frac{\pi}{2}$) 0.598 $\angle -177.6^\circ$ ($\theta_2 = \pi$) 0.474 $\angle -156.9^\circ$ ($\theta_2 = \frac{3\pi}{2}$)	0.683 $\angle 33.8^\circ$ 0.712 $\angle 28.8^\circ$ 0.771 $\angle 30.9^\circ$ 0.748 $\angle 35.7^\circ$	0.596 0.507 0.495 0.604	3.95 3.05 2.96 4.05
($\theta_1 = \pi/2$) 0.398 $\angle 15.99^\circ$	0.005 $\angle 95.36^\circ$	$C_V = 0.005 \angle -95.36^\circ$ $\Gamma_V = 0.2$	0.2 $\angle -1.4^\circ$ ($\theta_2 = 0$) 0.195 $\angle 90.1^\circ$ ($\theta_2 = \frac{\pi}{2}$) 0.2 $\angle -178.6^\circ$ ($\theta_2 = \pi$) 0.2 $\angle -90.1^\circ$ ($\theta_2 = \frac{3\pi}{2}$)	0.539 $\angle 38.5^\circ$ 0.582 $\angle 30.3^\circ$ 0.659 $\angle 34^\circ$ 0.628 $\angle 41.5^\circ$	0.501 0.491 0.591 0.598	3.00 2.93 3.89 3.98
($\theta_1 = \pi$) 0.331 $\angle -99.26^\circ$	0.249 $\angle 62.12^\circ$	$C_V = 0.241 \angle -62.12^\circ$ $\Gamma_V = 0.188$	0.368 $\angle -35.2^\circ$ ($\theta_2 = 0$) 0.115 $\angle -12.1^\circ$ ($\theta_2 = \frac{\pi}{2}$) 0.225 $\angle -109.6^\circ$ ($\theta_2 = \pi$) 0.416 $\angle -74.3^\circ$ ($\theta_2 = \frac{3\pi}{2}$)	0.539 $\angle 47^\circ$ 0.569 $\angle 38^\circ$ 0.652 $\angle 40.8^\circ$ 0.633 $\angle 48.8^\circ$	0.473 0.543 0.613 0.56	2.79 3.38 4.17 3.54
($\theta_1 = 3\pi/2$) 0.853 $\angle -63.34^\circ$	0.547 $\angle 94.15^\circ$	$C_V = 0.531 \angle -94.15^\circ$ $\Gamma_V = 0.142$	0.54 $\angle -78.9^\circ$ ($\theta_2 = 0$) 0.39 $\angle -95.6^\circ$ ($\theta_2 = \frac{\pi}{2}$) 0.559 $\angle -108.8^\circ$ ($\theta_2 = \pi$) 0.673 $\angle -93.3^\circ$ ($\theta_2 = \frac{3\pi}{2}$)	0.666 $\angle 51.8^\circ$ 0.673 $\angle 45.7^\circ$ 0.742 $\angle 46.3^\circ$ 0.74 $\angle 51.9^\circ$	0.526 0.606 0.597 0.485	3.22 4.07 3.97 2.88

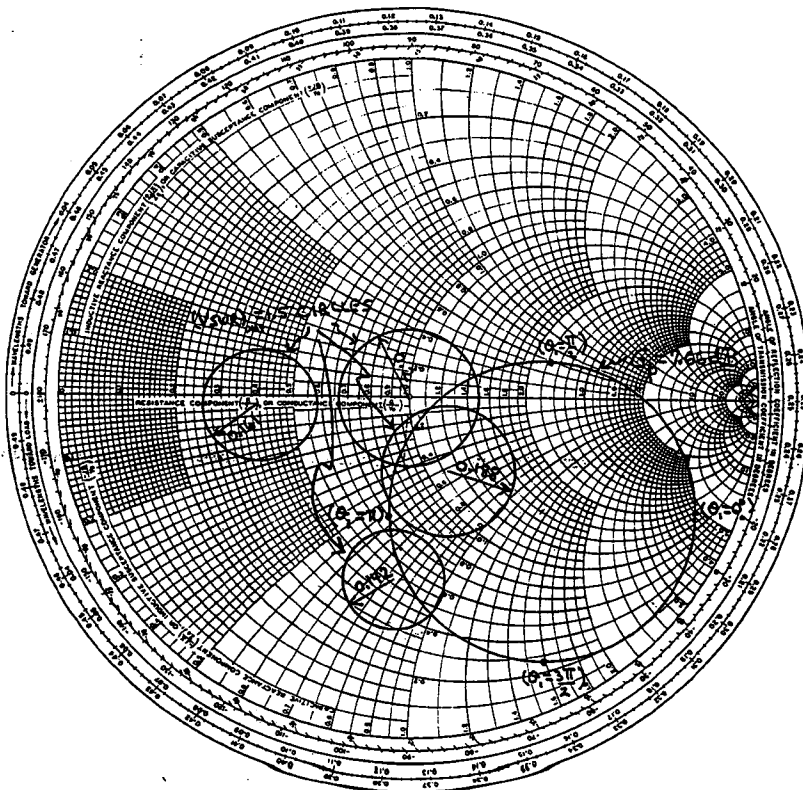FROM THESE CALCULATIONS IT IS SEEN THAT A DESIGN WITH $\Gamma_L = 0.331 \angle -99.26^\circ$ AND $\Gamma_L = 0.368 \angle -35.2^\circ$ RESULTS IN (VSWR)_{in} = 2.79 AND (VSWR)_{out} = 1.5.



3.31) (a) $K=1.344$, $\Delta=2.156 \angle -16.6^\circ \therefore$ POTENTIALLY UNSTABLE

(b) OUTPUT STABILITY CIRCLE: $C_L=0.261 \angle -36.3^\circ$, $r_L=0.409$


(c) FROM (3.6.6) (USING THE + SIGN): $\Gamma_{ML}=0.319 \angle -36.3^\circ$

(d) $G_{p,min}=G_{T,min}=44.82$ OR 16.51 dB

(e)

G_p	CENTER RADIUS
18 dB	$\begin{cases} C_p=0.31 \angle -36.3^\circ \\ r_p=0.234 \end{cases}$
21 dB	$\begin{cases} C_p=0.281 \angle -36.3^\circ \\ r_p=0.34 \end{cases}$
26 dB	$\begin{cases} C_p=0.266 \angle -36.3^\circ \\ r_p=0.39 \end{cases}$
36 dB	$\begin{cases} C_p=0.261 \angle -36.3^\circ \\ r_p=0.409 \end{cases}$

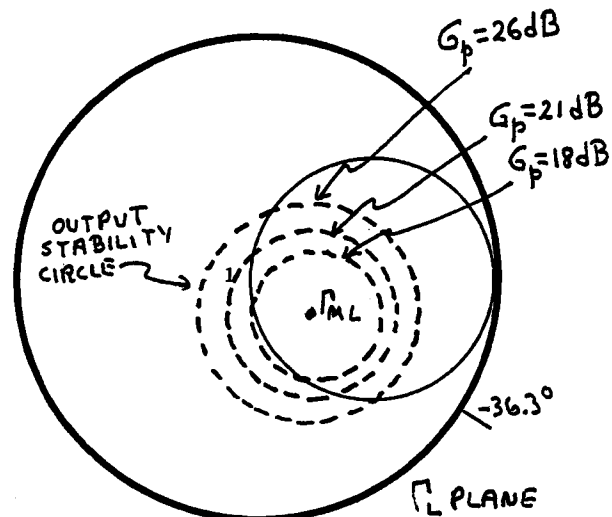THE 26 dB GAIN CIRCLE, THE 36 dB GAIN CIRCLE, AND THE OUTPUT STABILITY CIRCLE ALMOST COINCIDE.



(f) INPUT STABILITY CIRCLE: $C_n=0.102 \angle 107.4^\circ$, $r_n=0.44$

FROM (3.6.5) (USING THE + SIGN): $\Gamma_{mn}=0.127 \angle 107.44^\circ$

(g) $(VSWR)_{in}=(VSWR)_{out}=1$.

3.32) (a) $K=1.17$, $\Delta=0.368 \angle 27.91^\circ$ UNCONDITIONALLY STABLE

$G_{p,max}=9.24$ OR 9.66 dB, $G_p=9.66-1=8.66$ dB

FOR THE $G_p=8.66$ dB CIRCLE: $g_p=1.388$, $C_p=0.292 \angle -129.4^\circ$, $r_p=0.466$

(b) THE VALUES OF Γ_L ON THE 8.66 dB CIRCLE ARE:


$$\Gamma_L = C_p + r_p e^{j\theta_1} = 0.292 \angle -129.4^\circ + 0.466 e^{j\theta_1}$$

LETTING $\theta_1=0, \pi, \pi$, AND $\frac{3\pi}{2}$ WE OBTAIN

THE VALUES OF Γ_L SHOWN IN THE TABLE.

THE ASSOCIATED VALUES OF P_{IN} ARE ALSO SHOWN.

FOR $(VSWR)_{in}=1.5$ (OR $|\Gamma_a|=0.2$), USING (3.8.3) AND (3.8.4), THE CENTER AND RADIUS OF THE $(VSWR)_{in}=1.5$ CIRCLE ARE CALCULATED.

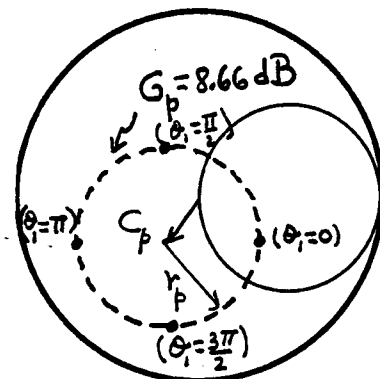

(C) THE VALUES OF Γ_L ON THE $(VSWR)_{in} = 1.5$ CIRCLE ARE GIVEN BY $\Gamma_L = C_{V_i} + \Gamma_i e^{j\theta_2}$. LETTING $\theta_2 = 0$ AND π , TWO VALUES OF Γ_L ON THE $(VSWR)_{in} = 1.5$ CIRCLE ARE CALCULATED (SEE THE TABLE). THE ASSOCIATED VALUES OF Γ_{OUT} , $|\Gamma_b|$, AND $(VSWR)_{OUT}$ ARE ALSO SHOWN

Γ_L	Γ_{IN}	$(VSWR)_{in} = 1.5$ CIRCLE	Γ_L	Γ_{OUT}	$ \Gamma_b $	$(VSWR)_{out}$
$(\theta_1 = 0)$		$C_{V_i} = 0.532 \angle -47.1^\circ$	$0.637 \angle -37.7^\circ (\theta_2 = 0)$	$0.311 \angle 129.5^\circ$	0.475	2.8
$0.36 \angle -38.8^\circ$	$0.548 \angle 47.1^\circ$	$\Gamma_{V_i} = 0.142$	$0.448 \angle -60.5^\circ (\theta_2 = \pi)$	$0.259 \angle 91.2^\circ$	0.304	1.875
$(\theta_1 = \pi/2)$		$C_{V_i} = 0.619 \angle -27.7^\circ$	$0.729 \angle -23.4^\circ (\theta_2 = 0)$	$0.314 \angle 161.7^\circ$	0.368	2.16
$0.304 \angle 127.6^\circ$	$0.634 \angle 27.9^\circ$	$\Gamma_{V_i} = 0.122$	$0.514 \angle -34.3^\circ (\theta_2 = \pi)$	$0.219 \angle 123.5^\circ$	0.419	2.44
$(\theta_1 = \pi)$		$C_{V_i} = 0.799 \angle -34.2^\circ$	$0.859 \angle -31.5^\circ (\theta_2 = 0)$	$0.501 \angle 153.7^\circ$	0.306	1.88
$0.689 \angle -160.9^\circ$	$0.81 \angle 34.2^\circ$	$\Gamma_{V_i} = 0.071$	$0.741 \angle -37.3^\circ (\theta_2 = \pi)$	$0.399 \angle 136.2^\circ$	0.483	2.87
$(\theta_1 = 3\pi/2)$		$C_{V_i} = 0.77 \angle -49.4^\circ$	$0.824 \angle -45.2^\circ (\theta_2 = 0)$	$0.518 \angle 124.3^\circ$	0.430	2.51
$0.716 \angle -105^\circ$	$0.782 \angle 49.4^\circ$	$\Gamma_{V_i} = 0.08$	$0.721 \angle -54.2^\circ (\theta_2 = \pi)$	$0.429 \angle 107.5^\circ$	0.415	2.42

FROM THESE CALCULATIONS IT IS SEEN THAT A DESIGN WITH $\Gamma_L = 0.689 \angle -160.9^\circ$ AND $\Gamma_A = 0.859 \angle -31.5^\circ$ GIVES: $G_p = 8.66 \text{ dB}$, $(VSWR)_{in} = 1.88$, $(VSWR)_{out} = 1.5$.

3.33) (a) FROM EXAMPLE 3.7.2, FOR THE $G_p = 10 \text{ dB}$ CIRCLE: $C_p = 0.572 \angle 97.2^\circ$, $\Gamma_p = 0.473$
 FROM (3.8.9) AND (3.8.10), WITH $C_{oo} = C_p$ AND $\Gamma_{oo} = \Gamma_p$, WE OBTAIN:
 $C_i = 1.131 \angle 170.6^\circ$ AND $\Gamma_i = 0.622$


(b) FOR $\Gamma_L = 0.1 \angle 97^\circ$, $\Gamma_{IN} = 0.52 \angle 179.32^\circ$,
 $\Gamma_A = \Gamma_{IN}^* = 0.52 \angle -179.32^\circ$

THEN $(VSWR)_{in} = 1$

FOR $(VSWR)_{in} = 2$ (OR $|\Gamma_A| = 0.333$),

WE OBTAIN FROM (3.8.3) AND (3.8.4):

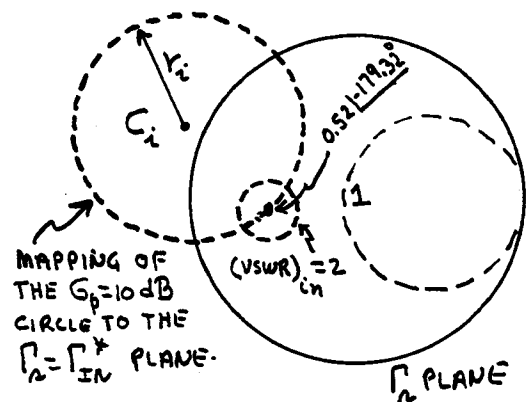$C_{V_i} = 0.477 \angle 179.32^\circ$, $\Gamma_{V_i} = 0.251$



3.34) $K=0.924$, $\Delta=0.137 \angle -139^\circ$ $\therefore$ POTENTIALLY UNSTABLE

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|} = \frac{8}{0.03} = 266.6 \text{ OR } 24.3 \text{ dB}$$

DESIGN FOR $G_p=20 \text{ dB}$ (i.e., 4.3 dB LESS THAN G_{MSG}).

OUTPUT STABILITY CIRCLE:

$$C_L = 2.26 \angle 40.1^\circ, \quad \gamma_L = 1.307$$

$G_p=20 \text{ dB}$ CONSTANT-GAIN CIRCLE: ($g_p=1.563$)

$$C_p = 0.505 \angle 40.1^\circ, \quad \gamma_p = 0.519$$

VALUES OF Γ_L ON $G_p=20 \text{ dB}$ CIRCLE:

$$\Gamma_L = C_p + \gamma_p e^{j\theta} = 0.505 \angle 40.1^\circ + 0.519 e^{j\theta}$$

THE TABLE SHOWS TWO VALUES OF Γ_L (i.e., for $\theta_1=\pi$ AND $\theta_2=\frac{3\pi}{2}$), THE ASSOCIATED VALUES OF $\Gamma_L = \Gamma_{IN}^*$, Γ_{OUT} , $|\Gamma_b|$, AND $(VSWR)_{OUT}$.



Γ_L	$\Gamma_L = \Gamma_{IN}^*$	$(VSWR)_{IN}$	Γ_{OUT}	$ \Gamma_b $	$(VSWR)_{OUT}$
($\theta_1=\pi$)					
$0.352 \angle 112.2^\circ$	$0.655 \angle 163.4^\circ$	1	$0.668 \angle -44.8^\circ$	0.667	30.25
($\theta_2=3\pi/2$)					
$0.432 \angle -26.6^\circ$	$0.607 \angle -179.2^\circ$	1	$0.674 \angle -34.3^\circ$	0.668	30.25

MAPPING OF THE $G_p=20 \text{ dB}$ CIRCLE TO THE $\Gamma_L = \Gamma_{IN}^*$ PLANE:

$$C_i = 0.823 \angle 175.3^\circ, \quad \gamma_i = 0.227$$

INPUT STABILITY CIRCLE: $C_i = 1.65 \angle 175.3^\circ, \quad \gamma_i = 0.679$

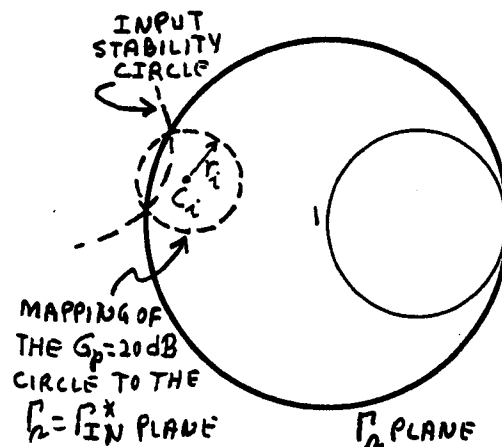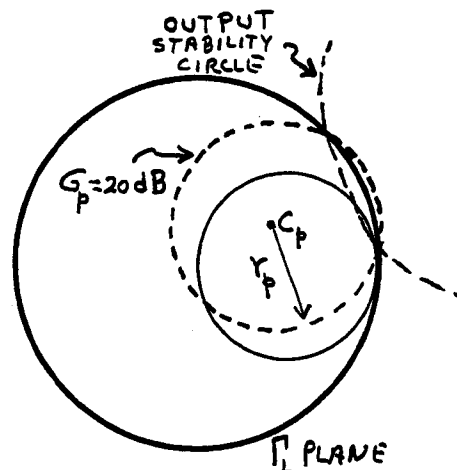THE VALUES OF $(VSWR)_{OUT} = 30.25$ SHOW THAT THE OUTPUT HAS TO BE MISMATCHED IN ORDER TO REDUCE THE GAIN TO 20 dB. THE DESIGNER CAN TRY TO REDUCE $(VSWR)_{OUT}$ BY RELAXING THE INPUT VSWR VALUE (SAY, LET $(VSWR)_{IN} \leq 1.5$), AS DISCUSSED IN EXAMPLE 3.8.2.



3.35) $K=0.875$, $\Delta=0.445 \angle 160.4^\circ$ $\therefore$ POTENTIALLY UNSTABLE

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|} = \frac{3.1}{0.125} = 24.8 \text{ OR } 13.9 \text{ dB}$$

DESIGN FOR $G_A=10 \text{ dB}$ (i.e, 3.9 dB LESS THAN G_{MSG})

INPUT STABILITY CIRCLE:

$$C_L = 3.303 \angle -173.2^\circ, \quad r_L = 2.392$$

$G_A=10 \text{ dB}$ CONSTANT-GAIN CIRCLE: ($g_a=1.041$)

$$C_a = 0.296 \angle -173.2^\circ, \quad r_a = 0.73$$

VALUES OF Γ_L ON THE $G_A=10 \text{ dB}$ CIRCLE:

$$\Gamma_L = C_a + r_a e^{j\theta_1} = 0.296 \angle -173.2^\circ + 0.73 e^{j\theta_1}$$

THE TABLE SHOWS TWO VALUES OF Γ_L (i.e, for $\theta_1=0$ AND $\theta_1=\frac{\pi}{2}$), THE ASSOCIATED VALUES OF $\Gamma_L=\Gamma_{OUT}^*$, Γ_{IN} , $|\Gamma_a|$, AND $(VSWR)_{ch}$.

Γ_L	$\Gamma_L = \Gamma_{OUT}^*$	$(VSWR)_{OUT}$	Γ_{IN}	$ \Gamma_a $	$(VSWR)_{ch}$
$(\theta_1=0)$ $0.437 \angle -4.6^\circ$	$0.405 \angle 70.8^\circ$	1	$0.565 \angle 172^\circ$	0.802	9.1
$(\theta_1=\pi/2)$ $0.755 \angle 112.9^\circ$	$0.08 \angle 133.5^\circ$	1	$0.624 \angle -171.9^\circ$	0.802	9.1



MAPPING OF THE $G_A=10 \text{ dB}$ CIRCLE TO THE $\Gamma_L=\Gamma_{OUT}^*$ PLANE:

$$C_o = 0.646 \angle 130.9^\circ \text{ AND } r_o = 0.566$$

OUTPUT STABILITY CIRCLE:

$$C_L = 9.33 \angle -49.1^\circ, \quad r_L = 10.19$$

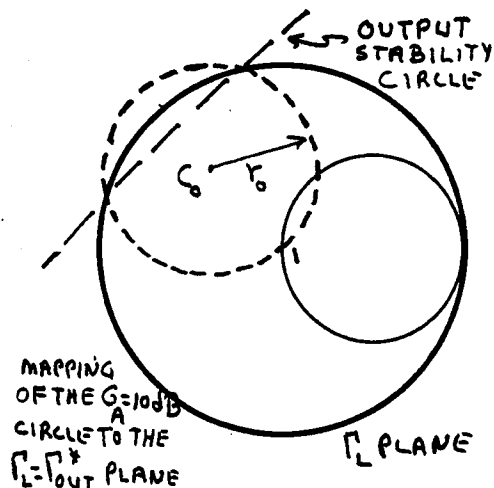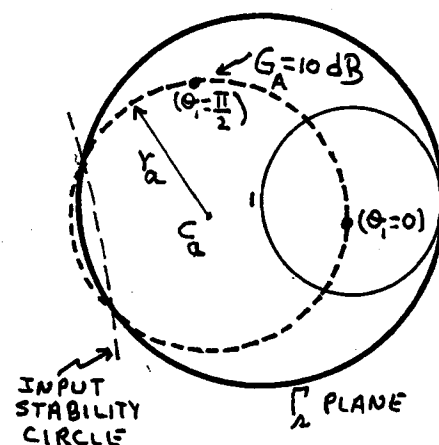THE VALUES OF $(VSWR)_{ch}=9.1$ SHOW THAT THE INPUT HAS TO BE MISMATCHED IN ORDER TO REDUCE THE GAIN TO 10 dB . (i.e, $G_A=10 \text{ dB}$). THE DESIGNER CAN TRY TO REDUCE $(VSWR)_{ch}$ BY RELAXING THE OUTPUT VSWR.



3.36) (2) dc model

$$(b) V_{TH} = \frac{24(4k)}{4k+16k} = 4.8V$$


$$R_{TH} = 4k || 16k = 3.2k\Omega$$

$$V_{TH} = I_B R_{TH} + 0.7 + I_C R_E \quad (I_C \approx I_E)$$

$$\therefore I_B = \frac{V_{TH} - 0.7}{R_{TH} + \beta R_E} = 40\mu A$$

$$I_C = \beta I_B = 4mA$$
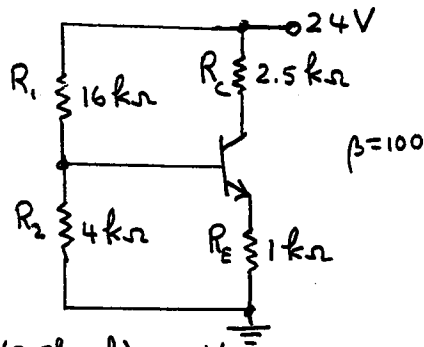
$$V_{CE} = V_{CC} - I_C (R_C + R_E) = 24 - 4m(2.5k + 1k) = 10V$$



(c) AT 500MHz THE $0.1\mu F$ ($Z_C = -j0.003\Omega$) ACT AS SHORT CIRCUITS TO THE AC SIGNAL. THUS, RFLC ARE NOT NEEDED IN SERIES WITH THE $16k\Omega$ AND $2.5k\Omega$ RESISTORS.

THE $100nH$ INDUCTOR ($Z_L = j314\Omega$) IMPEDANCE IS ABOUT 10% OF THE RESISTANCE OF $R_2 = 4k\Omega$. THUS, A RFL SHOULD BE USED IN SERIES WITH THE $4k\Omega$ RESISTOR.


(d) ac model

$$(e) Z = \frac{1}{\frac{1}{50\Omega} + j2\pi 500 \times 10^6 \times 50 \times 10^{-12}} = -j6.37\Omega$$

$$Z_{100nH} = \frac{1}{j2\pi 500 \times 10^6 \times 100 \times 10^{-9}} = j314.2\Omega$$

USING THE ZY CHART IT IS SIMPLE TO CALCULATE: $Z_L = 1.015 + j0.035$
AND $\Gamma_L = 0.02 \angle 65.8^\circ$

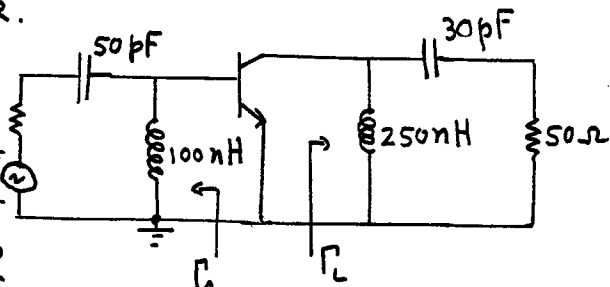SIMILARLY: $Z_L = 1.05 - j0.11$
AND $\Gamma_L = 0.06 \angle -61^\circ$




3.37) (a) dc model

$$(b) 20 = I_C R_C + V_{CE}$$

$$\text{OR } R_C = \frac{20 - 10}{5m} = 2k\Omega$$

$$V_{CE} = I_B R_B + 0.7$$
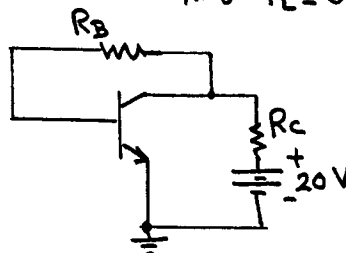
$$R_B = \frac{10 - 0.7}{\left(\frac{5m}{100}\right)} = 186k\Omega$$



THIS TYPE OF DC BIAS RESULTS IN A LARGE VALUE FOR R_B .

(c) ac model

$$\text{AT } f = 300MHz: Z_{30pF} = -j17.68\Omega,$$


$$Z_{70pF} = -j7.58\Omega, Z_{40nH} = j75.4\Omega$$

$$Z_{70nH} = j131.9\Omega$$

USING THE ZY SMITH CHART OR

SIMPLE CALCULATIONS, WE OBTAIN:
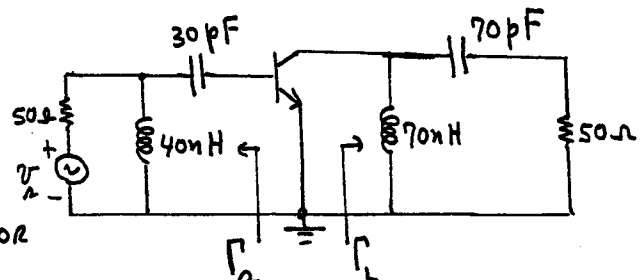
$$Z_L = 35\Omega + j5.2\Omega \text{ OR } \Gamma_L = 0.185 \angle 157.3^\circ; Z_L = 49.9 + j1.25\Omega \text{ OR } \Gamma_L = 0.96 \angle 0^\circ$$



$$3.38) \text{ LET } V_{CC} = 20 \text{ V}, R_E = \frac{10\% V_{CC}}{I_E} = \frac{0.1(20)}{10 \text{ m}} = 200 \Omega$$

$$V_{CC} = V_{CE} + I_C(R_C + R_E) \Rightarrow R_C + 200 = \frac{20 - 10}{4 \text{ m}} = 2.5 \text{ k}, \text{ OR } R_C = 2.3 \text{ k}\Omega$$

$$\text{FOR GOOD } \beta \text{ STABILITY LET } R_{TH} = \frac{\beta R_E}{10} = \frac{100(200)}{10} = 2 \text{ k}\Omega$$

$$V_{TH} = I_B R_{TH} + 0.75 + I_C R_E = \frac{4 \text{ m}}{100} (2 \text{ k}) + 0.75 + 4 \text{ m} (200) = 1.63 \text{ V}$$

$$R_1 = R_{TH} \frac{V_{CC}}{V_{TH}} = 2.3 \text{ k} \frac{20}{1.63} = 28.22 \text{ k}\Omega$$

$$R_2 = \frac{R_{TH}}{1 - V_{TH}/V_{CC}} = \frac{2.3 \text{ k}}{1 - (1.63/20)} = 2.5 \text{ k}\Omega$$

$$3.39) I_{C2} = 10 \text{ mA}. \text{ LET } I_3 = 20 \text{ mA}, \text{ THEN } I_{C1} = I_3 - I_{C2} = 20 \text{ m} - 10 \text{ m} = 10 \text{ mA}$$

$$\therefore R_4 = \frac{0.75}{I_{C1}} = \frac{0.75}{10 \text{ m}} = 75 \Omega. \text{ LET } V_{CC} = 20 \text{ V}$$

$$R_3 = \frac{V_{CC} - V_{CE,2}}{I_3} = \frac{20 - 10}{20 \text{ m}} = 500 \Omega$$

$$\text{FOR GOOD } \beta \text{ STABILITY LET } I_{R1} \approx I_{R2} = 20 I_{B1} = 20 \frac{10 \text{ m}}{100} = 2 \text{ mA},$$

$$V_{B,1} = V_{CE,2} - 0.75 = 9.25 \text{ V}$$

$$R_1 = \frac{V_{CC} - V_{B,1}}{I_{R1}} = \frac{20 - 9.25}{2 \text{ m}} = 5.37 \text{ k}\Omega$$

$$R_2 = \frac{V_{B,1}}{I_{R2}} = \frac{9.25}{2 \text{ m}} = 4.63 \text{ k}\Omega$$

$$3.40) (a) \text{ IN FIG. 3.9.2a: } V_{CC} = (I_B + I_C) R_C + I_B R_B + V_{BE} \quad (1)$$

$$\text{AND } I_C = h_{FE} I_B + (h_{FE} + 1) I_{CBO} \quad (2)$$

SUBSTITUTING (2) INTO (1) GIVES:

$$V_{CC} - V_{BE} = \left(\frac{I_C}{h_{FE}} - \frac{I_{CBO}(h_{FE} + 1)}{h_{FE}} \right) (R_C + R_B) + I_C R_C$$

$$\text{OR } I_C = \frac{h_{FE}(V_{CC} - V_{BE})}{R_B + R_C(h_{FE} + 1)} + \frac{I_{CBO}(h_{FE} + 1)(R_C + R_B)}{R_B + R_C(h_{FE} + 1)}$$

$$S_i = \frac{\partial I_C}{\partial I_{CBO}} = \frac{(h_{FE} + 1)(R_C + R_B)}{R_B + R_C(h_{FE} + 1)}$$

$$S_{V_{BE}} = \frac{\partial I_C}{\partial V_{BE}} = \frac{-h_{FE}}{R_B + R_C(h_{FE} + 1)}$$

IN THE DERIVATION OF $S_{h_{FE}}$ WE NEGLECT THE CONTRIBUTION FROM I_{CBO} . HENCE,

$$I_{C2} = \frac{h_{FE,2}(V_{CC} - V_{BE})}{R_B + R_C(h_{FE,2} - 1)} \quad \text{AND} \quad I_{C1} = \frac{h_{FE}(V_{CC} - V_{BE})}{R_B + R_C(h_{FE} - 1)}$$

$$\frac{I_{C2}}{I_{C1}} - 1 = \frac{h_{FE,2}[R_B + R_C(h_{FE} - 1)]}{h_{FE}[R_B + R_C(h_{FE,2} - 1)]} - 1 = \frac{(h_{FE,2} - h_{FE}) S_{i2}}{h_{FE} h_{FE,2}}$$

$$\text{OR } S_{h_{FE}} = \frac{\Delta I_C}{\Delta h_{FE}} = \frac{I_{C2} - I_{C1}}{h_{FE,2} - h_{FE}} = \frac{I_{C1} S_{i2}}{h_{FE} h_{FE,2}}$$

$$(b) \quad I_B = \frac{I_C}{h_{FE}} = \frac{10 \cdot 10^{-3}}{50} = 0.2 \text{ mA}, \quad R_B = \frac{V_{CE} - 0.7}{I_B} = \frac{10 - 0.7}{0.2 \cdot 10^{-3}} = 46.5 \text{ k}\Omega$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C + I_B} = \frac{20 - 10}{102 \cdot 10^{-3}} = 980 \Omega$$

(c) IF $h_{FE} = 100$, I_C INCREASES FROM 10 mA TO:

$$I_{C2} = \frac{h_{FE,2}(V_{CC} - 0.7)}{R_B + R_C(h_{FE,2} + 1)} \quad \text{WHERE } h_{FE,2} = 100$$

$$= \frac{100(20 - 0.7)}{46.5 \cdot 10^3 + 0.98 \cdot 10^3(100 + 1)} = 13.3 \text{ mA}$$

$$\text{AND } V_{CE} = V_{CC} - I_{C2} R_C = 20 - 13.3 \cdot 10^{-3}(0.98 \cdot 10^3) = 7 \text{ V}$$

$$3.41) \text{ LET } V_{CC} = 12 \text{ V}, \quad R_E = \frac{10\% V_{CC}}{I_C} = \frac{0.1(12)}{1 \text{ m}} = 1.2 \text{ k}\Omega$$

(a)

$$V_{CC} = V_{CE} + I_C(R_C + R_E) \Rightarrow R_C + 1.2 \text{ k} = \frac{12 - 6}{1 \text{ m}} = 6 \text{ k}\Omega \text{ OR } R_C = 4.8 \text{ k}\Omega.$$

$$\text{FROM } S_i = \frac{(\beta + 1)(R_{TH} + R_E)}{R_{TH} + (\beta + 1)R_E} \Rightarrow 5 = \frac{101(R_{TH} + 1.2 \text{ k})}{R_{TH} + (101)1.2 \text{ k}} \therefore R_{TH} = 5.05 \text{ k}\Omega$$

$$V_{TH} = I_B R_{TH} + 0.7 + I_C R_E = \frac{1 \text{ m}}{100}(4.8 \text{ k}) + 0.7 + 1 \text{ m}(1.2 \text{ k}) = 1.95 \text{ V}$$

$$R_1 = R_{TH} \frac{V_{CC}}{V_{TH}} = 5.05 \text{ k} \frac{12}{1.95} = 31.1 \text{ k}\Omega$$

$$R_2 = \frac{R_{TH}}{1 - V_{TH}/V_{CC}} = \frac{5.05 \text{ k}}{1 - 1.95/12} = 6.03 \text{ k}$$

$$(b) \quad I_{C_{B0,2}} = 1 \cdot 10^{-6} 2^{\frac{75-25}{10}} = 32 \mu\text{A}, \quad h_{FE,2} = 100 + \frac{0.5(75-25)}{100} 100 = 125$$

$$S_i = 5, \quad S_{V_{BE}} = \frac{-100}{5.05 \cdot 10^3 + (101)1.2 \cdot 10^3} = 0.8 \cdot 10^{-3}, \quad S_{h_{FE}} = \frac{10^{-3}(5.4)}{100(125)} = 4.3 \cdot 10^{-7}$$

$$\text{AT } 75^\circ\text{C: } I_C = \frac{125(1.95 - 0.7)}{5.05 \cdot 10^3 + (126)1.2 \cdot 10^3} + \frac{126(32 \cdot 10^{-6})(5.05 \cdot 10^3 + 1.2 \cdot 10^3)}{5.05 \cdot 10^3 + (126)1.2 \cdot 10^3}$$

$$= 1.16 \text{ mA}$$

$$3.42) \quad I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2 \Rightarrow 10\text{m} = 30\text{m} \left[1 + \frac{V_{GS}}{3} \right]^2 \therefore V_{GS} = -1.268\text{V}$$

$$R_S = \frac{-V_{GS}}{I_D} = \frac{1.268}{10\text{m}} = 126.8\ \Omega$$

$$\text{LET } V_{CC} = V_{EE} = 10\text{V} \text{ AND } I_{R_1} = 20\text{mA}, \text{ WHERE } I_{R_1} = I_C + I_D$$

$$\therefore I_C = 20\text{m} - 10\text{m} = 10\text{mA}$$

THE VOLTAGE AT THE GATE IS ZERO (I.E. ACROSS R_G). HENCE,

$$R_S = \frac{0 - (-V_{EE})}{I_C} = \frac{10}{10\text{m}} = 1\text{ k}\Omega$$

$$V_E = V_{DS} + V_{R_S} = 3 + 1.268 = 4.27\text{V}$$

$$\text{THEN, } R_1 = \frac{V_{CC} - V_E}{I_{R_1}} = \frac{10 - 4.27}{20\text{m}} = 287\ \Omega$$

$$\text{LET } I_{R_2} \approx I_{R_3} = 20 I_B = 20 \frac{10\text{m}}{100} = 2\text{mA}$$

$$V_B = V_E - 0.7 = 4.27 - 0.7 = 3.57\text{V}$$

$$R_2 = \frac{V_{CC} - V_B}{I_{R_2}} = \frac{10 - 3.57}{2\text{m}} = 3.21\text{ k}\Omega$$

$$R_3 = \frac{V_B}{I_{R_3}} = \frac{3.57}{2\text{m}} = 1.78\text{ k}\Omega$$