

SOLUTIONS MANUAL

MICROWAVE TRANSISTOR AMPLIFIERS

Analysis and Design

SECOND EDITION

Guillermo Gonzalez



PRENTICE HALL
Upper Saddle River, NJ 07458

Acquisitions Editor: *Eric Svendsen*
Project Editor: *Lorena Cerisano*
Production Manager: *Joan Eurell*
Production Coordinator: *Julia Meehan*

©1996 by Prentice-Hall, Inc.
Simon & Schuster / A Viacom Company
Upper Saddle River, New Jersey 07458

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission in writing from the publisher.

Printed in the United States of America


10 9 8 7 6 5 4 3 2 1

ISBN 0-13-271255-5

Prentice-Hall International (UK) Limited, *London*
Prentice-Hall of Australia Pty. Limited, *Sydney*
Prentice-Hall Canada Inc., *Toronto*
Prentice-Hall Hispanoamericana, S.A., *Mexico*
Prentice-Hall of India Private Limited, *New Delhi*
Prentice-Hall of Japan, Inc., *Tokyo*
Simon & Schuster Asia Pte. Ltd., *Singapore*
Editora Prentice-Hall do Brasil, Ltda., *Rio de Janeiro*

CONTENTS

CHAPTER	1	page 1
CHAPTER	2	page 19
CHAPTER	3	page 42
CHAPTER	4	page 71
CHAPTER	5	page 88

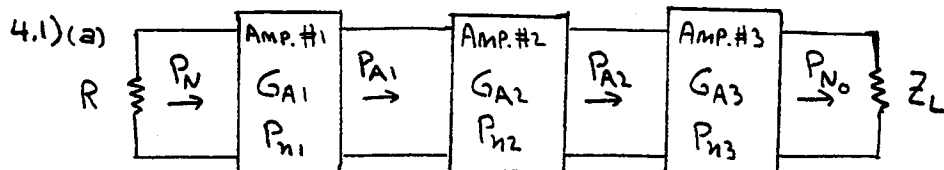

$$P_N = kTB \quad P_{A1} = G_{A1}P_N + P_{n1} \quad P_{A2} = G_{A2}P_{A1} + P_{n2} \quad P_{N0} = G_{A3}P_{A2} + P_{n3}$$

$$F = \frac{P_{N0}}{P_N G_{A1} G_{A2} G_{A3}} = \frac{G_{A3} G_{A2} G_{A1} P_N + G_{A3} G_{A2} P_{n1} + G_{A3} P_{n2} + P_{n3}}{P_N G_{A1} G_{A2} G_{A3}}$$

$$= 1 + \frac{P_{n1}}{P_N G_{A1}} + \frac{P_{n2}}{P_N G_{A1} G_{A2}} + \frac{P_{n3}}{P_N G_{A1} G_{A2} G_{A3}} \quad (1)$$

LET: $F_1 = 1 + \frac{P_{n1}}{P_N G_{A1}}$, $F_2 = 1 + \frac{P_{n2}}{P_N G_{A1} G_{A2}}$, $F_3 = 1 + \frac{P_{n3}}{P_N G_{A1} G_{A2} G_{A3}}$

THEREFORE, (1) CAN BE EXPRESSED IN THE FORM:

$$F = F_1 + \frac{F_2 - 1}{G_{A1}} + \frac{F_3 - 1}{G_{A1} G_{A2}}$$

(b) $F = 10^{0.1} + \frac{10^{0.3} - 1}{10^1} = 1.358 \text{ OR } 1.33 \text{ dB}$

4.2) (a) THE GAIN-CIRCLES ARE THE CONSTANT-GAIN G_A CIRCLES.

FROM FIG. P.2(a): $F_{min} = 3.3 \text{ dB}$, $\Gamma_{opt} \approx 0.56 \angle -155^\circ$.

γ_n IS EVALUATED BY READING A VALUE OF F AND ITS ASSOCIATED Γ_L , AND USING (4.3.4). FROM FIG. P.2(a) WE READ:

$F = 4.5 \text{ dB}$ AT $\Gamma_L \approx 0.56 \angle -94^\circ$. THEN

$$10^{0.45} = 10^{0.33} + \frac{4\gamma_n |0.56 \angle -94^\circ - 0.56 \angle -155^\circ|^2}{(1 - (0.56)^2) |1 + 0.56 \angle -155^\circ|^2} \Rightarrow \gamma_n = 0.108$$

FROM FIG. P.2(b): $F_{min} = 1.7 \text{ dB}$, $\Gamma_{opt} \approx 0.215 \angle 149^\circ$.

USING: $F = 3 \text{ dB}$ AT $\Gamma_L = 0.445 \angle 26^\circ$ WE OBTAIN $\gamma_n = 0.202$

(b) FOR THE $G_A = 10.7 \text{ dB}$ CIRCLE IN FIG. 4.3.4:

$$g_a = 4.158, \quad C_a = 0.574 \angle -154^\circ, \quad \gamma_a = 0.423$$

4.3) (a) THE $G_A = 14 \text{ dB}$ CIRCLE AND THE $F = 2 \text{ dB}$ CIRCLE INTERSECT AT TWO POINTS. THE VALUE OF Γ_L AT THESE THE POINTS ARE:

$$\Gamma_L \approx 0.5 \angle 160^\circ \text{ AND } \Gamma_L \approx 0.25 \angle -150^\circ$$

(b) LET $\Gamma_L = 0.5 \angle 160^\circ$, THEN $\Gamma_{OUT} = 0.657 \angle -73.3^\circ$

$$\text{FOR } (VSWR)_{OUT} = 1 : \Gamma_L = \Gamma_{OUT}^* = 0.657 \angle 73.3^\circ$$

$$\text{THEN, } \Gamma_{IN} = 0.8 \angle 165.6^\circ, \quad |\Gamma_a| = 0.678, \quad (VSWR)_{in} = 5.2$$

4.4) (a) $K=2.25$ AND $\Delta=0.246 \angle 112.8^\circ$ $\therefore$ UNCONDITIONALLY STABLE

(b) $G_{A,max} = \frac{|S_{21}|}{|S_{12}|} (K - \sqrt{K^2 - 1}) = 9.36$ OR 9.71 dB

(c) $G_A = 9.71 - 3 = 6.71 \text{ dB}$

FOR THE $G_A = 6.71 \text{ dB}$ CIRCLE: $g_a = 1.173$,

$C_a = 0.42 \angle 174.5^\circ$, $\gamma_a = 0.515$


(d) FOR THE 3dB NOISE CIRCLE:

$C_{F_n} = 0.405 \angle 145^\circ$, $\gamma_{F_n} = 0.388$

FOR THE 4dB NOISE CIRCLES:

$C_{F_n} = 0.279 \angle 145^\circ$, $\gamma_{F_n} = 0.616$

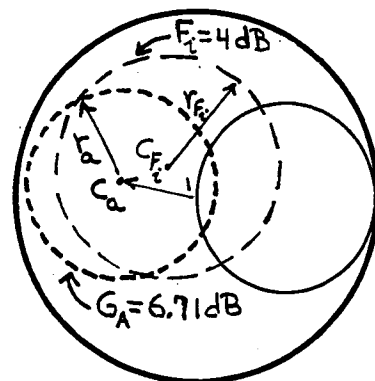THE $F_n = 4 \text{ dB}$ CIRCLE IS DRAWN ON THE SMITH CHART.



Γ_L PLANE


(e) FOR $G_{A,max}$: $\Gamma_L = \Gamma_{ML} = 0.667 \angle 174.5^\circ$, $\Gamma_L = \Gamma_{ML} = 0.587 \angle 102.2^\circ$.

$\therefore F = 10^{0.25} + \frac{4(\frac{5}{50}) |0.667 \angle 174.5^\circ - 0.5 \angle 145^\circ|^2}{(1 - (0.667)^2) |1 + 0.5 \angle 145^\circ|^2} = 1.97$ OR 2.95 dB

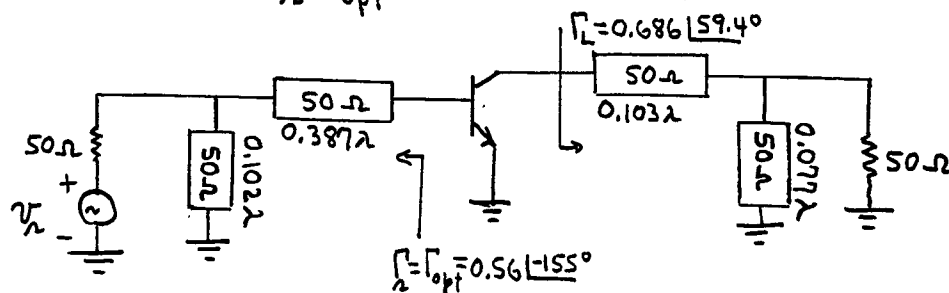4.5) $F_{min} = 3.3 \text{ dB}$, $\Gamma_{opt} = 0.56 \angle -155^\circ$, $\gamma_n = 0.108$

$K = 1.1$, $\Delta = 0.273 \angle 126.8^\circ$ $\therefore$ UNCONDITIONALLY STABLE

DESIGN WITH $\Gamma_L = \Gamma_{opt} = 0.56 \angle -155^\circ$ AND $\Gamma_L = \Gamma_{out}^* = 0.686 \angle 59.4^\circ$



$G_A = 16.67$ OR 12.2 dB


$G_T = G_A = 16.67$ OR 12.2 dB

$G_p = 20.62$ OR 13.1 dB

Also: $\Gamma_{IN} = 0.801 \angle 156.2^\circ$, $|\Gamma_a| = 0.438$, $(VSWR)_{in} = 2.6$, $(VSWR)_{out} = 1$.

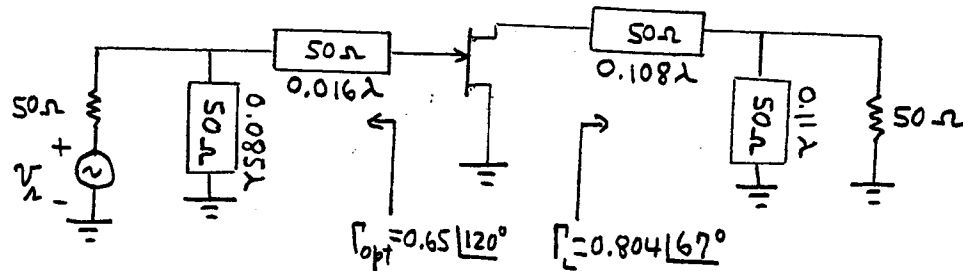4.6) $K=2.18$, $\Delta=0.555 \angle -178.3^\circ$ $\therefore$ UNCONDITIONALLY STABLE

DESIGN WITH $\Gamma_L = \Gamma_{opt} = 0.65 \angle 120^\circ$ AND $\Gamma_L = \Gamma_{out}^* = 0.804 \angle 67^\circ$



$$G_A = G_T = 75.6 \text{ OR } 18.8 \text{ dB}$$


$$\text{Also: } \Gamma_{IN} = 0.806 \angle -119.6^\circ, |\Gamma_a| = 0.327, (VSWR)_{in} = 1.97, (VSWR)_{out} = 1$$

4.7) $K=1.235$, $\Delta=0.175 \angle 166.2^\circ$ $\therefore$ UNCONDITIONALLY STABLE

$$G_{A,max} = 43.07 \text{ OR } 16.3 \text{ dB}, \Gamma_{in} = 0.787 \angle -170.1^\circ, \Gamma_{ML} = 0.749 \angle 44.8^\circ$$


Γ_L	$\Gamma_L = \Gamma_{out}^*$	Γ_{IN}	$ \Gamma_a $	$(VSWR)_{in}$	$G_A(\text{dB})$	$F(\text{dB})$
$0.2 \angle 155^\circ$	$0.528 \angle 41.7^\circ$	$0.704 \angle 170.8^\circ$	0.62	4.27	13.75	1.6
$0.32 \angle 172^\circ$	$0.559 \angle 42.9^\circ$	$0.715 \angle 170.8^\circ$	0.535	3.30	14.5	1.66
$0.43 \angle 180^\circ$	$0.592 \angle 43.7^\circ$	$0.726 \angle 170.7^\circ$	0.446	2.61	15.1	1.82
$0.59 \angle -174^\circ$	$0.650 \angle 44.5^\circ$	$0.747 \angle 170.6^\circ$	0.290	1.81	15.8	2.30
$0.787 \angle -170.1^\circ$	$0.749 \angle 44.8^\circ$	$0.787 \angle 170.1^\circ$	0	1	16.3	3.76

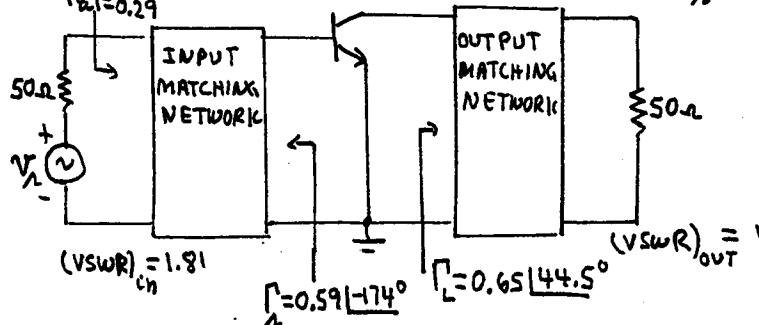THE DESIGN CAN BE PERFORMED WITH $\Gamma_L = 0.59 \angle -174^\circ$ AND $\Gamma_L = 0.65 \angle 44.5^\circ$.



$$G_A = 15.8 \text{ dB}$$

$$F = 2.3 \text{ dB}$$

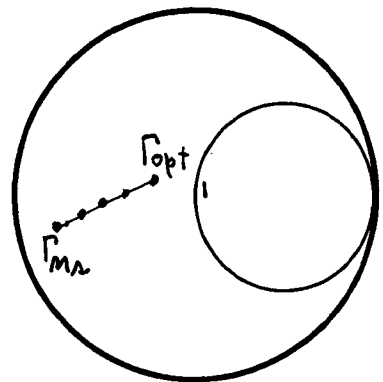

4.8) $K=0.96$, $\Delta=0.6 \angle -73.10^\circ$ $\therefore$ POTENTIALLY UNSTABLE


INPUT STABILITY CIRCLE: $C_1=1.34 \angle 62.7^\circ$, $\Gamma_1=0.345$

OUTPUT STABILITY CIRCLE: $C_2=1.55 \angle 47.2^\circ$, $\Gamma_2=0.56$

DESIGN WITH $\Gamma_1=\Gamma_{opt}=0.73 \angle 60^\circ$ AND $\Gamma_2=\Gamma_{out}^*=0.787 \angle 42.2^\circ$

BOTH Γ_{opt} AND Γ_L ARE IN THE STABLE REGION (AS EXPECTED).

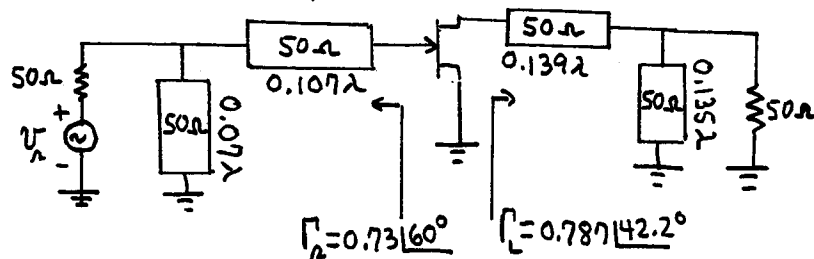A DESIGN FOR Γ_{opt} AND Γ_L IS SHOWN BELOW:



$$G_A = 14.9 \text{ dB}$$

$$F = 1.25 \text{ dB}$$

$$(VSWR)_{in} = 2.4$$

$$(VSWR)_{out} = 1$$

4.9) THIS TRANSISTOR IS POTENTIALLY UNSTABLE.

$G_{MSG} = 59.6$ OR 17.8 dB . LET US DESIGN FOR $G_A = 14 \text{ dB}$.


FIG. P4.2(b) SHOWS THAT THE $G_A = 14 \text{ dB}$ CIRCLE AND THE $F = 2 \text{ dB}$ CIRCLE INTERSECT AT TWO POINTS, NAMELY:

$\Gamma_1 \approx 0.5 \angle 160^\circ$ AND $\Gamma_1 \approx 0.25 \angle -150^\circ$

Γ_1	$G_A(\text{dB})$	$F(\text{dB})$	$\Gamma_2=\Gamma_{out}^*$	$(VSWR)_{out}$	Γ_{IN}	$ \Gamma_2 $	$(VSWR)_{in}$
$0.5 \angle 160^\circ$	13.6	2	$0.657 \angle 73.3^\circ$	1	$0.8 \angle 165.6^\circ$	0.678	5.2
$0.25 \angle -150^\circ$	13.5	1.9	$0.695 \angle 65.3^\circ$	1	$0.793 \angle 162.4^\circ$	0.683	5.3

SELECT $\Gamma_1=0.5 \angle 160^\circ$ AND $\Gamma_2=0.657 \angle 73.3^\circ$.

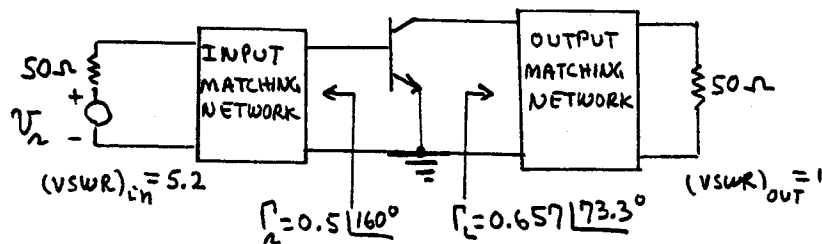$G_T=G_A=13.6 \text{ dB}$ AND $G_p=17.2 \text{ dB}$



4.10) TRANSISTOR #1: $K=0.869$, $\Delta=0.348 \angle -39.2^\circ$ $\therefore$ POTENTIALLY UNSTABLE

$$G_{msE} = 44 \text{ OR } 16.4 \text{ dB}$$

$$\text{INPUT STABILITY CIRCLE: } C_L = 16.75 \angle -37.3^\circ, \gamma_L = 17.61$$


$$\text{OUTPUT STABILITY CIRCLE: } C_L = 4.06 \angle 44.5^\circ, \gamma_L = 3.16$$

THE $G_A = 14 \text{ dB}$, 12 dB , AND 10 dB CIRCLES, THE $F_L = 2 \text{ dB}$, AND 2.5 dB CIRCLES, AND THE INPUT STABILITY CIRCLE ARE DRAWN IN THE SMITH CHART.

$G_A(\text{dB})$	C_a	γ_a
14	$0.561 \angle 142.7^\circ$	0.597
12	$0.35 \angle 142.7^\circ$	0.724
10	$0.219 \angle 142.7^\circ$	0.821

$F_L(\text{dB})$	C_{F_L}	γ_{F_L}
2	$0.306 \angle 77^\circ$	0.258
2.5	$0.254 \angle 77^\circ$	0.458

LET US TRY A DESIGN WITH Γ_L AT POINT "a": $\Gamma_L = 0.08 \angle 31^\circ$. WITH THIS VALUE OF Γ_L WE FIND: $\Gamma_L = \Gamma_{OUT}^* = 0.485 \angle 37.5^\circ$, $\Gamma_{IN} = 0.555 \angle -140^\circ$, $|\Gamma_a| = 0.577$, AND $(VSWR)_{in} = 3.7$. THE VALUE OF $(VSWR)_{in}$ CAN BE IMPROVED IF WE DESIGN FOR A HIGHER $(VSWR)_{out}$.

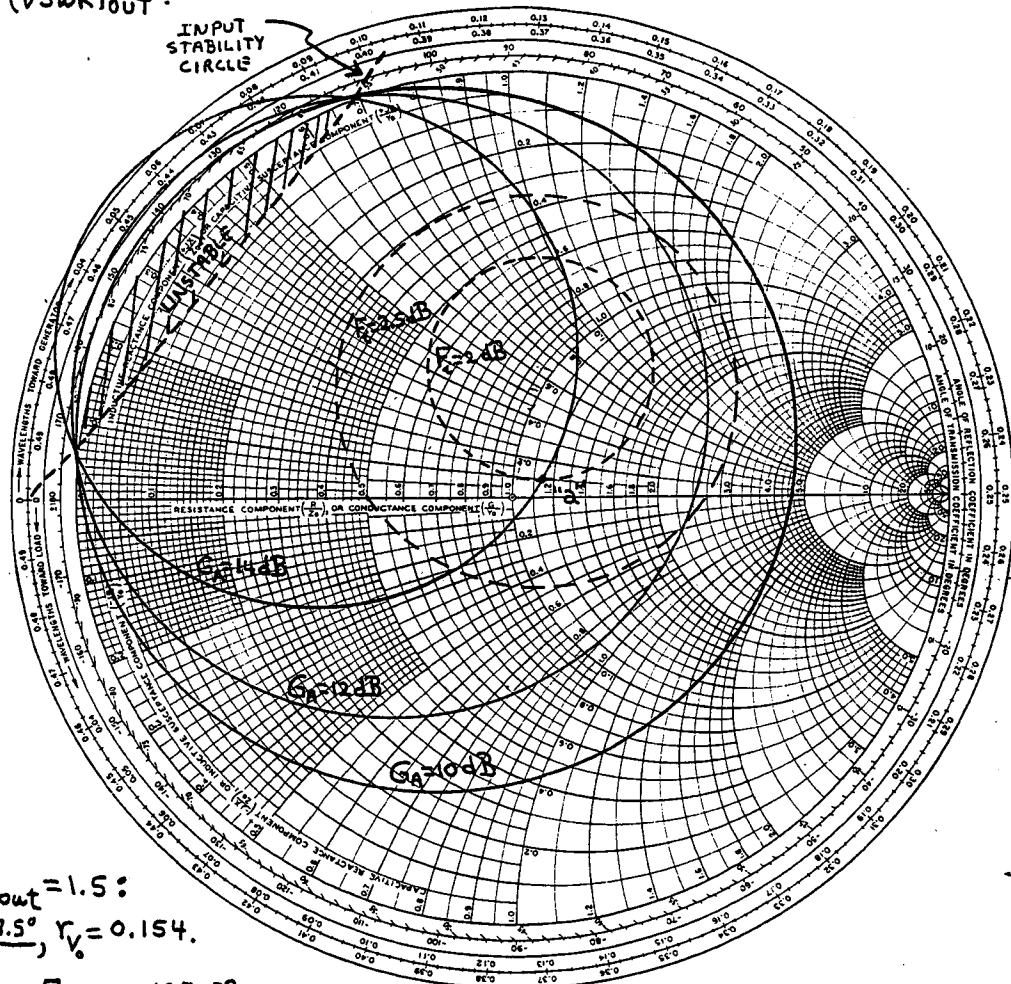

FOR $(VSWR)_{out} = 1.5$:

$$C_V = 0.47 \angle 37.5^\circ, \gamma_V = 0.154.$$

SELECTING $\Gamma_L = 0.32 \angle 37.5^\circ$ IT FOLLOWS THAT

$$\Gamma_{IN} = 0.449 \angle -134.7^\circ, |\Gamma_a| = 0.47, \text{ AND } (VSWR)_{in} = 2.78$$

TRANSISTOR #2 : THE DESIGN PROCEDURE IS SIMILAR TO THE ONE USED WITH TRANSISTOR #1. ONLY THE CALCULATIONS FOR THE G_A CIRCLES AND FOR THE NOISE CIRCLES ARE GIVEN.

$$K = 0.244, \Delta = 0.263 \angle 56.2^\circ \therefore \text{POTENTIALLY UNSTABLE}$$

$$G_{MSG} = 22.5 \text{ dB}$$

$$\text{INPUT STABILITY CIRCLE: } C_L = 2.04 \angle 172.2^\circ, \gamma_L = 1.55$$

$$\text{OUTPUT STABILITY CIRCLE: } C_L = 1.63 \angle 21.9^\circ, \gamma_L = 1.07$$

THE CALCULATIONS FOR THE $G_A = 18 \text{ dB}$ AND 16 dB CIRCLES, AND FOR THE $F_i = 1.2 \text{ dB}$ AND 1.5 dB CIRCLES ARE:

$G_A(\text{dB})$	C_a	γ_a	$F_i(\text{dB})$	C_{F_i}	γ_{F_i}
18	$0.376 \angle 172.2^\circ$	0.796	1.2	$0.39 \angle 32^\circ$	0.246
16	$0.255 \angle 172.2^\circ$	0.849	1.5	$0.35 \angle 32^\circ$	0.378

4.11) $K = 0.774, \Delta = 0.46 \angle -129.3^\circ \therefore \text{POTENTIALLY UNSTABLE.}$

$$G_{MSG} = 14.36 \text{ dB}$$

$$\text{INPUT STABILITY CIRCLE } \begin{cases} C_L = 2.06 \angle 120.3^\circ \\ \gamma_L = 1.19 \end{cases} \quad \text{OUTPUT STABILITY CIRCLE } \begin{cases} C_L = 334.6 \angle -65.4^\circ \\ \gamma_L = 335.4 \end{cases}$$

CONSIDER THE $G_p = 10 \text{ dB}$ AND 12 dB CIRCLES:

$G_p(\text{dB})$	C_p	γ_p
12	$0.58 \angle 114.6^\circ$	0.663
10	$0.366 \angle 114.6^\circ$	0.754

THE TRANSFORMATIONS OF THE $G_p = 12 \text{ dB}$ AND 10 dB CIRCLES TO THE $\Gamma_L = \Gamma_{IN}^*$ PLANE ARE SHOWN IN THE SMITH CHART. ALSO, THE $F_i = 1.2 \text{ dB}$ AND 1.5 dB CIRCLES ARE SHOWN, AS WELL AS ONE $(VSWR)_{in} = 2$ CIRCLE.

$$G_p = 12 \text{ dB CIRCLE IN THE } \Gamma_L = \Gamma_{IN}^* \text{ PLANE: } C_i = 0.959 \angle 120.3^\circ, \gamma_i = 0.366$$

$$G_p = 10 \text{ dB CIRCLE IN THE } \Gamma_L = \Gamma_{IN}^* \text{ PLANE: } C_i = 0.858 \angle 120.3^\circ, \gamma_i = 0.372$$


$$F_i = 1.2 \text{ dB CIRCLE IN THE } \Gamma_L \text{ PLANE: } C_{F_i} = 0.654 \angle 55^\circ, \gamma_{F_i} = 0.188$$

$$F_i = 1.5 \text{ dB CIRCLE IN THE } \Gamma_L \text{ PLANE: } C_{F_i} = 0.621 \angle 55^\circ, \gamma_{F_i} = 0.252$$

A POINT ON THE $G_p = 10 \text{ dB}$ CIRCLE IS $\Gamma_L = 0.416 \angle -57.3^\circ$. THEN, $\Gamma_{IN} = 0.62 \angle -97^\circ$. THE VALUE $\Gamma_L = \Gamma_{IN}^*$ RESULTS IN $(VSWR)_{in} = 1$, AND A VERY-HIGH NOISE FIGURE. THE CIRCLE $(VSWR)_{in} = 2$ IS DRAWN (I.E., $C_{V_i} = 0.576 \angle 97^\circ$ AND $\gamma_{V_i} = 0.214$). A CONVENIENT VALUE OF Γ_L IS AT POINT "a": $\Gamma_L = 0.56 \angle 79^\circ$, AND IT FOLLOWS THAT

Γ_L	Γ_L	$G_p(\text{dB})$	$F_i(\text{dB})$	Γ_{OUT}	$ \Gamma_a $	$(VSWR)_{in}$	$ \Gamma_b $	$(VSWR)_{out}$
$0.56 \angle 79^\circ$	$0.416 \angle -57.3^\circ$	10	1.5	$0.35 \angle -107^\circ$	0.286	1.8	0.664	4.9

IMPEDANCE OR ADMITTANCE COORDINATES

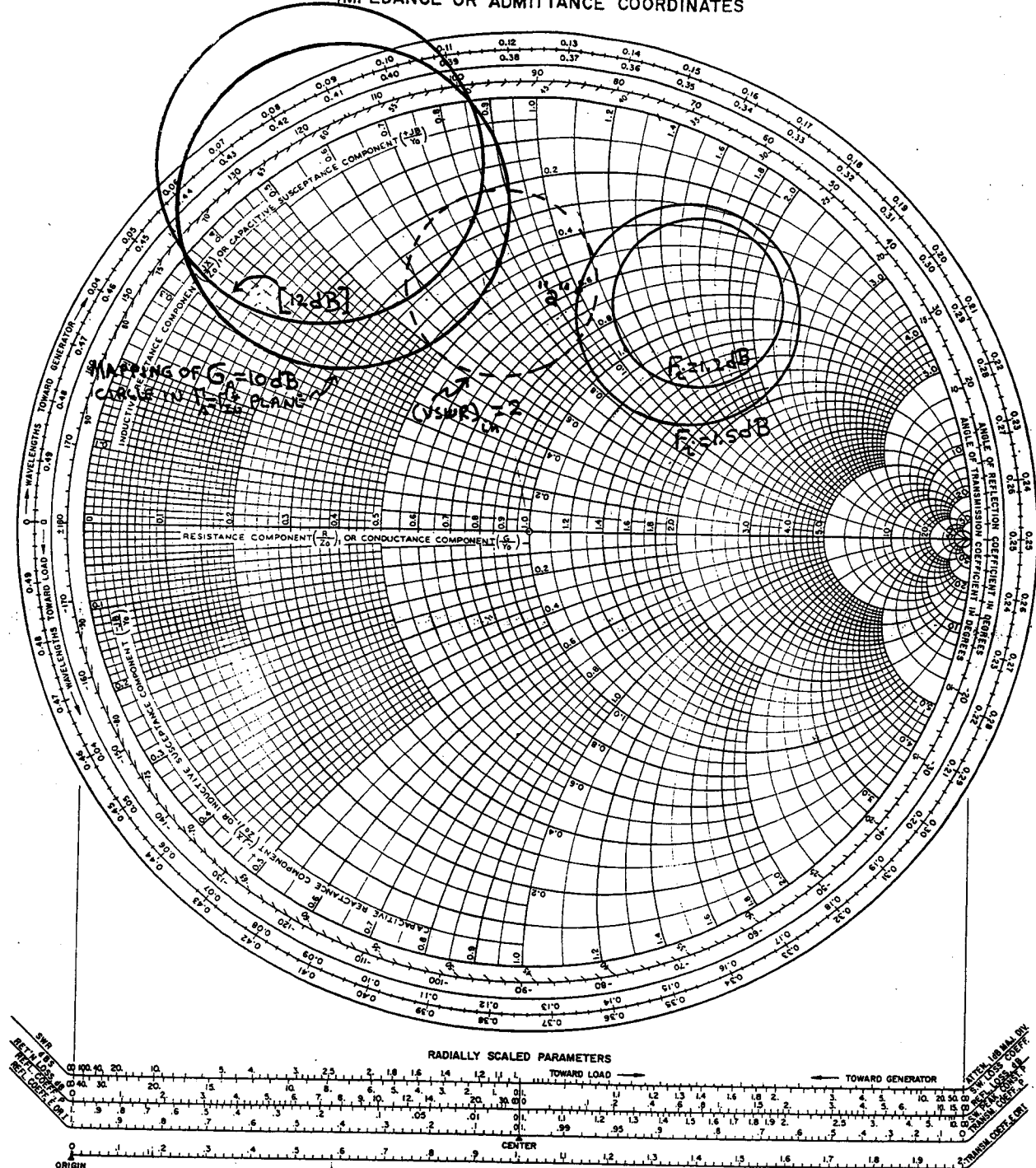

4.12) $K=1.04$, $\Delta=0.83 \angle -47.5^\circ$ $\therefore$ UNCONDITIONALLY STABLE

$G_{p,max} = 5.166$ OR 7.13 dB . CONSIDER THE $G_p=6 \text{ dB}$ AND 5 dB CIRCLES.

$G_p=6 \text{ dB}$ CIRCLE IN THE $\Gamma_L = \Gamma_{IN}^*$ PLANE: $C_L=0.257 \angle -10^\circ$, $\Gamma_L=0.443$


$G_p=5 \text{ dB}$ CIRCLE IN THE $\Gamma_L = \Gamma_{IN}^*$ PLANE: $C_L=0.223 \angle -10^\circ$, $\Gamma_L=0.541$

$F_L=2.1 \text{ dB}$ CIRCLE IN THE Γ_L PLANE: $C_{F_L}=0.569 \angle 71^\circ$, $\Gamma_{F_L}=0.185$

$F_L=2.3 \text{ dB}$ CIRCLE IN THE Γ_L PLANE: $C_{F_L}=0.539 \angle 71^\circ$, $\Gamma_{F_L}=0.262$

THESE CIRCLES ARE DRAWN IN THE SMITH CHART. SELECTING Γ_L AT POINT "A" RESULTS IN $F_L < 2.1 \text{ dB}$, $G_p=6 \text{ dB}$, AND $(VSWR)_{ch}=1$. THAT IS:

Γ_L	Γ_L	Γ_{IN}	Γ_{OUT}	$G_p(\text{dB})$	$F_L(\text{dB})$	$(VSWR)_{ch}$	$ \Gamma_b $	$(VSWR)_{OUT}$
$0.44 \angle 63^\circ$	$0.86 \angle 50.5^\circ$	$0.44 \angle -63^\circ$	$0.765 \angle -44.7^\circ$	6	2	1	0.355	2.1

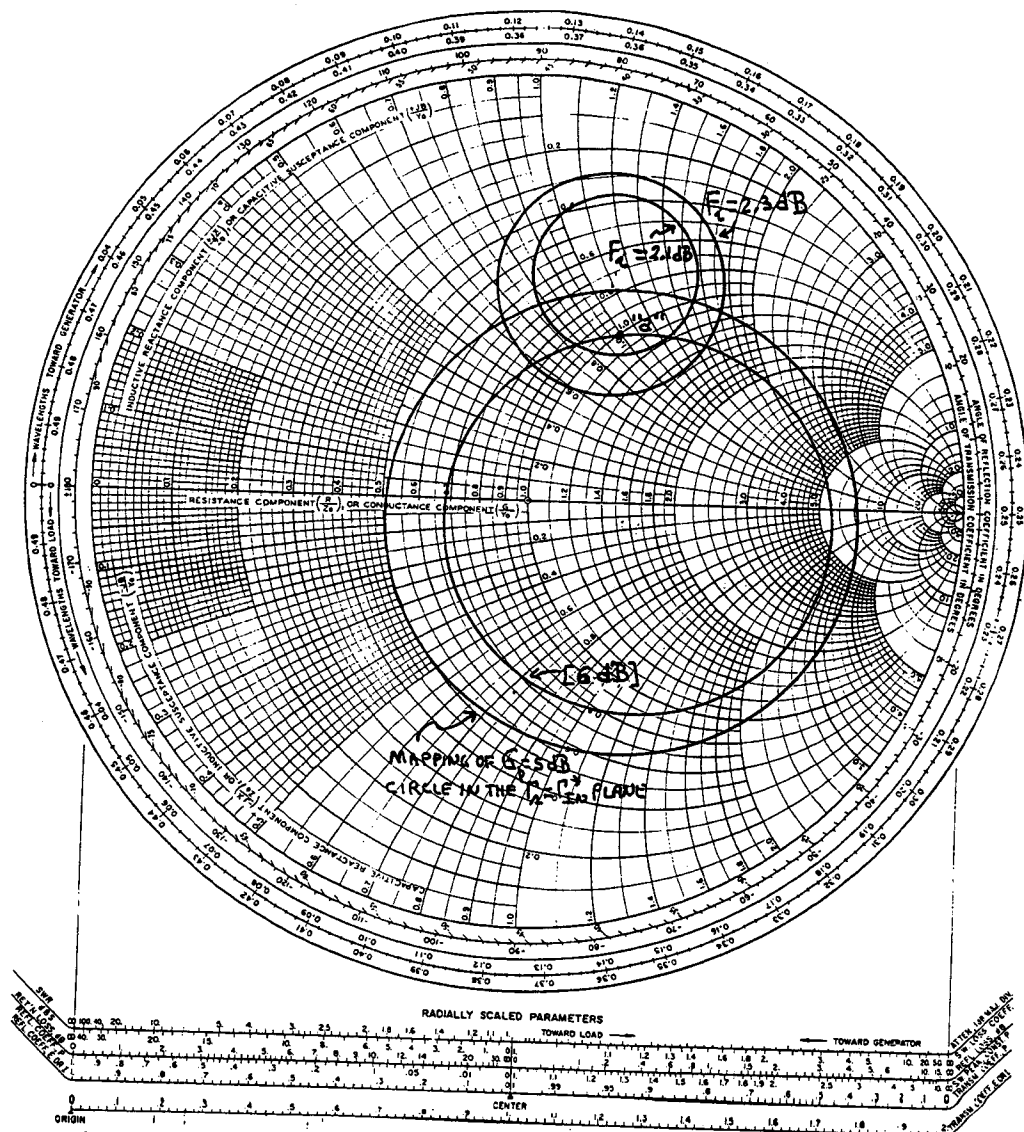

$$4.13) G_A(\text{dB}) = 14 + 14 + 14 - 7.5 + 16 + 16 = 66.5 \text{ dB}$$

THE NOISE FIGURE OF THE LNB IS DETERMINED BY THE NOISE FIGURE OF THE LNA (I.E., THE FIRST 3 AMPLIFIERS).

$$F = F_1 + \frac{F_2 - 1}{G_{A1}} + \frac{F_3 - 1}{G_{A1}G_{A2}} = 10^{0.05} + \frac{10^{0.09} - 1}{10^{1.4}} + \frac{10^{0.11} - 1}{10^{1.4}10^{1.4}} = 1.131 \text{ OR } 0.54 \text{ dB}$$

THE CONTRIBUTION TO F FROM THE MIXER, AMP. 5, AND AMP. 6 IS NEGLIGIBLE.

4.14) THE FOLLOWING CALCULATIONS ARE MADE:

$f(\text{MHz})$	$ S_{21} ^2$	$G_{A,\text{max}}$	$G_{L,\text{max}}$	$G_{TU,\text{max}}$
150	25 (14dB)	0.45 dB	7.6 dB	22 dB
250	16 (12dB)	0.38 dB	5.8 dB	18.2 dB
400	7.94 (9dB)	0.28 dB	4.6 dB	13.9 dB

OBSERVE THAT $G_{A,\text{max}}$ IS VERY SMALL AT THE THREE FREQUENCIES OF INTEREST. HENCE, ONLY THE LOAD MATCHING NETWORK WILL BE USED TO COMPENSATE FOR THE VARIATIONS IN $|S_{21}|^2$. THE INPUT MATCHING NETWORK CAN BE DESIGNED TO PROVIDE A GOOD (VSWR)_{in}, OR FOR $G_A = 0 \text{ dB}$.

FOR $G_{TU} = 12 \text{ dB}$, DESIGN G_L TO HAVE -2 dB AT 150 MHz, 0 dB AT 250 MHz, AND 3 dB AT 400 MHz.


$f(\text{MHz})$	$G_L(\text{dB})$	g_L	C_{g_L}	γ_{g_L}
150	-2	0.109	$0.378 \angle 6^\circ$	0.62
250	0	0.260	$0.494 \angle 15^\circ$	0.494
400	3	0.687	$0.7 \angle 26^\circ$	0.242

THE GAIN CIRCLES ARE DRAWN IN THE SMITH CHART. AFTER SOME TRIALS AND ERRORS, THE FOLLOWING MATCHING CIRCUIT WAS OBTAINED:

$$Z_{L1} = j\omega L_1$$


$$Y_{L2} = -j/\omega L_2$$

$$Z_{L3} = j\omega L_3$$

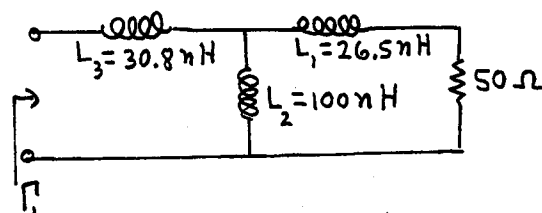

$f(\text{MHz})$	Z_{L1}	$\beta_{L1} = \frac{Z_{L1}}{50}$	Y_{L2}	y_{L2}	Z_{L2}	β_{L2}
150	$j24.97$	$j0.5$	$-j10.61 \text{ mS}$	$-j0.53$	$j29.03$	$j0.58$
250	$j41.62$	$j0.83$	$-j6.36 \text{ mS}$	$-j0.32$	$j48.4$	$j0.97$
400	$j66.6$	$j1.33$	$-j3.98 \text{ mS}$	$-j2$	$j77.4$	$j1.55$

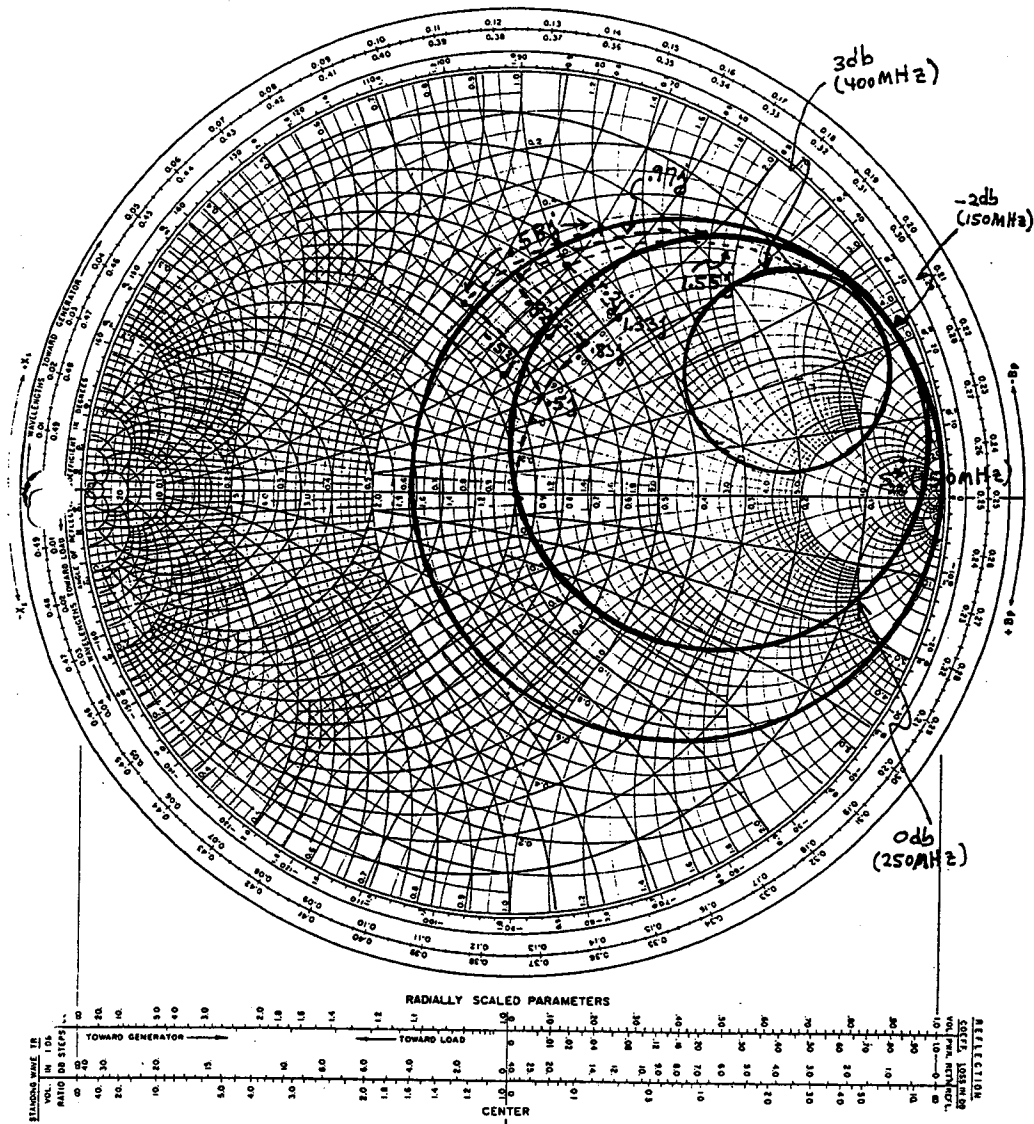NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES





$$4.15) \quad G_{TU} = G_A G_o G_L, \quad G_{TU}(\text{dB}) = G_A(\text{dB}) + G_o(\text{dB}) + G_L(\text{dB})$$

$f(\text{GHz})$	$G_{A,\text{max}}(\text{dB})$	$G_o = S_{21} ^2(\text{dB})$	$G_{L,\text{max}}(\text{dB})$	$G_{TU,\text{max}}(\text{dB})$
1	2.3	14.05	4.25	20.6
2	1.86	9.97	3.6	15.43

NOISE CIRCLES CALCULATIONS:


$f(\text{GHz})$	$F_i(\text{dB})$	C_{F_i}	γ_{F_i}
1	2	$0.395 \angle 23^\circ$	0.378
	3	$0.286 \angle 23^\circ$	0.591
	4	$0.212 \angle 23^\circ$	0.708
2	2	$0.377 \angle 88^\circ$	0.261
	3	$0.304 \angle 88^\circ$	0.477
	4	$0.244 \angle 88^\circ$	0.604

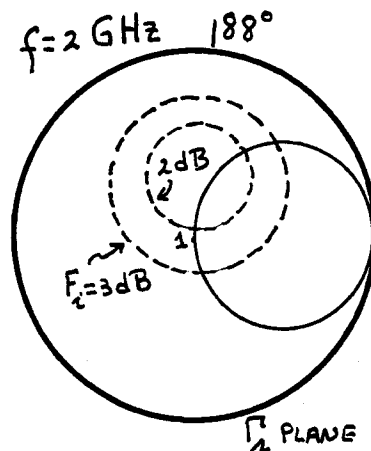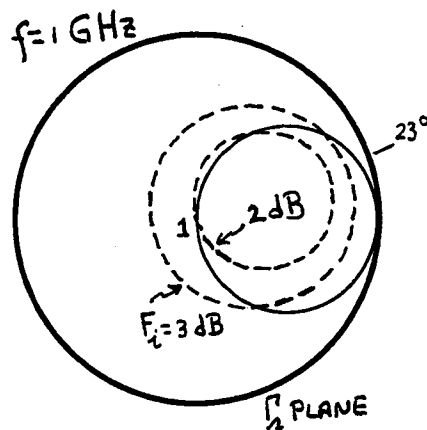

IT IS SEEN THAT THE NOISE FIGURE IS LESS THAN 3 dB AT 1 GHz AND 2 GHz WITH $\Gamma_L = 0$. THE INPUT MATCHING NETWORK IS DESIGNED WITH $\Gamma_L = 0$, AND IT FOLLOWS THAT $G_2 = 0 \text{ dB}$.

A DESIGN FOR $G_{TU} = 10 \text{ dB}$ REQUIRES THAT $G_L = -4 \text{ dB}$ AT 1 GHz, AND $G_L = 0 \text{ dB}$ AT 2 GHz. THAT IS,
 AT 1 GHz: $G_{TU} = 0 + 14.05 - 4 \approx 10 \text{ dB}$; AT 2 GHz: $G_{TU} = 0 + 9.97 + 0 \approx 10 \text{ dB}$

A MATCHING CIRCUIT FOR THIS DESIGN IS :

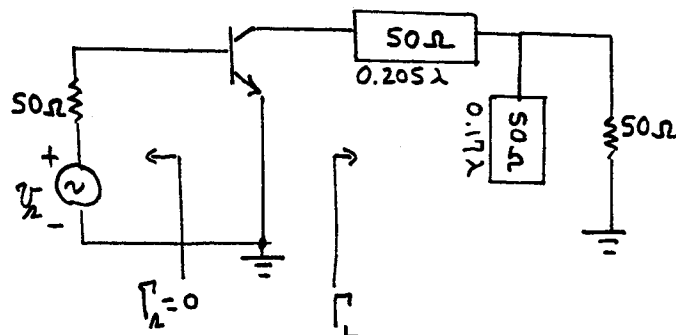

$$4.16) (a) \quad S_{11a} = S_{11b} = S_{11} \quad S_{21a} = S_{21b} = S_{21} \\ S_{12a} = S_{12b} = S_{12} \quad S_{22a} = S_{22b} = S_{22}$$

$$S_{11} = \frac{e^{-j\pi}}{2} (S_{11a} - S_{11b}) = 0, (VSWR)_{in} = 1$$

$$S_{22} = \frac{e^{-j\pi}}{2} (S_{22a} - S_{22b}) = 0, (VSWR)_{out} = 1$$

$$G_T = (0.5)^2 |S_{21a} + S_{21b}|^2 = (0.5)^2 [2(3.4)]^2 = 11.56 \text{ OR } 10.6 \text{ dB}$$

$$(b) \quad S_{11b} = 0.525 \angle 168^\circ, S_{12b} = 0.084 \angle 63^\circ, S_{21b} = 3.57 \angle 73.5^\circ, S_{22b} = 0.42 \angle -42.75^\circ$$

$$S_{11} = \frac{e^{-j\pi}}{2} (0.5 \angle 160^\circ - 0.525 \angle 168^\circ) = 0.038 \angle -125.2^\circ, (VSWR)_{in} = \frac{1+0.038}{1-0.038} = 1.08$$

$$S_{22} = \frac{e^{-j\pi}}{2} (0.4 \angle -45^\circ - 0.42 \angle -42.75^\circ) = 0.013 \angle -5^\circ, (VSWR)_{out} = \frac{1+0.013}{1-0.013} = 1.03$$

$$G_T = (0.5)^2 |3.4 \angle 70^\circ + 3.57 \angle 73.5^\circ|^2 = 12.13 \text{ OR } 10.8 \text{ dB}$$

4.17) (a) FOR IDENTICAL AMPLIFIERS: $S_{11} = S_{22} = 0$. THEN,

$$K = \frac{1 + |\Delta|^2}{2|S_{12}S_{21}|} = \frac{1 + |S_{12}S_{21}|^2}{2|S_{12}S_{21}|} = \frac{1 + P^2}{2P}, P = |S_{12}S_{21}|$$

THE MINIMUM VALUE OF K OCCURS WHEN $P=1$, AND IT IS $K=1$.

$$(b) \quad S_{11} = 0, S_{22} = 0$$

$$S_{21} = \frac{e^{-j\frac{\pi}{2}}}{2} (S_{21a} + S_{21b}) = \frac{e^{-j\frac{\pi}{2}}}{2} 2(-10.9 + j7.895) = 7.895 + j10.9$$

$$S_{12} = \frac{e^{-j\frac{\pi}{2}}}{2} (S_{12a} + S_{12b}) = \frac{e^{-j\frac{\pi}{2}}}{2} 2(0.009 + j0.015) = 0.015 - j0.009$$

$$P = |S_{12}S_{21}| = |0.017 \angle 13.46^\circ| = 0.235, |\Delta| < 1 \text{ AND}$$

$$K = \frac{1 + (0.235)^2}{2(0.235)} = 2.25 \therefore \text{UNCONDITIONALLY STABLE.}$$

$$4.18) \quad \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1/R_2 & -1/R_2 \\ \frac{g_m}{1+g_m R_1} - \frac{1}{R_2} & \frac{1}{R_2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\text{FROM TABLE 1.8.1: } y'_{11} = y_{11} Z_0 = \frac{Z_0}{R_2}, y'_{12} = y_{12} Z_0 = -\frac{Z_0}{R_2},$$

$$y'_{21} = y_{21} Z_0 = \frac{g_m Z_0}{1+g_m R_1} - \frac{Z_0}{R_2}, y'_{22} = y_{22} Z_0 = \frac{Z_0}{R_2}$$

$$\Delta_3 = (1 + y'_{11})(1 + y'_{22}) - y'_{12}y'_{21} = \left(1 + \frac{Z_0}{R_2}\right)^2 + \frac{Z_0}{R_2} \left(\frac{g_m Z_0}{1+g_m R_1} - \frac{Z_0}{R_2}\right)$$

$$\text{OR} \quad \Delta_3 = 1 + \frac{2Z_0}{R_2} + \frac{g_m Z_0^2}{R_2(1+g_m R_1)}$$

$$S_{11} = \frac{(1-y'_{11})(1+y'_{22}) + y'_{12}y'_{21}}{\Delta_3} = \frac{1}{\Delta_3} \left[\left(1 - \frac{Z_0}{R_2}\right) \left(1 + \frac{Z_0}{R_2}\right) + \frac{Z_0}{R_2} \left(\frac{Z_0}{R_2} - \frac{g_m Z_0}{1+g_m R_1} \right) \right]$$

$$\therefore S_{11} = \frac{1}{\Delta_3} \left[1 - \frac{g_m Z_0^2}{R_2(1+g_m R_1)} \right]$$

$$S_{22} = \frac{(1+y'_{11})(1-y'_{22}) + y'_{12}y'_{21}}{\Delta_3} = \frac{1}{\Delta_3} \left[1 - \frac{g_m Z_0^2}{R_2(1+g_m R_1)} \right]$$

$$S_{21} = \frac{-2y'_{21}}{\Delta_3} = \frac{-2}{\Delta_3} \left[\frac{g_m Z_0}{1+g_m R_1} - \frac{Z_0}{R_2} \right] = \frac{1}{\Delta_3} \left[\frac{-2g_m Z_0}{1+g_m R_1} + 2 \frac{Z_0}{R_2} \right]$$

$$S_{12} = \frac{-2y'_{12}}{\Delta_3} = \frac{-2}{\Delta_3} \left(-\frac{Z_0}{R_2} \right) = \frac{2Z_0}{\Delta_3 R_2}$$

4.19) IF S_{11} IS APPROXIMATED BY $0.97 \angle 0^\circ$, THE ASSOCIATED $\gamma_{b'e}$ IS $3.28 \text{ k}\Omega$.

$$G_T = 10 = |S_{21}|^2 \Rightarrow S_{21} = -3.16$$

FROM (4.4.10):

$$R_2 = Z_0(1 - S_{21}) = 50(1 + 3.16) = 208 \Omega$$

THE VALUE OF g_m FOR $(VSWR)_{in} \approx 1$ AND $(VSWR)_{out} \approx 1$ FOLLOWS FROM (4.4.9). THAT IS,

$$g_m = \frac{R_2}{Z_0^2} = \frac{208}{50^2} = 83 \text{ mS}$$

4.20) $G_T = 10 = |S_{21}|^2 \Rightarrow S_{21} = -3.16$.

$$\text{FROM (4.4.10): } R_2 = Z_0(1 - S_{21}) = 50(1 + 3.16) = 208 \Omega$$

AT THE LOWER FREQUENCIES THE VALUE OF $S_{11} = 0.65 \angle -74^\circ (6 + j14 \text{ mS})$ CORRESPONDS TO AN $\gamma_{b'e}$ OF 166.6Ω . HENCE, THE CONDITION $\gamma_{b'e} \gg R_2$ IS NOT SATISFIED, AND A SERIES FEEDBACK RESISTOR R_1 IS NEEDED.

$$\text{FROM (4.4.10): } g_{m(\text{min})} = \frac{1 + 3.16}{50} = 83 \text{ mS}$$


THE VALUE OF THE TRANSISTOR g_m AT THE LOWER FREQUENCIES (WITH $S_{21} \approx 3.4 \angle 180^\circ$) IS:

$$g_m = -\frac{S_{21}}{2Z_0} = \frac{3.4}{2(50)} = 34 \text{ mS}$$

SINCE $g_m > g_{m(\text{min})}$, R_1 IS CALCULATED USING (4.4.7):

$$R_1 = \frac{Z_0^2}{R_2} - \frac{1}{g_m} = \frac{50^2}{208} - \frac{1}{0.34} = 9 \Omega$$

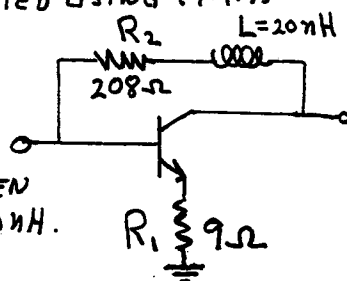AN INDUCTOR IS USUALLY NEEDED IN SERIES WITH R_2 IN ORDER TO REDUCE THE FEEDBACK AT THE HIGHER FREQUENCIES AND TO FLATTEN THE GAIN. TYPICAL VALUES OF L ARE 20 nH TO 30 nH .



(b) THE FEEDBACK CIRCUIT WAS SIMULATED USING THE HEWLETT-PACKARD MDS PROGRAM. THE RESULTS ARE:

$f(\text{MHz})$	S_{11}	S_{21}	S_{12}	S_{22}	$G_T = 10 \log S_{21} ^2$
100	0.057 $\angle -163^\circ$	3.27 $\angle 177.3^\circ$	0.183 $\angle -1.86^\circ$	0.044 $\angle 113.4^\circ$	10.3 dB
200	0.062 $\angle -146.6^\circ$	3.29 $\angle 174.5^\circ$	0.182 $\angle -3.8^\circ$	0.083 $\angle 95.4^\circ$	10.3 dB
400	0.086 $\angle -120.3^\circ$	3.35 $\angle 168.6^\circ$	0.177 $\angle -7.6^\circ$	0.161 $\angle 78.4^\circ$	10.5 dB
600	0.132 $\angle -105.3^\circ$	3.45 $\angle 161.7^\circ$	0.169 $\angle -11.4^\circ$	0.243 $\angle 66.4^\circ$	10.8 dB
800	0.196 $\angle -102.9^\circ$	3.52 $\angle 154^\circ$	0.157 $\angle -14.4^\circ$	0.32 $\angle 54.1^\circ$	10.9 dB
1000	0.27 $\angle -104.5^\circ$	3.56 $\angle 145.3^\circ$	0.142 $\angle -16.8^\circ$	0.393 $\angle 42.4^\circ$	11.0 dB
1500	0.46 $\angle -117.7^\circ$	3.38 $\angle 121.9^\circ$	0.102 $\angle -11.6^\circ$	0.518 $\angle 13.6^\circ$	10.6 dB

$$4.21) (a) Q_1 = \frac{X_c}{R} = \frac{1}{\omega_0 C R} = \frac{1}{2\pi 500 \cdot 10^6 (100 \cdot 10^{-12}) 5} = 0.637$$

$$Q_2 = \frac{f_0}{f_2 - f_1} = \frac{500 \cdot 10^6}{600 \cdot 10^6 - 400 \cdot 10^6} = 2.5$$

$$\Gamma_x = e^{-\pi(Q_2/Q_1)} = e^{-\pi(2.5/0.637)} = 4.4 \cdot 10^{-6}$$

$$(b) Q_1 = \frac{R}{X_c} = \omega_0 R C = 2\pi (9 \cdot 10^9) 50 (10^{-12}) = 2.83$$

$$Q_2 = \frac{f_0}{f_2 - f_1} = \frac{9 \cdot 10^9}{12 \cdot 10^9 - 6 \cdot 10^9} = 1.5$$

$$\Gamma_x = e^{-\pi(Q_2/Q_1)} = e^{-\pi(1.5/2.83)} = 0.19$$

$$4.22) \int_0^\infty \frac{1}{\omega^2} \ln \left| \frac{1}{\Gamma_x} \right| d\omega \leq \pi R C \Rightarrow \ln \left| \frac{1}{\Gamma_x} \right| \int_{\omega_a}^{\omega_b} \frac{d\omega}{\omega^2} = \pi R C$$

$$\text{OR } \ln \left| \frac{1}{\Gamma_x} \right| \left(\frac{1}{\omega_b} - \frac{1}{\omega_a} \right) = \pi R C \Rightarrow \ln \left| \frac{1}{\Gamma_x} \right| = \frac{\omega_a \omega_b \pi R C}{\omega_a - \omega_b} = \frac{-\pi \omega_0^2 R C}{\omega_b - \omega_a}$$

$$\text{OR } \ln \left| \frac{1}{\Gamma_x} \right| = -\frac{\pi Q_2}{Q_1} \text{ WHERE } \omega_0 = \sqrt{\omega_a \omega_b}, Q_2 = \frac{\omega_0}{\omega_b - \omega_a}, Q_1 = \frac{1}{\omega_0 R C}$$

$$\therefore \left| \frac{1}{\Gamma_x} \right| = e^{-\pi Q_2/Q_1}, \omega_0 \text{ IS THE GEOMETRIC MEAN OF } \omega_a \text{ AND } \omega_b.$$

$$\text{FOR: } \int_0^{\infty} \frac{1}{\omega^2} \ln \left| \frac{1}{\Gamma} \right| d\omega \leq \frac{\pi L}{R} \Rightarrow \ln |\Gamma_x| \left(\frac{1}{\omega_b} - \frac{1}{\omega_a} \right) = \frac{\pi L}{R}$$

$$\text{OR } \ln |\Gamma_x| = \frac{-\pi \omega_0^2 L}{(\omega_b - \omega_a) R} = -\pi \frac{Q_2}{Q_1} \Rightarrow |\Gamma_x| = e^{-\pi Q_2 / Q_1}$$

$$\text{WHERE } \omega_0 = \sqrt{\omega_a \omega_b}, \quad Q_2 = \frac{\omega_0}{\omega_b - \omega_a}, \quad Q_1 = \frac{R}{\omega_0 L}$$

$$\text{FOR: } \int_0^{\infty} \ln \left| \frac{1}{\Gamma} \right| d\omega \leq \frac{\pi R}{L} \Rightarrow \ln |\Gamma_x| = \frac{-\pi R}{(\omega_b - \omega_a) Q_1} = -\pi \frac{Q_2}{Q_1} \Rightarrow |\Gamma_x| = e^{-\pi Q_2 / Q_1}$$

$$\text{WHERE } Q_2 = \frac{\omega_0}{\omega_b - \omega_a}, \quad Q_1 = \frac{\omega_0 L}{R}$$

$$4.23) (a) \quad \Gamma_{IN} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} = \frac{S_{11} - \Delta \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\frac{\partial \Gamma_{IN}}{\partial \Gamma_L} = \frac{(1 - S_{22} \Gamma_L) S_{12} S_{21} + S_{12} S_{21} \Gamma_L S_{22}}{(1 - S_{22} \Gamma_L)^2}$$

$$\delta_{IN} = \left| \frac{d\Gamma_{IN}/\Gamma_{IN}}{d\Gamma_L/\Gamma_L} \right| = \left| \frac{\Gamma_L (1 - S_{22} \Gamma_L) [(1 - S_{22} \Gamma_L) S_{12} S_{21} + S_{12} S_{21} S_{22} \Gamma_L]}{(S_{11} - \Delta \Gamma_L) (1 - S_{22} \Gamma_L)^2} \right|$$

$$\delta_{IN} = \left| \frac{\Gamma_L (1 - S_{22} \Gamma_L) S_{12} S_{21} + S_{12} S_{21} S_{22} \Gamma_L^2}{(S_{11} - \Delta \Gamma_L) (1 - S_{22} \Gamma_L)} \right| = \frac{|S_{21}| |S_{12}| |\Gamma_L|}{|1 - S_{22} \Gamma_L| |S_{11} - \Delta \Gamma_L|}$$

$$(b) \quad |1 - S_{22} \Gamma_L| |S_{11} - \Delta \Gamma_L| = |S_{21} S_{12}| \delta_{IN} |\Gamma_L|$$

$$|S_{11} - \Delta \Gamma_L - S_{11} S_{22} \Gamma_L + S_{22} \Delta \Gamma_L^2 - S_{21} S_{12} \delta_{IN}^{-1} \Gamma_L| = 0$$

$$\left| \Gamma_L^2 - \Gamma_L \left(\frac{\Delta + S_{11} S_{22} + S_{12} S_{21} \delta_{IN}^{-1}}{S_{22} \Delta} \right) + \frac{S_{11}}{S_{22} \Delta} \right| = 0$$

$$\therefore |\Gamma_L| = \left| \alpha \pm \left| \alpha^2 - \frac{S_{11}}{S_{22} \Delta} \right|^{1/2} \right| \quad \text{WHERE } \alpha = \frac{\Delta + S_{11} S_{22} + S_{12} S_{21} \delta_{IN}^{-1}}{2 S_{22} \Delta}$$

$$(c) \quad \Gamma_{OUT} = S_{22} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{11} \Gamma_L} = \frac{S_{22} - \Delta \Gamma_L}{1 - S_{11} \Gamma_L}$$

$$\frac{\partial \Gamma_{OUT}}{\partial \Gamma_L} = \frac{(1 - S_{11} \Gamma_L) S_{12} S_{21} + S_{12} S_{21} \Gamma_L S_{11}}{(1 - S_{11} \Gamma_L)^2}$$

$$\delta_{OUT} = \left| \frac{\partial \Gamma_{OUT}/\Gamma_{OUT}}{\partial \Gamma_L/\Gamma_L} \right| = \left| \frac{\Gamma_L (1 - S_{11} \Gamma_L) [(1 - S_{11} \Gamma_L) S_{12} S_{21} + S_{12} S_{21} S_{11} \Gamma_L]}{(S_{22} - \Delta \Gamma_L) (1 - S_{11} \Gamma_L)^2} \right|$$

$$\delta_{OUT} = \left| \frac{\Gamma_L (1 - S_{11} \Gamma_L) S_{12} S_{21} + S_{12} S_{21} S_{11} \Gamma_L^2}{(S_{22} - \Delta \Gamma_L) (1 - S_{11} \Gamma_L)} \right| = \frac{|S_{21}| |S_{12}| |\Gamma_L|}{|1 - S_{11} \Gamma_L| |S_{22} - \Delta \Gamma_L|}$$

$$4.24) (a) \Gamma_A = S_{11}^* = 0.75 \angle 100^\circ \text{ AND } \Gamma_L = S_{22}^* = 0.7 \angle 50^\circ$$

$$(b) Y_A = \frac{1}{Z_A} = 7 - j23 \text{ mS}, Y_L = \frac{1}{Z_L} = 4 - j9 \text{ mS}$$

$$(BW)_{IN}^i = \frac{2f_0 G_{A,m}}{|B_{A,m}|} = \frac{2(8 \times 10^9) 0.007}{0.023} = 4.87 \text{ GHz}$$

$$(BW)_{OUT}^i = \frac{2f_0 G_{L,m}}{|B_{L,m}|} = \frac{2(8 \times 10^9)(0.004)}{0.009} = 7.11 \text{ GHz}$$

$$(c) (BW)_{IN} = 20\% (BW)_{IN}^i = 974 \text{ MHz}$$

$$Y_{IN} = 7 + j23 \text{ mS}$$

THE REQUIRED VALUE OF C'_{IN} (FROM (4.6.5)) IS:

$$C'_{IN} = \frac{B_{IN,m}}{\omega_0} \left[\frac{(BW)_{IN}^i}{(BW)_{IN}} - 1 \right] = \frac{23 \times 10^3}{2\pi(8 \times 10^9)} \left[\frac{4.87}{0.974} - 1 \right] = 1.83 \text{ pF}$$

$$(d) Y'_{IN} = Y_{IN} + j\omega C'_{IN} = (7 + j23) \times 10^{-3} + j2\pi(8 \times 10^9)(1.83 \times 10^{-12}) = 7 + j115 \text{ mS}$$

$$\Gamma'_{IN} = 0.98 \angle -160.4^\circ, \therefore \Gamma_A = \Gamma_{IN}^* = 0.98 \angle 160.4^\circ, \Gamma_L = S_{22}^* = 0.7 \angle 50^\circ$$

$$G_{TU,max} = \frac{1}{1 - (0.98)^2} (2.5)^2 \frac{1}{1 - (0.7)^2} = 309.4 \text{ OR } 24.9 \text{ dB}$$

$$4.25) \Gamma_{MA} = 0.476 \angle 166^\circ \Rightarrow Y_{MA} = 51 - j15 \text{ mS}$$

$$\Gamma_{ML} = 0.846 \angle 172^\circ \Rightarrow Y_{ML} = 3 - j14 \text{ mS}$$

$$(BW)_{IN}^i = \frac{2(4 \times 10^9) 0.051}{0.015} = 27.2 \text{ GHz}, (BW)_{OUT}^i = \frac{2(4 \times 10^9) 0.003}{0.014} = 1.714 \text{ GHz}$$

THE VALUE OF L'_{OUT} REQUIRED FOR $BW \approx (BW)_{OUT} = 400 \text{ MHz}$ IS

$$L'_{OUT} = \frac{1}{\omega_0 |B_{OUT,m}| \left[\frac{(BW)_{OUT}^i}{(BW)_{OUT}} - 1 \right]} = \frac{1}{2\pi(4 \times 10^9) 0.014 \left[\frac{1.714 \times 10^9}{0.4 \times 10^9} - 1 \right]} = 0.865 \text{ nH}$$

$$4.26) \text{ FROM (4.7.4): } P_{i,mds} = -174 + 10 \log 800 \times 10^6 + 5 + 3 = -76.97 \text{ dBm}$$

$$\text{FROM (4.7.5): } P_{o,mds} = P_{i,mds} + G_A = -76.97 + 30 = -46.97 \text{ dBm.}$$

(WITH $G_A = G_T$)

$$DR = P_{idB} - P_{o,mds} = 28 - (-46.97) = 74.97 \text{ dB}$$


$$P_{IP} = P_{idB} + 10 = 28 + 10 = 38 \text{ dBm}$$

$$DR_f = \frac{2}{3} (P_{IP} - P_{o,mds}) = \frac{2}{3} (38 - (-46.97)) = 69.3 \text{ dB}$$

FOR NO THIRD-ORDER IM:

$$P_{OUT} = P_{o,mds} + DR_f = -46.97 + 69.3 = 22.3 \text{ dBm}$$

4.27)

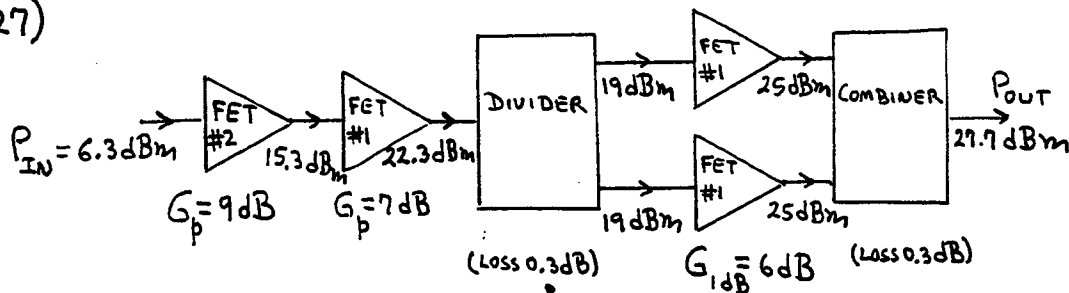

4.28) $K = 1.61$, $\Delta = 0.313 \angle 18.8^\circ$ $\therefore$ UNCONDITIONALLY STABLE


$$\Gamma_L = \Gamma_{LP} = 0.1 \angle 0^\circ \text{ AND } \Gamma_{\lambda} = \Gamma_{SP} = \Gamma_{IN}^* = 0.324 \angle 146.6^\circ$$

OUTPUT MATCHING CIRCUIT:


$$Z_{LP} = 61.1 \Omega$$

USING A $\lambda/4$ TRANSFORMER

$$Z_0 = \sqrt{61.1(50)} = 55.3 \Omega$$

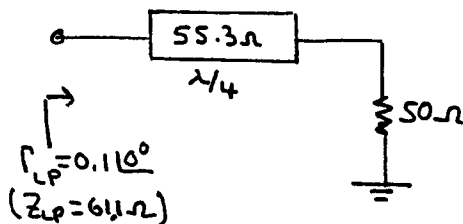

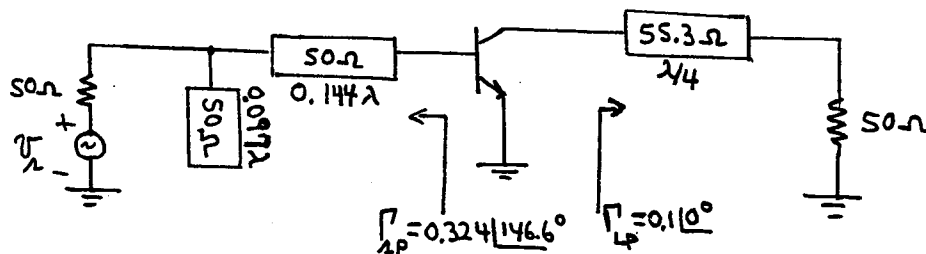INPUT MATCHING CIRCUIT: USE A SHUNT STUB (OPEN CIRCUIT) OF LENGTH 0.097λ FOLLOWED BY A SERIES TRANS. LINE OF LENGTH 0.144λ .



$$4.29) P_{IN} = \frac{E_{\lambda, rms}^2}{4(50)} = \frac{(79.5 \cdot 10^3)^2}{200} = 3.16 \cdot 10^{-5} \text{ W OR } -15 \text{ dBm}$$

$$P_{OUT} = P_{IN} + 13 + 13 + 10 + 9 = -15 + 45 = 30 \text{ dBm}$$

$$\text{OR } P_{OUT} = 1 \text{ W}$$

4.30) THE BLOCK DIAGRAM IS IDENTICAL TO THE ONE IN FIG. 4.7.18, EXCEPT THAT $Z_{\lambda} = 1.19 + j1.35 \Omega$ AND $Z_L = 8.1 - j4.1 \Omega$

4.31) YES.